

Chapter 6

1.
 - a. R_2 and R_3
 - b. E and R_3
 - c. R_2 and R_3
 - d. R_2 and R_3

2.
 - a. $E, R_1, R_2, R_3,$ and R_4
 - b. $E, R_1, R_2,$ and R_3
 - c. E and R_1
 - d. none

3.
 - a. R_3 and R_4, R_5 and R_6
 - b. E and R_1, R_6 and R_7

4.
 - a. $R_T = \frac{(36\ \Omega)(18\ \Omega)}{36\ \Omega + 18\ \Omega} = \mathbf{12\ \Omega}$

 - b. $R_T = \frac{1}{\frac{1}{1\ \text{k}\Omega} + \frac{1}{2\ \text{k}\Omega} + \frac{1}{30\ \text{k}\Omega}} + \frac{1}{1 \times 10^{-3}\ \text{S} + 0.5 \times 10^{-3}\ \text{S} + 33.33 \times 10^{-6}\ \text{S}}$
 $= \frac{1}{1.533 \times 10^{-3}\ \text{S}} = \mathbf{0.652\ \text{k}\Omega}$

 - c. $R_T = \frac{1}{\frac{1}{1.2\ \Omega} + \frac{1}{120\ \text{k}\Omega} + \frac{1}{12\ \text{k}\Omega}} = \frac{1}{8.3333 \times 10^{-6}\ \text{S} + 8.33 \times 10^{-3}\ \text{S} + 83.33 \times 10^{-3}\ \text{S}} = \frac{1}{92.49 \times 10^{-3}\ \text{S}}$
 $= \mathbf{10.81\ \Omega}$

5.
 - a. $R'_T = \frac{18\ \text{k}\Omega}{3} = 6\ \text{k}\Omega$
 $R_T = \frac{(6\ \text{k}\Omega)(6\ \text{k}\Omega)}{6\ \text{k}\Omega + 6\ \text{k}\Omega} = \mathbf{3\ \text{k}\Omega}$

 - b. $R'_T = \frac{22\ \Omega}{4} = 5.5\ \Omega, R_{T''} = \frac{10\ \Omega}{2} = 5\ \Omega$
 $R_T = \frac{(5.5\ \Omega)(5\ \Omega)}{5.5\ \Omega + 5\ \Omega} = \mathbf{2.62\ \Omega}$

 - c. $R_T = \frac{1}{\frac{1}{1\ \Omega} + \frac{1}{1\ \text{k}\Omega} + \frac{1}{1\ \text{M}\Omega}} = \frac{1}{1000 \times 10^{-3}\ \text{S} + 1 \times 10^{-3}\ \text{S} + 0.001 \times 10^{-3}\ \text{S}}$
 $= \frac{1}{1001.001 \times 10^{-3}\ \text{S}} = \mathbf{0.99\ \Omega}$

6.
 - a. $R_T = \frac{1}{\frac{1}{1\ \text{k}\Omega} + \frac{1}{1.2\ \text{k}\Omega} + \frac{1}{0.3\ \text{k}\Omega}} = \frac{1}{1 \times 10^{-3}\ \text{S} + 0.833 \times 10^{-3}\ \text{S} + 3.333 \times 10^{-3}\ \text{S}}$

$$= \frac{1}{5.166 \times 10^{-3} \text{S}} = \mathbf{193.57 \Omega}$$

$$\begin{aligned} \text{b. } R_T &= \frac{1}{\frac{1}{1 \text{ k}\Omega} + \frac{1}{1.2 \text{ k}\Omega} + \frac{1}{2.2 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega}} = \frac{1}{1 \times 10^{-3} \text{S} + 0.833 \times 10^{-3} \text{S} + 0.455 \times 10^{-3} \text{S} + 1 \times 10^{-3} \text{S}} \\ &= \frac{1}{3.288 \times 10^{-3} \text{S}} = \mathbf{304.14 \Omega} \end{aligned}$$

$$7. \quad \text{a. } R'_T = 3 \Omega \parallel 6 \Omega = 2 \Omega$$

$$R_T = 1.61 \Omega = \frac{(2 \Omega)(R)}{2 \Omega + R}, \quad R = \mathbf{8 \Omega}$$

$$\text{b. } R'_T = \frac{6 \text{ k}\Omega}{3} = 2 \text{ k}\Omega$$

$$R_T = 1.8 \text{ k}\Omega = \frac{(2 \text{ k}\Omega)(R)}{2 \text{ k}\Omega + R}, \quad R = \mathbf{18 \text{ k}\Omega}$$

$$\text{c. } R_T = 5.08 \text{ k}\Omega = \frac{(20 \text{ k}\Omega)(R)}{20 \text{ k}\Omega + R}, \quad R = \mathbf{6.8 \text{ k}\Omega}$$

$$8. \quad \text{a. } R_T = 1.02 \Omega = \frac{1}{\frac{1}{2.4 \text{ k}\Omega} + \frac{1}{R} + \frac{1}{6.8 \text{ k}\Omega}} = \frac{1}{416.67 \times 10^{-6} \text{S} + \frac{1}{R} + 147.06 \times 10^{-6} \text{S}}$$

$$1.02 \text{ k}\Omega = \frac{1}{563.73 \times 10^{-6} + \frac{1}{R}}$$

$$575 \times 10^{-3} + \frac{1.020 \text{ k}\Omega}{R} = 1$$

$$R = \frac{1.020 \text{ k}\Omega}{425 \times 10^{-3}} = \mathbf{2.4 \text{ k}\Omega}$$

$$\text{b. } R_T = 6 \text{ k}\Omega = \frac{R_1}{4}$$

$$R_1 = \mathbf{24 \text{ k}\Omega}$$

$$\text{c. } \frac{1}{1.11 \text{ k}\Omega} = \frac{1}{R} + \frac{1}{8.2 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega} + \frac{1}{2 \text{ k}\Omega}$$

$$900.9 \times 10^{-6} \text{S} = \frac{1}{R} + 121.95 \times 10^{-6} \text{S} + 100 \times 10^{-6} \text{S} + 500 \times 10^{-6} \text{S}$$

$$\frac{1}{R} = 178.95 \times 10^{-6} \text{S}$$

$$R = \frac{1}{178.95 \times 10^{-6} \text{S}} = 5.588 \text{ k}\Omega \cong \mathbf{5.6 \text{ k}\Omega}$$

$$9. \quad \text{a. } 1.2 \text{ k}\Omega$$

$$\text{b. } \text{about } 1 \text{ k}\Omega$$

- c.
$$R_T = \frac{1}{\frac{1}{1.2 \text{ k}\Omega} + \frac{1}{22 \text{ k}\Omega} + \frac{1}{220 \text{ k}\Omega} + \frac{1}{2.2 \text{ M}\Omega}}$$

$$= \frac{1}{833.333 \times 10^{-6} \text{ S} + 45.455 \times 10^{-6} \text{ S} + 4.545 \times 10^{-6} \text{ S} + 0.455 \times 10^{-6} \text{ S}}$$

$$= \frac{1}{883.788 \times 10^{-6} \text{ S}} = \mathbf{1.131 \text{ k}\Omega}$$
- d. $220 \text{ k}\Omega, 2.2 \text{ M}\Omega: R_T = \frac{(1.2 \text{ k}\Omega)(22 \text{ k}\Omega)}{1.2 \text{ k}\Omega + 22 \text{ k}\Omega} = \mathbf{1.138 \text{ k}\Omega}$
- e. R_T reduced.
10. a.
$$R_T = \frac{1}{\frac{1}{4 \Omega} + \frac{1}{2 \Omega} + \frac{1}{10 \Omega}} = \frac{1}{0.25 \text{ S} + 0.50 \text{ S} + 0.10 \text{ S}} = \frac{1}{0.85 \text{ S}} = \mathbf{1.18 \Omega}$$
- b. $\infty \Omega$
- c. $R_T = 3 \Omega \parallel 6 \Omega = \mathbf{2 \Omega}$
11. $24 \Omega \parallel 24 \Omega = 12 \Omega$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{12 \Omega} + \frac{1}{120 \Omega} \quad (\text{Two of the } 24 \Omega \text{ resistors "shorted" out.})$$

$$0.1 \text{ S} = \frac{1}{R_1} + 0.08333 \text{ S} + 0.00833 \text{ S}$$

$$0.1 \text{ S} = \frac{1}{R_1} + 0.09167 \text{ S}$$

$$\frac{1}{R_1} = 0.1 \text{ S} - 0.09167 \text{ S} = 0.00833 \text{ S}$$

$$R_1 = \frac{1}{0.00833 \text{ S}} = \mathbf{120 \Omega}$$
12. a.
$$R_T = \frac{(8 \Omega)(24 \Omega)}{8 \Omega + 24 \Omega} = \mathbf{6 \Omega}$$
- b. $V_{R_1} = V_{R_2} = \mathbf{36 \text{ V}}$
- c.
$$I_s = \frac{E}{R_T} = \frac{36 \text{ V}}{6 \Omega} = \mathbf{6 \text{ A}}$$

$$I_1 = \frac{V_{R_1}}{R_1} = \frac{36 \text{ V}}{8 \Omega} = \mathbf{4.5 \text{ A}}$$

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{36 \text{ V}}{24 \Omega} = \mathbf{1.5 \text{ A}}$$
- d. $I_s = I_1 + I_2$
 $6 \text{ A} = 4.5 \text{ A} + 1.5 \text{ A} = 6 \text{ A}$ (checks)

13. a. $I_1 = \frac{V_{R_1}}{R_1} = \frac{18 \text{ V}}{3 \Omega} = \mathbf{6 \text{ A}}, I_2 = \frac{V_{R_2}}{R_2} = \frac{18 \text{ V}}{9 \Omega} = \mathbf{2 \text{ A}}, I_3 = \frac{V_{R_3}}{R_3} = \frac{18 \text{ V}}{36 \Omega} = \mathbf{0.5 \text{ A}}$

b.
$$R_T = \frac{1}{\frac{1}{3 \Omega} + \frac{1}{9 \Omega} + \frac{1}{36 \Omega}} = \frac{1}{0.333 \text{ S} + 0.111 \text{ S} + 0.028 \text{ S}}$$

$$= \frac{1}{472 \times 10^{-3} \text{ S}} = \mathbf{2.12 \Omega}$$

c. $I_s = \frac{E}{R_T} = \frac{18 \text{ V}}{2.12 \Omega} = \mathbf{8.5 \text{ A}}$

d. $I_s = I_1 + I_2 + I_3 = 6 \text{ A} + 2 \text{ A} + 0.5 \text{ A} = \mathbf{8.5 \text{ A}}$

e. they match

14. a. $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{24 \text{ V}}{10 \text{ k}\Omega} = \mathbf{2.4 \text{ mA}}, I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{24 \text{ V}}{1.2 \text{ k}\Omega} = \mathbf{20 \text{ mA}},$
 $I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{24 \text{ V}}{6.8 \text{ k}\Omega} = \mathbf{3.53 \text{ mA}}$

b.
$$R_T = \frac{1}{\frac{1}{10 \text{ k}\Omega} + \frac{1}{1.2 \text{ k}\Omega} + \frac{1}{6.8 \text{ k}\Omega}} = \frac{1}{100 \times 10^{-6} \text{ S} + 833.333 \times 10^{-6} \text{ S} + 147.06 \times 10^{-6} \text{ S}}$$

$$= \frac{1}{1.08 \times 10^{-3} \text{ S}} = \mathbf{925.93 \Omega}$$

c. $I_s = \frac{E}{R_T} = \frac{24 \text{ V}}{925.93 \Omega} = \mathbf{25.92 \text{ mA}}$

d. $I_s = I_1 + I_2 + I_3 = 2.4 \text{ mA} + 20 \text{ mA} + 3.53 \text{ mA} = \mathbf{25.93 \text{ mA}}$

e. they match

15. a. $R_T \cong 900 \Omega$

b.
$$R_T = \frac{1}{\frac{1}{20 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega} + \frac{1}{91 \text{ k}\Omega}}$$

$$= \frac{1}{50 \times 10^{-6} \text{ S} + 100 \times 10^{-6} \text{ S} + 1 \times 10^{-3} \text{ S} + 10.99 \times 10^{-6} \text{ S}}$$

$$= \frac{1}{1.16 \times 10^{-3} \text{ S}} = \mathbf{862.07 \Omega}, \text{ very close}$$

c. I_3 the most, I_4 the least

- d. $I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{60 \text{ V}}{20 \text{ k}\Omega} = \mathbf{3.0 \text{ mA}}$, $I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{60 \text{ V}}{10 \text{ k}\Omega} = \mathbf{6 \text{ mA}}$
 $I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{60 \text{ V}}{1 \text{ k}\Omega} = \mathbf{60.0 \text{ mA}}$, $I_{R_4} = \frac{V_{R_4}}{R_4} = \frac{60 \text{ V}}{91 \text{ k}\Omega} = \mathbf{0.659 \text{ mA}}$
- e. $I_s = \frac{E}{R_T} = \frac{60 \text{ V}}{862.07 \text{ k}\Omega} = \mathbf{69.6 \text{ mA}}$
 $I_s = 3 \text{ mA} + 6 \text{ mA} + 60 \text{ mA} + 0.659 \text{ mA} = \mathbf{69.66 \text{ mA}}$ (checks)
- f. always greater
16. a. $R_T = 6 \Omega = \frac{(18 \Omega)(R_2)}{18 \Omega + R_2}$
 $108 \Omega + 6R_2 = 18R_2$
 $12R_2 = 108 \Omega$
 $R_2 = \frac{108 \Omega}{12} = \mathbf{9 \Omega}$
- b. $P = 81 \text{ W} = \frac{V^2}{R} = \frac{E^2}{R} = \frac{E^2}{9 \Omega}$
and $E^2 = (9)(81)$
or $E = \sqrt{729} = \mathbf{27 \text{ V}}$
17. a. $P = \frac{V^2}{R} = \frac{E^2}{R}$ and $E = \sqrt{PR} = \sqrt{(100 \text{ W})(4 \Omega)} = \sqrt{400} = \mathbf{20 \text{ V}}$
- b. $R_2 = \frac{E}{I_2} = \frac{20 \text{ V}}{2 \text{ A}} = \mathbf{10 \Omega}$
- c. $I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{20 \text{ V}}{10 \Omega} = \mathbf{2 \text{ A}}$
- d. $I_s = I_1 + I_2 + I_3 = 2 \text{ A} + 2 \text{ A} + \frac{20 \text{ V}}{4 \Omega} = 4 \text{ A} + 5 \text{ A} = \mathbf{9 \text{ A}}$
- e. $P_s = EI_s = (20 \text{ V})(9 \text{ A}) = \mathbf{180 \text{ W}}$
- f. $P_{R_1} = \frac{E^2}{R_1} = \frac{(20 \text{ V})^2}{10 \Omega} = \mathbf{40 \text{ W}}$, $P_{R_2} = \frac{E^2}{R_2} = \frac{(20 \text{ V})^2}{\left(\frac{20 \text{ V}}{2 \text{ A}}\right)} = \frac{400 \text{ W}}{10} = \mathbf{40 \text{ W}}$,
- g. $P_s = P_1 + P_2 + P_3$
 $180 \text{ W} = 40 \text{ W} + 40 \text{ W} + 100 \text{ W} = 180 \text{ W}$ (checks)

18.
$$I_3 = \frac{(20 \Omega)(10.8 \text{ A})}{20 \Omega + 4 \Omega} = \mathbf{9 \text{ A}}$$

$$E = V_{R_3} = I_3 R_3 = (9 \text{ A})(4 \Omega) = \mathbf{36 \text{ V}}$$

$$I_{R_1} = 12.3 \text{ A} - 10.8 \text{ A} = 1.5 \text{ A}$$

$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{36 \text{ V}}{1.5 \text{ A}} = \mathbf{24 \Omega}$$
19. a. $V = \mathbf{48 \text{ V}}$
- b. $I_2 = \frac{48 \text{ V}}{18 \text{ k}\Omega} = \mathbf{2.67 \text{ mA}}$
- c. $I_s = \frac{48 \text{ V}}{3 \text{ k}\Omega} + \frac{48 \text{ V}}{12 \text{ k}\Omega} + I_2 = 16 \text{ mA} + 4 \text{ mA} + 2.67 \text{ mA} = \mathbf{22.67 \text{ mA}}$
- d. $P = \frac{V^2}{R} = \frac{E^2}{R} = \frac{(48 \text{ V})^2}{12 \text{ k}\Omega} = \mathbf{192 \text{ mW}}$
20. a. $I_{R_2} \uparrow = 4 \text{ A} - 1 \text{ A} = 3 \text{ A}, R_2 = \frac{V_{R_2}}{I_2} = \frac{E}{I_2} = \frac{12 \text{ V}}{3 \text{ A}} = \mathbf{4 \Omega}$
- b. $R_3 = \frac{V_{R_3}}{I_3} = \frac{E}{I_3} = \frac{12 \text{ V}}{1 \text{ A}} = \mathbf{12 \Omega}$
- c. $I_1 \uparrow = \frac{12 \text{ V}}{2 \Omega} = 6 \text{ A}, I_s = I_1 + 4 \text{ A} = 6 \text{ A} + 4 \text{ A} = \mathbf{10 \text{ A}}$
21. –
22. a.
$$R_T = \frac{1}{\frac{1}{1 \text{ k}\Omega} + \frac{1}{4.7 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega}} = \frac{1}{1000 \times 10^{-6} \text{ S} + 212.77 \times 10^{-6} \text{ S} + 100 \times 10^{-6} \text{ S}}$$

$$= \frac{1}{1.313 \times 10^{-3} \text{ S}} = \mathbf{761.61 \Omega}$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{60 \text{ V}}{1 \text{ k}\Omega} = \mathbf{60 \text{ mA}}, I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{60 \text{ V}}{4.7 \text{ k}\Omega} = \mathbf{12.77 \text{ mA}}$$

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{60 \text{ V}}{10 \text{ k}\Omega} = \mathbf{6 \text{ mA}}$$
- b. $P_{R_1} = V_{R_1} \cdot I_{R_1} = (60 \text{ V})(60 \text{ mA}) = \mathbf{3.6 \text{ W}}$


$$P_{R_2} = V_{R_2} \cdot I_{R_2} = (60 \text{ V})(12.77 \text{ mA}) = \mathbf{766.2 \text{ mW}}$$

$$P_{R_3} = V_{R_3} \cdot I_{R_3} = (60 \text{ V})(6 \text{ mA}) = \mathbf{360 \text{ W}}$$

- c. $I_s = \frac{E}{R_T} = \frac{60 \text{ V}}{761.61 \Omega} = \mathbf{78.78 \text{ mA}}$
 $P_s = E_s I_s = (60 \text{ V})(78.78 \text{ mA}) = \mathbf{4.73 \text{ W}}$
d. $P_s = \mathbf{4.73 \text{ W}} = 3.6 \text{ W} + 766.2 \text{ mW} + 360 \text{ mW} = \mathbf{4.73 \text{ W}}$ (checks)
e. $R_1 =$ the smallest parallel resistor

23. a. $I_{\text{bulb}} = \frac{E}{R_{\text{bulb}}} = \frac{120 \text{ V}}{1.8 \text{ k}\Omega} = \mathbf{66.667 \text{ mA}}$
b. $R_T = \frac{R}{N} = \frac{1.8 \text{ k}\Omega}{8} = \mathbf{225 \Omega}$
c. $I_s = \frac{E}{R_T} = \frac{120 \text{ V}}{225 \Omega} = \mathbf{0.533 \text{ A}}$
d. $P = \frac{V^2}{R} = \frac{(120 \text{ V})^2}{1.8 \text{ k}\Omega} = \mathbf{8 \text{ W}}$
e. $P_s = 8(8 \text{ W}) = \mathbf{64 \text{ W}}$
f. none, I_s drops by 66.667 mA

24. Network redrawn:

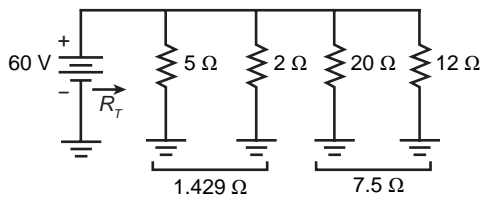

$$R_T = 1.429 \Omega \parallel 7.5 \Omega = 1.2 \Omega$$

$$P_s = \frac{E^2}{R_T} = \frac{(60 \text{ V})^2}{1.2 \Omega} = \mathbf{3 \text{ kW}}$$

25. a. $5 \times 60 \text{ W} = 300 \text{ W}$
 $I_{\text{bulbs}} = \frac{300 \text{ W}}{120 \text{ V}} = \mathbf{2.5 \text{ A}}$
 $I_{\text{micro}} = \frac{1200 \text{ W}}{120 \text{ V}} = \mathbf{10 \text{ A}}$
 $I_{\text{TV}} = \frac{320 \text{ W}}{120 \text{ V}} = \mathbf{2.67 \text{ A}}$
 $I_{\text{DVD}} = \frac{25 \text{ W}}{120 \text{ V}} = \mathbf{208.33 \text{ mA}}$
b. $I_s = \Sigma I = 2.5 \text{ A} + 10 \text{ A} + 2.67 \text{ A} + 208.33 \text{ mA} = \mathbf{15.38 \text{ A}}$
No

- c. $R_T = \frac{E}{I_s} = \frac{120 \text{ V}}{15.38 \text{ A}} = \mathbf{7.8 \Omega}$
- d. $P_s = E I_s = (120 \text{ V})(15.38 \text{ A}) = \mathbf{1,845.60 \text{ W}}$
- e. $P_s = 1845.60 \text{ W} = 300 \text{ W} + 1200 \text{ W} + 320 \text{ W} + 25 \text{ W} = \mathbf{1845 \text{ W}}$ (checks)
26. a. $8 \Omega \parallel 12 \Omega = 4.8 \Omega$, $4.8 \Omega \parallel 4 \Omega = 2.182 \Omega$
 $I_1 = \frac{24 \text{ V} + 8 \text{ V}}{2.182 \Omega} = \mathbf{14.67 \text{ A}}$
- b. $P_4 = \frac{V^2}{R} = \frac{(24 \text{ V} + 8 \text{ V})^2}{4 \Omega} = \mathbf{256 \text{ W}}$
- c. $I_2 = I_1 = \mathbf{14.67 \text{ A}}$
27. $I_s = 8 \text{ mA} + 6 \text{ mA} = \mathbf{14 \text{ mA}}$
 $I_2 = 6 \text{ mA} - 2 \text{ mA} = \mathbf{4 \text{ mA}}$
28. a. $\Sigma I_i = \Sigma I_o$
 $5 \text{ A} + 7 \text{ A} + 3 \text{ A} = 9 \text{ A} + I$
 $15 \text{ A} = 9 \text{ A} + I$
 $\mathbf{6 \text{ A} = I}$
- b. $\Sigma I_i = \Sigma I_o$
 $8 \text{ mA} = 2 \text{ mA} + I_1$
 $I_1 = 8 \text{ mA} - 2 \text{ mA} = \mathbf{6 \text{ mA}}$
 $\Sigma I_i = \Sigma I_o$
 $I_1 + 9 \text{ mA} = I_2$
 $I_2 = 6 \text{ mA} + 9 \text{ mA} = \mathbf{15 \text{ mA}}$
 $\Sigma I_i = \Sigma I_o$
 $I_2 = 10 \text{ mA} + I_3$
 $I_3 = 15 \text{ mA} - 10 \text{ mA} = \mathbf{5 \text{ mA}}$
29. a. $\Sigma I_i = \Sigma I_o$
 $8 \text{ A} = 3 \text{ A} + I_2$
 $I_2 = 8 \text{ A} - 3 \text{ A} = \mathbf{5 \text{ A}}$, $I_3 = \mathbf{3 \text{ A}}$
 $\Sigma I_i = \Sigma I_o$
 $I_2 + I_3 = I_4$
 $I_4 = 5 \text{ A} + 3 \text{ A} = \mathbf{8 \text{ A}}$
- b. $\Sigma I_i = \Sigma I_o$
 $I_s = 36 \text{ mA} + 4 \text{ mA} = \mathbf{40 \text{ mA}}$
 $\Sigma I_i = \Sigma I_o$
 $36 \text{ mA} = I_3 + 20 \text{ mA}$
 $I_3 = 36 \text{ mA} - 20 \text{ mA} = \mathbf{16 \text{ mA}}$
 $\Sigma I_i = \Sigma I_o$
 $4 \text{ mA} + 20 \text{ mA} = I_4$
 $I_4 = \mathbf{24 \text{ mA}}$
 $I_5 = I_s = \mathbf{40 \text{ mA}}$

30. $I_{R_2} = 5 \text{ mA} - 2 \text{ mA} = 3 \text{ mA}$
 $E = V_{R_2} = (3 \text{ mA})(4 \text{ k}\Omega) = \mathbf{12 \text{ V}}$
 $R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{12 \text{ V}}{(9 \text{ mA} - 5 \text{ mA})} = \frac{12 \text{ V}}{4 \text{ mA}} = \mathbf{3 \text{ k}\Omega}$
 $R_3 = \frac{V_{R_3}}{I_{R_3}} = \frac{12 \text{ V}}{2 \text{ mA}} = \mathbf{6 \text{ k}\Omega}$
 $R_T = \frac{E}{I_T} = \frac{12 \text{ V}}{9 \text{ mA}} = \mathbf{1.33 \text{ k}\Omega}$
31. a. $R_1 = \frac{E}{I_1} = \frac{10 \text{ V}}{2 \text{ A}} = \mathbf{5 \Omega}$
 $I_2 = I - I_1 = 3 \text{ A} - 2 \text{ A} = \mathbf{1 \text{ A}}$
 $R = \frac{E}{I_2} = \frac{10 \text{ V}}{1 \text{ A}} = \mathbf{10 \Omega}$
- b. $E = I_1 R_1 = (2 \text{ A})(6 \Omega) = \mathbf{12 \text{ V}}$
 $I_2 = \frac{E}{R_2} = \frac{12 \text{ V}}{9 \Omega} = \mathbf{1.33 \text{ A}}$
 $I_3 = \frac{P}{V} = \frac{12 \text{ W}}{12 \text{ V}} = \mathbf{1 \text{ A}}$
 $R_3 = \frac{E}{I_3} = \frac{12 \text{ V}}{1 \text{ A}} = \mathbf{12 \Omega}$
 $I = I_1 + I_2 + I_3 = 2 \text{ A} + 1.33 \text{ A} + 1 \text{ A} = \mathbf{4.33 \text{ A}}$
32. a. $I_1 = \frac{64 \text{ V}}{1 \text{ k}\Omega} = \mathbf{64 \text{ mA}}$
 $I_3 = \frac{64 \text{ V}}{4 \text{ k}\Omega} = \mathbf{16 \text{ mA}}$
 $I_s = I_1 + I_2 + I_3$
 $I_2 = I_s - I_1 - I_3 = 100 \text{ mA} - 64 \text{ mA} - 16 \text{ mA} = \mathbf{20 \text{ mA}}$
 $R = \frac{E}{I_2} = \frac{64 \text{ V}}{20 \text{ mA}} = \mathbf{3.2 \text{ k}\Omega}$
 $I = I_2 + I_3 = 20 \text{ mA} + 16 \text{ mA} = \mathbf{36 \text{ mA}}$

$$\text{b. } P = \frac{V_1^2}{R_1} \Rightarrow V_1 = \sqrt{PR_1} = \sqrt{(30 \text{ W})(30 \Omega)} = \mathbf{30 \text{ V}}$$

$$E = V_1 = \mathbf{30 \text{ V}}$$

$$I_1 = \frac{E}{R_1} = \frac{30 \text{ V}}{30 \Omega} = \mathbf{1 \text{ A}}$$

$$\text{Because } R_3 = R_2, I_3 = I_2, \text{ and } I_s = I_1 + I_2 + I_3 = I_1 + 2I_2$$

$$2 \text{ A} = 1 \text{ A} + 2I_2$$

$$I_2 = \frac{1}{2}(1 \text{ A}) = 0.5 \text{ A}$$

$$I_3 = \mathbf{0.5 \text{ A}}$$

$$R_2 = R_3 = \frac{E}{I_2} = \frac{30 \text{ V}}{0.5 \text{ A}} = \mathbf{60 \Omega}$$

$$P_{R_2} = I_2^2 R_2 = (0.5 \text{ A})^2 \cdot 60 \Omega = \mathbf{15 \text{ W}}$$

$$33. \quad I_2 = \frac{6 \Omega}{12 \Omega} I_1 = \frac{1}{2} I_1 = \frac{1}{2}(9 \text{ A}) = \mathbf{4.5 \text{ A}}$$

$$I_3 = \frac{6 \Omega}{2 \Omega} I_1 = 3I_1 = 3(9 \text{ A}) = \mathbf{27 \text{ A}}$$

$$I_4 = \frac{6 \Omega}{18 \Omega} I_1 = \frac{1}{3} I_1 = \frac{1}{3}(9 \text{ A}) = 3 \text{ A}$$

$$I_T = I_1 + I_2 + I_3 + I_4 = 9 \text{ A} + 4.5 \text{ A} + 27 \text{ A} + 3 \text{ A} = \mathbf{43.5 \text{ A}}$$

$$34. \quad \text{a. } I_1 = \frac{8 \text{ k}\Omega(20 \text{ mA})}{2 \text{ k}\Omega + 8 \text{ k}\Omega} = \mathbf{16 \text{ mA}}$$

$$I_2 = 20 \text{ mA} - 16 \text{ mA} = \mathbf{4 \text{ mA}}$$

$$\text{b. } I_{2.4 \text{ k}\Omega} = 2.5 \text{ A} = \frac{1 \text{ k}\Omega(I_T)}{1 \text{ k}\Omega + 2.4 \text{ k}\Omega} = \frac{1 \text{ k}\Omega(I_T)}{3.4 \text{ k}\Omega}$$

$$\text{and } I_T = \frac{3.4 \text{ k}\Omega(2.5 \text{ A})}{1 \text{ k}\Omega} = \mathbf{8.5 \text{ A}}$$

$$I_1 = I_T - 2.5 \text{ A} = 8.5 \text{ A} - 2.5 \text{ A} = \mathbf{6 \text{ A}}$$

$$35. \quad \text{a. } R_T = \frac{1}{\frac{1}{4 \Omega} + \frac{1}{8 \Omega} + \frac{1}{12 \Omega}} = \frac{1}{250 \times 10^{-3} \text{ S} + 125 \times 10^{-3} \text{ S} + 83.333 \times 10^{-3} \text{ S}}$$

$$= \frac{1}{458.333 \times 10^{-3}} = 2.18 \Omega$$

$$I_x = \frac{R_T}{R_x} I, \quad I_1 = \frac{2.18 \Omega}{4 \Omega} (6 \text{ A}) = \mathbf{3.27 \text{ A}}$$

$$I_2 = \frac{2.18 \Omega}{8 \Omega} (6 \text{ A}) = \mathbf{1.64 \text{ A}}$$

$$I_3 = \frac{2.18 \Omega}{12 \Omega} (6 \text{ A}) = \mathbf{1.09 \text{ A}}$$

$$I_4 = \mathbf{6 \text{ A}}$$

- b. $4\ \Omega \parallel 4\ \Omega = 2\ \Omega$

$$I_2 = \frac{20\ \Omega(8\ \text{A})}{20\ \Omega + 2\ \Omega + 8\ \Omega} = \frac{20\ \Omega(8\ \text{A})}{30\ \Omega} = \mathbf{5.33\ \text{A}}$$

$$I_1 = \frac{I_2}{2} = \frac{5.33\ \text{A}}{2} = \mathbf{2.67\ \text{A}}$$

$$I_3 = 8\ \text{A} - I_2 = 8\ \text{A} - 5.33\ \text{A} = \mathbf{2.67\ \text{A}}$$

$$I_4 = \mathbf{8\ \text{A}}$$
36. a. $I_1 \cong \frac{9}{10}(10\ \text{A}) = \mathbf{9\ \text{A}}$
- b. $I_1/I_2 = 10\ \Omega/1\ \Omega = 10$, $I_2 = \frac{I_1}{10} = \frac{9\ \text{A}}{10} \cong \mathbf{0.9\ \text{A}}$
- c. $I_1/I_3 = 1\ \text{k}\Omega/1\ \Omega = 1000$, $I_3 = I_1/1000 = 9\ \text{A}/1000 \cong \mathbf{9\ \text{mA}}$
- d. $I_1/I_4 = 100\ \text{k}\Omega/1\ \Omega = 100,000$, $I_4 = I_1/100,000 = 9\ \text{A}/100,000 \cong \mathbf{90\ \mu\text{A}}$
- e. very little effect, $1/100,000$
- f.
$$R_T = \frac{1}{\frac{1}{1\ \Omega} + \frac{1}{10\ \Omega} + \frac{1}{1\ \text{k}\Omega} + \frac{1}{100\ \text{k}\Omega}}$$

$$= \frac{1}{1\ \text{S} + 0.1\ \text{S} + 1 \times 10^{-3}\ \text{S} + 10 \times 10^{-6}\ \text{S}}$$

$$= \frac{1}{1.10\ \text{S}} = 0.91\ \Omega$$

$$I_x = \frac{R_T}{R_x} I, \quad I_1 = \frac{0.91\ \Omega}{1\ \Omega} (10\ \text{A}) = \mathbf{9.1\ \text{A}}$$
 excellent (9 A)
- g. $I_2 = \frac{0.91\ \Omega}{10\ \Omega} (10\ \text{A}) = \mathbf{0.91\ \text{A}}$ excellent (0.9 A)
- h. $I_3 = \frac{0.91\ \Omega}{1\ \text{k}\Omega} (10\ \text{A}) = \mathbf{9.1\ \text{mA}}$ excellent (9 mA)
- i. $I_4 = \frac{0.91\ \Omega}{100\ \text{k}\Omega} (10\ \text{A}) = \mathbf{91\ \mu\text{A}}$ excellent (90 μA)
37. a. CDR: $I_{36\Omega} = \frac{3\ \Omega I}{3\ \Omega + 36\ \Omega} = 1\ \text{A}$, $I = \frac{39\ \Omega(1\ \text{A})}{3\ \Omega} = \mathbf{13\ \text{A}} = I_2$

$$I_1 = I - 1\ \text{A} = 13\ \text{A} - 1\ \text{A} = \mathbf{12\ \text{A}}$$
- b. $I_3 = I = 24\ \text{mA}$, $V_{12\text{k}\Omega} = IR = (4\ \text{mA})(12\ \text{k}\Omega) = 48\ \text{V}$

$$I_2 = \frac{V}{R} = \frac{48\ \text{V}}{4\ \text{k}\Omega} = \mathbf{12\ \text{mA}}$$

$$I_1 = I - 4\ \text{mA} - I_2$$

$$= 24\ \text{mA} - 4\ \text{mA} - 12\ \text{mA}$$

$$= \mathbf{8\ \text{mA}}$$
38. a. $R = 3(2\ \text{k}\Omega) = \mathbf{6\ \text{k}\Omega}$

- b. $I_1 = \frac{6 \text{ k}\Omega(32 \text{ mA})}{6 \text{ k}\Omega + 2 \text{ k}} = \mathbf{24 \text{ mA}}$
 $I_2 = \frac{I_1}{3} = \frac{24 \text{ mA}}{3} = \mathbf{8 \text{ mA}}$
39. $84 \text{ mA} = I_1 + I_2 + I_3 = I_1 + 2I_1 + 2I_2 = I_1 + 2I_1 + 2(2I_1)$
 $84 \text{ mA} = I_1 + 2I_1 + 4I_1 = 7I_1$
and $I_1 = \frac{84 \text{ mA}}{7} = 12 \text{ mA}$
 $I_2 = 2I_1 = 2(12 \text{ mA}) = 24 \text{ mA}$
 $I_3 = 2I_2 = 2(24 \text{ mA}) = 48 \text{ mA}$
 $R_1 = \frac{V_{R_1}}{I_1} = \frac{24 \text{ V}}{12 \text{ mA}} = \mathbf{2 \text{ k}\Omega}$
 $R_2 = \frac{V_{R_2}}{I_2} = \frac{24 \text{ V}}{24 \text{ mA}} = \mathbf{1 \text{ k}\Omega}$
 $R_3 = \frac{V_{R_3}}{I_3} = \frac{24 \text{ V}}{48 \text{ mA}} = \mathbf{0.5 \text{ k}\Omega}$
40. a. $P_L = V_L I_L$
 $72 \text{ W} = 12 \text{ V} \cdot I_L$
 $I_L = \frac{72 \text{ W}}{12 \text{ V}} = 6 \text{ A}$
 $I_1 = I_2 = \frac{I_L}{2} = \frac{6 \text{ A}}{2} = \mathbf{3 \text{ A}}$
- b. $P_{\text{source}} = EI = (12 \text{ V})(3 \text{ A}) = \mathbf{36 \text{ W}}$
- c. $P_{s_1} + P_{s_2} = 36 \text{ W} + 36 \text{ W} = \mathbf{72 \text{ W}}$ (the same)
- d. $I_{\text{drain}} = \mathbf{6 \text{ A}}$ (twice as much)
41. $R_T = 8 \Omega \parallel 56 \Omega = 7 \Omega$
 $I_2 = I_3 = \frac{E}{R_T} = \frac{12 \text{ V}}{7 \Omega} = \mathbf{1.71 \text{ A}}$
 $I_1 = \frac{1}{2} I_2 = \frac{1}{2} (1.71 \text{ A}) = \mathbf{0.86 \text{ A}}$
42. $I_{8 \Omega} = \frac{16 \text{ V}}{8 \Omega} = 2 \text{ A}, \quad I = 5 \text{ A} - 2 \text{ A} = \mathbf{3 \text{ A}}$
 $I_R = 5 \text{ A} + 3 \text{ A} = 8 \text{ A}, \quad R = \frac{V_R}{I_R} = \frac{16 \text{ V}}{8 \text{ A}} = \mathbf{2 \Omega}$
43. a. $V_2 = \frac{22 \text{ k}\Omega(20 \text{ V})}{22 \text{ k}\Omega + 4.7 \text{ k}\Omega} = \mathbf{16.48 \text{ V}}$
- b. $R'_T = 11 \text{ M}\Omega \parallel 22 \text{ k}\Omega = 21.956 \text{ k}\Omega$

$$V_2 = \frac{21.956 \text{ k}\Omega(20 \text{ V})}{21.956 \text{ k}\Omega + 4.7 \text{ k}\Omega} = \mathbf{16.47 \text{ V}} \text{ (very close to ideal)}$$

c. $R_m = 20 \text{ V}[20,000 \text{ }\Omega/\text{V}] = 400 \text{ k}\Omega$
 $R'_T = 400 \text{ k}\Omega \parallel 22 \text{ k}\Omega = 20.853 \text{ k}\Omega$

$$V_2 = \frac{20.853 \text{ k}\Omega(20 \text{ V})}{20.853 \text{ k}\Omega + 4.7 \text{ k}\Omega} = \mathbf{16.32 \text{ V}} \text{ (still very close to ideal)}$$

d. a. $V_2 = \frac{200 \text{ k}\Omega(20 \text{ V})}{200 \text{ k}\Omega + 100 \text{ k}\Omega} = \mathbf{13.33 \text{ V}}$

b. $R'_T = 200 \text{ k}\Omega \parallel 11 \text{ M}\Omega = 196.429 \text{ k}\Omega$
 $V_2 = \frac{(196.429 \text{ k}\Omega)(20 \text{ V})}{196.429 \text{ k}\Omega + 100 \text{ k}\Omega} = \mathbf{13.25 \text{ V}}$ (very close to ideal)

c. $R_m = 400 \text{ k}\Omega$
 $R'_T = 400 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 133.333 \text{ k}\Omega$
 $V_2 = \frac{(133.333 \text{ k}\Omega)(20 \text{ V})}{133.333 \text{ k}\Omega + 100 \text{ k}\Omega} = \mathbf{11.43 \text{ V}}$ (a 1.824 V drop from $R_{\text{int}} = 11 \text{ M}\Omega$ level)

e. DMM level of 11 M Ω not a problem for most situations
 VOM level of 400 k Ω can be a problem for some situations.

44. a. $V_{ab} = \mathbf{20 \text{ V}}$

b. $V_{ab} = \frac{11 \text{ M}\Omega(20 \text{ V})}{11 \text{ M}\Omega + 1 \text{ M}\Omega} = \mathbf{18.33 \text{ V}}$

c. $R_m = 200 \text{ V}[20,000 \text{ }\Omega/\text{V}] = 4 \text{ M}\Omega$
 $V_{ab} = \frac{4 \text{ M}\Omega(20 \text{ V})}{4 \text{ M}\Omega + 1 \text{ M}\Omega} = 16.0 \text{ V}$ (significant drop from ideal)
 $R_m = 20 \text{ V}[20,000 \text{ }\Omega/\text{V}] = 400 \text{ k}\Omega$
 $V_{ab} = \frac{400 \text{ k}\Omega(20 \text{ V})}{400 \text{ k}\Omega + 1 \text{ M}\Omega} = \mathbf{5.71 \text{ V}}$ (significant error)

45. not operating properly, 6 k Ω not connected

$$R_T = \frac{6 \text{ V}}{3.5 \text{ mA}} = 1.71 \text{ k}\Omega$$

$$R_T = 3 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 1.71 \text{ k}\Omega$$

46. $V_{ab} = E + I_{4 \text{ k}\Omega} \cdot R_{4 \text{ k}\Omega}$

$$I_{4 \text{ k}\Omega} = \frac{12 \text{ V} - 4 \text{ V}}{1 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{8 \text{ V}}{5 \text{ k}\Omega} = 1.6 \text{ mA}$$

$$V_{ab} = 4 \text{ V} + (1.6 \text{ mA})(4 \text{ k}\Omega) = 4 \text{ V} + 6.4 \text{ V} = 10.4 \text{ V}$$

4 V supply connected in reverse so that

$$I = \frac{12 \text{ V} + 4 \text{ V}}{1 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{16 \text{ V}}{5 \text{ k}\Omega} = 3.2 \text{ mA}$$

and $V_{ab} = 12 \text{ V} - (3.2 \text{ mA})(1 \text{ k}\Omega) = 12 \text{ V} - 3.2 \text{ V} = 8.8 \text{ V}$ obtained