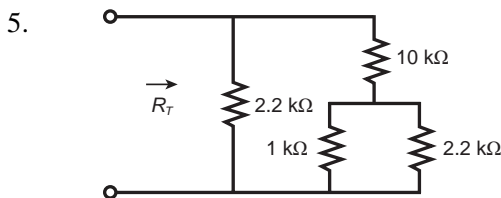


Chapter 7

1.
 - a. $R_1, R_2,$ and E are in series; R_3, R_4 and R_5 are in parallel
 - b. E and R_1 are in series; R_2, R_3 and R_4 are in parallel.
 - c. E and R_1 are in series; R_2, R_3 and R_4 are in parallel.
2.
 - a. E_1 and R_1 in series; R_2 and R_3 in parallel.
 - b. E and R_1 in series, $R_2, R_3,$ and R_4 in parallel.
 - c. E, R_1, R_4 and R_6 are in parallel; R_2 and R_5 are in parallel.
3.
 - a. $R_T = 4 \Omega + 10 \Omega \parallel (4 \Omega + 4 \Omega) + 4 \Omega = 4 \Omega + 10 \Omega \parallel 8 \Omega + 4 \Omega$
 $= 4 \Omega + 4.44 \Omega + 4 \Omega = \mathbf{12.44 \Omega}$
 - b. $R_T = 10 \Omega + \frac{10 \Omega}{2} = 10 \Omega + 5 \Omega = \mathbf{15 \Omega}$
 - c. $R_T = 6.8 \Omega + 10 \Omega \parallel (8.2 \Omega + 1.2 \Omega)$
 $= 6.8 \Omega + 10 \Omega \parallel 9.4 \Omega$
 $= 6.8 \Omega + 4.85 \Omega = \mathbf{11.65 \Omega}$
4.
 - a. $R_T = \frac{4 \Omega}{2} + 10 \Omega = 2 \Omega + 10 \Omega = \mathbf{12 \Omega}$
 - b. $R_T = \mathbf{10 \Omega}$
 - c. $R_T = 2 \Omega + 8 \Omega \parallel (4 \Omega + 6 \Omega \parallel 12 \Omega)$
 $= 2 \Omega + 8 \Omega \parallel (4 \Omega + 4 \Omega)$
 $= 2 \Omega + 8 \Omega \parallel 8 \Omega = 2 \Omega + 4 \Omega$
 $= \mathbf{6 \Omega}$



$$\begin{aligned}
 R_T &= 2.2 \text{ k}\Omega \parallel (10 \text{ k}\Omega + 1 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega) \\
 &= 2.2 \text{ k}\Omega \parallel (10 \text{ k}\Omega + 687.5 \Omega) \\
 &= 2.2 \text{ k}\Omega \parallel 10.687 \text{ k}\Omega = \mathbf{1.82 \text{ k}\Omega}
 \end{aligned}$$

6. $R_T = 7.2 \text{ k}\Omega = R_1 \parallel \left(R_1 + \frac{R_1}{2} \right) = R_1 \parallel 1.5R_1$
 so that $7.2 \text{ k}\Omega = \frac{(R_1)(1.5R_1)}{R_1 + 1.5R_1} = \frac{1.5R_1^2}{2.5R_1} = \frac{1.5R_1}{2.5}$
 and $R_1 = \frac{2.5(7.2 \text{ k}\Omega)}{1.5} = \mathbf{1.2 \text{ k}\Omega}$

7.
 - a. **yes**
 - b. $I_2 = I_s - I_1 = 10 \text{ A} - 4 \text{ A} = \mathbf{6 \text{ A}}$
 - c. **yes**
 - d. $V_3 = E - V_2 = 14 \text{ V} - 8 \text{ V} = \mathbf{6 \text{ V}}$
 - e. $R'_T = 4 \Omega \parallel 2 \Omega = 1.33 \Omega$, $R''_T = 4 \Omega \parallel 6 \Omega = 2.4 \Omega$
 $R_T = R'_T + R''_T = 1.33 \Omega + 2.4 \Omega = \mathbf{3.73 \Omega}$

$$f. \quad R_T' = R_T'' = \frac{20 \Omega}{2} = 10 \Omega, \quad R_T = R_T' + R_T'' = 10 \Omega + 10 \Omega = 20 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{20 \Omega} = 1 \text{ A}$$

$$g. \quad P_s = EI_s = P_{\text{absorbed}} = (20 \text{ V})(1 \text{ A}) = 20 \text{ W}$$

$$8. \quad a. \quad R_T' = R_1 \parallel R_2 = 10 \Omega \parallel 15 \Omega = 6 \Omega$$

$$R_T = R_T' \parallel (R_3 + R_4) = 6 \Omega \parallel (10 \Omega + 2 \Omega) = 6 \Omega \parallel 12 \Omega = 4 \Omega$$

$$b. \quad I_s = \frac{E}{R_T} = \frac{36 \text{ V}}{4 \Omega} = 9 \text{ A}, \quad I_1 = \frac{E}{R_T'} = \frac{36 \text{ V}}{6 \Omega} = 6 \text{ A}$$

$$I_2 = \frac{E}{R_3 + R_4} = \frac{36 \text{ V}}{10 \Omega + 2 \Omega} = \frac{36 \text{ V}}{12 \Omega} = 3 \text{ A}$$

$$I_1 = I_s - I_2 = 6 \text{ A} - 3 \text{ A} = 3 \text{ A}$$

$$c. \quad V_a = I_2 R_4 = (3 \text{ A})(2 \Omega) = 6 \text{ V}$$

$$9. \quad a. \quad R_T = 11 \Omega + \frac{27 \Omega}{3} = 11 \Omega + 9 \Omega = 20 \Omega$$


$$I_s = \frac{E}{R_T} = \frac{60 \text{ V}}{20 \Omega} = 3 \text{ A}$$

$$b. \quad V_1 = I_s R_1 = (3 \text{ A})(11 \Omega) = 33 \text{ V}$$

$$V_3 = I_s \left(\frac{27 \Omega}{3} \right) = (3 \text{ A})(9 \Omega) = 27 \text{ V}$$

$$\text{or } V_3 = E - V_1 = 60 \text{ V} - 33 \text{ V} = 27 \text{ V}$$

10. Redrawn:

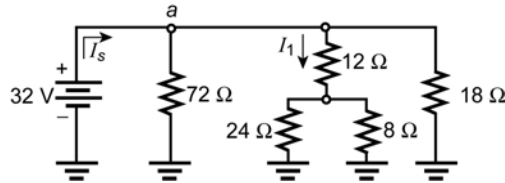

$$a. \quad V_a = 32 \text{ V}$$

$$8 \Omega \parallel 24 \Omega = 6 \Omega$$

$$V_b = \frac{6 \Omega (32 \text{ V})}{6 \Omega + 12 \Omega} = 10.67 \text{ V}$$


$$b. \quad I_1 = \frac{32 \text{ V}}{12 \Omega + 6 \Omega} = \frac{32 \text{ V}}{18 \Omega} = 1.78 \text{ A}$$

$$R_T = 72 \Omega \parallel \underbrace{18 \Omega \parallel 18 \Omega}_{9 \Omega} = 8.12 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{32 \text{ V}}{8.12 \Omega} = 3.94 \text{ A}$$

$$11. \quad a. \quad V_a = 36 \text{ V}, \quad V_b = 60 \text{ V}, \quad V_c = \frac{5 \text{ k}\Omega (60 \text{ V})}{5 \text{ k}\Omega + 10 \text{ k}\Omega} = 20 \text{ V}$$

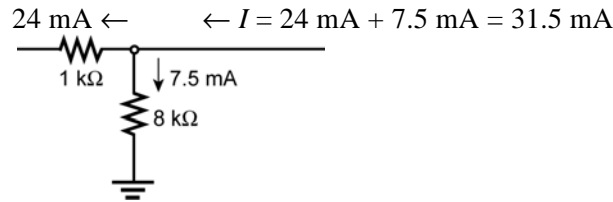b. $I_1 = \frac{60 \text{ V} - 36 \text{ V}}{1 \text{ k}\Omega} = 24 \text{ mA}$,
 $I_{8\text{k}\Omega} = \frac{60 \text{ V}}{8 \text{ k}\Omega} = 7.5 \text{ mA}$, $I_{10\text{k}\Omega} = \frac{60 \text{ V}}{15 \text{ k}\Omega} = 4 \text{ mA}$



$\leftarrow I_2 = 31.5 \text{ mA} + 4 \text{ mA} = 35.5 \text{ mA}$

12. a. $R'_T = 1.2 \text{ k}\Omega + 6.8 \text{ k}\Omega = 8 \text{ k}\Omega$, $R''_T = 2 \text{ k}\Omega \parallel R'_T = 2 \text{ k}\Omega \parallel 8 \text{ k}\Omega = 1.6 \text{ k}\Omega$
 $R'''_T = R''_T + 2.4 \text{ k}\Omega = 1.6 \text{ k}\Omega + 2.4 \text{ k}\Omega = 4 \text{ k}\Omega$
 $R_T = 1 \text{ k}\Omega \parallel R'''_T = 1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$

b. $I_s = \frac{E}{R_T} = \frac{48 \text{ V}}{0.8 \text{ k}\Omega} = 60 \text{ mA}$

c. $V = \frac{R'_T E}{R'_T + 2.4 \text{ k}\Omega} = \frac{(1.6 \text{ k}\Omega)(48 \text{ V})}{1.6 \text{ k}\Omega + 2.4 \text{ k}\Omega} = 19.2 \text{ V}$


13. $R_T = 2R \parallel 2R \parallel (R + R) = 2R \parallel 2R \parallel 2R = \frac{2R}{3}$

$R_T = \frac{E}{I} = \frac{120 \text{ V}}{8 \text{ A}} = 15 \Omega$

$15 \Omega = \frac{2R}{3}$ and $R = \frac{3}{2}(15 \Omega) = 22.5 \Omega$

$2R = 45 \Omega$

14.

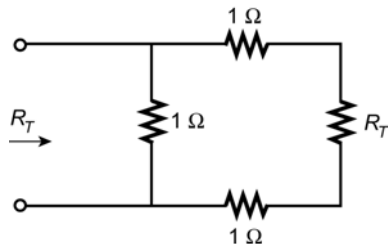

$R_T = 1 \Omega \parallel (1 \Omega + 1 \Omega + R_T) = 1 \Omega \parallel (2 \Omega + R_T)$

$= \frac{2 \Omega + R_T}{1 \Omega + 2 \Omega + R_T} = \frac{2 \Omega + R_T}{3 \Omega + R_T}$

$R_T(3 \Omega + R_T) = 2 \Omega + R_T$

$3R_T + R_T^2 = 2 \Omega + R_T$

$R_T^2 + 2R_T - 2 \Omega = 0$

$R_T = \frac{-2 \pm \sqrt{(2)^2 - 4(1)(-2)}}{2}$

$= \frac{-2 \pm \sqrt{4+8}}{2} = \frac{2 \pm \sqrt{12}}{2} = \frac{-2 \pm 3.464}{2}$

$R_T = -1 \pm 1.732 = 0.732 \Omega$ or -2.732Ω

Since $R_T < 1 \Omega$ and positive choose $R_T = 0.732 \Omega$

15. a. $R_T = (R_1 \parallel R_2 \parallel R_3) \parallel (R_6 + R_4 \parallel R_5)$
 $= (12 \text{ k}\Omega \parallel 12 \text{ k}\Omega \parallel 3 \text{ k}\Omega) \parallel (10.4 \text{ k}\Omega + 9 \text{ k}\Omega \parallel 6 \text{ k}\Omega)$
 $= (6 \text{ k}\Omega \parallel 3 \text{ k}\Omega) \parallel (10.4 \text{ k}\Omega + 3.6 \text{ k}\Omega)$
 $= 2 \text{ k}\Omega \parallel 14 \text{ k}\Omega = 1.75 \text{ k}\Omega$
 $I_s = \frac{E}{R_T} = \frac{28 \text{ V}}{1.75 \text{ k}\Omega} = \mathbf{16 \text{ mA}}, \quad I_2 = \frac{E}{R_2} = \frac{28 \text{ V}}{12 \text{ k}\Omega} = \mathbf{2.33 \text{ mA}}$
 $R' = R_1 \parallel R_2 \parallel R_3 = 2 \text{ k}\Omega$
 $R'' = R_6 + R_4 \parallel R_5 = 14 \text{ k}\Omega$
 $I_6 = \frac{R'(I_s)}{R' + R''} = \frac{2 \text{ k}\Omega(16 \text{ mA})}{2 \text{ k}\Omega + 14 \text{ k}\Omega} = \mathbf{2 \text{ mA}}$

b. $V_1 = E = \mathbf{28 \text{ V}}$
 $R' = R_4 \parallel R_5 = 6 \text{ k}\Omega \parallel 9 \text{ k}\Omega = 3.6 \text{ k}\Omega$
 $V_5 = I_6 R' = (2 \text{ mA})(3.6 \text{ k}\Omega) = \mathbf{7.2 \text{ V}}$

c. $P = \frac{V_{R_3}^2}{R_3} = \frac{(28 \text{ V})^2}{3 \text{ k}\Omega} = \mathbf{261.33 \text{ mW}}$


16. a. $I_1 \downarrow = \frac{24 \text{ V}}{4 \Omega} = \mathbf{6 \text{ A}}; \quad V_{R_2} = 24 \text{ V} - 8 \text{ V} = 16 \text{ V}, \quad I_2 \downarrow = V_{R_2} / R_2 = 16 \text{ V} / 2 \Omega = \mathbf{8 \text{ A}}$
 $I_1 \downarrow = \frac{8 \text{ V}}{10 \Omega} = \mathbf{0.8 \text{ A}}, \quad I = I_1 + I_2 = 6 \text{ A} + 8 \text{ A} = \mathbf{14 \text{ A}}$

17. $I_1 = \frac{20 \text{ V}}{47 \Omega} = \mathbf{425.5 \text{ mA}}$
 $I_2 = \frac{14 \text{ V}}{160 \Omega \parallel 270 \Omega} = \frac{14 \text{ V}}{100.47 \Omega} = \mathbf{139.35 \text{ mA}}$

18. a. $R' = R_4 + R_5 = 14 \Omega + 6 \Omega = 20 \Omega$
 $R'' = R_2 \parallel R' = 20 \Omega \parallel 20 \Omega = 10 \Omega$
 $R''' = R'' + R_1 = 10 \Omega + 10 \Omega = 20 \Omega$
 $R_T = R_3 \parallel R''' = 5 \Omega \parallel 20 \Omega = \mathbf{4 \Omega}$
 $I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{4 \Omega} = \mathbf{5 \text{ A}}$
 $I_1 = \frac{20 \text{ V}}{R_1 + R''} = \frac{20 \text{ V}}{10 \Omega + 10 \Omega} = \frac{20 \text{ V}}{20 \Omega} = \mathbf{1 \text{ A}}$
 $I_3 = \frac{20 \text{ V}}{5 \Omega} = \mathbf{4 \text{ A}}$
 $I_4 = \frac{I_1}{2} = (\text{since } R' = R_2) = \frac{1 \text{ A}}{2} = \mathbf{0.5 \text{ A}}$

- b. $V_a = I_3 R_3 - I_4 R_5 = (4 \text{ A})(5 \Omega) - (0.5 \text{ A})(6 \Omega) = 20 \text{ V} - 3 \text{ V} = \mathbf{17 \text{ V}}$
 $V_{bc} = \left(\frac{I_1}{2} \right) R_2 = (0.5 \text{ A})(20 \Omega) = \mathbf{10 \text{ V}}$
19. a. $I_1 = \frac{E_1 - E_2}{R_1} = \frac{20 \text{ V} - 15 \text{ V}}{3 \Omega} = \mathbf{1.67 \text{ A}}$
- b. $I_2 = \frac{E_2}{R_2 + R_3 \parallel R_5} = \frac{15 \text{ V}}{3 \Omega + 6 \Omega \parallel 6 \Omega} = \frac{15 \text{ V}}{3 \Omega + 3 \Omega} = \frac{15 \text{ V}}{6 \Omega} = \mathbf{2.5 \text{ A}}$
 $I_3 = \frac{1}{2} I_2 = \frac{1}{2} (2.5 \text{ A}) = \mathbf{1.25 \text{ A}}$
- c. $V_a = E_2 - I_2 R_2 = 15 \text{ V} - (2.5 \text{ A})(3 \Omega) = 15 \text{ V} - 7.5 \text{ V} = \mathbf{7.5 \text{ V}}$
20. a. $I_E = \frac{V_E}{R_E} = \frac{2 \text{ V}}{1 \text{ k}\Omega} = \mathbf{2 \text{ mA}}$
 $I_C = I_E = \mathbf{2 \text{ mA}}$
- b. $I_B = \frac{V_{R_B}}{R_B} = \frac{V_{CC} - (V_{BE} + V_E)}{R_B} = \frac{8 \text{ V} - (0.7 \text{ V} + 2 \text{ V})}{220 \text{ k}\Omega}$
 $= \frac{8 \text{ V} - 2.7 \text{ V}}{220 \text{ k}\Omega} = \frac{5.3 \text{ V}}{220 \text{ k}\Omega} = \mathbf{24 \mu\text{A}}$
- c. $V_B = V_{BE} + V_E = \mathbf{2.7 \text{ V}}$
 $V_C = V_{CC} - I_C R_C = 8 \text{ V} - (2 \text{ mA})(2.2 \text{ k}\Omega) = 8 \text{ V} - 4.4 \text{ V} = \mathbf{3.6 \text{ V}}$
- d. $V_{CE} = V_C - V_E = 3.6 \text{ V} - 2 \text{ V} = \mathbf{1.6 \text{ V}}$
 $V_{BC} = V_B - V_C = 2.7 \text{ V} - 3.6 \text{ V} = \mathbf{-0.9 \text{ V}}$
21. a. $I_2 = \frac{E_1}{R_2 + R_3} = \frac{2 \text{ V}}{4 \Omega + 18 \Omega} = \frac{22 \text{ V}}{22 \Omega} = \mathbf{1 \text{ A}}$
- b. $+22 \text{ V} + V_1 - 22 \text{ V} = 0, V_1 = 22 \text{ V} - 22 \text{ V} = \mathbf{0 \text{ V}}$
- c. $I_1 = I_2 + \frac{V_1}{R_1} = 1 \text{ A} + \frac{0 \text{ V}}{R_1} = \mathbf{1 \text{ A}}$

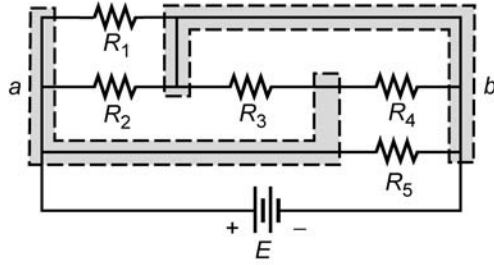22. a. All resistors in parallel (between terminals a & b)



$$\begin{aligned}
 R_T &= 16 \Omega \parallel 16 \Omega \parallel 8 \Omega \parallel 4 \Omega \parallel 32 \Omega \\
 &= 8 \Omega \parallel 8 \Omega \parallel 4 \Omega \parallel 32 \Omega \\
 &= 4 \Omega \parallel 4 \Omega \parallel 32 \Omega \\
 &= 2 \Omega \parallel 32 \Omega = \mathbf{1.88 \Omega}
 \end{aligned}$$

- b. All in parallel. Therefore, $V_1 = V_4 = E = \mathbf{32 \text{ V}}$

c. $I_3 = V_3/R_3 = 32 \text{ V}/4 \Omega = \mathbf{8 \text{ A} \leftarrow}$

d. $I_s = I_1 + I_2 + I_3 + I_4 + I_5$

$$\begin{aligned}
 &= \frac{32 \text{ V}}{16 \Omega} + \frac{32 \text{ V}}{8 \Omega} + \frac{32 \text{ V}}{4 \Omega} + \frac{32 \text{ V}}{32 \Omega} + \frac{32 \text{ V}}{16 \Omega} \\
 &= 2 \text{ A} + 4 \text{ A} + 8 \text{ A} + 1 \text{ A} + 2 \text{ A} \\
 &= 17 \text{ A} \\
 R_T &= \frac{E}{I_s} = \frac{32 \text{ V}}{17 \text{ A}} = \mathbf{1.88 \Omega} \text{ as above}
 \end{aligned}$$

23. a. $V_a = -6 \text{ V}$, $V_b = -20 \text{ V}$

b. $I_{5 \Omega} \downarrow = \frac{20 \text{ V}}{5 \Omega} = 4 \text{ A}$

$$I_{2 \Omega} \rightarrow = \frac{V_{ab}}{2 \Omega} = \frac{14 \text{ V}}{2 \Omega} = 7 \text{ A}$$

$$I_{3 \Omega} \uparrow = \frac{6 \text{ V}}{3 \Omega} = 2 \text{ A}$$

$$I_{3 \Omega} = I_{2 \Omega} + I_{6 \text{V}} \uparrow, I_{6 \text{V}} = I_{3 \Omega} - I_{2 \Omega} = 2 \text{ A} - 7 \text{ A} = -5 \text{ A}$$

$$I + I_{6 \text{V}} = I_{5 \Omega}, I = I_{5 \Omega} - I_{6 \text{V}} = 4 \text{ A} - (-5 \text{ A}) = \mathbf{9 \text{ A}}$$

c. $V_{ab} = V_a - V_b = (-6 \text{ V}) - (-20 \text{ V}) = -6 \text{ V} + 20 \text{ V} = \mathbf{+14 \text{ V}}$

24. a. Applying Kirchoff's voltage law in the CCW direction in the upper "window":

$$\begin{aligned}
 +18 \text{ V} + 20 \text{ V} - V_{8\Omega} &= 0 \\
 V_{8\Omega} &= 38 \text{ V} \\
 I_{8\Omega} &= \frac{38 \text{ V}}{8 \Omega} = 4.75 \text{ A} \\
 I_{3\Omega} &= \frac{18 \text{ V}}{3 \Omega + 6 \Omega} = \frac{18 \text{ V}}{9 \Omega} = 2 \text{ A}
 \end{aligned}$$

$$\text{KCL: } I_{18\text{V}} = 4.75 \text{ A} + 2 \text{ A} = \mathbf{6.75 \text{ A}}$$

b. $V = (I_{3\Omega})(6 \Omega) + 20 \text{ V} = (2 \text{ A})(6 \Omega) + 20 \text{ V} = 12 \text{ V} + 20 \text{ V} = \mathbf{32 \text{ V}}$

25. $I_2 R_2 = I_3 R_3$ and $I_2 = \frac{I_3 R_3}{R_2} = \frac{2 R_3}{20} = \frac{R_3}{10}$ (since the voltage across parallel elements is the same)

$$I_1 = I_2 + I_3 = \frac{R_3}{10} + 2$$


$$\text{KVL: } 120 = I_1 12 + I_3 R_3 = \left(\frac{R_3}{10} + 2 \right) 12 + 2 R_3$$

$$\text{and } 120 = 1.2 R_3 + 24 + 2 R_3$$

$$3.2 R_3 = 96 \Omega$$

$$R_3 = \frac{96 \Omega}{3.2} = \mathbf{30 \Omega}$$

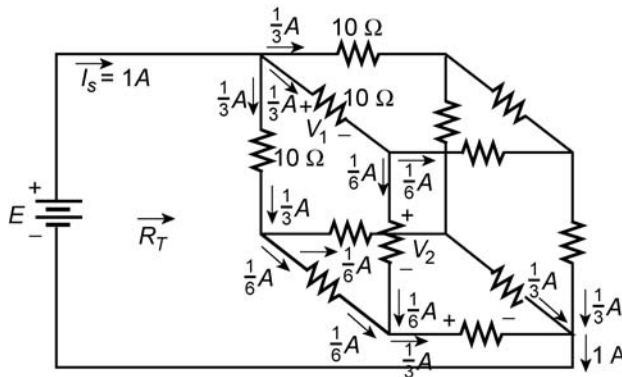26. Assuming $I_s = 1 \text{ A}$, the current I_s will divide as determined by the load appearing in each branch. Since balanced I_s will split equally between all three branches.



$$V_1 = \left(\frac{1}{3} \text{ A} \right) (10 \Omega) = \frac{10}{3} \text{ V}$$

$$V_2 = \left(\frac{1}{6} \text{ A} \right) (10 \Omega) = \frac{10}{6} \text{ V}$$

$$V_3 = \left(\frac{1}{3} \text{ A} \right) (10 \Omega) = \frac{10}{3} \text{ V}$$

$$E = V_1 + V_2 + V_3 = \frac{10}{3} \text{ V} + \frac{10}{6} \text{ V} + \frac{10}{3} \text{ V} = 8.33 \text{ V}$$

$$R_T = \frac{E}{I} = \frac{8.33 \text{ V}}{1 \text{ A}} = \mathbf{8.33 \Omega}$$

27. a. $R'_T = R_5 \parallel (R_6 + R_7) = 6 \Omega \parallel 3 \Omega = 2 \Omega$
 $R''_T = R_3 \parallel (R_4 + R'_T) = 4 \Omega \parallel (2 \Omega + 2 \Omega) = 2 \Omega$
 $R_T = R_1 + R_2 + R''_T = 3 \Omega + 5 \Omega + 2 \Omega = 10 \Omega$
 $I = \frac{240 \text{ V}}{10 \Omega} = \mathbf{24 \text{ A}}$

b. $I_4 = \frac{4 \Omega(I)}{4 \Omega + 4} = \frac{4 \Omega(24 \text{ A})}{8} = 12 \text{ A}$
 $I_7 = \frac{6 \Omega(12 \text{ A})}{6 \Omega + 3} = \frac{72 \text{ A}}{9} = \mathbf{8 \text{ A}}$

c. $V_3 = I_3 R_3 = (I - I_4) R_3 = (24 \text{ A} - 12 \text{ A}) 4 \Omega = \mathbf{48 \text{ V}}$
 $V_5 = I_5 R_5 = (I_4 - I_7) R_5 = (4 \text{ A}) 6 \Omega = \mathbf{24 \text{ V}}$
 $V_7 = I_7 R_7 = (8 \text{ A}) 2 \Omega = \mathbf{16 \text{ V}}$

d. $P = I_7^2 R_7 = (8 \text{ A})^2 2 \Omega = \mathbf{128 \text{ W}}$
 $P = EI = (240 \text{ V})(24 \text{ A}) = \mathbf{5760 \text{ W}}$

28. a. $R'_T = R_4 \parallel (R_6 + R_7 + R_8) = 2 \Omega \parallel 7 \Omega = 1.56 \Omega$
 $R''_T = R_2 \parallel (R_3 + R_5 + R'_T) = 2 \Omega \parallel (4 \Omega + 1 \Omega + 1.56 \Omega) = 1.53 \Omega$
 $R_T = R_1 + R''_T = 4 \Omega + 1.53 \Omega = \mathbf{5.53 \Omega}$

b. $I = 40 \text{ V} / 5.53 \Omega = \mathbf{7.23 \text{ A}}$

c. $I_3 = \frac{2 \Omega(I)}{2 \Omega + 6.56} = \frac{2 \Omega(7.23 \text{ A})}{2 \Omega + 6.56 \Omega} = 1.69 \text{ A}$
 $I_7 = \frac{2 \Omega(1.69 \text{ A})}{2 \Omega + 7 \Omega} = 0.375 \text{ mA}$
 $P_{R_7} = I^2 R = (0.375 \text{ A})^2 2 \Omega = \mathbf{0.281 \text{ W}}$

29. a. $E = (40 \text{ mA})(1.6 \text{ k}\Omega) = \mathbf{64 \text{ V}}$

b. $R_{L_2} = \frac{48 \text{ V}}{12 \text{ mA}} = \mathbf{4 \text{ k}\Omega}$
 $R_{L_3} = \frac{24 \text{ V}}{8 \text{ mA}} = \mathbf{3 \text{ k}\Omega}$

c. $I_{R_1} = 72 \text{ mA} - 40 \text{ mA} = 32 \text{ mA}$
 $I_{R_2} = 32 \text{ mA} - 12 \text{ mA} = 20 \text{ mA}$
 $I_{R_3} = 20 \text{ mA} - 8 \text{ mA} = 12 \text{ mA}$

$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{64 \text{ V} - 48 \text{ V}}{32 \text{ mA}} = \frac{16 \text{ V}}{32 \text{ mA}} = \mathbf{0.5 \text{ k}\Omega}$$

$$R_2 = \frac{V_{R_2}}{I_{R_2}} = \frac{48 \text{ V} - 24 \text{ V}}{20 \text{ mA}} = \frac{24 \text{ V}}{20 \text{ mA}} = \mathbf{1.2 \text{ k}\Omega}$$

$$R_3 = \frac{V_{R_3}}{I_{R_3}} = \frac{24 \text{ V}}{12 \text{ mA}} = \mathbf{2 \text{ k}\Omega}$$

30. $I_{R_1} = 40 \text{ mA}$

$$I_{R_2} = 40 \text{ mA} - 10 \text{ mA} = 30 \text{ mA}$$

$$I_{R_3} = 30 \text{ mA} - 20 \text{ mA} = 10 \text{ mA}$$

$$I_{R_5} = 40 \text{ mA}$$

$$I_{R_4} = 40 \text{ mA} - 4 \text{ mA} = 36 \text{ mA}$$

$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{120 \text{ V} - 100 \text{ V}}{40 \text{ mA}} = \frac{20 \text{ V}}{40 \text{ mA}} = \mathbf{0.5 \text{ k}\Omega}$$

$$R_2 = \frac{V_{R_2}}{I_{R_2}} = \frac{100 \text{ V} - 40 \text{ V}}{30 \text{ mA}} = \frac{60 \text{ V}}{30 \text{ mA}} = \mathbf{2 \text{ k}\Omega}$$

$$R_3 = \frac{V_{R_3}}{I_{R_3}} = \frac{40 \text{ V}}{10 \text{ mA}} = \mathbf{4 \text{ k}\Omega}$$

$$R_4 = \frac{V_{R_4}}{I_{R_4}} = \frac{36 \text{ V}}{36 \text{ mA}} = \mathbf{1 \text{ k}\Omega}$$

$$R_5 = \frac{V_{R_5}}{I_{R_5}} = \frac{60 \text{ V} - 36 \text{ V}}{40 \text{ mA}} = \frac{24 \text{ V}}{40 \text{ mA}} = \mathbf{0.6 \text{ k}\Omega}$$

$$P_1 = I_1^2 R_1 = (40 \text{ mA})^2 0.5 \text{ k}\Omega = \mathbf{0.8 \text{ W}}$$
 (1 watt resistor)

$$P_2 = I_2^2 R_2 = (30 \text{ mA})^2 2 \text{ k}\Omega = \mathbf{1.8 \text{ W}}$$
 (2 watt resistor)


$$P_3 = I_3^2 R_3 = (10 \text{ mA})^2 4 \text{ k}\Omega = \mathbf{0.4 \text{ W}}$$
 (1/2 watt or 1 watt resistor)

$$P_4 = I_4^2 R_4 = (36 \text{ mA})^2 1 \text{ k}\Omega = \mathbf{1.3 \text{ W}}$$
 (2 watt resistor)

$$P_5 = I_5^2 R_5 = (40 \text{ mA})^2 0.6 \text{ k}\Omega = \mathbf{0.96 \text{ W}}$$
 (1 watt resistor)

All power levels less than **2 W**. Four less than **1 W**.

31.

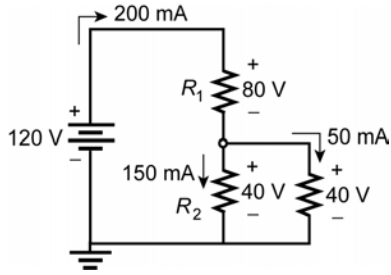

$$R_1 = \frac{80 \text{ V}}{200 \text{ mA}} = 400 \Omega \Rightarrow \mathbf{390 \Omega}$$

$$R_2 = \frac{40 \text{ V}}{150 \text{ mA}} = 266.67 \Omega \Rightarrow \mathbf{270 \Omega}$$

32. a. **yes**, $R_L \gg R_{\max}$ (potentiometer)

$$\text{b. VDR: } V_{R_2} = 3 \text{ V} = \frac{R_2(12 \text{ V})}{R_1 + R_2} = \frac{R_2(12 \text{ V})}{1 \text{ k}\Omega}$$

$$R_2 = \frac{3 \text{ V}(1 \text{ k}\Omega)}{12 \text{ V}} = 0.25 \text{ k}\Omega = \mathbf{250 \Omega}$$

$$R_1 = 1 \text{ k}\Omega - 0.25 \text{ k}\Omega = 0.75 \text{ k}\Omega = \mathbf{750 \Omega}$$

c. $V_{R_1} = E - V_L = 12 \text{ V} - 3 \text{ V} = 9 \text{ V}$ (Chose V_{R_1} rather than $V_{R_2 \parallel R_L}$ since numerator of VDR

$$V_{R_1} = 9 \text{ V} = \frac{R_1(12 \text{ V})}{R_1 + (R_2 \parallel R_L)} \quad \text{equation "cleaner"}$$

$$9R_1 + 9(R_2 \parallel R_L) = 12R_1$$

$$\left. \begin{aligned} R_1 &= 3(R_2 \parallel R_L) \\ R_1 + R_2 &= 1 \text{ k}\Omega \end{aligned} \right\} 2 \text{ eq. } 2 \text{ unk. } (R_L = 10 \text{ k}\Omega)$$

$$R_1 = \frac{3R_2R_L}{R_2 + R_L} \Rightarrow \frac{3R_2 \cdot 10 \text{ k}\Omega}{R_2 + 10 \text{ k}\Omega}$$

$$\text{and } R_1(R_2 + 10 \text{ k}\Omega) = 30 \text{ k}\Omega R_2$$

$$R_1R_2 + 10 \text{ k}\Omega R_1 = 30 \text{ k}\Omega R_2$$

$$R_1 + R_2 = 1 \text{ k}\Omega: (1 \text{ k}\Omega - R_2)R_2 + 10 \text{ k}\Omega (1 \text{ k}\Omega - R_2) = 30 \text{ k}\Omega R_2$$

$$R_2^2 + 39 \text{ k}\Omega R_2 - 10 \text{ k}\Omega^2 = 0$$

$$R_2 = 0.255 \text{ k}\Omega, -39.255 \text{ k}\Omega$$

$$R_2 = \mathbf{255 \Omega}$$

$$R_1 = 1 \text{ k}\Omega - R_2 = \mathbf{745 \Omega}$$

33. a.
$$V_{ab} = \frac{80 \Omega(40 \text{ V})}{100 \Omega} = \mathbf{32 \text{ V}}$$

$$V_{bc} = 40 \text{ V} - 32 \text{ V} = \mathbf{8 \text{ V}}$$

b. $80 \Omega \parallel 1 \text{ k}\Omega = 74.07 \Omega$

$20 \Omega \parallel 10 \text{ k}\Omega = 19.96 \Omega$

$$V_{ab} = \frac{74.07 \Omega(40 \text{ V})}{74.07 \Omega + 19.96 \Omega} = \mathbf{31.51 \text{ V}}$$

$$V_{bc} = 40 \text{ V} - 31.51 \text{ V} = \mathbf{8.49 \text{ V}}$$

c.
$$P = \frac{(31.51 \text{ V})^2}{80 \Omega} + \frac{(8.49 \text{ V})^2}{20 \Omega} = 12.411 \text{ W} + 3.604 \text{ W} = \mathbf{16.02 \text{ W}}$$

$$d. \quad P = \frac{(32 \text{ V})^2}{80 \Omega} + \frac{(8 \text{ V})^2}{20 \Omega} = 12.8 \text{ W} + 3.2 \text{ W} = \mathbf{16 \text{ W}}$$

The applied loads dissipate less than 20 mW of power.

$$34. \quad I = \frac{12 \text{ V}}{10 \text{ k}\Omega} = \mathbf{1.2 \text{ mA}}$$

$$V_{ab} = V_a - V_b = 12 \text{ V} - (-18 \text{ V}) = \mathbf{30 \text{ V}}$$


$$35. \quad 36 \text{ k}\Omega \parallel 6 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 3.6 \text{ k}\Omega$$

$$V = \frac{3.6 \text{ k}\Omega(45 \text{ V})}{3.6 \text{ k}\Omega + 6 \text{ k}\Omega} = 16.88 \text{ V} \neq 27 \text{ V}. \text{ Therefore, } \mathbf{not} \text{ operating properly!}$$

6 kΩ resistor "open"

$$R' = 12 \text{ k}\Omega \parallel 36 \text{ k}\Omega = 9 \text{ k}\Omega, \quad V = \frac{R'(45 \text{ V})}{R' + 6 \text{ k}\Omega} = \frac{9 \text{ k}\Omega(45 \text{ V})}{9 \text{ k}\Omega + 6 \text{ k}\Omega} = \mathbf{27 \text{ V}}$$

36. Network redrawn:

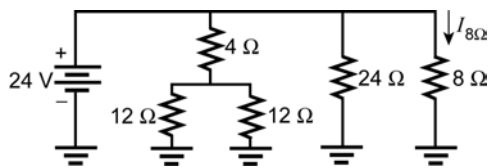

$$I_{8\Omega} = I_{6\Omega} = \frac{24 \text{ V}}{8 \Omega} = 3 \text{ A}$$

$$P_{6\Omega} = I^2 R = (3 \text{ A})^2 \cdot 6 \Omega = \mathbf{54 \text{ W}}$$

$$37. \quad a. \quad R_{10} + R_{11} \parallel R_{12} = 1 \Omega + 2 \Omega \parallel 2 \Omega = 2 \Omega$$

$$R_4 \parallel (R_5 + R_6) = 10 \Omega \parallel 10 \Omega = 5 \Omega$$

$$R_1 + R_2 \parallel (R_3 + 5 \Omega) = 3 \Omega + 6 \Omega \parallel 6 \Omega = 6 \Omega$$

$$R_T = 2 \Omega \parallel 3 \Omega \parallel 6 \Omega = 2 \Omega \parallel 2 \Omega = 1 \Omega$$

$$I = 12 \text{ V} / 1 \Omega = \mathbf{12 \text{ A}}$$

$$b. \quad I_1 = 12 \text{ V} / 6 \Omega = 2 \text{ A}$$

$$I_3 = \frac{6 \Omega(2 \text{ A})}{6 \Omega + 6 \Omega} = 1 \text{ A}$$


$$I_4 = \frac{1 \text{ A}}{2} = \mathbf{0.5 \text{ A}}$$

$$c. \quad I_6 = I_4 = \mathbf{0.5 \text{ A}}$$

$$d. \quad I_{10} = \frac{12 \text{ A}}{2} = \mathbf{6 \text{ A}}$$

38. a. $I_{CS} = \mathbf{1\ mA}$
- b. $R_{\text{shunt}} = \frac{R_m I_{CS}}{I_{\text{max}} - I_{CS}} = \frac{(100\ \Omega)(1\ \text{mA})}{20\ \text{A} - 1\ \text{mA}} \cong \frac{0.1}{20}\ \Omega = \mathbf{5\ m\Omega}$
39. 25 mA: $R_{\text{shunt}} = \frac{(1\ \text{k}\Omega)(50\ \mu\text{A})}{25\ \text{mA} - 0.05\ \text{mA}} \cong \mathbf{2\ \Omega}$
- 50 mA: $R_{\text{shunt}} = \frac{(1\ \text{k}\Omega)(50\ \mu\text{A})}{50\ \text{mA} - 0.05\ \text{mA}} = \mathbf{1\ \Omega}$
- 100 mA: $R_{\text{shunt}} \cong \mathbf{0.5\ \Omega}$
40. a. $R_s = \frac{V_{\text{max}} - V_{FS}}{I_{CS}} = \frac{15\ \text{V} - (50\ \mu\text{A})(1\ \text{k}\Omega)}{50\ \mu\text{A}} = \mathbf{300\ \text{k}\Omega}$
- b. $\Omega/\text{V} = 1/I_{CS} = 1/50\ \mu\text{A} = \mathbf{20,000}$
41. 5 V: $R_s = \frac{5\ \text{V} - (1\ \text{mA})(1000\ \Omega)}{1\ \text{mA}} = \mathbf{4\ \text{k}\Omega}$
- 50 V: $R_s = \frac{50\ \text{V} - 1\ \text{V}}{1\ \text{mA}} = \mathbf{49\ \text{k}\Omega}$
- 500 V: $R_s = \frac{500\ \text{V} - 1\ \text{V}}{1\ \text{mA}} = \mathbf{499\ \text{k}\Omega}$
42. $10\ \text{M}\Omega = (0.5\ \text{V})(\Omega/\text{V}) \Rightarrow \Omega/\text{V} = 20 \times 10^6$
- $I_{CS} = 1/(\Omega/\text{V}) = \frac{1}{20 \times 10^6} = \mathbf{0.05\ \mu\text{A}}$
43. a. $R_s = \frac{E}{I_m} - R_m - \frac{\text{zero adjust}}{2} = \frac{3\ \text{V}}{100\ \mu\text{A}} - 1\ \text{k}\Omega - \frac{2\ \text{k}\Omega}{2} = \mathbf{28\ \text{k}\Omega}$
- b. $xI_m = \frac{E}{R_{\text{series}}} + R_m + \frac{\text{zero adjust}}{2} + R_{\text{unk}}$
- $R_{\text{unk}} = \frac{E}{xI_m} - \left(R_{\text{series}} + R_m + \frac{\text{zero adjust}}{2} \right)$
- $= \frac{3\ \text{V}}{x100\ \mu\text{A}} - 30\ \text{k}\Omega \Rightarrow \frac{30 \times 10^3}{x} - 30 \times 10^3$
- $x = \frac{3}{4}, R_{\text{unk}} = \mathbf{10\ \text{k}\Omega}; x = \frac{1}{2}, R_{\text{unk}} = \mathbf{30\ \text{k}\Omega}; x = \frac{1}{4}, R_{\text{unk}} = \mathbf{90\ \text{k}\Omega}$
44. —

45. a. Network redrawn:

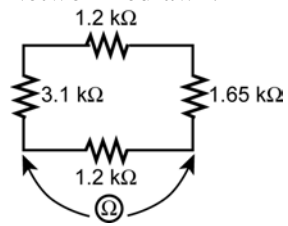

$$\begin{aligned} R_{\text{ohmmeter}} &= 1.2 \text{ k}\Omega \parallel (3.1 \text{ k}\Omega + 1.2 \text{ k}\Omega + 1.65 \text{ k}\Omega) \\ &= 1.2 \text{ k}\Omega \parallel 5.95 \text{ k}\Omega \\ &= \mathbf{1 \text{ k}\Omega} \end{aligned}$$

- b. All three resistors are in parallel

$$R_{\text{ohmmeter}} = \frac{R}{N} = \frac{18 \Omega}{3} = \mathbf{6 \Omega}$$