

Chapter 8

1.
 - a. $I_1 = \frac{8 \Omega(6\text{A})}{8 \Omega + 2 \Omega} = \mathbf{4.8 \text{ A}}$ $I_2 = 6 \text{ A} - I_1 = 6 \text{ A} - 4.8 \text{ A} = \mathbf{1.2 \text{ A}}$
 - b. $V_s = I_1 R_1 = (4.8 \text{ A})(2 \Omega) = \mathbf{9.6 \text{ V}}$
2.
 - a. $I_1 = I_2 = \mathbf{20 \text{ mA}}$
 - b. $V_2 = I_2 R_2 = (20 \text{ mA})(3.3 \text{ k}\Omega) = \mathbf{66 \text{ V}}$
 $V_s = I R_T = (20 \text{ mA})((1.2 \text{ k}\Omega + 3.3 \text{ k}\Omega) = 20 \text{ mA}(4.5 \text{ k}\Omega) = \mathbf{90 \text{ V}}$
3. $E + V_{R_1} - V_s = 0$, $V_{R_1} = (8 \text{ mA})(2.7 \text{ k}\Omega) = 21.6 \text{ V}$
 $V_s = E + V_{R_1} = 10 \text{ V} + 21.6 \text{ V} = \mathbf{31.6 \text{ V}^+}$
4.
 - a. $V_s = E = \mathbf{24 \text{ V}}$
 - b. $I_2 = \frac{E}{R_1 + R_2} = \frac{24 \text{ V}}{1 \Omega + 3 \Omega} = \frac{24 \text{ V}}{4 \Omega} = \mathbf{6 \text{ A}}$
 - c. $I + I_s = I_2$, $I_s = I_2 - I = 6 \text{ A} - 2 \text{ A} = \mathbf{4 \text{ A}}$
5. $V_I = V_2 = V_s = I R_T = 0.6 \text{ A}[6 \Omega \parallel 24 \Omega \parallel 24 \Omega] = 0.6 \text{ A}[6 \Omega \parallel 12 \Omega] = 2.4 \text{ V}$
 $I_2 = \frac{V_2}{R_2} = \frac{2.4 \text{ V}}{24 \Omega} = \mathbf{0.1 \text{ A}}$
 $V_3 = \frac{R_3 V_s}{R_3 + R_4} = \frac{16 \Omega(2.4 \text{ V})}{24 \Omega} = \mathbf{1.6 \text{ V}}$
6.
 - a. $I_1 = \frac{E}{R_1} = \frac{24 \text{ V}}{2 \Omega} = \mathbf{12 \text{ A}}$, $I_{R_2} = \frac{E}{R_2 + R_3} = \frac{24 \text{ V}}{6 \Omega + 2 \Omega} = \frac{24 \text{ V}}{8 \Omega} = 3 \text{ A}$
 KCL: $I + I_s - I_1 - I_{R_2} = 0$
 $I_s = I_1 + I_{R_2} - I = 12 \text{ A} + 3 \text{ A} - 4 \text{ A} = \mathbf{11 \text{ A}}$
 - b. $V_s = E = 24 \text{ V}$
 VDR: $V_3 = \frac{R_3 E}{R_2 + R_3} = \frac{2 \Omega(24 \text{ V})}{6 \Omega + 2 \Omega} = \frac{48 \text{ V}}{8 \Omega} = \mathbf{6 \text{ V}}$
7.
 - a. $I = \frac{E}{R_s} = \frac{22 \text{ V}}{4.7 \Omega} = \mathbf{4.68 \text{ A}}$, $R_p = R_s = \mathbf{4.7 \Omega}$
 - b. $I = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{9 \text{ V}}{1.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \frac{9 \text{ V}}{3.4 \text{ k}\Omega} = \mathbf{2.65 \text{ A}}$
 $R_p = \mathbf{3.4 \text{ k}\Omega}$

8. a. $E = IR_p = (6 \text{ A})(12 \Omega) = \mathbf{72 \text{ V}}$, $R_s = \mathbf{12 \Omega}$
 b. $R_p = R_1 \parallel R_2 = 2.7 \text{ k}\Omega \parallel 8.1 \text{ k}\Omega = 2.03 \text{ k}\Omega$
 $E = IR_p = (18 \text{ mA})(2.03 \text{ k}\Omega) = \mathbf{36.54 \text{ V}}$, $R_s = \mathbf{2.03 \text{ k}\Omega}$

9. a. CDR: $I_L = \frac{R_s(I)}{R_s + R_L} = \frac{(91 \Omega)(12 \text{ mA})}{91 \Omega + 10 \Omega} = \mathbf{10.81 \text{ mA}}$
 b. $E_s = IR = (12 \text{ mA})(91 \Omega) = \mathbf{1.092 \text{ V}}$
 $R_s = 91 \Omega$
 $I = \frac{E_s}{R_s + R_L} = \frac{1.092 \text{ V}}{91 \Omega + 10 \Omega} = \mathbf{10.81 \text{ mA}}$

10. a. $E = IR_2 = (2 \text{ A})(5.6 \Omega) = \mathbf{11.2 \text{ V}}$, $R = \mathbf{5.6 \Omega}$
 b. $E_T = 12 \text{ V} + 11.2 \text{ V} = \mathbf{23.2 \text{ V}}$, $R_T = 10 \Omega + 5.6 \Omega = \mathbf{15.6 \Omega}$

c. $I_3 = \frac{E_T}{R_T + 91 \Omega} = \frac{23.2 \text{ V}}{15.6 \Omega + 91 \Omega} = \mathbf{217.64 \text{ mA}}$


11. a. $I_T = 6.2 \text{ A} - 1.2 \text{ A} + 0.8 \text{ A} = 7 \text{ A} - 1.2 \text{ A} = \mathbf{5.8 \text{ A}}$
 b. $V_s = I_T R = (5.8 \text{ A})(4 \Omega) = \mathbf{23.2 \text{ V}}$

12. $I_T \uparrow = 7 \text{ A} - 3 \text{ A} = 4 \text{ A}$
 CDR: $I_1 = \frac{R_2(I_T)}{R_1 + R_2} = \frac{6 \Omega(4 \text{ A})}{4 \Omega + 6 \Omega} = \mathbf{2.4 \text{ A}}$
 $V_2 = I_1 R_1 = (2.4 \text{ A})(4 \Omega) = \mathbf{9.6 \text{ V}}$

13. a. $I_T = \frac{E_2}{R_2} - \frac{E_1}{R_1} = \frac{20 \text{ V}}{2 \Omega} - \frac{9 \text{ V}}{3 \Omega}$
 $= 10 \text{ A} - 3 \text{ A} = \mathbf{7 \text{ A} \downarrow}$

- b. $V_{ab} = -I_T(R_1 \parallel R_2 \parallel R_3)$
 $= -7 \text{ A}(3 \Omega \parallel 6 \Omega \parallel 2 \Omega)$
 $= -7 \text{ A}(1 \Omega)$
 $= \mathbf{-7 \text{ V}}$

- c. $I_3 = \frac{7 \text{ V}}{6 \Omega} = \mathbf{1.17 \text{ A} \uparrow}$

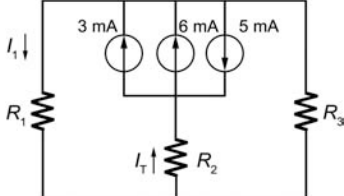14. a.  $I_T = 3 \text{ mA} + 6 \text{ mA} - 5 \text{ mA} = 4 \text{ mA} \uparrow$
 $I_{R_1} = \frac{R_3 I_T}{R_1 + R_3} = \frac{1 \text{ k}\Omega(4 \text{ mA})}{2.2 \text{ k}\Omega + 1 \text{ k}\Omega} = 1.25 \text{ mA}$
 $V_1 = I_{R_1}(R_1) = (1.25 \text{ mA})(2.2 \text{ k}\Omega) = \mathbf{2.75 \text{ V}}$

15. a. $\begin{array}{l} \overrightarrow{I_1} \downarrow \overleftarrow{I_3} \\ \downarrow I_2 \end{array}$
$$\begin{array}{l} 4 - 4I_1 - 8I_3 = 0 \\ 6 - 2I_2 - 8I_3 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

$$I_1 = -\frac{1}{7} \text{ A}, I_2 = \frac{5}{7} \text{ A}, I_3 = \frac{4}{7} \text{ A}$$

$$I_{R_1} = I_1 = -\frac{1}{7} \text{ A}, I_{R_2} = I_2 = \frac{5}{7} \text{ A}, I_{R_3} = I_3 = \frac{4}{7} \text{ A}$$


b. $V_a = I_3 R_3 = \left(\frac{4}{7} \text{ A}\right)(8 \Omega) = \mathbf{4.57 \text{ V}}$

16. a. $\begin{array}{l} \overrightarrow{I_1} \uparrow \overrightarrow{I_3} \\ \downarrow I_2 \end{array}$
$$\begin{array}{l} 10 + 12 - 3I_3 - 4I_1 = 0 \\ 12 - 3I_3 - 12I_2 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

$$\begin{array}{l} I_1 = \mathbf{3.06 \text{ A}} \\ I_2 = \mathbf{0.19 \text{ A}} \\ I_3 = \mathbf{3.25 \text{ A}} \end{array}$$

$$I_{R_1} = I_1 = 3.06 \text{ A}, I_{R_3} = I_2 = \mathbf{0.19 \text{ A}} = I_{12\Omega}$$

$$I_{R_2} = I_3 = 3.25 \text{ A}$$

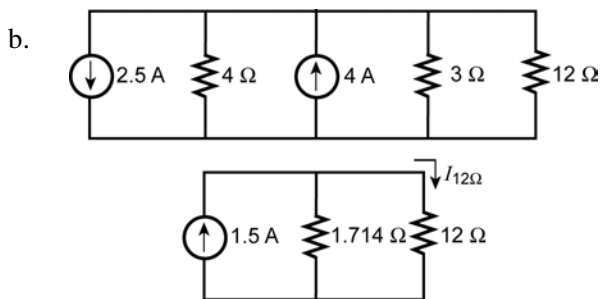


$$I_{12\Omega} = \frac{(1.714 \Omega)(1.5 \text{ A})}{1.714 \Omega + 12 \Omega} = \mathbf{0.19 \text{ A}}$$

c. the same

17. $\begin{array}{l} \overrightarrow{I_1} \downarrow \overleftarrow{I_3} \\ \downarrow I_2 \end{array}$
$$\begin{array}{l} 10 - I_1 5.6 \text{ k}\Omega - I_3 2.2 \text{ k}\Omega + 20 = 0 \\ -20 + I_3 2.2 \text{ k}\Omega + I_2 3.3 \text{ k}\Omega - 30 = 0 \\ I_1 + I_2 = I_3 \end{array}$$

$$I_1 = I_{R_1} = \mathbf{1.45 \text{ mA}}, I_2 = I_{R_2} = \mathbf{8.51 \text{ mA}}, I_3 = I_{R_3} = \mathbf{9.96 \text{ mA}}$$

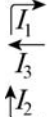
18. a. 
$$\begin{aligned} -1.2 \text{ k}\Omega I_1 + 9 - 8.2 \text{ k}\Omega I_3 &= 0 \\ -10.2 \text{ k}\Omega I_2 + 8.2 \text{ k}\Omega I_3 + 6 &= 0 \\ I_2 + I_3 &= I_1 \end{aligned}$$

$$I_1 = \mathbf{2.03 \text{ mA}}, I_2 = \mathbf{1.23 \text{ mA}}, I_3 = \mathbf{0.8 \text{ mA}}$$

$$I_{R_1} = I_1 = 2.03 \text{ mA}$$

$$I_{R_2} = I_3 = 0.8 \text{ mA}$$
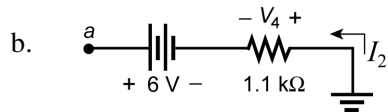
$$I_{R_3} = I_{R_4} = I_2 = \mathbf{1.23 \text{ mA}} = I_{9.1\text{k}\Omega}$$



19.
$$V_4 = I_2 R_4 = (1.23 \text{ mA})(1.1 \text{ k}\Omega) = 1.35 \text{ V}$$

$$V_a = 6 \text{ V} - V_4 = 6 \text{ V} - 1.35 \text{ V} = \mathbf{4.65 \text{ V}}$$

$$I_1 = I_{R_1} \text{ (CW)}, I_2 = I_{R_2} \text{ (down)}, I_3 = I_{R_3} \text{ (CW)}, I_4 = I_{R_4} \text{ (down)}$$

$$I_5 = I_{R_5} \text{ (CW)}$$

a.
$$\begin{aligned} E_1 - I_1 R_1 - I_2 R_2 &= 0 \\ I_2 R_2 - I_3 R_3 - I_4 R_4 &= 0 \\ I_4 R_4 - I_5 R_5 - E_2 &= 0 \\ I_1 &= I_2 + I_3 \\ I_3 &= I_4 + I_5 \end{aligned}$$

b.
$$\begin{aligned} E_1 - I_2(R_1 + R_2) - I_3 R_1 &= 0 \\ I_2 R_2 - I_3(R_3 + R_4) + I_5 R_4 &= 0 \\ I_3 R_4 - I_5(R_4 + R_5) - E_2 &= 0 \end{aligned}$$

c.
$$\begin{aligned} I_2(R_1 + R_2) + I_3 R_1 + 0 &= E_1 \\ I_2(R_2) - I_3(R_3 + R_4) + I_5 R_4 &= 0 \\ 0 + I_3 R_4 - I_5(R_4 + R_5) &= E_2 \end{aligned}$$

$$3I_2 + 2I_3 + 0 = 10$$

$$1I_2 - 9I_3 + 5I_5 = 0$$

$$0 + 5I_3 - 8I_5 = 6$$

d.
$$I_3 = I_{R_3} = \mathbf{-63.69 \text{ mA}} \text{ (CW)}$$

20. a. $\begin{array}{l} \overrightarrow{I_1} \downarrow \overrightarrow{I_2} \downarrow \\ 4 - 4I_1 - 8(I_1 - I_2) = 0 \\ -8(I_2 - I_1) - 2I_2 - 6 = 0 \end{array}$

$$I_1 = -\frac{1}{7} \text{ A}, I_2 = -\frac{5}{7} \text{ A}$$

$$I_{R_1} = I_1 = -\frac{1}{7} \text{ A}$$

$$I_{R_2} = I_2 = -\frac{5}{7} \text{ A}$$

$$I_{R_3} = I_1 - I_2 = \left(-\frac{1}{7} \text{ A}\right) - \left(-\frac{5}{7} \text{ A}\right) = \frac{4}{7} \text{ A (dir. of } I_1)$$

b. $V_a = I_{R_3} R_3 = \left(\frac{4}{7} \text{ A}\right)(8 \Omega) = \mathbf{4.57 \text{ V}}$

21. a. $\begin{array}{l} \overrightarrow{I_1} \downarrow \overrightarrow{I_2} \downarrow \\ -10 - 4I_1 - 3(I_1 - I_2) - 12 = 0 \\ 12 - 3(I_2 - I_1) - 12I_2 = 0 \end{array}$

$$I_1 = -3.06 \text{ A}, I_2 = 0.19 \text{ A}$$

$$I_{E_1} = \mathbf{3.06 \text{ A (CCW)}}$$

$$I_{E_2} = 3.06 \text{ A} + 0.19 \text{ A} = \mathbf{3.25 \text{ A (up)}}$$

$$I_{R_2} = I_1 - I_2 = (-3.06 \text{ A}) - (0.19 \text{ A}) = \mathbf{-3.25 \text{ A}}$$

b. $P_{E_2} = I_{E_2} E_2 = (3.25 \text{ A})(12 \text{ V}) = \mathbf{39 \text{ W}}$

$$P_{R_3} = I_{R_3}^2 R_3 = (0.19 \text{ A})^2 12 \Omega = \mathbf{433.2 \text{ mW}}$$

22. a. $\begin{array}{l} \overrightarrow{I_1} \downarrow \overrightarrow{I_2} \downarrow \\ 10 - I_1(5.6 \text{ k}\Omega) - 2.2 \text{ k}\Omega(I_1 - I_2) + 20 = 0 \\ -20 - 2.2 \text{ k}\Omega(I_2 - I_1) - I_2 3.3 \text{ k}\Omega - 30 = 0 \end{array}$

$$I_1 = 1.45 \text{ mA}, I_2 = 8.51 \text{ mA}$$

$$I_{R_1} = I_1 = \mathbf{1.45 \text{ mA}}, I_{R_2} = I_2 = \mathbf{8.51 \text{ mA}}$$

$$I_{R_3} = I_2 - I_1 = \mathbf{7.06 \text{ mA (direction of } I_2)}$$

b. $V_{3.3\text{k}\Omega} = I_2 R_2 = (8.51 \text{ mA})(3.3 \text{ k}\Omega) = \mathbf{28.1 \text{ V}}$

23. a. $\begin{array}{l} \overrightarrow{I_1} \downarrow \\ \overrightarrow{I_2} \downarrow \\ -I_1(1.2 \text{ k}\Omega) + 9 - 8.2 \text{ k}\Omega(I_1 - I_2) = 0 \\ -I_2(1.1 \text{ k}\Omega) + 6 - I_2(9.1 \text{ k}\Omega) - 8.2 \text{ k}\Omega(I_2 - I_1) = 0 \end{array}$

$$I_1 = 2.03 \text{ mA}, I_2 = 1.23 \text{ mA}$$

$$I_{R_1} = I_1 = \mathbf{2.03 \text{ mA}}, I_{R_3} = I_{R_4} = I_2 = \mathbf{1.23 \text{ mA}}$$

$$I_{R_2} = I_1 - I_2 = 2.03 \text{ mA} - 1.23 \text{ mA} = \mathbf{0.80 \text{ mA (direction of } I_1)}$$

b. $V_a = 6 \text{ V} - I_2(1.1 \text{ k}\Omega) = 6 \text{ V} - (1.23 \text{ mA})(1.1 \text{ k}\Omega) = 6 \text{ V} - 1.35 \text{ V} = \mathbf{4.65 \text{ V}}$

$$\begin{array}{rcl}
24. \quad a. & \begin{array}{l} I_1 \downarrow \\ I_2 \downarrow \\ I_3 \downarrow \end{array} & \begin{array}{l} 10 - I_1 2 - 1(I_1 - I_2) = 0 \\ -1(I_2 - I_1) - I_2 4 - 5(I_2 - I_3) = 0 \\ -5(I_3 - I_2) - I_3 3 - 6 = 0 \end{array} \\
& & \hline
& & \begin{array}{l} 3I_1 - I_2 + 0 = 10 \\ -1I_1 + 10I_2 - 5I_3 = 0 \\ 0 - 5I_2 + 8I_3 = -6 \end{array} \\
& & \hline
& & I_1 = \mathbf{3.31 \text{ A}}, I_2 = \mathbf{-63.69 \text{ mA}}, I_3 = \mathbf{-789.8 \text{ mA}}
\end{array}$$

b, c. Ignore

$$\begin{array}{l}
d. \quad I_{10V} \uparrow = I_1 = \mathbf{3.31 \text{ A}} \\
I_{6V} \uparrow = -I_3 = -(-789.8 \text{ mA}) = \mathbf{789.8 \text{ mA}}
\end{array}$$

$$\begin{array}{rcl}
25. \quad a. & \begin{array}{l} I_1 \downarrow \\ I_2 \downarrow \\ I_3 \downarrow \end{array} & \begin{array}{l} -I_1 2.2 \text{ k}\Omega - (I_1 - I_2)9.1 \text{ k}\Omega + 18 \text{ V} = 0 \\ -18 \text{ V} - (I_2 - I_1)9.1 \text{ k}\Omega - 7.5 \text{ k}\Omega I_2 - (I_2 - I_3)6.8 \text{ k}\Omega = 0 \\ -6.8 \text{ k}\Omega(I_3 - I_2) - 3 \text{ V} - 3.3 \text{ k}\Omega I_3 = 0 \end{array} \\
& & \hline
\end{array}$$

$$\begin{array}{l}
\text{with} \\
11.3 \text{ k}\Omega I_1 - 9.1 \text{ k}\Omega I_2 = 18 \text{ V} \\
23.4 \text{ k}\Omega I_2 - 9.1 \text{ k}\Omega I_1 - 6.8 \text{ k}\Omega I_3 = -18 \text{ V} \\
10.1 \text{ k}\Omega I_3 - 6.8 \text{ k}\Omega I_2 = -3 \text{ V}
\end{array}$$

$$\begin{array}{l}
\text{or} \\
11.3 \text{ k}\Omega I_1 - 9.1 \text{ k}\Omega I_2 = 18 \text{ V} \\
-9.1 \text{ k}\Omega I_2 + 23.4 \text{ k}\Omega I_2 - 6.8 \text{ k}\Omega I_3 = -18 \text{ V} \\
-6.8 \text{ k}\Omega I_2 + 10.1 \text{ k}\Omega I_3 = -3 \text{ V}
\end{array}$$

$$b. \quad I_1 = \mathbf{1.21 \text{ mA}}, I_2 = \mathbf{-0.48 \text{ mA}}, I_3 = \mathbf{-0.62 \text{ mA}}$$

$$\begin{array}{l}
c. \quad I_{E_1} \downarrow = I_1 - I_2 = 1.21 \text{ mA} - (-0.48 \text{ mA}) = \mathbf{1.69 \text{ mA}} \\
I_{E_2} \uparrow = -I_3 = -(-0.62 \text{ mA}) = \mathbf{0.62 \text{ mA}}
\end{array}$$

$$\begin{array}{rcl}
26. \quad a. & \begin{array}{l} I_1 \downarrow \\ I_2 \downarrow \\ I_3 \downarrow \end{array} & \begin{array}{l} -4 I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0 \\ -3(I_2 - I_1) - 10 I_2 - 15 - 4(I_2 - I_3) = 0 \\ -7 I_3 - 4(I_3 - I_1) - 4(I_3 - I_2) = 0 \end{array} \\
& & \hline
\end{array}$$

$$b. \quad I_1 = \mathbf{-430.4 \text{ mA}}, I_2 = \mathbf{-1.05 \text{ A}}, I_3 = \mathbf{-395.1 \text{ mA}}$$


$$c. \quad I_{R_5} = I_1 = \mathbf{-430.4 \text{ mA}}$$

$$\begin{array}{rcl}
27. \quad a. & \begin{array}{l} I_1 \downarrow \\ I_2 \downarrow \\ I_4 \downarrow \\ I_3 \downarrow \end{array} & \begin{array}{l} -6.8 \text{ k}\Omega I_1 - 4.7 \text{ k}\Omega(I_1 - I_2) + 6 - 2.2 \text{ k}\Omega(I_1 - I_4) = 0 \\ -6 - 4.7 \text{ k}\Omega(I_2 - I_1) - 8.2 \text{ k}\Omega (I_2 - I_3) = 0 \\ -1.1 \text{ k}\Omega I_3 - 22 \text{ k}\Omega(I_3 - I_4) - 8.2 \text{ k}\Omega(I_3 - I_2) - 9 = 0 \\ -1.2 \text{ k}\Omega I_4 - 2 \text{ k}\Omega(I_4 - I_1) - 22 \text{ k}\Omega(I_4 - I_3) = 0 \end{array} \\
& & \hline
\end{array}$$

b. $I_1 = -0.597 \text{ mA}, I_2 = -2.13 \text{ mA}, I_3 = -2.27 \text{ mA}, I_4 = -2.03 \text{ mA}$

c. $I_{6V} = I_1 - I_2 = -0.597 \text{ mA} - (-2.13 \text{ mA}) = 1.53 \text{ mA}$
 $P_{6V} = E I_{6V} = (6 \text{ V})(1.53 \text{ mA}) = \mathbf{9.18 \text{ mW}}$

28. a. Network redrawn:

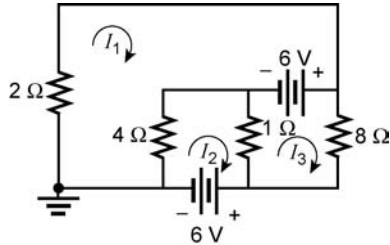

b. $-2I_1 - 6 - 4I_1 + 4I_2 = 0$
 $-4I_2 + 4I_1 - 1I_2 + 1I_3 - 6 = 0$
 $-1I_3 + 1I_2 + 6 - 8I_3 = 0$

c. $I_1 = -3.8 \text{ A}, I_2 = -4.20 \text{ A}, I_3 = 0.20 \text{ A}$

d. $P_{E_2} = E_2 I_3 = (6 \text{ V})(0.2 \text{ A}) = 1.2 \text{ W}$
 $P_{E_1} = E_1 I_2 = (6 \text{ V})(4.2 \text{ A}) = 25.2 \text{ W}$
 $P_T = P_{E_1} + P_{E_2} = 1.2 \text{ W} + 25.2 \text{ W} = \mathbf{26.4 \text{ W}}$



29. a. $20 \text{ V} - I_B(270 \text{ k}\Omega) - 0.7 \text{ V} - I_E(0.51 \text{ k}\Omega) = 0$
 $I_E(0.51 \text{ k}\Omega) + 8 \text{ V} + I_C(2.2 \text{ k}\Omega) - 20 \text{ V} = 0$
 $I_E = I_B + I_C$

$I_B = \mathbf{63.02 \mu\text{A}}, I_C = \mathbf{4.42 \text{ mA}}, I_E = \mathbf{4.48 \text{ mA}}$

b. $V_B = 20 \text{ V} - I_B(270 \text{ k}\Omega) = 20 \text{ V} - (63.02 \mu\text{A})(270 \text{ k}\Omega) = 20 \text{ V} - 17.02 \text{ V} = \mathbf{2.98 \text{ V}}$
 $V_E = I_E R_E = (4.48 \text{ mA})(510 \Omega) = \mathbf{2.28 \text{ V}}$
 $V_C = 20 \text{ V} - I_C(2.2 \text{ k}\Omega) = 20 \text{ V} - (4.42 \text{ mA})(2.2 \text{ k}\Omega) = 20 \text{ V} - 9.72 \text{ V} = \mathbf{10.28 \text{ V}}$

c. $\beta \cong I_C/I_B = 4.42 \text{ mA}/63.02 \mu\text{A} = \mathbf{70.14}$

30.

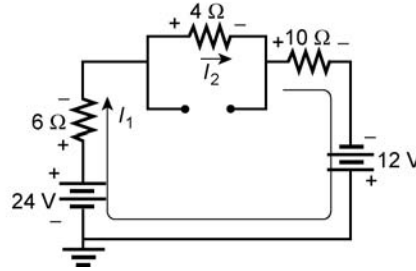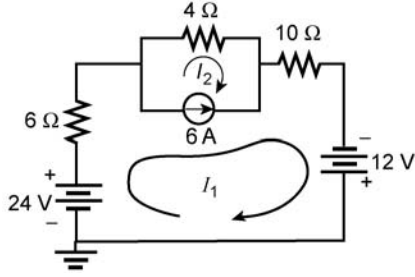

$$24 \text{ V} - 6I_1 - 4I_2 - 10I_1 + 12 \text{ V} = 0$$

$$\text{and } 16I_1 + 4I_2 = 36$$

$$I_1 - I_2 = 6 \text{ A}$$

$$I_1 = I_2 + 6 \text{ A}$$

$$16[I_2 + 6 \text{ A}] + 4I_2 = 36$$

$$16I_2 + 96 + 4I_2 = 36$$

$$20I_2 = -60$$



$$I_2 = -3 \text{ A}$$

$$I_1 = I_2 + 6 \text{ A} = -3 \text{ A} + 6 \text{ A} = 3 \text{ A}$$

$$I_{24\text{V}} = I_{6\Omega} = I_{10\Omega} = I_{12\text{V}} = 3 \text{ A (CW)}$$

$$I_{4\Omega} = 3 \text{ A (CCW)}$$

31.

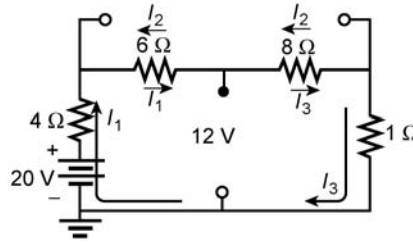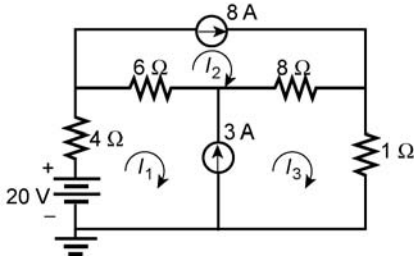

$$20 \text{ V} - 4I_1 - 6(I_1 - I_2) - 8(I_3 - I_2) - 1I_3 = 0$$

$$10I_1 - 14I_2 + 9I_3 = 20$$

$$I_3 - I_1 = 3 \text{ A}$$

$$I_2 = 8 \text{ A}$$

$$10I_1 - 14(8 \text{ A}) + 9[I_1 + 3 \text{ A}] = 20$$

$$19I_1 = 105$$

$$I_1 = 5.526 \text{ A}$$

$$I_3 = I_1 + 3 \text{ A} = 5.526 \text{ A} + 3 \text{ A} = 8.526 \text{ A}$$

$$I_2 = 8 \text{ A}$$

$$I_{20\text{V}} = I_{4\Omega} = 5.53 \text{ A (dir. of } I_1)$$

$$I_{6\Omega} = I_2 - I_1 = 2.47 \text{ A (dir. of } I_2)$$

$$I_{8\Omega} = I_3 - I_2 = 0.53 \text{ A (dir. of } I_3)$$

$$I_{1\Omega} = 8.53 \text{ A (dir. of } I_3)$$

32. a. $\overrightarrow{I_1} \overrightarrow{I_2}$ $(4 + 8)I_1 - 8I_2 = 4$
 $(8 + 2)I_2 - 8I_1 = -6$

b. $I_{8\Omega} \downarrow = I_1 - I_2 = \left(-\frac{1}{7} \text{ A}\right) - \left(-\frac{5}{7} \text{ A}\right) = \frac{4}{7} \text{ A}$

33. a. $\overrightarrow{I_1} \overrightarrow{I_2}$ $(4 + 3)I_1 - 3I_2 = -10 - 12$
 $(3 + 12)I_2 - 3I_1 = 12$

b. $I_{3\Omega} \uparrow = I_2 - I_1 = 0.19 \text{ A} - (-3.06 \text{ A}) = \mathbf{3.25 \text{ A}}$

34. a. $\overrightarrow{I_1} \overrightarrow{I_2}$

$$I_1(5.6 \text{ k}\Omega + 2.2 \text{ k}\Omega) - 2.2 \text{ k}\Omega (I_2) = 10 + 20$$

$$I_2(2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega) - 2.2 \text{ k}\Omega (I_1) = -20 - 30$$

b. $I_{E_1} = I_1 = \mathbf{1.45 \text{ mA}}$, $I_{E_2} \uparrow = \mathbf{8.51 \text{ mA}}$,
 $I_{E_3} \downarrow = I_1 - I_2 = (1.45 \text{ mA}) - (-8.5 \text{ mA}) = \mathbf{9.96 \text{ mA}}$

35. a. $\overrightarrow{I_1} \overrightarrow{I_2} \overrightarrow{I_3}$
 $I_1(2 + 1) - 1I_2 = 10$
 $I_2(1 + 4 + 5) - 1I_1 - 5I_3 = 0$
 $I_3(5 + 3) - 5I_2 = -6$

b. $I_1 = \mathbf{3.31 \text{ A}}$, $I_2 = \mathbf{-63.69 \text{ mA}}$, $I_3 = \mathbf{-789.8 \text{ mA}}$

c. $I_{R_2} = I_1 - I_2 = (3.31 \text{ A}) - (-63.69 \text{ mA}) = \mathbf{3.37 \text{ A}}$

36. a. $\overrightarrow{I_1} \overrightarrow{I_2} \overrightarrow{I_3}$

$$(2.2 \text{ k}\Omega + 9.1 \text{ k}\Omega)I_1 - 9.1 \text{ k}\Omega I_2 = 18$$

$$(9.1 \text{ k}\Omega + 7.5 \text{ k}\Omega + 6.8 \text{ k}\Omega)I_2 - 9.1 \text{ k}\Omega I_1 - 6.8 \text{ k}\Omega I_3 = -18$$

$$(6.8 \text{ k}\Omega + 3.3 \text{ k}\Omega)I_3 - 6.8 \text{ k}\Omega I_2 = -3$$

b. $I_1 = \mathbf{1.21 \text{ mA}}$, $I_2 = \mathbf{-0.48 \text{ mA}}$, $I_3 = \mathbf{-0.62 \text{ mA}}$

c. $I_{E_1} \downarrow = I_1 - I_2 = 1.21 \text{ mA} - (-0.48 \text{ mA}) = \mathbf{1.69 \text{ mA}}$
 $I_{E_2} \uparrow = -I_3 = -(-0.62 \text{ mA}) = \mathbf{0.62 \text{ mA}}$

37. a. $(3 \Omega + 6 \Omega)I_1 - 6 \Omega I_2 = 9 \text{ V}$
 $(6 \Omega + 2 \Omega)I_2 - 6 \Omega I_1 = 20 \text{ V}$

$$\begin{aligned} 9 \Omega I_1 - 6 \Omega I_2 &= 9 \text{ V} \\ -6 \Omega I_1 + 8 \Omega I_2 &= 20 \text{ V} \end{aligned}$$

$$I_1 = \mathbf{5.33 \text{ A}}, I_2 = \mathbf{6.5 \text{ A}}$$

b. $V_{ab} = 2 \Omega (I_2) - 20 \text{ V} = 2 \Omega(6.5 \text{ A}) - 20 \text{ V} = 13 \text{ V} - 20 \text{ V} = \mathbf{-7 \text{ V}}$

38. a. $\begin{matrix} I_1 \downarrow & I_2 \downarrow \\ I_4 \downarrow & I_3 \downarrow \end{matrix}$ $I_1(6.8 \text{ k}\Omega + 4.7 \text{ k}\Omega - 2.2 \text{ k}\Omega) - 4.7 \text{ k}\Omega (I_2) - 2.2 \text{ k}\Omega I_4 = 6$
 $I_2(4.7 \text{ k}\Omega + 8.2 \text{ k}\Omega) - 4.7 \text{ k}\Omega(I_1) - 8.2 \text{ k}\Omega(I_3) = -6$
 $I_3(8.2 \text{ k}\Omega + 1.1 \text{ k}\Omega + 22 \text{ k}\Omega) - 8.2 \text{ k}\Omega I_2 - 22 \text{ k}\Omega I_4 = -9$
 $I_4(2.2 \text{ k}\Omega + 1.2 \text{ k}\Omega + 22 \text{ k}\Omega) - 22 \text{ k}\Omega(I_3) - 2.2 \text{ k}\Omega(I_1) = 0$

b. $I_1 = \mathbf{-0.597 \text{ mA}}, I_2 = \mathbf{-2.13 \text{ mA}}, I_3 = \mathbf{-2.27 \text{ mA}}, I_4 = \mathbf{-2.03 \text{ mA}}$

c. $I_{22\text{k}\Omega} = I_4 - I_3 = -2.03 \text{ mA} - (-2.27 \text{ mA}) = \mathbf{240 \mu\text{A}}$
 $V_{22\text{k}\Omega} = IR = (240 \times 10^{-6} \text{ A})(22 \text{ k}\Omega) = \mathbf{5.28 \text{ V}}$

39. a. $\begin{matrix} I_1 \downarrow & I_2 \downarrow \\ I_3 \downarrow & \end{matrix}$ $I_1(1 \Omega + 2 \Omega) - I_2 2 \Omega = 12$
 $I_2(2 \Omega + 10 \Omega) - I_1 2 \Omega - I_3 10 \Omega = -20 \text{ V}$
 $I_3(10 \Omega + 8 \Omega) - I_2 10 \Omega = 20 \text{ V}$

$$\begin{aligned} 3I_1 - 2I_2 &= 12 \\ -2I_1 + 12I_2 - 10I_3 &= -20 \\ -10I_2 + 18I_3 &= 20 \end{aligned}$$

b. $I_1 = \mathbf{3.884 \text{ A}}, I_2 = \mathbf{-0.174 \text{ A}}, I_3 = \mathbf{1.01 \text{ A}}$

c. $V_a = \mathbf{0 \text{ V}}$
 $V_b = I_3 8 \Omega = (1.01 \text{ A})(8 \Omega) = \mathbf{8.08 \text{ V}}$

d. $V_{ab} = V_a - V_b = 0 \text{ V} - 8.08 \text{ V} = \mathbf{-8.08 \text{ V}}$

40.

a.



$$\begin{aligned} I_1(2\ \Omega + 4\ \Omega) - I_2 4\ \Omega &= -6\ \text{V} \\ I_2(4\ \Omega + 1\ \Omega) - I_1 4\ \Omega - I_3 1\ \Omega &= -6\ \text{V} \\ I_3(1\ \Omega + 8\ \Omega) - I_2 1\ \Omega &= 6\ \text{V} \end{aligned}$$

$$\begin{aligned} 6I_1 - 4I_2 &= -6\ \text{V} \\ -4I_1 + 5I_2 - I_3 &= -6\ \text{V} \\ -I_2 + 9I_3 &= 6\ \text{V} \end{aligned}$$

b. $I_1 = -3.8\ \text{A}, I_2 = -4.20\ \text{A}, I_3 = 0.2\ \text{A}$

$$\begin{aligned} I_{R_1} &= I_1 - I_2 = -3.8\ \text{A} - (-4.20\ \text{A}) \\ &= -3.8\ \text{A} + 4.20\ \text{A} \\ &= \mathbf{0.4\ \text{A}} \end{aligned}$$

c. $I_{1\Omega} = I_2 - I_3 = -4.20\ \text{A} - 0.2\ \text{A}$
 $= -4.4\ \text{A}$

$$\begin{aligned} {}^+V_{1\Omega} &= (I_{1\Omega})(1\ \Omega) = (-4.4\ \text{A})(1\ \Omega) \\ &= \mathbf{-4.4\ \text{V}} \end{aligned}$$

41.

a.



At V_1 : $\sum I_i = \sum I_o$

$$0 = \frac{V_1}{2\ \Omega} + 5\ \text{A} + \frac{V_1 - V_2}{8\ \Omega}$$

At V_2 : $\sum I_i = \sum I_o$

$$\frac{V_1 - V_2}{8\ \Omega} = 3\ \text{A} + \frac{V_2}{4\ \Omega}$$

and $V_1 \left[\frac{1}{2} + \frac{1}{8} \right] - V_2 \left[\frac{1}{8} \right] = -5$

$$-V_1 \left[\frac{1}{8} \right] + V_2 \left[\frac{1}{8} + \frac{1}{4} \right] = -3$$

b. $V_1 = -10.27\ \text{V}, V_2 = -11.36\ \text{V}$

c. $V_{8\Omega} = V_1 - V_2 = -10.27\ \text{V} - (-11.36\ \text{V}) = \mathbf{1.09\ \text{V}}$

d. $I_{2\Omega} \uparrow = \frac{V_1}{2\ \Omega} = \frac{10.27\ \text{V}}{2\ \Omega} = \mathbf{5.14\ \text{A}}$

$$I_{4\Omega} \uparrow = \frac{V_2}{4\ \Omega} = \frac{11.36\ \text{V}}{4\ \Omega} = \mathbf{2.84\ \text{A}}$$

42. a. $\begin{matrix} V_1 \\ \circ \end{matrix} \quad \begin{matrix} V_2 \\ \circ \end{matrix}$
 At V_1 : $\Sigma I_i = \Sigma I_o$

$$0 = \frac{V_1}{8 \Omega} + 12 \text{ A} + I_{6\Omega} \text{ and } V_1 - I6\Omega - 54 \text{ V} - V_2 = 0$$

$$\text{or } I = \frac{V_1 - V_2 - 54 \text{ V}}{6 \Omega} = \frac{V_1}{6 \Omega} + \frac{V_2}{6 \Omega} - 9 \text{ A}$$

so that $0 = \frac{V_1}{8 \Omega} + 12 \text{ A} + \frac{V_1}{6 \Omega} - \frac{V_2}{6 \Omega} - 9 \text{ A}$

or $V_1 \left[\frac{1}{8 \Omega} + \frac{1}{6 \Omega} \right] - V_2 \left[\frac{1}{6 \Omega} \right] = -12 \text{ A} + 9 \text{ A} = -3 \text{ A}$

At V_2 : $\Sigma I_i = \Sigma I_o$

$$I = \frac{V_2}{20 \Omega} + \frac{V_2}{5 \Omega}$$

or $\frac{V_1}{6 \Omega} - \frac{V_2}{6 \Omega} - 9 \text{ A} = \frac{V_2}{20 \Omega} + \frac{V_2}{5 \Omega}$

and $V_2 \left[\frac{1}{6 \Omega} + \frac{1}{20 \Omega} + \frac{1}{5 \Omega} \right] - V_1 \left[\frac{1}{6 \Omega} \right] = -9 \text{ A}$

resulting in $V_1 \left[\frac{1}{8 \Omega} + \frac{1}{6 \Omega} \right] - V_2 \left[\frac{1}{6 \Omega} \right] = -3 \text{ A}$

$$-V_1 \left[\frac{1}{6 \Omega} \right] + V_2 \left[\frac{1}{6 \Omega} + \frac{1}{20 \Omega} + \frac{1}{5 \Omega} \right] = -9 \text{ A}$$

b. $V_1 = -29.29 \text{ V}$, $V_2 = -33.34 \text{ V}$

c. $I_{20\Omega} \uparrow = \frac{V_2}{20 \Omega} = \frac{33.34 \text{ V}}{20 \Omega} = 1.67 \text{ A}$

43. a. $\begin{matrix} V_1 \\ \circ \end{matrix} \quad \begin{matrix} V_2 \\ \circ \end{matrix}$

At V_1 : $\Sigma I_i = \Sigma I_o$

$$4 \text{ A} = \frac{V_1}{2 \Omega} + \frac{V_1 - V_2}{4 \Omega} + 2 \text{ A}$$

At V_2 : $\Sigma I_i = \Sigma I_o$

$$2 \text{ A} + \frac{V_1 - V_2}{4 \Omega} = \frac{V_2}{20 \Omega} + \frac{V_2}{5 \Omega}$$

or $V_1 \left[\frac{1}{2} + \frac{1}{4} \right] - V_2 \left[\frac{1}{4} \right] = 2$

$$-V_1 \left[\frac{1}{4} \right] + V_2 \left[\frac{1}{4} + \frac{1}{20} + \frac{1}{5} \right] = 2$$

b. $V_1 = 4.8 \text{ V}$, $V_2 = 6.4 \text{ V}$