

Chapter 10

$$1. \quad (a) \quad \mathcal{E} = k \frac{Q_1}{r^2} = \frac{(9 \times 10^9)(4 \mu\text{C})}{(1 \text{ m})^2} = \mathbf{36 \times 10^3 \text{ N/C}}$$

$$(b) \quad \mathcal{E} = k \frac{Q_1}{r^2} = \frac{(9 \times 10^9)(4 \mu\text{C})}{(1 \text{ mm})^2} = \mathbf{36 \times 10^9 \text{ N/C}}$$

$$\mathcal{E}(1 \text{ mm}): \mathcal{E}(2 \text{ m}) = 36 \times 10^9: 36 \times 10^3 = \mathbf{1 \times 10^6}$$

$$2. \quad \mathcal{E} = \frac{kQ}{r^2} \Rightarrow \sqrt{\frac{kQ}{\mathcal{E}}} = \sqrt{\frac{(9 \times 10^9)(2 \mu\text{C})}{72 \text{ N/C}}} = \mathbf{15.81 \text{ m}}$$

$$3. \quad C = \frac{Q}{V} = \frac{1200 \mu\text{C}}{24 \text{ V}} = \mathbf{50 \mu\text{F}}$$

$$4. \quad Q = CV = (0.15 \mu\text{F})(120 \text{ V}) = \mathbf{18 \mu\text{C}}$$

$$5. \quad a. \quad 1'' \left[\frac{1 \text{ m}}{39.37''} \right] = 25.4 \text{ mm}$$

$$\mathcal{E} = \frac{V}{d} = \frac{500 \text{ mV}}{25.4 \text{ mm}} = \mathbf{19.69 \text{ V/m}}$$

$$b. \quad \frac{25.4 \text{ mm}}{100} = 0.254 \text{ mm}$$

$$\mathcal{E} = \frac{V}{d} = \frac{500 \text{ mV}}{0.254 \text{ mm}} = \mathbf{1.97 \text{ kV/m}}$$

$$6. \quad V = \frac{Q}{C} = \frac{160 \mu\text{C}}{6.8 \mu\text{F}} = 23.53 \text{ V}$$

$$\mathcal{E} = \frac{V}{d} = \frac{23.53 \text{ V}}{5 \text{ mm}} = \mathbf{4.71 \text{ kV/m}}$$

$$7. \quad 0.1'' \left[\frac{1 \text{ m}}{39.37''} \right] = 2.54 \text{ mm}$$

$$C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (1) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = \mathbf{348.43 \text{ pF}}$$

$$8. \quad C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (2.5) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = \mathbf{871.06 \text{ pF}}$$


$$9. \quad C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} \Rightarrow d = \frac{8.85 \times 10^{-12} (4) (0.15 \text{ m}^2)}{2 \mu\text{F}} = \mathbf{2.66 \mu\text{m}}$$

10. $C = \epsilon_r C_o \Rightarrow \epsilon_r = \frac{C}{C_o} = \frac{6.8 \text{ nF}}{1360 \text{ pF}} = \mathbf{5 \text{ (mica)}}$
11. a. $C = 8.85 \times 10^{-12} (7) \frac{(0.08 \text{ m}^2)}{0.2 \text{ mm}} = \mathbf{24.78 \text{ nF}}$
- b. $\mathcal{E} = \frac{V}{d} = \frac{80 \text{ V}}{0.2 \text{ mm}} = \mathbf{400 \text{ kV/m}}$
- c. $Q = CV = (24.78 \text{ nF})(200 \text{ V}) = \mathbf{4.96 \mu\text{C}}$
12. a. $C = \frac{1}{2} (4.7 \mu\text{F}) = \mathbf{2.35 \mu\text{F}}$
- b. $C = 2(4.7 \mu\text{F}) = \mathbf{9.4 \mu\text{F}}$
- c. $C = 20(4.7 \mu\text{F}) = \mathbf{94 \mu\text{F}}$
- d. $C = \frac{(4) \left(\frac{1}{3} \right)}{\left(\frac{1}{4} \right)} (4.7 \mu\text{F}) = \mathbf{25.1 \mu\text{F}}$
13. $d = \frac{8.85 \times 10^{-12} \epsilon_r A}{C} = \frac{(8.85 \times 10^{-12})(5)(0.02 \text{ m}^2)}{6800 \text{ pF}} = 130.15 \mu\text{m}$
- $$d = 130.15 \cancel{\mu\text{m}} \left[\frac{10^{-6} \cancel{\mu\text{m}}}{1 \cancel{\mu\text{m}}} \right] \left[\frac{39.37 \cancel{\text{in.}}}{1 \cancel{\text{in.}}} \right] \left[\frac{1000 \text{ mils}}{1 \cancel{\text{in.}}} \right] = 5.12 \text{ mils}$$
- $$5.12 \cancel{\text{mils}} \left[\frac{5000 \text{ V}}{1 \cancel{\text{mils}}} \right] = \mathbf{25.6 \text{ kV}}$$
14. mica: $\frac{1200 \text{ V}}{5000 \text{ V}} = 1200 \text{ V} \left[\frac{\cancel{\text{mil}}}{5000 \text{ V}} \right] = 0.24 \text{ mils}$
- $$0.24 \text{ mils} \left[\frac{\cancel{\text{mil}}}{1000 \text{ mils}} \right] \left[\frac{1 \text{ m}}{39.37 \cancel{\text{in.}}} \right] = \mathbf{6.10 \mu\text{m}}$$
15. $\frac{200}{1 \times 10^6} (22 \mu\text{F})/^{\circ}\text{C} = 4400 \text{ pF}/^{\circ}\text{C}$
- $$\frac{4400 \text{ pF}}{^{\circ}\text{C}} [\Delta T] = \frac{4400 \text{ pF}}{^{\circ}\text{C}} [80^{\circ}\text{C}] = \mathbf{0.35 \mu\text{F}}$$
16. $J = \pm 5\%$, Size $\Rightarrow 40 \text{ pF} \pm 2 \text{ pF}$, $\mathbf{38 \text{ pF} \rightarrow 42 \text{ pF}}$
17. $F = \pm 1\%$, Size $\Rightarrow 47 \times 10^1 \mu\text{F} = 470 \mu\text{F} \pm 4.7 \mu\text{F}$, $\mathbf{465.3 \mu\text{F} \rightarrow 474.7 \mu\text{F}}$
18. $K = \pm 10\%$, Size $\Rightarrow 18 \times 10^2 \text{ pF} = \mathbf{1800 \text{ pF} \pm 180 \text{ pF}}$, $\mathbf{1620 \text{ pF} \rightarrow 1980 \text{ pF}}$
19. a. $\tau = RC = (10 \times 10^3 \Omega)(10 \mu\text{F}) = \mathbf{100 \text{ ms}}$

- b. $v_C = E(1 - e^{-t/\tau}) = 20 \text{ V}(1 - e^{-t/100 \text{ ms}})$
- c. $1\tau = 0.632(20 \text{ V}) = 12.64 \text{ V}$, $3\tau = 0.95(20 \text{ V}) = 19 \text{ V}$
 $5\tau = 0.993(20 \text{ V}) = 19.87 \text{ V}$

d. $i_C = \frac{20 \text{ V}}{10 \text{ k}\Omega} e^{-t/\tau} = 2 \text{ mA} e^{-t/100 \text{ ms}}$
 $v_R = E e^{-t/\tau} = 20 \text{ V} e^{-t/100 \text{ ms}}$

e.

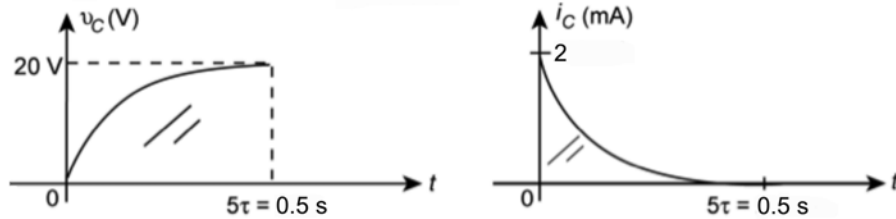

20. a. $\tau = RC = (100 \text{ k}\Omega)(10 \mu\text{F}) = 1 \text{ s}$
- b. $v_C = E(1 - e^{-t/\tau}) = 20 \text{ V}(1 - e^{-t/1 \text{ s}})$
- c. $1\tau = 12.64 \text{ V}$, $3\tau = 19 \text{ V}$, $5\tau = 19.87 \text{ V}$
- d. $i_C = \frac{20 \text{ V}}{100 \text{ k}\Omega} e^{-t/\tau} = 200 \mu\text{A} e^{-t/1 \text{ s}}$
 $v_R = E e^{-t/\tau} = 20 \text{ V} e^{-t/1 \text{ s}}$

e. Same as problem 21 with $5\tau = 5 \text{ s}$ and $I_m = 200 \mu\text{A}$


21. a. $\tau = RC = (2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega)1 \mu\text{F} = (5.5 \text{ k}\Omega)(1 \mu\text{F}) = 5.5 \text{ ms}$
- b. $v_C = E(1 - e^{-t/\tau}) = 100 \text{ V}(1 - e^{-t/5.5 \text{ ms}})$
- c. $1\tau = 63.21 \text{ V}$, $3\tau = 95.02 \text{ V}$, $5\tau = 99.33 \text{ V}$

d. $i_C = \frac{E}{R_T} e^{-t/\tau} = \frac{100 \text{ V}}{5.5 \text{ k}\Omega} e^{-t/\tau} = 18.18 \text{ mA} e^{-t/5.5 \text{ ms}}$

$$V_{R_2} = \frac{3.3 \text{ k}\Omega (100 \text{ V})}{3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 60 \text{ V}$$

$$v_{R_2} = 60 \text{ V} e^{-t/5.5 \text{ ms}}$$


e.

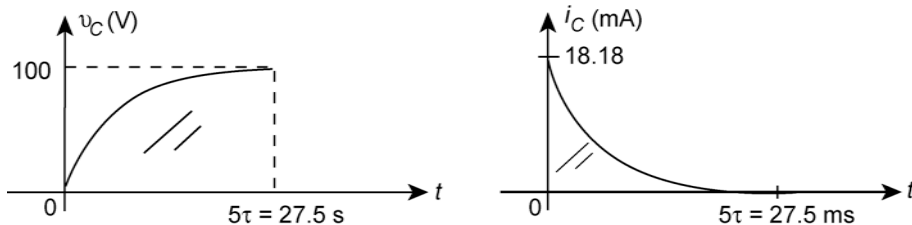

22. a. $R = 68 \text{ k}\Omega + 22 \text{ k}\Omega = 90 \text{ k}\Omega$
 $\tau = RC = (90 \text{ k}\Omega)(18 \text{ }\mu\text{F}) = \mathbf{1.62 \text{ s}}$

b. $v_C = E(1 - e^{-t/\tau}) = (80 \text{ V} - 30 \text{ V})(1 - e^{-t/\tau})$
 $v_C = \mathbf{50 \text{ V}(1 - e^{-t/1.62\text{s}})}$

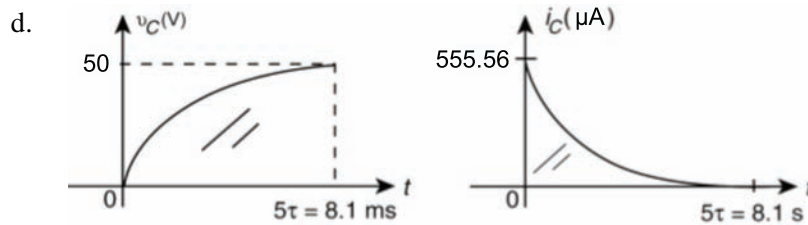c. $i_C = \frac{E}{R} e^{-t/\tau} = \frac{50 \text{ V}}{90 \text{ k}\Omega} e^{-t/\tau} = \mathbf{555.56 \text{ }\mu\text{A}e^{-t/1.62\text{s}}}$



23. a. $\mathbf{100 \text{ }\mu\text{s}}$

b. $v_C = 12 \text{ V}(1 - e^{-50\mu\text{s}/100\mu\text{s}}) = 12 \text{ V}(1 - e^{-0.5}) = 12 \text{ V}(1 - 0.607)$
 $= 12 \text{ V}(.393) = \mathbf{4.72 \text{ V}}$

c. $v_C = 12 \text{ V}(1 - e^{-1\text{ms}/100\mu\text{s}}) = 12 \text{ V}(1 - e^{-10}) = 12 \text{ V}(1 - 45.4 \times 10^{-6})$
 $\cong 12 \text{ V}(999.95 \times 10^{-3}) \cong \mathbf{12 \text{ V}}$

24. a. $\tau = 20 \text{ ms}, 5\tau = 5(20 \text{ ms}) = \mathbf{100 \text{ ms}}$

b. $\tau = RC, R = \frac{\tau}{C} = \frac{20 \text{ ms}}{10 \text{ }\mu\text{F}} = \mathbf{2 \text{ k}\Omega}$

c. $v_C(20 \text{ ms}) = 40 \text{ mV}(1 - e^{-20\text{ms}/20\text{ms}}) = 40 \text{ mV}(1 - e^{-1})$
 $= 40 \text{ mV}(1 - .368) = 40 \text{ mV}(0.632) = \mathbf{25.28 \text{ mV}}$

d. $v_C = 40 \text{ mV}(1 - e^{-10}) = 40 \text{ mV}(1 - 45 \times 10^{-6}) \cong \mathbf{40 \text{ mV}}$

e. $Q = CV = (10 \text{ }\mu\text{F})(40 \text{ mV}) = \mathbf{0.4 \text{ }\mu\text{C}}$

f. $\tau = RC = (1000 \times 10^6 \Omega)(10 \text{ }\mu\text{F}) = 10 \times 10^3 \text{ s}$

$$5\tau = 50 \times 10^3 \text{ s} \left[\frac{1 \text{ min}}{60 \text{ s}} \right] \left[\frac{1 \text{ h}}{60 \text{ min}} \right] = \mathbf{13.89 \text{ h}}$$

25. a. $\tau = RC = (4.7 \text{ k}\Omega)(56 \text{ }\mu\text{F}) = \mathbf{263.2 \text{ ms}}$

b. $v_C = E(1 - e^{-t/\tau}) = \mathbf{22 \text{ V}(1 - e^{-t/263.2\text{ms}})}$


$$i_C = \frac{E}{R} e^{-t/\tau} = \frac{22 \text{ V}}{4.7 \text{ k}\Omega} e^{-t/263.2\text{ms}} = \mathbf{4.68 \text{ mA}e^{-t/263.2\text{ms}}}$$

c. $v_C(1 \text{ s}) = 22 \text{ V}(1 - e^{-1\text{s}/263.2\text{ms}}) = 22 \text{ V}(1 - e^{-3.8})$
 $= 22 \text{ V}(1 - 22.37 \times 10^{-3}) = \mathbf{21.51 \text{ V}}$

$$i_C(1 \text{ s}) = 4.68 \text{ mA}e^{-1\text{s}/263.2\text{ms}} = 4.68 \text{ mA}(22.37 \times 10^{-3}) = \mathbf{0.105 \text{ mA}}$$

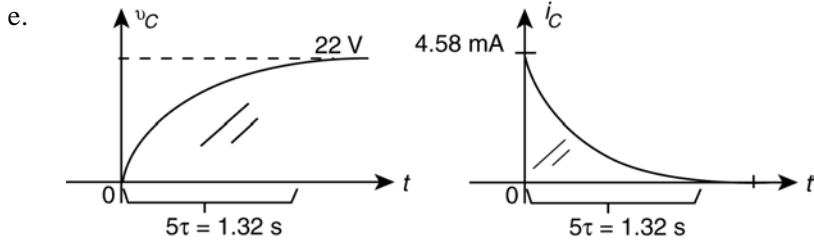d. $v_C = \mathbf{21.51 \text{ V}e^{-t/263.2\text{ms}}}$


$$i_C = \frac{21.51 \text{ V}}{4.7 \text{ k}\Omega} e^{-t/263.2\text{ms}} = \mathbf{4.58 \text{ mA}e^{-t/263.2\text{ms}}}$$




26. a. $\tau = RC = (3 \text{ k}\Omega + 2 \text{ k}\Omega)(2 \text{ }\mu\text{F}) = 10 \text{ ms}$
 $v_C = 30 \text{ V}(1 - e^{-t/10\text{ms}})$
 $i_C = \frac{30 \text{ V}}{5 \text{ k}\Omega} e^{-t/10\text{ms}} = 6 \text{ mA} e^{-t/10\text{ms}}$
 $v_{R_1} = i_C R_1 = (6 \text{ mA})(3 \text{ k}\Omega)e^{-t/10\text{ms}} = 18 \text{ V}e^{-t/10\text{ms}}$


b. 100ms: $e^{-10} = 45.4 \times 10^{-6}$
 $v_C = 30 \text{ V}(1 - 45.4 \times 10^{-6}) = 30 \text{ V}$
 $i_C = 6 \text{ mA}(45.4 \times 10^{-6}) = 0.27 \text{ }\mu\text{A}$
 $v_{R_1} = 18 \text{ V}(45.4 \times 10^{-6}) = 0.82 \text{ mV}$

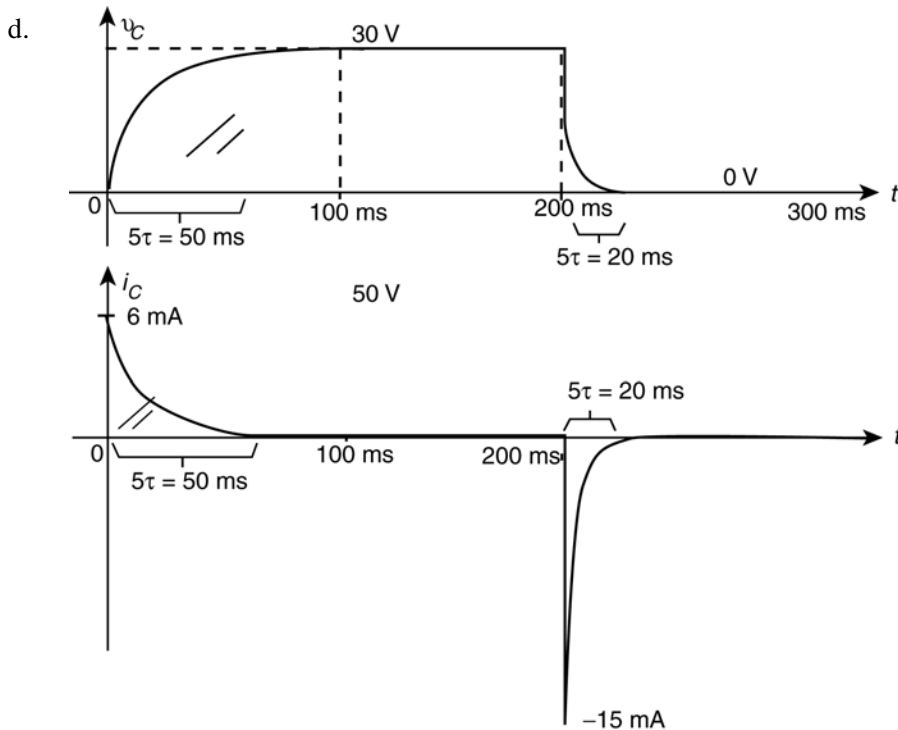c. 200 ms: $\tau' = R_2 C = (2 \text{ k}\Omega)(2 \text{ }\mu\text{F}) = 4 \text{ ms}$
 $v_C = 30 \text{ V}e^{-t/4\text{ms}}$
 $i_C = -\frac{30 \text{ V}}{2 \text{ k}\Omega} e^{-t/4\text{ms}} = -15 \text{ mA}e^{-t/4\text{ms}}$
 At $t = 0$: $v_{R_2} = i_C R_2 = (6 \text{ mA})(2 \text{ k}\Omega)e^{-t/10 \text{ ms}}$
 $= 12 \text{ V}e^{-t/10 \text{ ms}}$
 At $t = 200 \text{ ms}$: $v_{R_2} = -(15 \text{ mA})(2 \text{ k}\Omega)e^{-t/4 \text{ ms}}$
 $= -30 \text{ V}e^{-t/4 \text{ ms}}$



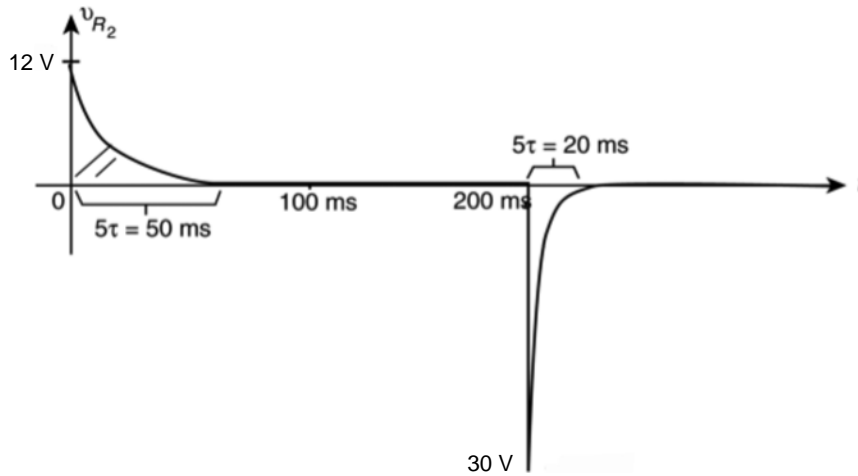

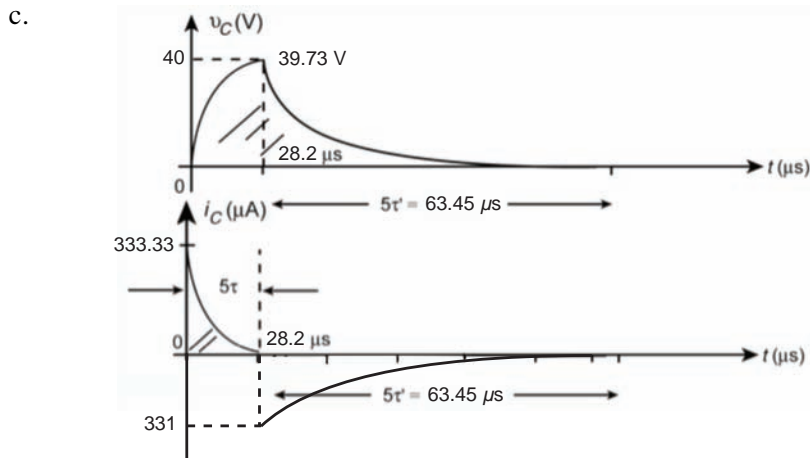27. a. $\tau = RC = (120 \text{ k}\Omega)(47 \text{ pF}) = 5.64 \mu\text{s}$
 $v_C = 40 \text{ V}(1 - e^{-t/5.64\mu\text{s}})$
 $i_C = \frac{40 \text{ V}}{120 \text{ k}\Omega} e^{-t/5.64\mu\text{s}} = 333.33 \mu\text{A}e^{-t/5.64\mu\text{s}}$
- b. $\tau = RC = (270 \text{ k}\Omega)(47 \text{ pF}) = 12.69 \mu\text{s}$
 At 5τ
 $v_C = 40 \text{ V}(1 - e^{-5\tau/\tau})$
 $= 40 \text{ V}(1 - e^{-5}) = 40 \text{ V}(1 - 6.74 \times 10^{-3})$
 $= 39.73 \text{ V}$
 $\therefore v_C = 39.73 \text{ V}e^{-t/12.69\mu\text{s}}$
 $i_C = -\frac{39.73 \text{ V}}{270 \text{ k}\Omega} e^{-t/12.69\mu\text{s}} = -331 \mu\text{A}e^{-t/12.69\mu\text{s}}$



28. a. $\tau = RC = (2 \text{ m}\Omega)(1000 \text{ }\mu\text{F}) = 2 \text{ }\mu\text{s}$
 $5\tau = 10 \text{ }\mu\text{s}$



b. $I_m = \frac{V}{R} = \frac{12 \text{ V}}{2 \text{ m}\Omega} = 6 \text{ kA}$

c. yes

29. a. $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \text{ }\mu\text{F}) = 22.1 \text{ ms}$, $V_f = 40 \text{ V}$, $V_i = 6 \text{ V}$
 $v_C = 40 \text{ V} + (6 \text{ V} - 40 \text{ V})e^{-t/22.1\text{ms}}$
 $v_C = 40 \text{ V} - 34 \text{ V}e^{-t/22.1\text{ms}}$

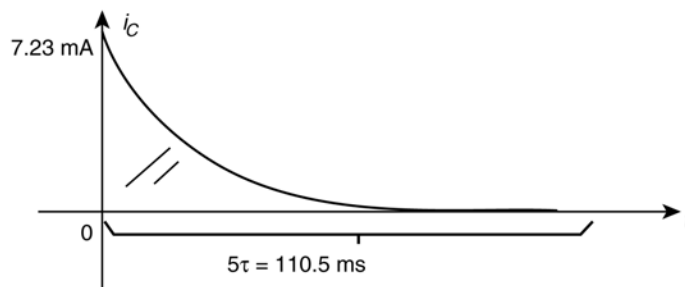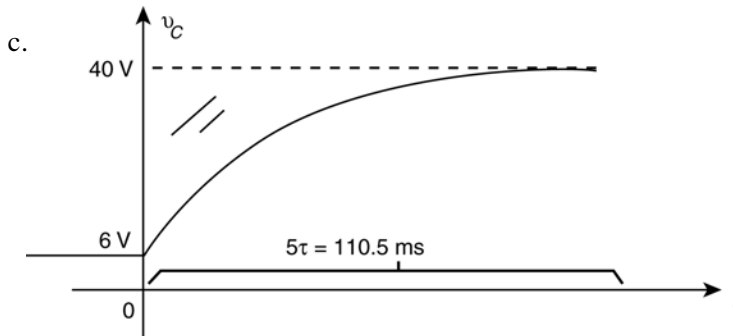b. Initially $V_R = E + v_C = 40 \text{ V} - 6 \text{ V} = 34 \text{ V}$


$i_C = \frac{V_R}{R} e^{-t/\tau} = \frac{34 \text{ V}}{4.7 \text{ k}\Omega} e^{-t/22.1\text{ms}} = 7.23 \text{ mA} e^{-t/22.1\text{ms}}$



30. a. $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \text{ }\mu\text{F}) = 22.1 \text{ ms}$, $V_f = 40 \text{ V}$, $V_i = -40 \text{ V}$
 $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $= 40 \text{ V} + (-40 \text{ V} - 40 \text{ V})e^{-t/22.1\text{ms}}$
 $v_C = 40 \text{ V} - 80 \text{ V}e^{-t/22.1\text{ms}}$

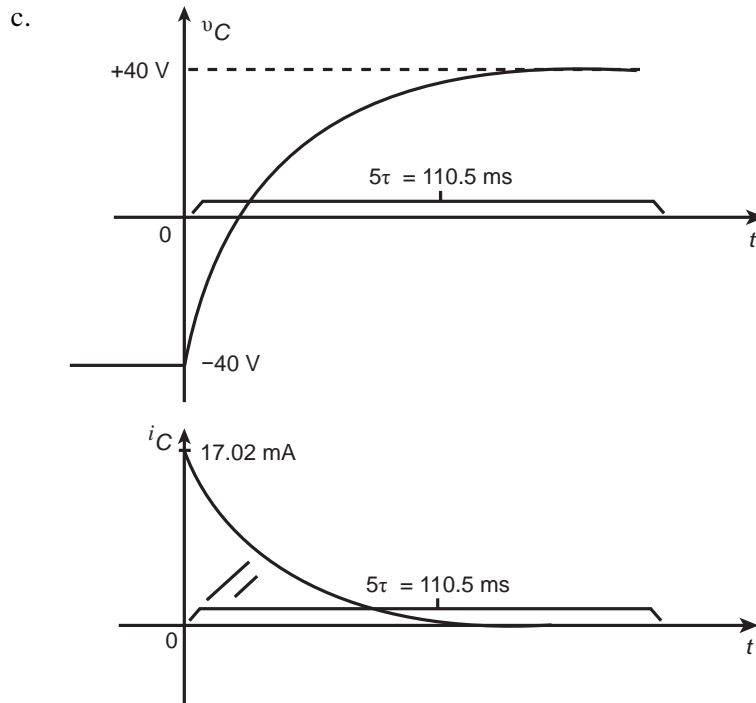
b. Initially $V_R = E + v_C = 40 \text{ V} - (-40 \text{ V}) = 80 \text{ V}$

and $i_C = \frac{V_R}{R} = \frac{80 \text{ V}}{4.7 \text{ k}\Omega} e^{-t/22.1\text{ms}} = 17.02 \text{ mA} e^{-t/22.1\text{ms}}$






31. a. $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \text{ }\mu\text{F}) = 22.1 \text{ ms}$, $V_f = 40 \text{ V}$, $V_i = 40 \text{ V}$
 $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $= 40 \text{ V} + (40 \text{ V} - 40 \text{ V})e^{-t/\tau}$
 $= 40 \text{ V} + 0e^{-t/\tau}$
 $v_C = \mathbf{40 \text{ V}}$

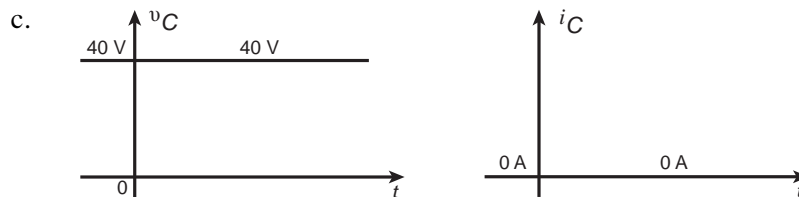
b. Initially $V_R = E - v_C = 40 \text{ V} - 40 \text{ V} = 0 \text{ V}$
and $i_C = \frac{V_R}{R} e^{-t/\tau} = \frac{0 \text{ V}}{R} e^{-t/\tau} = \mathbf{0 \text{ A}}$



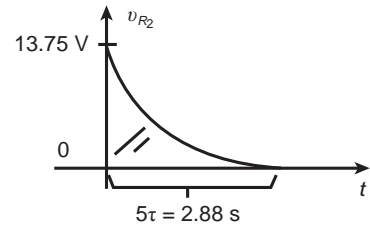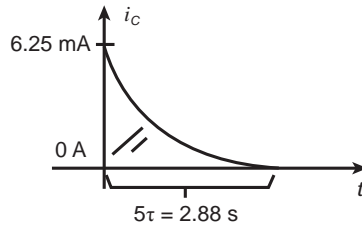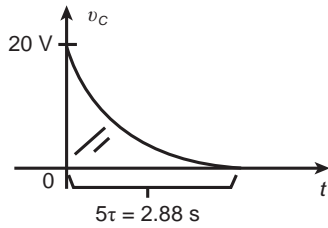32. $\tau = RC = (R_1 + R_2)(C) = (1 \text{ k}\Omega + 2.2 \text{ k}\Omega)(180 \text{ }\mu\text{F}) = (3.2 \text{ k}\Omega)(180 \text{ }\mu\text{F}) = 576 \text{ ms}$
 $v_C = \mathbf{20 \text{ V}} e^{-t/576\text{ms}}$
 $i_C = \frac{V_i}{R_1 + R_2} e^{-t/\tau} = \frac{20 \text{ V}}{3.2 \text{ k}\Omega} e^{-t/576\text{ms}} = \mathbf{6.25 \text{ mA}} e^{-t/576\text{ms}}$
VDR: $V_{R_2} = \frac{2.2 \text{ k}\Omega (20 \text{ V})}{2.2 \text{ k}\Omega + 1 \text{ k}\Omega} = 13.75 \text{ V}$
 $v_{R_2} = \mathbf{13.75 \text{ V}} e^{-t/576\text{ms}}$




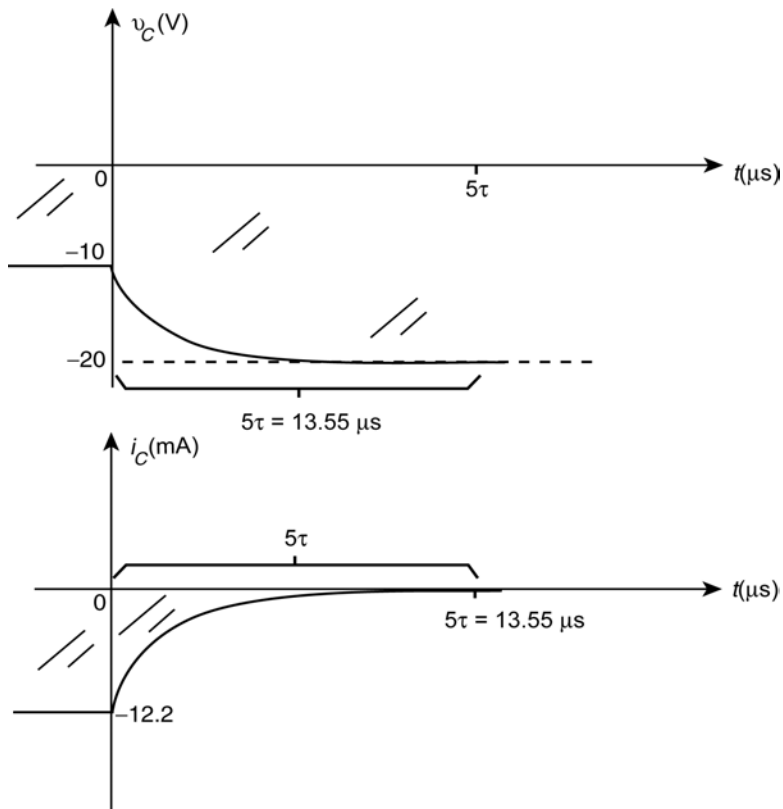33. $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $\tau = RC = (820 \Omega)(3300 \text{ pF}) = 2.71 \mu\text{s}$, $V_f = -20 \text{ V}$, $V_i = -10 \text{ V}$
 $v_C = -20 \text{ V} + (-10 \text{ V} - (-20 \text{ V}))e^{-t/2.71\mu\text{s}}$
 $v_C = -20 \text{ V} + 10 \text{ V}e^{-t/2.71\mu\text{s}}$
 $I_m = \frac{-(20 \text{ V} - 10 \text{ V})}{820 \Omega} = \frac{-10 \text{ V}}{820 \Omega} = -12.2 \text{ mA}$
 $i_C = i_R = -12.2 \text{ mA}e^{-t/2.71\mu\text{s}}$




34. a. $R = 10 \text{ k}\Omega + 8.2 \text{ k}\Omega = 18.2 \text{ k}\Omega$
 $\tau = RC = (18.2 \text{ k}\Omega)(6.8 \mu\text{F}) = 123.76 \text{ ms}$
 $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $V_f = 20 \text{ V} + 40 \text{ V} = 60 \text{ V}$
 $V_i = -8 \text{ V}$
 $v_C = 60 \text{ V} + (-8 \text{ V} - 60 \text{ V})e^{-t/123.76 \text{ ms}}$
 $v_C = 60 \text{ V} - 68 \text{ V}e^{-t/123.76 \text{ ms}}$
 $I_m = \frac{8 \text{ V} + 20 \text{ V} + 40 \text{ V}}{18.2 \text{ k}\Omega} = 3.74 \text{ mA}$
 $i_C = 3.74 \text{ mA}e^{-t/123.76 \text{ ms}}$

b.

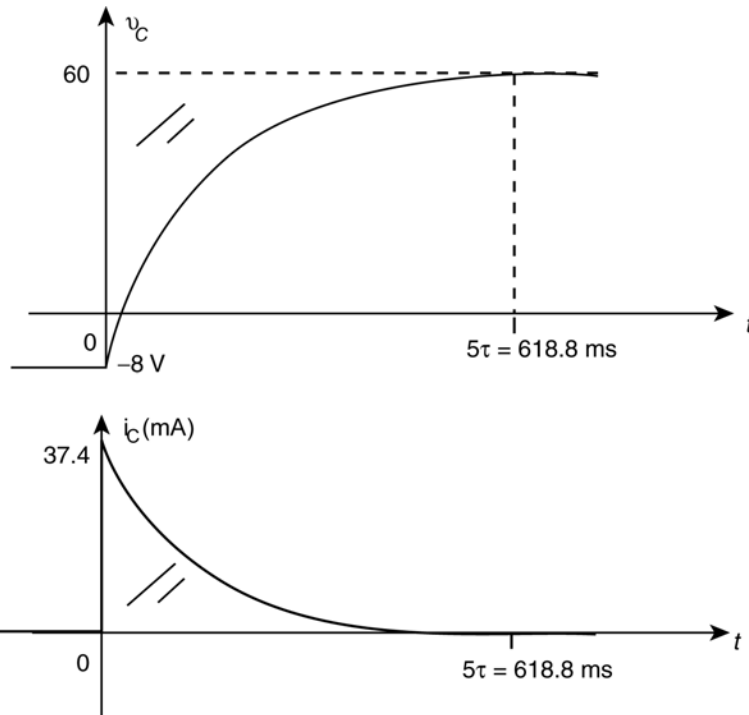


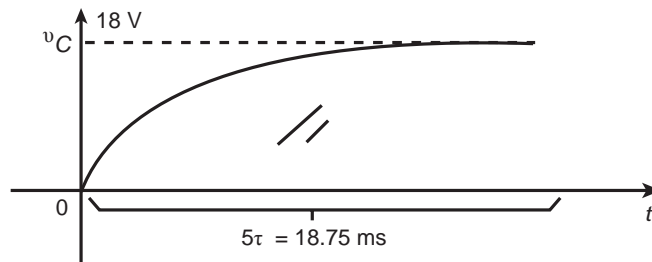35. a. $C\tau = 20 \mu\text{F} + 47 \mu\text{F} = 67 \mu\text{F}$
 $\tau = RC = (56 \text{ k}\Omega)(67 \mu\text{F}) = 3.75 \text{ s}$
 $v_C = 18 \text{ V}(1 - e^{-t/3.75 \text{ s}})$



- b. $v_C = 18 \text{ V}(1 - e^{-10\text{s}/5.75 \text{ s}})$
 $= 18 \text{ V}(1 - e^{-2.67})$
 $= 18 \text{ V}(1 - 69.25 \times 10^{-3})$
 $= 18 \text{ V}(0.931)$
 $= 16.76 \text{ V}$
- c. $v_C = 18 \text{ V}(1 - e^{-5})$
 $= 18 \text{ V}(1 - 6.74 \times 10^{-3})$
 $= 18 \text{ V}(.993)$
 $= 17.88 \text{ V}$
 $Q_{20\mu\text{F}} = CV = (20 \mu\text{F})(17.88 \text{ V}) = 357.6 \mu\text{C}$
 $Q_{47\mu\text{F}} = CV = (47 \mu\text{F})(17.88 \text{ V}) = 840.36 \mu\text{C}$

36. a. Network redrawn:

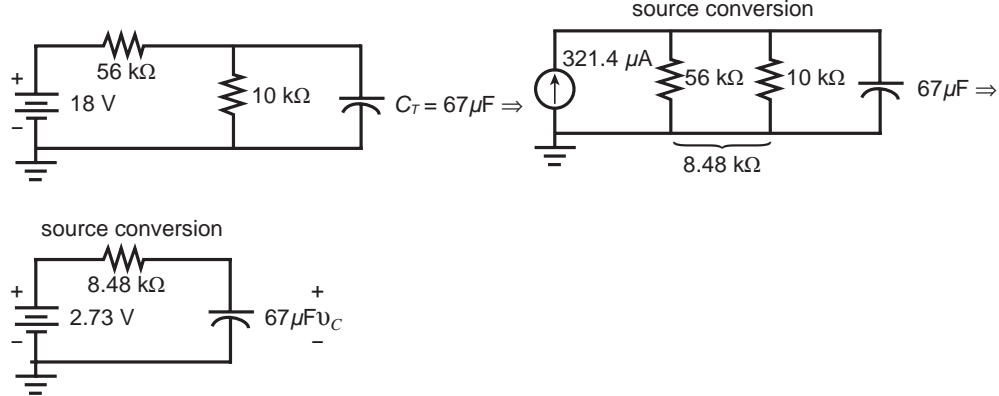

$$\tau = RC = (8.48 \text{ k}\Omega)(67 \mu\text{F}) = 568.2 \text{ ms}$$

$$v_C = 2.73 \text{ V}(1 - e^{-t/568.2 \text{ ms}})$$

- b. $v_C = 2.73 \text{ V}(1 - e^{-10\text{s}/568.2 \text{ ms}})$
 $= 2.73 \text{ V}(1 - e^{-17.6})$
 $= 2.73 \text{ V}(1 - 22.72 \times 10^{-9})$
 $\cong 2.73 \text{ V}$
- c. $v_C = 2.73 \text{ V}(1 - e^{-5}) = 2.73 \text{ V}(0.993) = 2.72 \text{ V}$
 $Q_{20\mu\text{F}} = CV = (20 \mu\text{F})(2.72 \text{ V}) = 54.4 \mu\text{C}$
 $Q_{47\mu\text{F}} = CV = (47 \mu\text{F})(2.72 \text{ V}) = 127.84 \mu\text{C}$

37. a. $v_C = 140 \text{ mV}(1 - e^{-1\text{ms}/2 \text{ ms}}) = 140 \text{ mV}(1 - e^{-0.5}) = 140 \text{ mV}(1 - 0.6065)$
 $= 140 \text{ mV}(0.3935) = 55.59 \text{ mV}$
- b. $v_C = 140 \text{ mV}(1 - e^{-10}) = 140 \text{ mV}(1 - 45.4 \times 10^{-6})$
 $\cong 139.99 \text{ mV}$
- c. $100 \text{ mV} = 140 \text{ mV}(1 - e^{-t/2 \text{ ms}})$
 $0.714 = 1 - e^{-t/2 \text{ ms}}$
 $0.286 = e^{-t/2 \text{ ms}}$
 $\log_e 0.286 = \log_e e^{-t/2 \text{ ms}}$
 $1.252 = -t/2 \text{ ms}$
 $t = 1.252 (2 \text{ ms}) = 2.5 \text{ ms}$
- d. $v_C = 138 \text{ mV} = 140 \text{ mV}(1 - e^{t/2 \text{ ms}})$
 $0.986 = 1 - e^{-t/2 \text{ ms}}$
 $-14 \times 10^{-3} = -e^{-t/2 \text{ ms}}$
 $\log_e 14 \times 10^{-3} = -t/2 \text{ ms}$
 $-4.268 = -t/2 \text{ ms}$
 $t = (4.268)(2 \text{ ms}) = 8.54 \mu\text{s}$

$$\begin{aligned}
38. \quad \tau &= RC = (33 \text{ k}\Omega)(20 \text{ }\mu\text{F}) = 0.66 \text{ s} \\
v_C &= 12 \text{ V}(1 - e^{-t/0.66 \text{ s}}) \\
8 \text{ V} &= 12 \text{ V}(1 - e^{-t/0.66 \text{ s}}) \\
8 \text{ V} &= 12 \text{ V} - 12 \text{ V}(1 - e^{-t/0.66 \text{ s}}) \\
-4 \text{ V} &= -12 \text{ V}e^{-t/0.66 \text{ s}} \\
0.333 &= e^{-t/0.66 \text{ s}} \\
\log_e 0.333 &= -t/0.66 \text{ s} \\
-1.0996 &= -t/0.66 \text{ s} \\
t &= 1.0996(0.66 \text{ s}) = \mathbf{0.73 \text{ s}}
\end{aligned}$$

$$\begin{aligned}
39. \quad t &= -\tau \log_e \left(1 - \frac{v_C}{E} \right) \\
10 \text{ s} &= -\tau \log_e \left(1 - \frac{12 \text{ V}}{20 \text{ V}} \right) \\
&\quad \underbrace{\hspace{1.5cm}}_{.4} \\
&\quad \underbrace{\hspace{1.5cm}}_{-916.29 \times 10^{-3}} \\
\tau &= \frac{10 \text{ s}}{0.916} = 10.92 \text{ s} \\
\tau = RC &\Rightarrow R = \frac{\tau}{C} = \frac{10.92 \text{ s}}{200 \text{ }\mu\text{F}} = \mathbf{54.60 \text{ k}\Omega}
\end{aligned}$$

$$\begin{aligned}
40. \quad \text{a.} \quad \tau &= RC = (12 \text{ k}\Omega + 8.2 \text{ k}\Omega)(6.8 \text{ }\mu\text{F}) = 137.36 \text{ ms} \\
v_C &= 60 \text{ V}(1 - e^{-t/\tau}) \\
48 \text{ V} &= 60 \text{ V}(1 - e^{-t/\tau}) \\
0.8 &= 1 - e^{-t/\tau} \\
0.2 &= 1 - e^{-t/\tau} \\
\log_e 0.2 &= \log_e e^{-t/\tau} \\
-1.61 &= -t/\tau \\
t &= (1.61)\tau = (1.61)(137.36 \text{ ms}) = \mathbf{221.15 \text{ ms}}
\end{aligned}$$

$$\begin{aligned}
\text{b.} \quad i_C &= \frac{E}{R} e^{-t/\tau} = \frac{60 \text{ V}}{20.2 \text{ k}\Omega} e^{-t/\tau} \\
&= 2.97 \text{ mA} e^{-t/137.36 \text{ ms}} \\
i_C(221.15 \text{ ms}) &= 2.97 \text{ mA} e^{-221.15 \text{ ms}/137.36 \text{ ms}} \\
&= 2.97 \text{ mA} e^{-1.61} \\
&= 2.97 \text{ mA} (199.89 \times 10^{-3}) \\
&= \mathbf{0.594 \text{ mA}}
\end{aligned}$$

$$\begin{aligned}
\text{c.} \quad t &= 2\tau \\
i_C &= 2.97 \text{ mA} e^{-2\tau/\tau} = 2.97 \text{ mA} e^{-2} \\
&= 0.4 \text{ mA} \quad \underbrace{\hspace{1.5cm}}_{0.135}
\end{aligned}$$


$$P = EI = (60 \text{ V})(0.4 \text{ mA}) = \mathbf{24 \text{ mW}}$$

41. a. $v_m = v_R = Ee^{-t/\tau} = 60 \text{ V}e^{-1/2} = 60 \text{ V}e^{-1}$
 $= 60 \text{ V}(0.3679)$
 $= \mathbf{22.07 \text{ V}}$


b. $i_C = \frac{E}{R}e^{-t/\tau} = \frac{60 \text{ V}}{10 \text{ M}\Omega}e^{-2t/\tau} = 6 \mu\text{A}e^{-2}$
 $= 6 \mu\text{A}(0.1353)$
 $= \mathbf{0.81 \mu\text{A}}$

c. $v_C = E(1 - e^{-t/\tau})$ $\tau = RC = (10 \text{ M}\Omega)(0.2 \mu\text{F}) = 2 \text{ s}$
 $50 \text{ V} = 60 \text{ V}(1 - e^{-t/2 \text{ s}})$
 $0.8333 = 1 - e^{-t/2 \text{ s}}$
 $\log_e 0.1667 = -t/2 \text{ s}$
 $t = -(2 \text{ s})(-1.792)$
 $= \mathbf{3.58 \text{ s}}$


42. a. Thevenin's theorem:

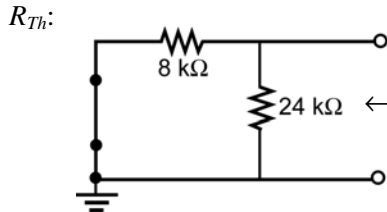

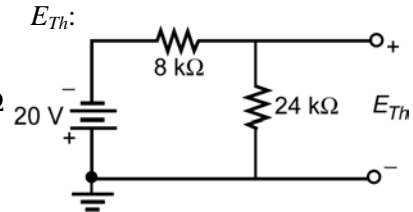$\leftarrow R_{Th} = 8 \text{ k}\Omega \parallel 24 \text{ k}\Omega$
 $= 6 \text{ k}\Omega$




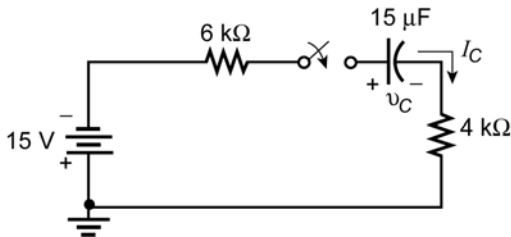$E_{Th} = \frac{-24 \text{ k}\Omega (20 \text{ V})}{24 \text{ k}\Omega + 8 \text{ k}\Omega} = -15 \text{ V}$



$\tau = RC = (10 \text{ k}\Omega)(15 \mu\text{F}) = 0.15 \text{ s}$
 $v_C = E(1 - e^{-t/\tau})$
 $= \mathbf{-15 \text{ V}(1 - e^{-t/0.15 \text{ s}})}$

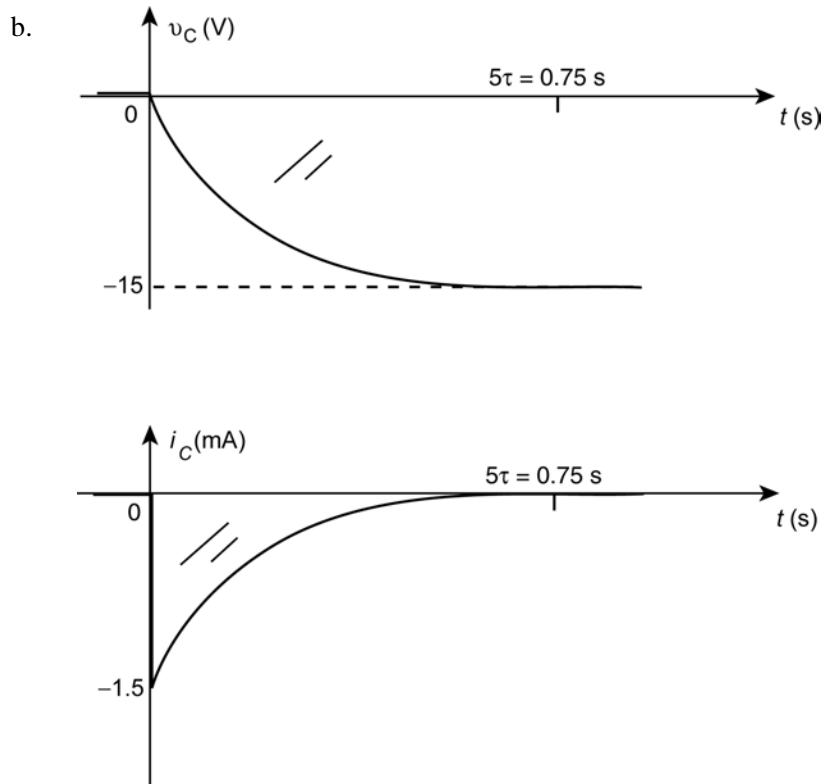$i_C = \frac{E}{R}e^{-t/\tau} = -\frac{15 \text{ V}}{10 \text{ k}\Omega}e^{-t/0.15} = \mathbf{-1.5 \text{ mA}e^{-t/0.15 \text{ s}}}$



43. a. Source conversion and combining series resistors:

$$E = -(4 \text{ mA})(6.8 \text{ k}\Omega) = -27.2 \text{ V}$$

$$R_T = 6.8 \text{ k}\Omega + 1.5 \text{ k}\Omega = 8.3 \text{ k}\Omega$$

$$V_f = -27.2 \text{ V}, V_i = 10 \text{ V}$$

$$\tau = RC = (8.3 \text{ k}\Omega)(2.2 \mu\text{F}) = 18.26 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-t/\tau}$$



$$= -27.2 \text{ V} + (10 \text{ V} - (-27.2 \text{ V}))e^{-t/18.26 \text{ ms}}$$

$$v_C = -27.2 \text{ V} + 37.2 \text{ V}e^{-t/18.26 \text{ ms}}$$


$$v_R(0+) = -27.2 \text{ V} - (-27.2 \text{ V})e^{-t/18.26 \text{ ms}} = -37.2 \text{ V}$$

$$i_C = -\frac{32.7 \text{ V}}{8.3 \text{ k}\Omega} e^{-t/18.26 \text{ ms}}$$
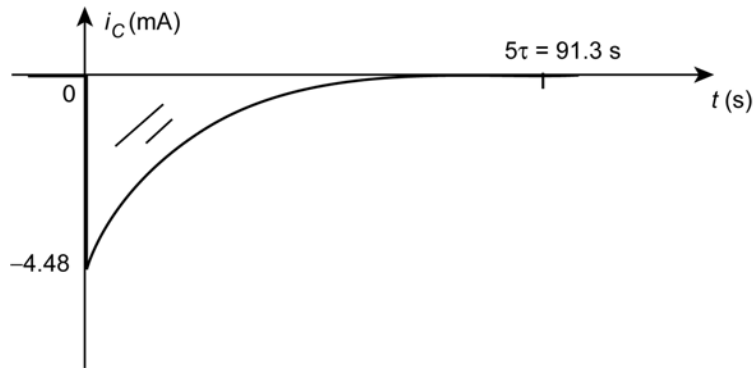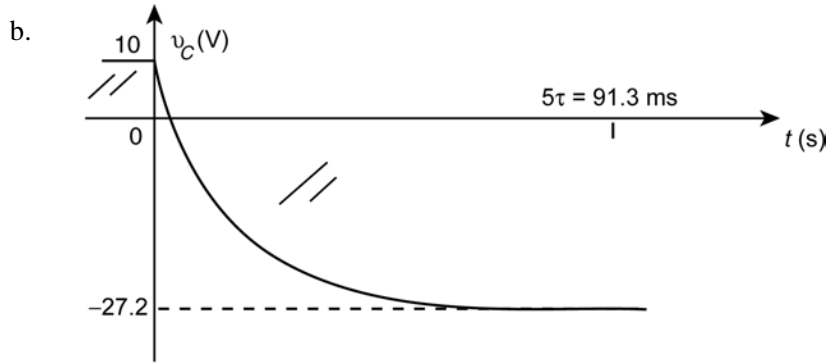
$$i_C = -4.48 \text{ mA}e^{-t/18.26 \text{ ms}}$$



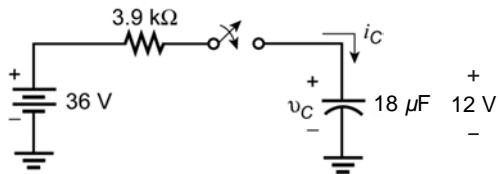44. a. $R_{Th} = 3.9 \text{ k}\Omega + 0 \text{ }\Omega \parallel 1.8 \text{ k}\Omega = 3.9 \text{ k}\Omega$
 $E_{Th} = 36 \text{ V}$



$$\tau = RC = (3.9 \text{ k}\Omega)(18 \text{ }\mu\text{F}) = 70.2 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-t/\tau}$$



$$= 36 \text{ V} + (+12 \text{ V} - 36 \text{ V})e^{-t/70.2 \text{ ms}}$$

$$v_C = \mathbf{36 \text{ V} - 24 \text{ V}e^{-t/70.2 \text{ ms}}}$$

$$v_R(0+) = 24 \text{ V} - 12 \text{ V} = 24 \text{ V}$$

$$i_C = \frac{24 \text{ V}}{3.9 \text{ k}\Omega} e^{-t/70.2 \text{ ms}}$$

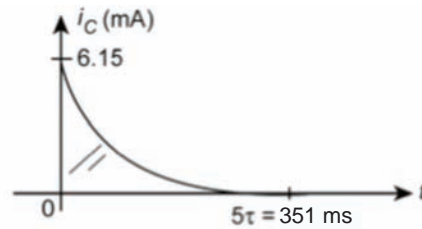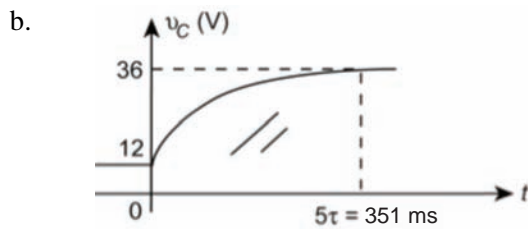
$$i_C = \mathbf{6.15 \text{ mA}e^{-t/70.2 \text{ ms}}}$$



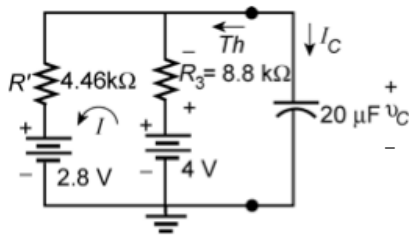45. Source conversion:

$$E = IR_1 = (5 \text{ mA})(0.56 \text{ k}\Omega) = 2.8 \text{ V}$$

$$R' = R_1 + R_2 = 0.56 \text{ k}\Omega + 3.9 \text{ k}\Omega = 4.46 \text{ k}\Omega$$




$$R_{Th} = 4.46 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega = 2.69 \text{ k}\Omega$$

$$I = \frac{4 \text{ V} - 2.8 \text{ V}}{6.8 \text{ k}\Omega + 4.46 \text{ k}\Omega} = \frac{1.2 \text{ V}}{11.26 \text{ k}\Omega} = 0.107 \text{ mA}$$

$$E_{Th} = 4 \text{ V} - (0.107 \text{ mA})(6.8 \text{ k}\Omega)$$

$$= 4 \text{ V} - 0.727 \text{ V}$$

$$= 3.27 \text{ V}$$

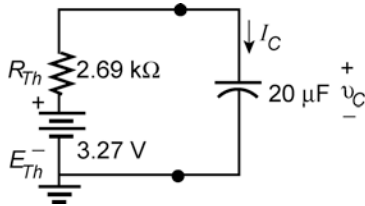

$$v_C = 3.27 \text{ V}(1 - e^{-t/\tau})$$


$$\tau = RC = (2.69 \text{ k}\Omega)(20 \mu\text{F})$$

$$= 53.80 \text{ ms}$$


$$v_C = 3.27 \text{ V}(1 - e^{-t/53.80 \text{ ms}})$$

$$i_C = \frac{3.27 \text{ V}}{2.69 \text{ k}\Omega} e^{-t/\tau}$$
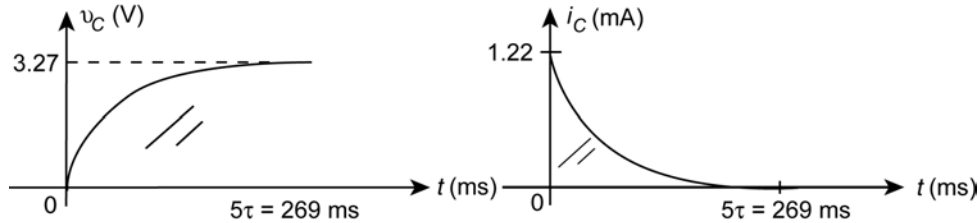
$$= 1.22 \text{ mA} e^{-t/53.80 \text{ ms}}$$



46. a.

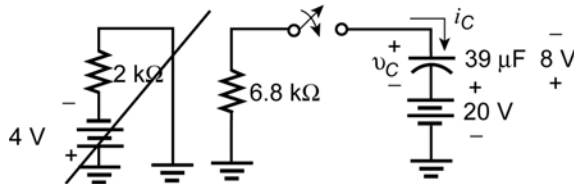

$$\tau = RC = (6.8 \text{ k}\Omega)(39 \mu\text{F}) = 265.2 \text{ ms}$$

$$v_C = V_f + (V_i - V_f)e^{-t/\tau}$$


$$= -20 \text{ V} + (-8 \text{ V} - (-20 \text{ V}))e^{-t/265.2 \text{ ms}}$$

$$v_C = -20 \text{ V} + 12 \text{ V}e^{-t/265.2 \text{ ms}}$$


$$v_R(0+) = +8 \text{ V} - 20 \text{ V} = -12 \text{ V}$$

$$i_C = -\frac{12 \text{ V}}{6.8 \text{ k}\Omega} e^{-t/265.2 \text{ ms}}$$
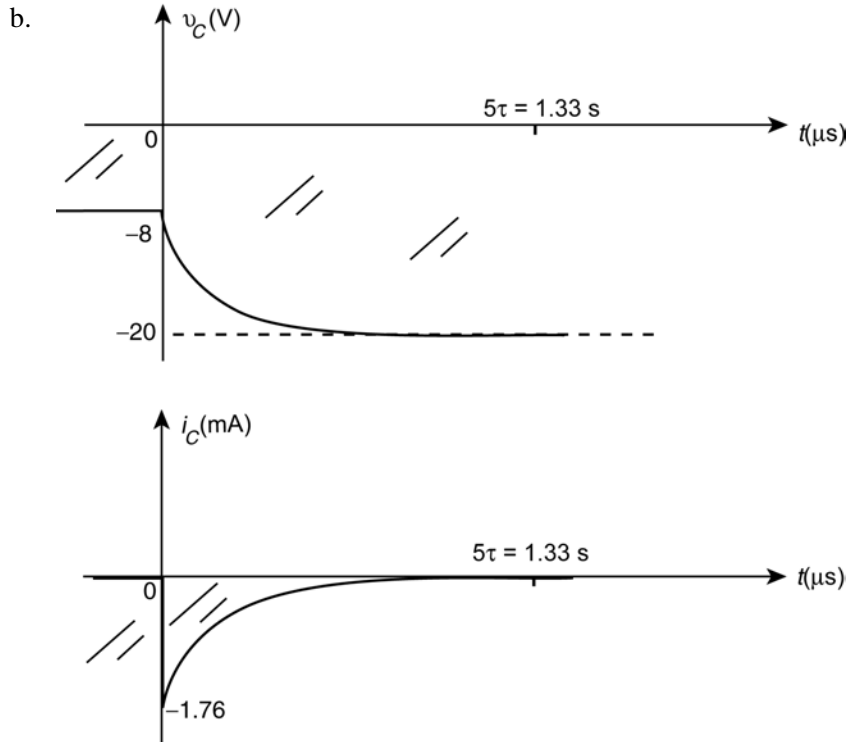
$$i_C = -1.76 \text{ mA}e^{-t/265.2 \text{ ms}}$$



47. a.

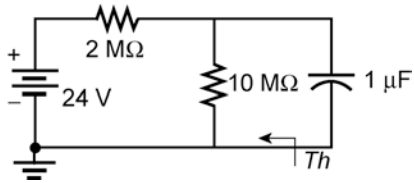

$$R_{Th} = 2 \text{ M}\Omega \parallel 10 \text{ M}\Omega = 1.67 \text{ M}\Omega$$

$$E_{Th} = \frac{10 \text{ M}\Omega(24 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 20 \text{ V}$$

$$\begin{aligned} v_C &= E_{Th}(1 - e^{-t/\tau}) \\ &= 20 \text{ V}(1 - e^{-4t/\tau}) \\ &= 20 \text{ V}(1 - e^{-4}) \\ &= 20 \text{ V}(1 - 0.0183) \\ &= \mathbf{19.63 \text{ V}} \end{aligned}$$

$$\tau = R_{Th}C = (1.67 \text{ M}\Omega)(1 \mu\text{F}) = 1.67 \text{ s}$$

$$i_C = \frac{E}{R} e^{-t/\tau}$$

$$3 \mu\text{A} = \frac{20 \text{ V}}{1.67 \text{ M}\Omega} e^{-t/1.67\text{s}}$$

$$0.25 = e^{-t/1.67\text{s}}$$

$$\log_e 0.25 = -t/1.67 \text{ s}$$

$$\begin{aligned} t &= -(1.67 \text{ s})(-1.39) \\ &= \mathbf{2.32 \text{ s}} \end{aligned}$$

c. $v_{\text{meter}} = v_C$

$$v_C = E_{Th}(1 - e^{-t/\tau})$$

$$10 \text{ V} = 20 \text{ V}(1 - e^{-t/1.67\text{s}})$$

$$0.5 = 1 - e^{-t/1.67\text{s}}$$

$$-0.5 = -e^{-t/1.67\text{s}}$$

$$\log_e 0.5 = -t/1.67 \text{ s}$$

$$\begin{aligned} t &= -(1.67 \text{ s})(-0.69) \\ &= \mathbf{1.15 \text{ s}} \end{aligned}$$


$$48. \quad i_{C_{av}} = C \frac{\Delta v_C}{\Delta t}$$

$$0 \rightarrow 1 \text{ ms: } i_C = 2 \times 10^{-6} \frac{(20 \text{ V})}{1 \text{ ms}} = \mathbf{40 \text{ mA}}$$

$$1 \rightarrow 3 \text{ ms: } i_C = 2 \times 10^{-6} \frac{(0 \text{ V})}{1 \text{ ms}} = \mathbf{0 \text{ mA}}$$

$$3 \rightarrow 6 \text{ ms: } i_C = -2 \times 10^{-6} \frac{(10 \text{ V})}{3 \text{ ms}} = \mathbf{-6.67 \text{ mA}}$$
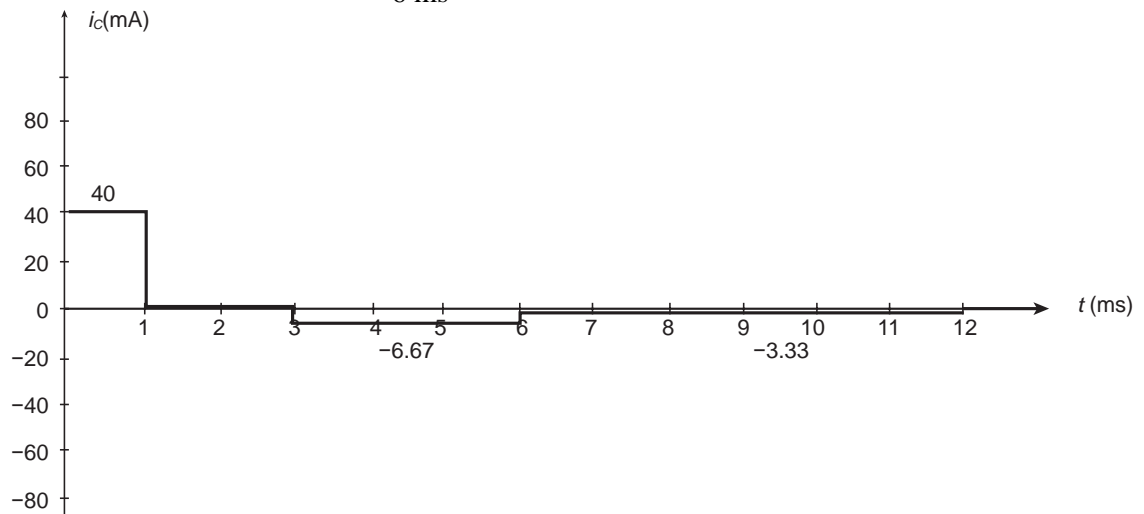
$$6 \rightarrow 12 \text{ ms: } i_C = -2 \times 10^{-6} \frac{(10 \text{ V})}{6 \text{ ms}} = \mathbf{-3.33 \text{ mA}}$$



$$49. \quad i_{C_{av}} = C \frac{\Delta v_C}{\Delta t}$$

$$0 \rightarrow 20 \mu\text{s: } i_C = -4.7 \mu\text{F} \frac{(5 \text{ V})}{20 \mu\text{s}} = \mathbf{-1.18 \text{ A}}$$


$$20 \rightarrow 30 \mu\text{s: } i_C = 4.7 \mu\text{F} \frac{(10 \text{ V})}{10 \mu\text{s}} = \mathbf{4.7 \text{ A}}$$

$$30 \rightarrow 60 \mu\text{s: } i_C = -4.7 \mu\text{F} \frac{(10 \text{ V})}{30 \mu\text{s}} = \mathbf{-1.57 \text{ A}}$$


$$60 \rightarrow 70 \mu\text{s: } i_C = 4.7 \mu\text{F} \frac{(0 \text{ V})}{10 \mu\text{s}} = \mathbf{0 \text{ A}}$$

$$70 \rightarrow 80 \mu\text{s: } i_C = 4.7 \mu\text{F} \frac{(10 \text{ V})}{10 \mu\text{s}} = \mathbf{4.7 \text{ A}}$$
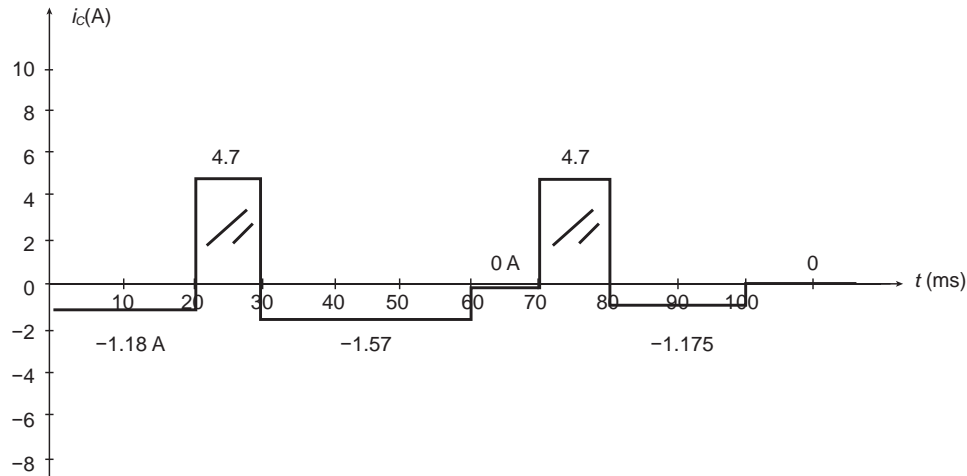
$$80 \mu\text{s} \rightarrow 100 \mu\text{s: } i_C = -4.7 \mu\text{F} \frac{(5 \text{ V})}{20 \mu\text{s}} = \mathbf{-1.175 \text{ A}}$$



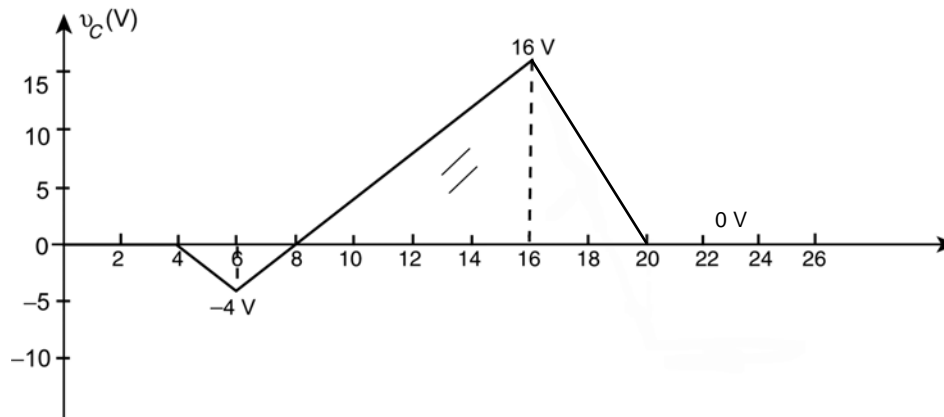50. $i_C = C \frac{\Delta v_C}{\Delta t} \Rightarrow \Delta v_C = \frac{\Delta t}{C}(i_C)$
- 0 → 4 ms: $i_C = 0 \text{ mA}$ $\Delta v_C = 0 \text{ V}$
- 4 → 6 ms: $i_C = -40 \text{ mA}$ $\Delta v_C = \frac{(2 \text{ ms})}{20 \mu\text{F}}(-40 \text{ mA}) = -4 \text{ V}$
- 6 → 16 ms: $i_C = +40 \text{ mA}$ $\Delta v_C = \frac{(10 \text{ ms})}{20 \mu\text{F}}(40 \text{ mA}) = +20 \text{ V}$
- 16 → 20 ms: $i_C = -80 \text{ mA}$ $\Delta v_C = \frac{(4 \text{ ms})}{20 \mu\text{F}}(-80 \text{ mA}) = -16 \text{ V}$
- 20 → 25 ms: $i_C = 0 \text{ mA}$ $\Delta v_C = 0 \text{ V}$



51. $6 \mu\text{F} + 4 \mu\text{F} = 10 \mu\text{F}$, $8 \mu\text{F} + 12 \mu\text{F} = 20 \mu\text{F}$
 $10 \mu\text{F} \parallel 20 \mu\text{F} = \mathbf{6.67 \mu\text{F}}$
52. $C'_T = 6 \mu\text{F} \parallel 12 \mu\text{F} = 4 \mu\text{F}$
 $C''_T = C'_T + 12 \mu\text{F} = 4 \mu\text{F} + 12 \mu\text{F} = 16 \mu\text{F}$
 $6 \mu\text{F} \parallel 6 \mu\text{F} = 3 \mu\text{F}$
 $3 \mu\text{F} \parallel 16 \mu\text{F} = 2.53 \mu\text{F}$
 $C_T = \mathbf{2.53 \mu\text{F}}$

53. $10 \mu\text{F} \parallel 100 \mu\text{F} = 9.09 \mu\text{F}$
 $20 \mu\text{F} + 9.09 \mu\text{F} = 29.09 \mu\text{F}$
 $Q_T = C_T E = (29.09 \mu\text{F})(20 \text{ V}) = \mathbf{581.8 \mu\text{C}}$
 $Q_{20\mu\text{F}} = CV = (20 \mu\text{F})(20 \text{ V}) = \mathbf{400 \mu\text{C}}$
 $V_{20\mu\text{F}} = \mathbf{20 \text{ V}}$
 $Q'_T = C'_T E = (9.09 \mu\text{F})(20 \text{ V}) = 181.8 \mu\text{C}$
 $Q'_T = Q_{10\mu\text{F}} = Q_{100\mu\text{F}} = \mathbf{181.8 \mu\text{C}}$
 $V_{10\mu\text{F}} = \frac{Q}{C} = \frac{181.8 \mu\text{C}}{10 \mu\text{F}} = \mathbf{18.18 \text{ V}}$
 $V_{100\mu\text{F}} = \frac{Q}{C} = \frac{181.8 \mu\text{C}}{100 \mu\text{F}} = \mathbf{1.818 \text{ V}}$
54. $360 \mu\text{F} + 200 \mu\text{F} = 560 \mu\text{F}$
 $470 \mu\text{F} \parallel 560 \mu\text{F} = 255.53 \mu\text{F}$
 $Q_T = Q_3 = C_T E = (255.53 \mu\text{F})(56 \text{ V}) = \mathbf{14.5 \text{ mC}}$
 $V_3 = \frac{Q_3}{C_3} = \frac{14.5 \text{ mC}}{470 \mu\text{F}} = \mathbf{30.4 \text{ V}}$
 $V_1 = V_2 = E - V_3 = 56 \text{ V} - 30.4 \text{ V} = \mathbf{25.6 \text{ V}}$
 $Q_1 = V_1 C_1 = (25.6 \text{ V})(360 \mu\text{F}) = \mathbf{9.2 \text{ mC}}$
 $Q_2 = V_2 C_2 = (25.6 \text{ V})(200 \mu\text{F}) = \mathbf{5.1 \text{ mC}}$
55. steady state – ignore $10 \text{ k}\Omega$ resistor
 $330 \mu\text{F} + 120 \mu\text{F} = 450 \mu\text{F}$
 $C_T = 220 \mu\text{F} \parallel 450 \mu\text{F} = 147.76 \mu\text{F}$
 $Q_T = Q_1 = C_T E = (147.76 \mu\text{F})(20 \text{ V}) = \mathbf{2.96 \text{ mC}}$
 $V_1 = \frac{Q_1}{C_1} = \frac{2.96 \text{ mC}}{220 \mu\text{F}} = \mathbf{13.45 \text{ V}}$
 $V_3 = V_2 = E - V_1 = 20 \text{ V} - 13.45 \text{ V} = \mathbf{6.55 \text{ V}}$
 $Q_2 = C_2 V_2 = (330 \mu\text{F})(6.55 \text{ V}) = \mathbf{2.16 \text{ mC}}$
 $Q_3 = C_3 V_3 = (120 \mu\text{F})(6.55 \text{ V}) = \mathbf{0.786 \text{ mC}}$
56. $V_{4\text{k}\Omega} = \frac{4 \text{ k}\Omega(48 \text{ V})}{4 \text{ k}\Omega + 2 \text{ k}\Omega} = \mathbf{32 \text{ V}} = V_{0.08\mu\text{F}}$
 $Q_{0.08\mu\text{F}} = (0.08 \mu\text{F})(32 \text{ V}) = \mathbf{2.56 \mu\text{C}}$
 $V_{0.04\mu\text{F}} = \mathbf{48 \text{ V}}$
 $Q_{0.04\mu\text{F}} = (0.04 \mu\text{F})(48 \text{ V}) = \mathbf{1.92 \mu\text{C}}$
57. $W_C = \frac{1}{2} CV^2 = \frac{1}{2} (120 \text{ pF})(12 \text{ V})^2 = \mathbf{8,640 \text{ pJ}}$
58. $W = \frac{Q^2}{2C} \Rightarrow Q = \sqrt{2CW} = \sqrt{2(6 \mu\text{F})(1200 \text{ J})} = \mathbf{0.12 \text{ C}}$
59. a. $V_{200\mu\text{F}} = \frac{(220 \text{ k}\Omega + 3.3 \text{ k}\Omega)(12 \text{ V})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 9.85 \text{ V}$
 $V_{100\mu\text{F}} = \frac{(3.3 \text{ k}\Omega)(12 \text{ V})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 5.91 \text{ V}$

$$W_{200\mu\text{F}} = \frac{1}{2}(200 \mu\text{F})(9.85 \text{ V})^2 = \mathbf{970 \text{ mJ}}$$

$$W_{100\mu\text{F}} = \frac{1}{2}(100 \mu\text{F})(5.91 \text{ V})^2 = \mathbf{1.75 \text{ mJ}}$$

60. a. $W_C = \frac{1}{2}CV^2 = \frac{1}{2}(1000 \mu\text{F})(100 \text{ V})^2 = \mathbf{5 \text{ pJ}}$
- b. $Q = CV = (1000 \mu\text{F})(100 \text{ V}) = \mathbf{0.1 \text{ C}}$
- c. $I = Q/t = 0.1 \text{ C}/(1/2000) = \mathbf{200 \text{ A}}$
- d. $P = V_{av}I_{av} = W/t = 5 \text{ J}/(1/2000 \text{ s}) = \mathbf{10,000 \text{ W}}$
- e. $t = Q/I = 0.1 \text{ C}/10 \text{ mA} = \mathbf{10 \text{ s}}$