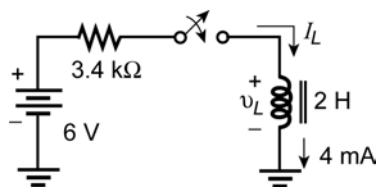


18. a. Source conversion:




$$\tau = \frac{L}{R} = \frac{2 \text{ H}}{3.4 \text{ k}\Omega} = 588.2 \mu\text{s}$$

$$i_L = I_f + (I_i - I_f)e^{-t/\tau}$$

$$I_f = \frac{6 \text{ V}}{3.4 \text{ k}\Omega} = 1.76 \text{ mA}$$

$$i_L = 1.76 \text{ mA} + (4 \text{ mA} - 1.76 \text{ mA})e^{-t/588.2\mu\text{s}}$$
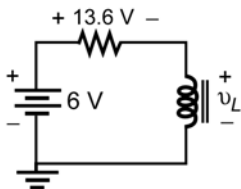
$$i_L = \mathbf{1.76 \text{ mA} + 2.24 \text{ mA} e^{-t/588.2\mu\text{s}}}$$





$$v_R(0+) = 4 \text{ mA}(3.4 \text{ k}\Omega) = 13.6 \text{ V}$$


$$\text{KVL: } +6 \text{ V} - 13.6 \text{ V} - v_L(0+) = 0$$

$$v_L(0+) = -7.6 \text{ V}$$
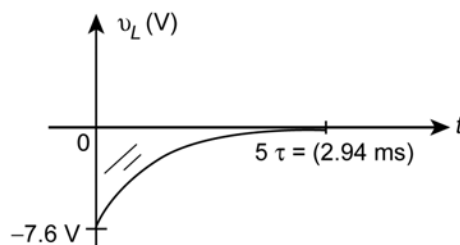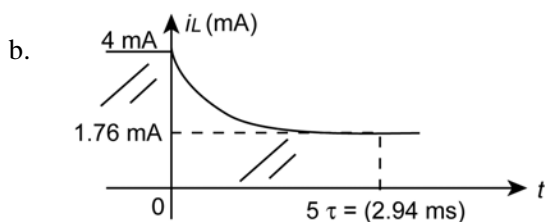
$$v_L = \mathbf{-7.6 \text{ V} e^{-t/588.2\mu\text{s}}}$$



19. a.

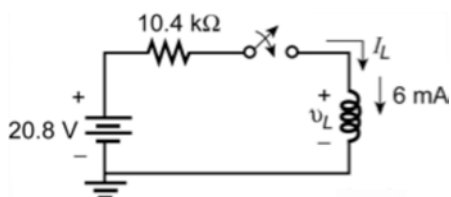


$$I_f = \frac{20.8 \text{ V}}{10.4 \text{ k}\Omega} = 2 \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{200 \text{ mH}}{10.4 \text{ k}\Omega} = 19.23 \mu\text{s}$$

$$i_L = I_f + (I_i - I_f)e^{-t/\tau}$$

$$= 2 \text{ mA} + (6 \text{ mA} - 2 \text{ mA})e^{-t/19.23\mu\text{s}}$$
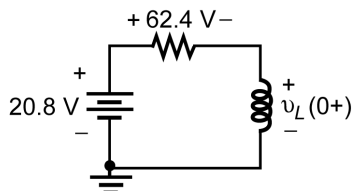
$$i_L = \mathbf{2 \text{ mA} + 4 \text{ mA} e^{-t/19.23\mu\text{s}}}$$





$$\text{KVL: } 20.8 \text{ V} - 62.4 \text{ V} - v_L(0+) = 0$$

$$v_L(0+) = -41.60 \text{ V}$$


$$v_L = \mathbf{-41.6 \text{ V} e^{-t/19.23\mu\text{s}}}$$

b.

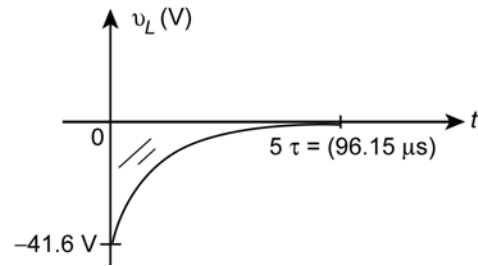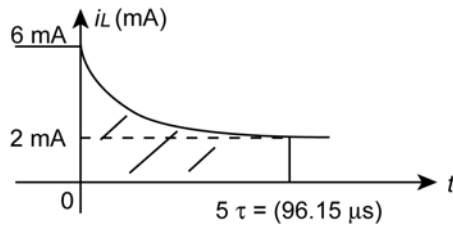

20.

a.

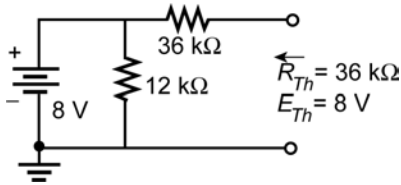

$$\tau = \frac{L}{R} = \frac{10 \text{ mH}}{36 \text{ k}\Omega} = 0.278 \mu\text{s}$$



$$v_L = 8 \text{ V} e^{-t/0.278 \mu\text{s}}, i_L = \frac{E}{R} (1 - e^{-t/\tau}) = 0.222 \text{ mA} (1 - e^{-t/0.278 \mu\text{s}})$$

b.  $5\tau \Rightarrow$  steady state

$$\tau' = \frac{L}{R} = \frac{10 \text{ mH}}{12 \text{ k}\Omega + 36 \text{ k}\Omega} = 0.208 \mu\text{s}$$

$$i_L = I_m e^{-t/\tau'} = 0.222 \text{ mA} e^{-t/0.208 \mu\text{s}}$$
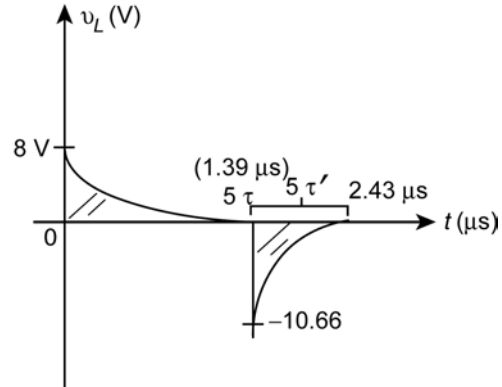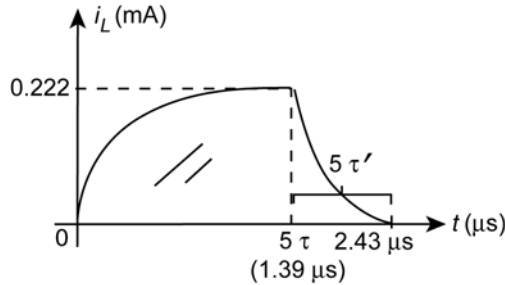
$$v_L = -(0.222 \text{ mA})(48 \text{ k}\Omega) e^{-t/\tau} = -10.66 \text{ V} e^{-t/0.308 \mu\text{s}}$$



21.

a.

$$\tau = \frac{L}{R} = \frac{4.7 \text{ mH}}{2 \text{ k}\Omega} = 2.35 \mu\text{s}$$

$$i_L = \frac{E}{R} (1 - e^{-t/\tau}) = \frac{12 \text{ V}}{2 \text{ k}\Omega} (1 - e^{-t/2.35 \mu\text{s}}) = 6 \text{ mA} (1 - e^{-t/2.35 \mu\text{s}})$$

$$v_L = E e^{-t/\tau} = 12 \text{ V} e^{-t/2.35 \mu\text{s}}$$

b.  $i_L = 6 \text{ mA} (1 - e^{-t/2.35 \mu\text{s}}) = 6 \text{ mA} (1 - e^{-1 \mu\text{s}/2.35 \mu\text{s}}) = 6 \text{ mA} (1 - e^{-0.426})$   
 $= 6 \text{ mA} (1 - .653) = 6 \text{ mA} (.347) = 2.08 \text{ mA}$


$$\tau' = \frac{L}{R_1 + R_2} = \frac{4.7 \text{ mH}}{12 \text{ k}\Omega} = 392 \text{ ns}$$

$$i_L = 2.08 \text{ mA} e^{-t/392 \text{ ns}}$$


$$v_L = 12 \text{ V} e^{-t/2.35 \mu\text{s}} = 12 \text{ V} e^{-1 \mu\text{s}/2.35 \mu\text{s}} = 12 \text{ V} e^{-0.426}$$

$$= 12 \text{ V} (.653) = 7.84 \text{ V}$$

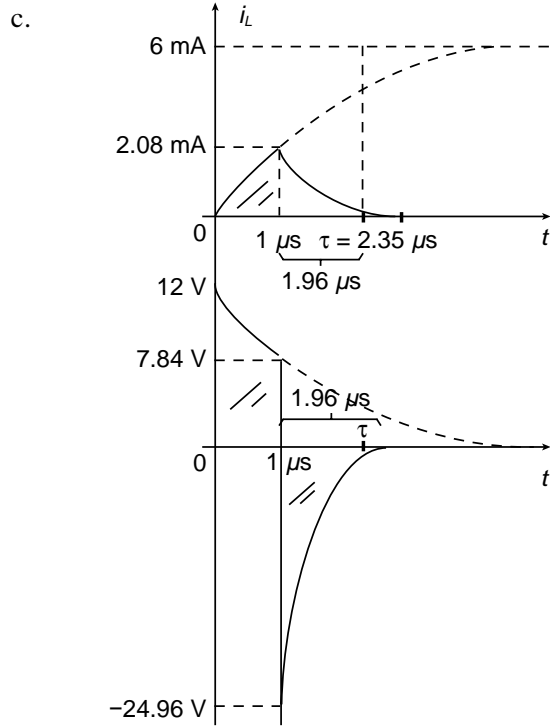At  $t = 0^+$  after switch moved  
 $v_L = -(2.08 \text{ mA})(12 \text{ k}\Omega) = -24.96 \text{ V}$   
 and  $v_L = -24.96 \text{ V}e^{-t/392 \text{ ns}}$   
 $5\tau' = 1.96 \mu\text{s}$




22. a.

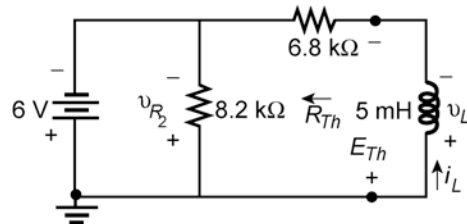

$$R_{Th} = 6.8 \text{ k}\Omega$$

$$E_{Th} = 6 \text{ V}$$

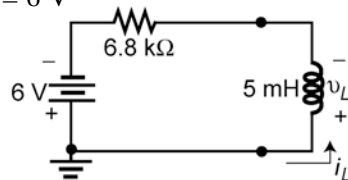


$$\tau = \frac{L}{R} = \frac{5 \text{ mH}}{6.8 \text{ k}\Omega} = 0.74 \mu\text{s}$$

$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{6 \text{ V}}{6.8 \text{ k}\Omega}(1 - e^{-t/\tau}) = 0.88 \text{ mA}(1 - e^{-t/0.74\mu\text{s}})$$

$$v_L = Ee^{-t/\tau} = 6 \text{ V}e^{-t/0.74\mu\text{s}}$$

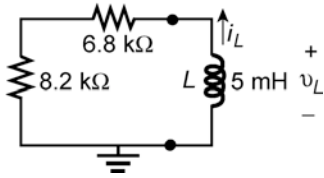- b. Assume steady state and  $I_L = 0.88 \text{ mA}$




$$\tau' = \frac{L}{R} = \frac{5 \text{ mH}}{15 \text{ k}\Omega} = 0.33 \mu\text{s}$$

$$i_L = I_m e^{-t/\tau'} = \mathbf{0.88 \text{ mA}} e^{-t/0.33\mu\text{s}}$$


$$v_L = -V_m e^{-t/\tau'}$$

$$V_m = I_m R = (0.88 \text{ mA})(15 \text{ k}\Omega) = 13.23 \text{ V}$$
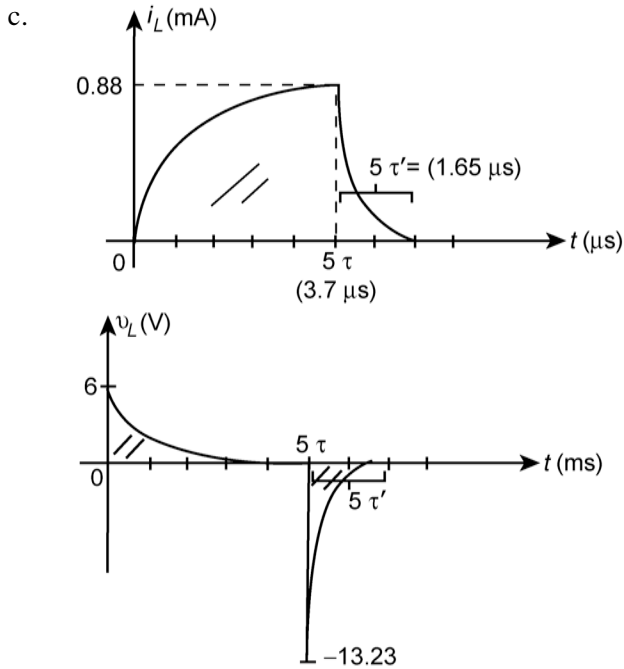
$$v_L = \mathbf{-13.23 \text{ V}} e^{-t/0.33\mu\text{s}}$$



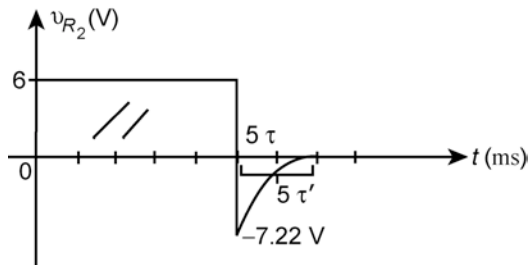- d.  $V_{R_2 \text{ max}} = I_m R_2 = (0.88 \text{ mA})(8.2 \text{ k}\Omega) = 7.22 \text{ V}$



23. a.  $R_{Th} = 2 \text{ k}\Omega + 2.2 \text{ k}\Omega + 6.2 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 6.22 \text{ k}\Omega$   
 $E_{Th} = \frac{6.2 \text{ k}\Omega(12 \text{ V})}{6.2 \text{ k}\Omega + 3 \text{ k}\Omega} = 8.09 \text{ V}$   
 $I_f = \frac{8.09 \text{ V}}{6.22 \text{ k}\Omega} = 1.3 \text{ mA}$ ,  $\tau = \frac{L}{R} = \frac{47 \text{ mH}}{6.22 \text{ k}\Omega} = 7.56 \mu\text{s}$