

Chapter 18

1. –

2. $Z = -j5 \Omega + 2 \Omega \angle 0^\circ \parallel 5 \Omega \angle 90^\circ = -j5 \Omega + 1.72 \Omega + j0.69 \Omega = 4.64 \Omega \angle -68.24^\circ$

$$I = \frac{E}{Z} = \frac{60 \text{ V} \angle 30^\circ}{4.64 \Omega \angle -68.24^\circ} = 12.93 \text{ A} \angle 98.24^\circ$$

3. $Z = 10 \Omega \angle 0^\circ \parallel 6 \Omega \angle 90^\circ = 5.15 \Omega \angle 59.04^\circ$

$$E = IZ = (2 \text{ A} \angle 120^\circ)(5.15 \Omega \angle 59.04^\circ) = 10.30 \text{ V} \angle 179.04^\circ$$

4. a. $I = \frac{\mu V}{R} = \frac{16 \text{ V}}{4 \times 10^3} = 4 \times 10^{-3} \text{ V}$
 $Z = 4 \text{ k}\Omega \angle 0^\circ$

b. $V = (hI)(R) = (50 \text{ I})(50 \text{ k}\Omega) = 2.5 \times 10^6 \text{ I}$
 $Z = 50 \text{ k}\Omega \angle 0^\circ$

5. Clockwise mesh currents:

$$\begin{aligned} E - I_1 Z_1 - I_1 Z_2 + I_2 Z_2 &= 0 \\ -I_2 Z_2 + I_1 Z_2 - I_2 Z_3 - E_2 &= 0 \end{aligned}$$

$$\begin{aligned} [Z_1 + Z_2]I_1 - Z_2 I_2 &= E_1 \\ -Z_2 I_1 + [Z_2 + Z_3]I_2 &= -E_2 \end{aligned}$$

$$Z_1 = R_1 \angle 0^\circ = 4 \Omega \angle 0^\circ$$

$$Z_2 = X_L \angle 90^\circ = 6 \Omega \angle 90^\circ$$

$$Z_3 = X_C \angle -90^\circ = 8 \Omega \angle -90^\circ$$

$$E_1 = 10 \text{ V} \angle 0^\circ, E_2 = 40 \text{ V} \angle 60^\circ$$

$$I_{R_1} = I_1 = \frac{\begin{vmatrix} E_1 & -Z_2 \\ -E_2 & [Z_2 + Z_3] \end{vmatrix}}{\begin{vmatrix} [Z_1 + Z_2] & -Z_2 \\ -Z_2 & [Z_2 + Z_3] \end{vmatrix}} = \frac{[Z_2 + Z_3]E_1 - Z_2 E_2}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = 5.15 \text{ A} \angle -24.5^\circ$$

6. By interchanging the right two branches, the general configuration of Problem 5 will result and

$$\begin{aligned} I_1(Z_1 + Z_2) - I_2 Z_2 &= E_1 - E_2 \\ I_2(Z_2 + Z_3) - I_1 Z_2 &= E_2 \end{aligned}$$

$$\begin{aligned} \text{and } I_1(Z_1 + Z_2) - I_2 Z_2 &= E_1 - E_2 \\ -I_1 Z_2 + I_2(Z_2 + Z_3) &= E_2 \end{aligned}$$

$$Z_1 = R_1 = 50 \Omega \angle 0^\circ$$

$$Z_2 = X_C \angle -90^\circ = 40 \Omega \angle -90^\circ$$


$$Z_3 = X_C \angle -90^\circ = 60 \Omega \angle -90^\circ$$

$$E_1 = 5 \text{ V} \angle 30^\circ$$

$$E_2 = 20 \text{ V} \angle 0^\circ$$

$$I_{50\Omega} = I_1 = 145.45 \text{ mA} \angle 187.59^\circ$$

7. a.

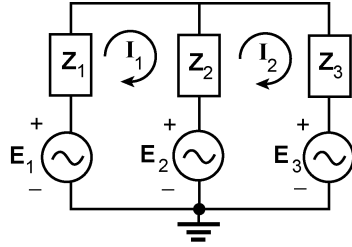

$$\mathbf{Z}_1 = 12 \Omega + j12 \Omega = 16.971 \Omega \angle 45^\circ$$

$$\mathbf{Z}_2 = 3 \Omega \angle 0^\circ$$

$$\mathbf{Z}_3 = -j1 \Omega$$

$$\mathbf{E}_1 = 20 \text{ V} \angle 50^\circ$$

$$\mathbf{E}_2 = 60 \text{ V} \angle 70^\circ$$

$$\mathbf{E}_3 = 40 \text{ V} \angle 0^\circ$$

$$\mathbf{I}_1[\mathbf{Z}_1 + \mathbf{Z}_2] - \mathbf{Z}_2\mathbf{I}_2 = \mathbf{E}_1 - \mathbf{E}_2$$

$$\mathbf{I}_2[\mathbf{Z}_2 + \mathbf{Z}_3] - \mathbf{Z}_2\mathbf{I}_1 = \mathbf{E}_2 - \mathbf{E}_3$$

$$(\mathbf{Z}_1 + \mathbf{Z}_2)\mathbf{I}_1 - \mathbf{Z}_2\mathbf{I}_2 = \mathbf{E}_1 - \mathbf{E}_2$$

$$-\mathbf{Z}_2\mathbf{I}_1 + (\mathbf{Z}_2 + \mathbf{Z}_3)\mathbf{I}_2 = \mathbf{E}_2 - \mathbf{E}_3$$

Using determinants:

$$\mathbf{I}_{R_1} = \mathbf{I}_1 = \frac{(\mathbf{E}_1 - \mathbf{E}_2)(\mathbf{Z}_2 + \mathbf{Z}_3) + \mathbf{Z}_2(\mathbf{E}_2 - \mathbf{E}_3)}{\mathbf{Z}_1\mathbf{Z}_2 + \mathbf{Z}_1\mathbf{Z}_3 + \mathbf{Z}_2\mathbf{Z}_3} = 2.55 \text{ A} \angle 132.72^\circ$$

8. Clockwise mesh currents:

$$\mathbf{E}_1 - \mathbf{I}_1\mathbf{Z}_1 - \mathbf{I}_1\mathbf{Z}_2 + \mathbf{I}_2\mathbf{Z}_2 = 0$$

$$-\mathbf{I}_2\mathbf{Z}_2 + \mathbf{I}_1\mathbf{Z}_2 - \mathbf{I}_2\mathbf{Z}_3 - \mathbf{I}_2\mathbf{Z}_4 + \mathbf{I}_3\mathbf{Z}_4 = 0$$

$$-\mathbf{I}_3\mathbf{Z}_4 + \mathbf{I}_2\mathbf{Z}_4 - \mathbf{I}_3\mathbf{Z}_5 - \mathbf{E}_2 = 0$$

$$[\mathbf{Z}_1 + \mathbf{Z}_2]\mathbf{I}_1 \quad -\mathbf{Z}_2 \mathbf{I}_2 \quad + 0 = \mathbf{E}_1$$

$$-\mathbf{Z}_2 \mathbf{I}_1 + [\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4]\mathbf{I}_2 \quad - \mathbf{Z}_4 \mathbf{I}_3 = 0$$

$$0 \quad -\mathbf{Z}_4 \mathbf{I}_2 + [\mathbf{Z}_4 + \mathbf{Z}_5]\mathbf{I}_3 = -\mathbf{E}_2$$

$$X_{L_1} = \omega L_1 = (2\pi)(2 \text{ kHz})(110 \mu\text{H})$$

$$= 1.38 \Omega$$

$$X_{L_2} = \omega L_2 = (2\pi)(2 \text{ kHz})(220 \mu\text{H})$$

$$= 2.76 \Omega$$

$$X_{C_1} = \frac{1}{\omega C_1} = \frac{1}{2\pi(2 \text{ kHz})(39 \mu\text{F})}$$

$$= 3.62 \Omega$$

$$X_{C_2} = \frac{1}{\omega C_2} = \frac{1}{2\pi(2 \text{ kHz})(39 \mu\text{F})}$$

$$= 2.04 \Omega$$

$$\mathbf{Z}_1 = 4 \Omega + j1.38 \Omega$$

$$\mathbf{Z}_2 = -j3.62 \Omega$$

$$\mathbf{Z}_3 = j2.76 \Omega$$

$$\mathbf{Z}_4 = -j2.04 \Omega$$

$$\mathbf{Z}_5 = 8 \Omega \angle 0^\circ$$


$$\mathbf{E}_1 = 6 \text{ V} \angle 0^\circ$$

$$\mathbf{E}_2 = 120 \text{ V} \angle 120^\circ$$

$$\mathbf{I}_{R_1} = \mathbf{I}_3 = \frac{[\mathbf{Z}_2\mathbf{Z}_4]\mathbf{E}_1 + [\mathbf{Z}_2^2 - [\mathbf{Z}_1 + \mathbf{Z}_2][\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4]]\mathbf{E}_2}{[\mathbf{Z}_1 + \mathbf{Z}_2][\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4][\mathbf{Z}_4 + \mathbf{Z}_5] - [\mathbf{Z}_1 + \mathbf{Z}_2]\mathbf{Z}_4^2 - [\mathbf{Z}_4 + \mathbf{Z}_5]\mathbf{Z}_2^2}$$

$$= \frac{1000 \text{ V} \angle -64.5^\circ}{124.4 \Omega \angle -68.34^\circ} = 8.04 \text{ A} \angle 3.84^\circ$$

9.

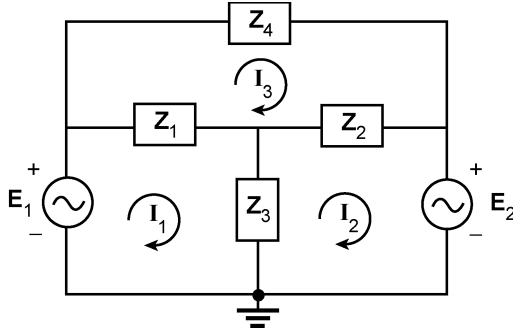

$$\begin{aligned} Z_1 &= 15 \Omega \angle 0^\circ, Z_2 = 15 \Omega \angle 0^\circ \\ Z_3 &= -j10 \Omega = 10 \Omega \angle -90^\circ \\ Z_4 &= 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ \\ E_1 &= 220 \text{ V} \angle 0^\circ \\ E_2 &= 100 \text{ V} \angle 90^\circ \end{aligned}$$

$$\begin{aligned} I_1(Z_1 + Z_3) - I_2Z_3 - I_3Z_1 &= E_1 \\ I_2(Z_2 + Z_3) - I_1Z_3 - I_3Z_2 &= -E_2 \\ I_3(Z_1 + Z_2 + Z_4) - I_1Z_1 - I_2Z_2 &= 0 \end{aligned}$$


$$\begin{array}{rcl} I_1(Z_1 + Z_3) - I_2Z_3 & - I_3Z_1 & = E_1 \\ -I_1Z_3 & + I_2(Z_2 + Z_3) - I_3Z_2 & = -E_2 \\ -I_1Z_1 & - I_2Z_2 & + I_3(Z_1 + Z_2 + Z_4) = 0 \end{array}$$

Applying determinants:

$$\begin{aligned} I_3 &= \frac{-(Z_1 + Z_3)(Z_2)E_2 - Z_1Z_3E_2 + E_1[Z_2Z_3 + Z_1(Z_2 + Z_3)]}{(Z_1 + Z_3)[(Z_2 + Z_3)(Z_1 + Z_2 + Z_4) - Z_3^2] + Z_3[Z_3(Z_1 + Z_2 + Z_4) - Z_1Z_2] - Z_1[-Z_2Z_3 - Z_1(Z_2 + Z_3)]} \\ &= 48.33 \text{ A} \angle -77.57^\circ \end{aligned}$$

or $I_3 = \frac{E_1 - E_2}{Z_4}$ if one carefully examines the network!

10.

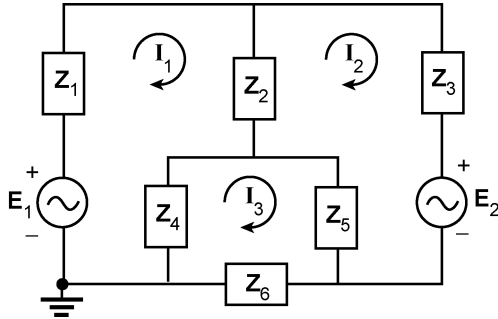

$$\begin{aligned} Z_1 &= 5 \Omega \angle 0^\circ, Z_2 = 5 \Omega \angle 90^\circ \\ Z_3 &= 4 \Omega \angle 0^\circ, Z_4 = 6 \Omega \angle -90^\circ \\ Z_5 &= 4 \Omega \angle 0^\circ, Z_6 = 6 \Omega + j8 \Omega \\ E_1 &= 20 \text{ V} \angle 0^\circ, E_2 = 40 \text{ V} \angle 60^\circ \end{aligned}$$


$$\begin{aligned} I_1(Z_1 + Z_2 + Z_4) - I_2Z_2 - I_3Z_4 &= E_1 \\ I_2(Z_2 + Z_3 + Z_5) - I_1Z_2 - I_3Z_5 &= -E_2 \\ I_3(Z_4 + Z_5 + Z_6) - I_1Z_4 - I_2Z_5 &= 0 \end{aligned}$$

$$\begin{array}{rcl} (Z_1 + Z_2 + Z_4) I_1 & - Z_2 I_2 & - Z_4 I_3 = E_1 \\ -Z_2 I_1 + (Z_2 + Z_3 + Z_5) I_2 & & - Z_5 I_3 = -E_2 \\ -Z_4 I_1 & - Z_5 I_2 + (Z_4 + Z_5 + Z_6) I_3 & = 0 \end{array}$$

Using $Z' = Z_1 + Z_2 + Z_4$, $Z'' = Z_2 + Z_3 + Z_5$, $Z''' = Z_4 + Z_5 + Z_6$ and determinants:

$$\begin{aligned} I_{R_1} = I_1 &= \frac{E_1(Z''Z''' - Z_5^2) - E_2(Z_2Z''' + Z_4Z_5)}{Z'(Z''Z''' - Z_5^2) - Z_2(Z_2Z''' + Z_4Z_5) - Z_4(Z_2Z_5 + Z_4Z'')} \\ &= 3.04 \text{ A} \angle 169.12^\circ \end{aligned}$$

11.

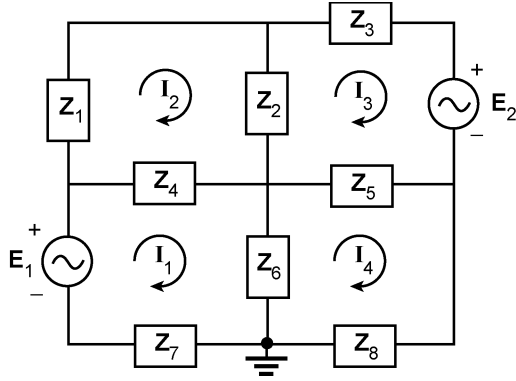

$$\begin{aligned} Z_1 &= 10 \Omega + j20 \Omega & Z_2 &= -j20 \Omega \\ Z_3 &= 80 \Omega \angle 0^\circ & Z_4 &= 6 \Omega \angle 0^\circ \\ Z_5 &= 15 \Omega \angle 90^\circ & Z_6 &= 10 \Omega \angle 0^\circ \\ Z_7 &= 5 \Omega \angle 0^\circ & Z_8 &= 5 \Omega - j20 \Omega \\ E_1 &= 25 \text{ V } \angle 0^\circ & E_2 &= 75 \text{ V } \angle 20^\circ \end{aligned}$$


$$\begin{aligned} I_1(Z_4 + Z_6 + Z_7) - I_2Z_4 - I_4Z_6 &= E_1 \\ I_2(Z_1 + Z_2 + Z_4) - I_1Z_4 - I_3Z_2 &= 0 \\ I_3(Z_2 + Z_3 + Z_5) - I_2Z_2 - I_4Z_5 &= -E_2 \\ I_4(Z_5 + Z_6 + Z_8) - I_1Z_6 - I_3Z_5 &= 0 \end{aligned}$$

$$\begin{array}{cccc} (Z_4 + Z_6 + Z_7) I_1 & -Z_4 I_2 & + 0 & -Z_6 I_4 = E_1 \\ -Z_4 I_1 + (Z_1 + Z_2 + Z_4) I_2 & -Z_2 I_3 & + 0 & = 0 \\ 0 & -Z_2 I_2 + (Z_2 + Z_3 + Z_5) I_3 & -Z_5 I_4 & = -E_2 \\ -Z_6 I_1 & + 0 & -Z_5 I_3 + (Z_5 + Z_6 + Z_7) I_4 & = 0 \end{array}$$

Applying determinants:

$$I_{R_1} = I_{80\Omega} = 0.68 \text{ A } \angle -162.9^\circ$$

12.

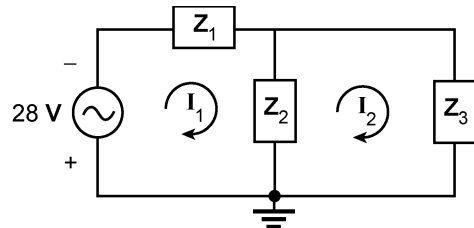


$$\begin{aligned} Z_1 &= 5 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= 1 \text{ k}\Omega + j4 \text{ k}\Omega = 4.123 \text{ k}\Omega \angle 75.96^\circ \end{aligned}$$

$$\begin{aligned} I_1(Z_1 + Z_2) - Z_2 I_2 &= -28 \text{ V} \\ I_2(Z_2 + Z_3) - Z_2 I_1 &= 0 \end{aligned}$$

$$\begin{aligned} (Z_1 + Z_2) I_1 - Z_2 I_2 &= -28 \text{ V} \\ -Z_2 I_1 + (Z_2 + Z_3) I_2 &= 0 \end{aligned}$$

$$I_L = I_2 = \frac{-Z_2 28 \text{ V}}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} = -3.17 \times 10^{-3} \text{ V } \angle 137.29^\circ$$

13.

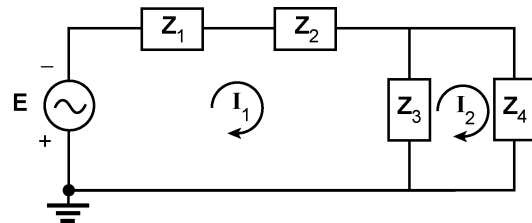

Source Conversion:

$$\begin{aligned} E &= (I \angle \theta)(R_p \angle 0^\circ) \\ &= (50 \text{ I})(40 \text{ k}\Omega \angle 0^\circ) \\ &= 2 \times 10^6 \text{ I } \angle 0^\circ \\ Z_1 &= R_s = R_p = 40 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= -j0.2 \text{ k}\Omega \\ Z_3 &= 8 \text{ k}\Omega \angle 0^\circ \\ Z_4 &= 4 \text{ k}\Omega \angle 90^\circ \end{aligned}$$

$$\begin{aligned} I_1(Z_1 + Z_2 + Z_3) - Z_3 I_2 &= -E \\ I_2(Z_3 + Z_4) - Z_3 I_1 &= 0 \end{aligned}$$

$$\begin{aligned} (\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3)\mathbf{I}_1 - \mathbf{Z}_3\mathbf{I}_2 &= -\mathbf{E} \\ -\mathbf{Z}_3\mathbf{I}_1 + (\mathbf{Z}_3 + \mathbf{Z}_4)\mathbf{I}_2 &= 0 \end{aligned}$$

$$\mathbf{I}_L = \mathbf{I}_2 = \frac{-\mathbf{Z}_3\mathbf{E}}{(\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3)(\mathbf{Z}_3 + \mathbf{Z}_4) - \mathbf{Z}_3^2} = 42.91 \text{ I } \angle 149.31^\circ$$

14. $6\mathbf{V}_x - \mathbf{I}_1 1 \text{ k}\Omega - 10 \text{ V } \angle 0^\circ = 0$
 $10 \text{ V } \angle 0^\circ - \mathbf{I}_2 4 \text{ k}\Omega - \mathbf{I}_2 2 \text{ k}\Omega = 0$

$$\mathbf{V}_x = \mathbf{I}_2 2 \text{ k}\Omega$$


$$\begin{aligned} -\mathbf{I}_1 1 \text{ k}\Omega + \mathbf{I}_2 12 \text{ k}\Omega &= 10 \text{ V } \angle 0^\circ \\ -\mathbf{I}_2 6 \text{ k}\Omega &= -10 \text{ V } \angle 0^\circ \end{aligned}$$

$$\mathbf{I}_2 = \mathbf{I}_{2\text{k}\Omega} = \frac{10 \text{ V } \angle 0^\circ}{6 \text{ k}\Omega} = 1.67 \text{ mA } \angle 0^\circ = \mathbf{I}_{2\text{k}\Omega}$$

$$\begin{aligned} -\mathbf{I}_1 1 \text{ k}\Omega + (1.667 \text{ mA } \angle 0^\circ)(12 \text{ k}\Omega) &= 10 \text{ V } \angle 0^\circ \\ -\mathbf{I}_1 1 \text{ k}\Omega + 20 \text{ V } \angle 0^\circ &= 10 \text{ V } \angle 0^\circ \\ -\mathbf{I}_1 1 \text{ k}\Omega &= -10 \text{ V } \angle 0^\circ \end{aligned}$$

$$\mathbf{I}_1 = \mathbf{I}_{1\text{k}\Omega} = \frac{10 \text{ V } \angle 0^\circ}{1 \text{ k}\Omega} = 10 \text{ mA } \angle 0^\circ$$

15.

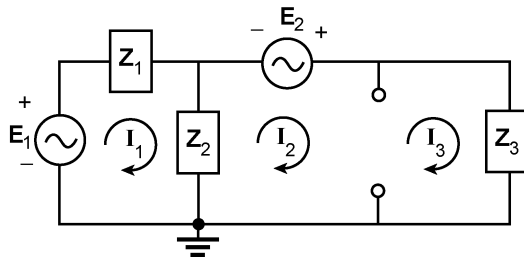

$$\begin{aligned} \mathbf{E}_1 &= 5 \text{ V } \angle 0^\circ \\ \mathbf{E}_2 &= 20 \text{ V } \angle 0^\circ \\ \mathbf{Z}_1 &= 2.2 \text{ k}\Omega \angle 0^\circ \\ \mathbf{Z}_2 &= 5 \text{ k}\Omega \angle 90^\circ \\ \mathbf{Z}_3 &= 10 \text{ k}\Omega \angle 0^\circ \\ \mathbf{I} &= 4 \text{ mA } \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{E}_1 - \mathbf{I}_1\mathbf{Z}_1 - \mathbf{Z}_2(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ -\mathbf{Z}_2(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{E}_2 - \mathbf{I}_3\mathbf{Z}_3 &= 0 \end{aligned}$$

$$\mathbf{I}_3 - \mathbf{I}_2 = \mathbf{I}$$


Substituting, we obtain:

$$\begin{aligned} \mathbf{I}_1(\mathbf{Z}_1 + \mathbf{Z}_2) - \mathbf{I}_2\mathbf{Z}_2 &= \mathbf{E}_1 \\ \mathbf{I}_1\mathbf{Z}_2 - \mathbf{I}_2(\mathbf{Z}_2 + \mathbf{Z}_3) &= \mathbf{I}\mathbf{Z}_3 - \mathbf{E}_2 \end{aligned}$$

Determinants:

$$\begin{aligned} \mathbf{I}_1 &= 1.39 \text{ mA } \angle -126.48^\circ, \mathbf{I}_2 = 1.341 \text{ mA } \angle -10.56^\circ, \mathbf{I}_3 = 2.693 \text{ mA } \angle -174.8^\circ \\ \mathbf{I}_{10\text{k}\Omega} = \mathbf{I}_3 &= 2.69 \text{ mA } \angle -174.8^\circ \end{aligned}$$

16.

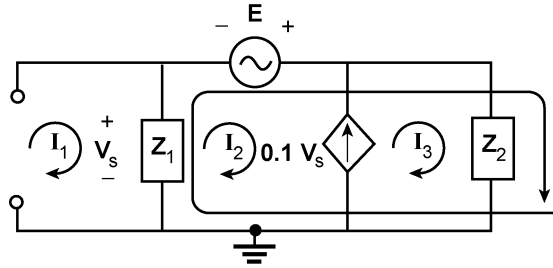

$$\begin{aligned} Z_1 &= 1 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 4 \text{ k}\Omega + j6 \text{ k}\Omega \\ E &= 10 \text{ V} \angle 0^\circ \end{aligned}$$

$$\begin{aligned} -Z_1(I_2 - I_1) + E - I_3 Z_3 &= 0 \\ I_1 = 6 \text{ mA} \angle 0^\circ, 0.1 V_s &= I_3 - I_2, V_s = (I_1 - I_2)Z_1 \end{aligned}$$


Substituting:

$$\begin{aligned} (1 \text{ k}\Omega)I_2 + (4 \text{ k}\Omega + j6 \text{ k}\Omega)I_3 &= 16 \text{ V} \angle 0^\circ \\ (99 \Omega)I_2 + I_3 &= 0.6 \text{ V} \angle 0^\circ \end{aligned}$$

Determinants:

$$I_3 = I_{6 \text{ k}\Omega} = 1.38 \text{ mA} \angle -56.31^\circ$$

17.

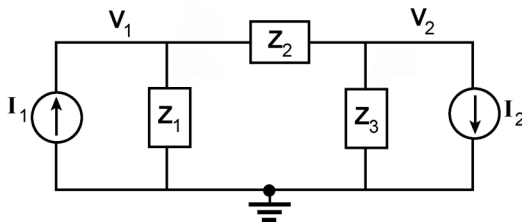

$$\begin{aligned} Z_1 &= 4 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 1 \text{ k}\Omega \angle 90^\circ \\ Z_3 &= 8 \text{ k}\Omega \angle -90^\circ \\ I_1 &= 3 \text{ mA} \angle 0^\circ \\ I_2 &= 5 \text{ mA} \angle 30^\circ \end{aligned}$$

$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} \right] - \frac{1}{Z_2} V_2 = I_1$$

$$V_2 \left[\frac{1}{Z_2} + \frac{1}{Z_3} \right] - \frac{1}{Z_2} V_1 = -I_2$$


$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} \right] - V_2 \left[\frac{1}{Z_2} \right] = I_1$$

$$-V_1 \left[\frac{1}{Z_2} \right] + V_2 \left[\frac{1}{Z_2} + \frac{1}{Z_3} \right] = -I_2$$

$$V_1 = \frac{\begin{vmatrix} I_1 & -\frac{1}{Z_2} \\ -I_2 & \left(\frac{1}{Z_2} + \frac{1}{Z_3}\right) \end{vmatrix}}{\begin{vmatrix} \left(\frac{1}{Z_1} + \frac{1}{Z_2}\right) & -\frac{1}{Z_2} \\ -\frac{1}{Z_2} & \left(\frac{1}{Z_2} + \frac{1}{Z_3}\right) \end{vmatrix}} = 11.99 \text{ V } \angle -154.53^\circ$$

$$V_2 = \frac{\begin{vmatrix} \left(\frac{1}{Z_1} + \frac{1}{Z_2}\right) & I_1 \\ -\frac{1}{Z_2} & -I_2 \end{vmatrix}}{\begin{vmatrix} \left(\frac{1}{Z_1} + \frac{1}{Z_2}\right) & -\frac{1}{Z_2} \\ -\frac{1}{Z_2} & \left(\frac{1}{Z_2} + \frac{1}{Z_3}\right) \end{vmatrix}} = 14.46 \text{ V } \angle -131.28^\circ$$

18.

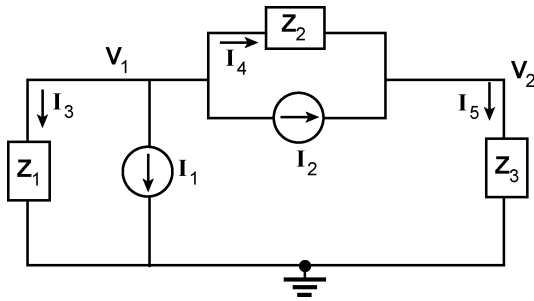

$$Z_1 = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$

$$Z_2 = 2 \Omega \angle 0^\circ$$

$$Z_3 = 6 \Omega \angle 0^\circ \parallel 8 \Omega \angle -90^\circ$$

$$= 4.8 \Omega \angle -36.87^\circ$$

$$I_1 = 0.6 \text{ A } \angle 20^\circ$$

$$I_2 = 4 \text{ A } \angle 80^\circ$$

$$0 = I_1 + I_3 + I_4 + I_2$$

$$0 = I_1 + \frac{V_1}{Z_1} + \frac{V_1 - V_2}{Z_2} + I_2$$

$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} \right] - V_2 \left[\frac{1}{Z_2} \right] = -I_1 - I_2$$

$$\text{or } \underline{V_1[Y_1 + Y_2] - V_2[Y_2] = -I_1 - I_2}$$

$$I_2 + I_4 = I_5$$

$$I_2 + \frac{V_1 - V_2}{Z_2} = \frac{V_2}{Z_3}$$

$$V_2 \left[\frac{1}{Z_2} + \frac{1}{Z_3} \right] - V_1 \left[\frac{1}{Z_2} \right] = +I_2$$

$$\text{or } \underline{V_2[Y_2 + Y_3] - V_1[Y_2] = I_2}$$


$$\text{and } \begin{cases} [Y_1 + Y_2]V_1 - Y_2V_2 = -I_1 - I_2 \\ -Y_2V_1 + [Y_2 + Y_3]V_2 = I_2 \end{cases}$$

Applying determinants:

$$V_1 = \frac{-[Y_2 + Y_3][I_1 + I_2] + Y_2 I_2}{Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_3} = 5.12 \text{ V } \angle -79.36^\circ$$

$$V_2 = \frac{Y_1 I_2 - I_1 Y_2}{Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_3} = 2.71 \text{ V } \angle 39.96^\circ$$

19.

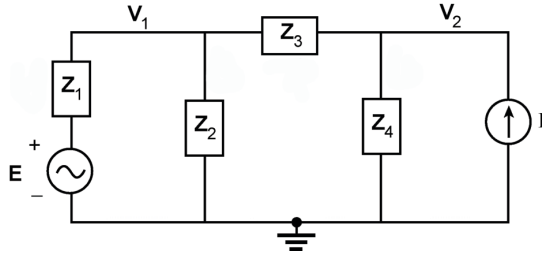

$$Z_1 = 5 \Omega \angle 0^\circ$$

$$Z_4 = 2 \Omega \angle 0^\circ$$

$$E = 30 \text{ V } \angle 50^\circ$$

$$I = 4 \text{ A } \angle 90^\circ$$

$$X_L = 2\pi fL = 2\pi(10 \text{ kHz})(0.1 \text{ mH}) = 6.28 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \text{ kHz})(4.7 \mu\text{F})}$$

$$= 3.39 \Omega$$

$$Z_2 = 6.28 \Omega \angle 90^\circ$$


$$Z_3 = 3.39 \Omega \angle -90^\circ$$

$$\left. \begin{aligned} V_1[Y_1 + Y_2 + Y_3] - V_2 Y_3 &= E_1 Y_1 \\ -V_1[Y_3] + V_2[Y_3 + Y_4] &= +I \end{aligned} \right\} \text{ after source conversion.}$$

Using determinants:

$$V_1 = 17.92 \text{ V } \angle 59.25^\circ \text{ and } V_2 = 13.95 \text{ V } \angle 93.64^\circ$$

20.

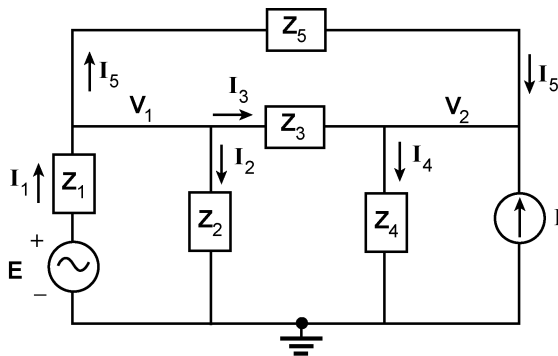

$$Z_1 = 10 \Omega \angle 0^\circ$$

$$Z_2 = 10 \Omega \angle 0^\circ$$

$$Z_3 = 4 \Omega \angle 90^\circ$$

$$Z_4 = 2 \Omega \angle 0^\circ$$

$$Z_5 = 8 \Omega \angle -90^\circ$$

$$E = 50 \text{ V } \angle 120^\circ$$

$$I = 0.8 \text{ A } \angle 70^\circ$$

$$I_1 = I_2 + I_5$$

$$\frac{E - V_1}{Z_1} = \frac{V_1}{Z_2} + \frac{(V_1 - V_2)}{Z_5} + \frac{V_1 - V_2}{Z_3} \Rightarrow V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_5} \right] - V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_5} \right] = \frac{E}{Z_1}$$

$$\text{or } V_1[Y_1 + Y_2 + Y_3 + Y_5] - V_2[Y_3 + Y_5] = E_1 Y_1$$

$$I_3 + I_5 = I_4 + I$$

$$\frac{V_1 - V_2}{Z_3} + \frac{V_1 - V_2}{Z_5} = \frac{V_2}{Z_4} + I \Rightarrow V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_4} + \frac{1}{Z_5} \right] - V_1 \left[\frac{1}{Z_3} + \frac{1}{Z_5} \right] = -I$$

$$\text{or } V_2[Y_3 + Y_4 + Y_5] - V_1[Y_3 + Y_5] = -I$$


resulting in

$$\begin{aligned} V_1[Y_1 + Y_2 + Y_3 + Y_5] - V_2[Y_3 + Y_5] &= E_1 Y_1 \\ -V_1[Y_3 + Y_5] + V_2[Y_3 + Y_4 + Y_5] &= -I \end{aligned}$$

Applying determinants:

$$V_1 = 19.78 \text{ V } \angle 132.48^\circ \text{ and } V_2 = 13.37 \text{ V } \angle 98.78^\circ$$

21.

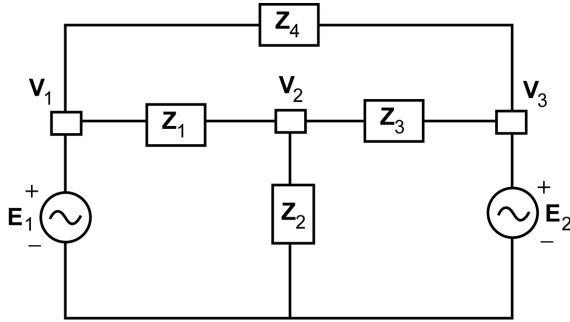

$$\begin{aligned} Z_1 &= 15 \Omega \angle 0^\circ \\ Z_2 &= 10 \Omega \angle -90^\circ \\ Z_3 &= 15 \Omega \angle 0^\circ \\ Z_4 &= 3 \Omega + j4 \Omega \end{aligned}$$

$$V_2 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right] - \frac{1}{Z_1} V_1 - \frac{1}{Z_3} V_3 = 0$$


$$V_2 \left[\frac{1}{15 \Omega} + \frac{1}{-j10 \Omega} + \frac{1}{15 \Omega} \right] - \frac{1}{15 \Omega} [220 \text{ V } \angle 0^\circ] - \frac{1}{15 \Omega} [100 \text{ V } \angle 90^\circ] = 0$$

$$V_2 [133.34 \times 10^{-3} + j100 \times 10^{-3}] = 14.67 + j6.67$$

$$V_2 = \frac{16.05 \text{ V } \angle 24.55^\circ}{166.67 \times 10^{-3} \angle 36.37^\circ} = 96.30 \text{ V } \angle -12.32^\circ$$

$$V_1 = E_1 = 220 \text{ V } \angle 0^\circ, V_3 = E_2 = 100 \text{ V } \angle 90^\circ$$

22.

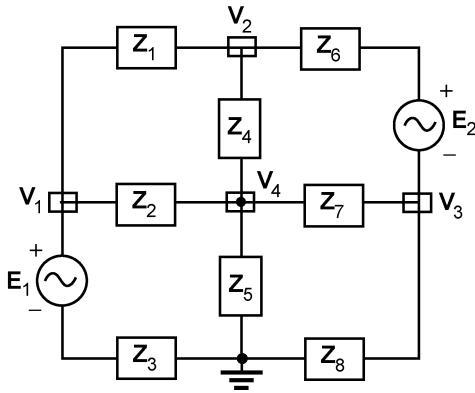

$$\begin{aligned} Z_1 &= 10 \Omega + j20 \Omega \\ Z_2 &= 6 \Omega \angle 0^\circ \\ Z_3 &= 5 \Omega \angle 0^\circ \\ Z_4 &= 20 \Omega \angle -90^\circ \\ Z_5 &= 10 \Omega \angle 0^\circ \\ Z_6 &= 80 \Omega \angle 0^\circ \\ Z_7 &= 15 \Omega \angle 90^\circ \\ Z_8 &= 5 \Omega - j20 \Omega \end{aligned}$$

$$\begin{aligned} E_1 &= 25 \text{ V } \angle 0^\circ \\ E_2 &= 75 \text{ V } \angle 20^\circ \end{aligned}$$

$$V_1: \frac{V_1 - V_2}{Z_1} + \frac{V_1 - V_4}{Z_2} + \frac{V_1 - E_1}{Z_3} = 0$$

$$V_2: \frac{V_2 - V_1}{Z_1} + \frac{V_2 - V_4}{Z_4} + \frac{V_2 - E_2 - V_3}{Z_6} = 0$$

$$V_3: \frac{V_3 + E_2 - V_2}{Z_6} + \frac{V_3 - V_4}{Z_7} + \frac{V_3}{Z_8} = 0$$

$$V_4: \frac{V_4 - V_1}{Z_2} + \frac{V_4 - V_2}{Z_4} + \frac{V_4 - V_3}{Z_7} + \frac{V_4}{Z_5} = 0$$


Rearranging:

$$\begin{aligned} \mathbf{V}_1 \left(\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} \right) - \frac{\mathbf{V}_2}{\mathbf{Z}_1} - \frac{\mathbf{V}_4}{\mathbf{Z}_2} &= \frac{\mathbf{E}_1}{\mathbf{Z}_3} \\ \mathbf{V}_2 \left(\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_4} + \frac{1}{\mathbf{Z}_6} \right) - \frac{\mathbf{V}_1}{\mathbf{Z}_1} - \frac{\mathbf{V}_4}{\mathbf{Z}_4} - \frac{\mathbf{V}_3}{\mathbf{Z}_6} &= \frac{\mathbf{E}_2}{\mathbf{Z}_6} \\ \mathbf{V}_3 \left(\frac{1}{\mathbf{Z}_6} + \frac{1}{\mathbf{Z}_7} + \frac{1}{\mathbf{Z}_8} \right) - \frac{\mathbf{V}_2}{\mathbf{Z}_6} - \frac{\mathbf{V}_4}{\mathbf{Z}_7} &= -\frac{\mathbf{E}_2}{\mathbf{Z}_6} \\ \mathbf{V}_4 \left(\frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_4} + \frac{1}{\mathbf{Z}_7} + \frac{1}{\mathbf{Z}_5} \right) - \frac{\mathbf{V}_1}{\mathbf{Z}_2} - \frac{\mathbf{V}_2}{\mathbf{Z}_4} - \frac{\mathbf{V}_3}{\mathbf{Z}_7} &= 0 \end{aligned}$$

Setting up and then using determinants:

$$\begin{aligned} \mathbf{V}_1 &= 14.62 \text{ V } \angle -5.86^\circ, \mathbf{V}_2 = 35.03 \text{ V } \angle -37.69^\circ \\ \mathbf{V}_3 &= 32.4 \text{ V } \angle -73.34^\circ, \mathbf{V}_4 = 5.67 \text{ V } \angle 23.53^\circ \end{aligned}$$

23.

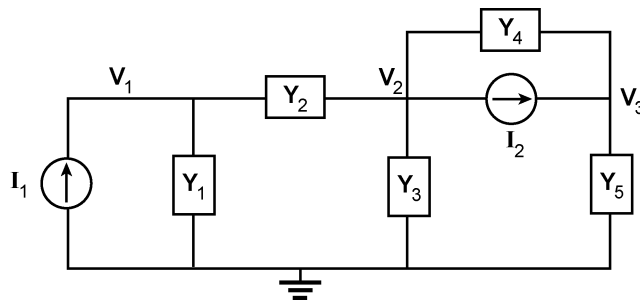

$$\begin{aligned} \mathbf{Y}_1 &= \frac{1}{4 \Omega \angle 0^\circ} \\ &= 0.25 \text{ S } \angle 0^\circ \\ \mathbf{Y}_2 &= \frac{1}{1 \Omega \angle 90^\circ} \\ &= 1 \text{ S } \angle -90^\circ \\ \mathbf{Y}_3 &= \frac{1}{5 \Omega \angle 0^\circ} \\ &= 0.2 \text{ S } \angle 0^\circ \\ \mathbf{Y}_4 &= \frac{1}{4 \Omega \angle -90^\circ} \\ &= 0.25 \text{ S } \angle 90^\circ \\ \mathbf{Y}_5 &= \frac{1}{8 \Omega \angle 90^\circ} \\ &= 0.125 \text{ S } \angle -90^\circ \\ \mathbf{I}_1 &= 2 \text{ A } \angle 30^\circ \\ \mathbf{I}_2 &= 3 \text{ A } \angle 150^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_1[\mathbf{Y}_1 + \mathbf{Y}_2] - \mathbf{Y}_2\mathbf{V}_2 &= \mathbf{I}_1 \\ \mathbf{V}_2[\mathbf{Y}_2 + \mathbf{Y}_3 + \mathbf{Y}_4] - \mathbf{Y}_2\mathbf{V}_1 - \mathbf{Y}_4\mathbf{V}_3 &= -\mathbf{I}_2 \\ \mathbf{V}_3[\mathbf{Y}_4 + \mathbf{Y}_5] - \mathbf{Y}_4\mathbf{V}_2 &= \mathbf{I}_2 \end{aligned}$$


$$\begin{aligned} [\mathbf{Y}_1 + \mathbf{Y}_2]\mathbf{V}_1 & & - \mathbf{Y}_2 \mathbf{V}_2 & & + 0 & = \mathbf{I}_1 \\ -\mathbf{Y}_2\mathbf{V}_1 + [\mathbf{Y}_2 + \mathbf{Y}_3 + \mathbf{Y}_4]\mathbf{V}_2 & & & & - \mathbf{Y}_4 \mathbf{V}_3 & = -\mathbf{I}_2 \\ 0 & & - \mathbf{Y}_4 \mathbf{V}_2 + [\mathbf{Y}_4 + \mathbf{Y}_5]\mathbf{V}_3 & & & = \mathbf{I}_2 \end{aligned}$$

$$\begin{aligned} \mathbf{V}_1 &= \frac{\mathbf{I}_1 [\mathbf{Y}_2 + \mathbf{Y}_3 + \mathbf{Y}_4](\mathbf{Y}_4 + \mathbf{Y}_5) - \mathbf{I}_2[\mathbf{Y}_2 \mathbf{Y}_5]}{[\mathbf{Y}_1 + \mathbf{Y}_2] [\mathbf{Y}_2 + \mathbf{Y}_3 + \mathbf{Y}_4](\mathbf{Y}_4 + \mathbf{Y}_5) - \mathbf{Y}_2^2(\mathbf{Y}_4 + \mathbf{Y}_5) = \mathbf{Y}_\Delta} \\ &= 5.74 \text{ V } \angle 122.76^\circ \end{aligned}$$

$$V_2 = \frac{I_1 Y_2 (Y_4 + Y_5) - I_2 Y_5 (Y_1 + Y_2)}{Y_\Delta} = 4.04 \text{ V } \angle 145.03^\circ$$

$$V_3 = \frac{I_2 [(Y_1 + Y_2)(Y_3 + Y_4) - Y_2^2] - Y_2 Y_4 I_1}{Y_\Delta} = 25.94 \text{ V } \angle 78.07^\circ$$

24.

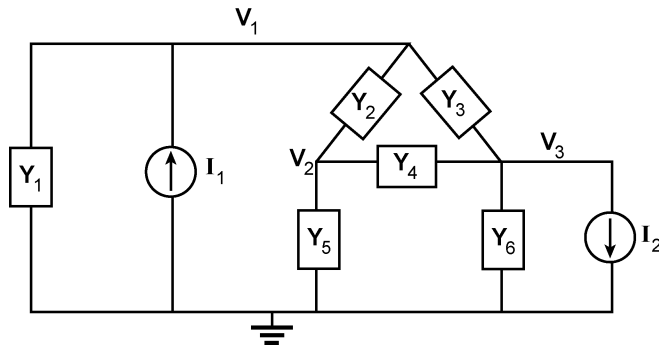

$$\begin{aligned} V_1[Y_1 + Y_2 + Y_3] - Y_2 V_2 - Y_3 V_3 &= I_1 \\ V_2[Y_2 + Y_4 + Y_5] - Y_2 V_1 - Y_4 V_3 &= 0 \\ V_3[Y_3 + Y_4 + Y_6] - Y_3 V_1 - Y_4 V_2 &= -I_2 \end{aligned}$$

$$\begin{array}{rcl} [Y_1 + Y_2 + Y_3]V_1 & - & Y_2 V_2 & - & Y_3 V_3 & = & I_1 \\ -Y_2 V_1 & + & [Y_2 + Y_4 + Y_5]V_2 & - & Y_4 V_3 & = & 0 \\ -Y_3 V_1 & - & Y_4 V_2 & + & [Y_3 + Y_4 + Y_6]V_3 & = & -I_2 \end{array}$$

$$Y_1 = \frac{1}{4 \Omega \angle 0^\circ} = 0.25 \text{ S } \angle 0^\circ$$

$$Y_2 = \frac{1}{6 \Omega \angle 0^\circ} = 0.167 \text{ S } \angle 0^\circ$$

$$Y_3 = \frac{1}{8 \Omega \angle 0^\circ} = 0.125 \text{ S } \angle 0^\circ$$

$$Y_4 = \frac{1}{2 \Omega \angle -90^\circ} = 0.5 \text{ S } \angle 90^\circ$$

$$Y_5 = \frac{1}{5 \Omega \angle 90^\circ} = 0.2 \text{ S } \angle -90^\circ$$

$$Y_6 = \frac{1}{4 \Omega \angle 90^\circ} = 0.25 \text{ S } \angle -90^\circ$$

$$I_1 = 4 \text{ A } \angle 0^\circ$$

$$I_2 = 6 \text{ A } \angle 90^\circ$$

$$V_1 = \frac{I_1 [(Y_2 + Y_4 + Y_5)(Y_3 + Y_4 + Y_6) - Y_4^2] - I_2 [Y_2 Y_4 + Y_3 (Y_3 + Y_4 + Y_6)]}{Y_\Delta = (Y_1 + Y_2 + Y_3) [(Y_2 + Y_4 + Y_5)(Y_3 + Y_4 + Y_6) - Y_4^2] - Y_2 [Y_2 (Y_3 + Y_4 + Y_6) + Y_3 Y_4] - Y_3 [Y_2 Y_4 + Y_3 (Y_2 + Y_4 + Y_5)]}$$

$$= 15.13 \text{ V } \angle 1.29^\circ$$

$$V_2 = \frac{I_1 [(Y_2)(Y_3 + Y_4 + Y_6) + Y_3 Y_4] + I_2 [Y_4 (Y_1 + Y_2 + Y_3) - Y_2 Y_3]}{Y_\Delta} = 17.24 \text{ V } \angle 3.73^\circ$$

$$V_3 = \frac{I_1 [(Y_3)(Y_2 + Y_4 + Y_5) + Y_2 Y_4] + I_2 [Y_2^2 - (Y_1 + Y_2 + Y_3)(Y_2 + Y_4 + Y_5)]}{Y_\Delta}$$

$$= 10.59 \text{ V } \angle -0.11^\circ$$

25. Left node: V_1

$$\sum I_i = \sum I_o$$

$$4I_x = I_x + 5 \text{ mA } \angle 0^\circ + \frac{V_1 - V_2}{2 \text{ k}\Omega}$$

Right node: V_2

$$\sum I_i = \sum I_o$$

$$8 \text{ mA } \angle 0^\circ = \frac{V_2}{1 \text{ k}\Omega} + \frac{V_2 - V_1}{2 \text{ k}\Omega} + 4I_x$$


$$\text{Insert } I_x = \frac{V_1}{4 \text{ k}\Omega \angle -90^\circ}$$

Rearrange, reduce and 2 equations with 2 unknowns result:

$$\begin{aligned} \mathbf{V}_1[1.803 \angle 123.69^\circ] + \mathbf{V}_2 &= 10 \\ \mathbf{V}_1[2.236 \angle 116.57^\circ] + 3 \mathbf{V}_2 &= 16 \end{aligned}$$

Determinants: $\mathbf{V}_1 = 4.37 \text{ V} \angle -128.66^\circ$
 $\mathbf{V}_2 = \mathbf{V}_{1\text{k}\Omega} = 2.25 \text{ V} \angle 17.63^\circ$

26.

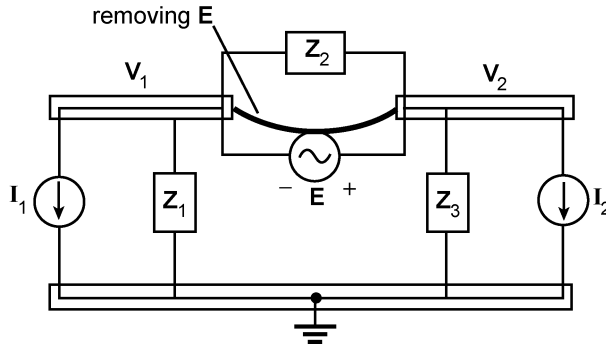

$$\begin{aligned} \mathbf{Z}_1 &= 1 \text{ k}\Omega \angle 0^\circ \\ \mathbf{Z}_2 &= 2 \text{ k}\Omega \angle 90^\circ \\ \mathbf{Z}_3 &= 3 \text{ k}\Omega \angle -90^\circ \\ \mathbf{I}_1 &= 12 \text{ mA} \angle 0^\circ \\ \mathbf{I}_2 &= 4 \text{ mA} \angle 0^\circ \\ \mathbf{E} &= 10 \text{ V} \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \sum \mathbf{I}_i &= \sum \mathbf{I}_o \\ 0 &= \mathbf{I}_1 + \frac{\mathbf{V}_1}{\mathbf{Z}_1} + \frac{\mathbf{V}_2}{\mathbf{Z}_3} + \mathbf{I}_2 \\ \text{and } \frac{\mathbf{V}_1}{\mathbf{Z}_1} + \frac{\mathbf{V}_2}{\mathbf{Z}_3} &= -\mathbf{I}_1 - \mathbf{I}_2 \\ \text{with } \mathbf{V}_2 - \mathbf{V}_1 &= \mathbf{E} \end{aligned}$$

Substituting and rearranging:

$$\mathbf{V}_1 \left[\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_3} \right] = -\mathbf{I}_1 - \mathbf{I}_2 - \frac{\mathbf{E}}{\mathbf{Z}_3}$$

and solving for \mathbf{V}_1 :

$$\begin{aligned} \mathbf{V}_1 &= 15.4 \text{ V} \angle 178.2^\circ \\ \text{with } \mathbf{V}_2 = \mathbf{V}_C &= 5.41 \text{ V} \angle 174.87^\circ \end{aligned}$$

27. Left node: \mathbf{V}_1

$$\begin{aligned} \sum \mathbf{I}_i &= \sum \mathbf{I}_o \\ 2 \text{ mA} \angle 0^\circ &= 12 \text{ mA} \angle 0^\circ + \frac{\mathbf{V}_1}{2 \text{ k}\Omega} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{1 \text{ k}\Omega} \end{aligned}$$

$$\text{and } 1.5 \mathbf{V}_1 - \mathbf{V}_2 = -10$$


Right node: \mathbf{V}_2

$$\begin{aligned} \sum \mathbf{I}_i &= \sum \mathbf{I}_o \\ 0 &= 2 \text{ mA} \angle 0^\circ + \frac{\mathbf{V}_2 - \mathbf{V}_1}{1 \text{ k}\Omega} - \frac{\mathbf{V}_2 - 6 \text{ V}_x}{3.3 \text{ k}\Omega} \end{aligned}$$

$$\text{and } 2.7 \mathbf{V}_1 - 3.7 \mathbf{V}_2 = -6.6$$

Using determinants: $\mathbf{V}_1 = \mathbf{V}_{2\text{k}\Omega} = -10.67 \text{ V} \angle 0^\circ = 10.67 \text{ V} \angle 180^\circ$
 $\mathbf{V}_2 = -6 \text{ V} \angle 0^\circ = 6 \text{ V} \angle 180^\circ$

28.

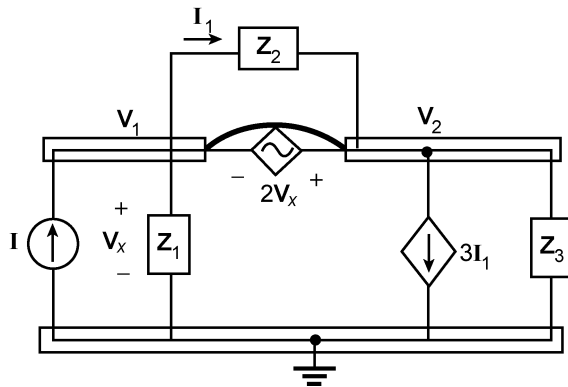

$$\begin{aligned} Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 1 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= 1 \text{ k}\Omega \angle 0^\circ \\ I &= 5 \text{ mA} \angle 0^\circ \end{aligned}$$


$$\begin{aligned} V_1: I &= \frac{V_1}{Z_1} + 3I_1 + \frac{V_2}{Z_3} \\ \text{with } I_1 &= \frac{V_1 - V_2}{Z_2} \\ \text{and } V_2 - V_1 &= 2V_x = 2V_1 \text{ or } V_2 = 3V_1 \end{aligned}$$

Substituting will result in:

$$\begin{aligned} V_1 \left[\frac{1}{Z_1} + \frac{3}{Z_2} \right] + 3V_1 \left[\frac{1}{Z_3} - \frac{3}{Z_2} \right] &= I \\ \text{or } V_1 \left[\frac{1}{Z_1} - \frac{6}{Z_2} + \frac{3}{Z_3} \right] &= I \end{aligned}$$

$$\begin{aligned} \text{and } V_1 = V_x &= -2 \text{ V} \angle 0^\circ \\ \text{with } V_2 &= -6 \text{ V} \angle 0^\circ \end{aligned}$$

29.

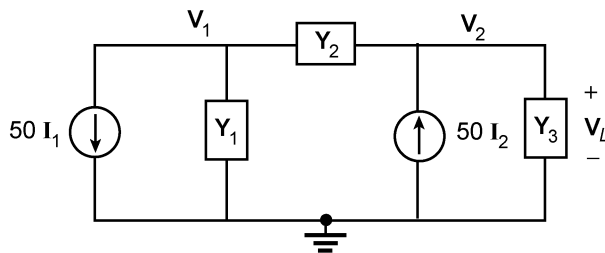

$$\begin{aligned} I_1 &= \frac{E_i \angle \theta}{R_1 \angle 0^\circ} = 1 \times 10^{-3} E_i \\ Y_1 &= \frac{1}{50 \text{ k}\Omega} = 0.02 \text{ mS} \angle 0^\circ \\ Y_2 &= \frac{1}{1 \text{ k}\Omega} = 1 \text{ mS} \angle 0^\circ \\ Y_3 &= 0.02 \text{ mS} \angle 0^\circ \\ I_2 &= (V_1 - V_2)Y_2 \end{aligned}$$

$$\begin{aligned} V_1(Y_1 + Y_2) - Y_2V_2 &= -50I_1 \\ V_2(Y_2 + Y_3) - Y_2V_1 &= 50I_2 = 50(V_1 - V_2)Y_2 = 50Y_2V_1 - 50Y_2V_2 \end{aligned}$$

$$\begin{aligned} (Y_1 + Y_2)V_1 - Y_2V_2 &= -50I_1 \\ -51Y_2V_1 + (51Y_2 + Y_3)V_2 &= 0 \end{aligned}$$

$$V_L = V_2 = \frac{-(50)(51)Y_2I_1}{(Y_1 + Y_2)(51Y_2 + Y_3) - 51Y_2^2} = -2451.92 E_i$$


30. a. yes

$$\frac{\mathbf{Z}_1}{\mathbf{Z}_3} = \frac{\mathbf{Z}_2}{\mathbf{Z}_4}$$

$$\frac{5 \times 10^3 \angle 0^\circ}{2.5 \times 10^3 \angle 90^\circ} = \frac{8 \times 10^3 \angle 0^\circ}{4 \times 10^3 \angle 90^\circ}$$

$$2 \angle -90^\circ = 2 \angle -90^\circ \text{ (balanced)}$$

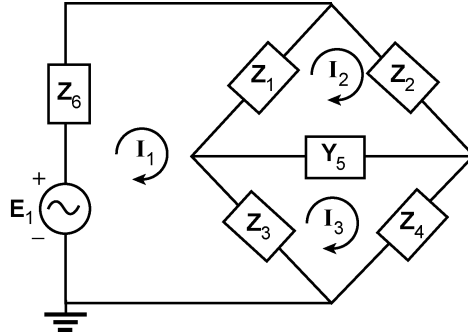b. $\mathbf{Z}_1 = 5 \text{ k}\Omega \angle 0^\circ$, $\mathbf{Z}_2 = 8 \text{ k}\Omega \angle 0^\circ$
 $\mathbf{Z}_3 = 2.5 \text{ k}\Omega \angle 90^\circ$, $\mathbf{Z}_4 = 4 \text{ k}\Omega \angle 90^\circ$
 $\mathbf{Z}_5 = 5 \text{ k}\Omega \angle -90^\circ$, $\mathbf{Z}_6 = 1 \text{ k}\Omega \angle 0^\circ$



$$\begin{aligned} \mathbf{I}_1[\mathbf{Z}_1 + \mathbf{Z}_3 + \mathbf{Z}_6] - \mathbf{Z}_1\mathbf{I}_2 - \mathbf{Z}_3\mathbf{I}_3 &= \mathbf{E} \\ \mathbf{I}_2[\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5] - \mathbf{Z}_1\mathbf{I}_1 - \mathbf{Z}_5\mathbf{I}_3 &= 0 \\ \mathbf{I}_3[\mathbf{Z}_3 + \mathbf{Z}_4 + \mathbf{Z}_5] - \mathbf{Z}_3\mathbf{I}_1 - \mathbf{Z}_5\mathbf{I}_2 &= 0 \end{aligned}$$


$$\begin{aligned} [\mathbf{Z}_1 + \mathbf{Z}_3 + \mathbf{Z}_6]\mathbf{I}_1 & & - \mathbf{Z}_1\mathbf{I}_2 & & - \mathbf{Z}_3\mathbf{I}_3 & = \mathbf{E} \\ -\mathbf{Z}_1\mathbf{I}_1 + [\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5]\mathbf{I}_2 & & & & - \mathbf{Z}_5\mathbf{I}_3 & = 0 \\ -\mathbf{Z}_3\mathbf{I}_1 & & - \mathbf{Z}_5\mathbf{I}_2 + [\mathbf{Z}_3 + \mathbf{Z}_4 + \mathbf{Z}_5]\mathbf{I}_3 & & & = 0 \end{aligned}$$

$$\mathbf{I}_2 = \frac{\mathbf{E}[\mathbf{Z}_1(\mathbf{Z}_3 + \mathbf{Z}_4 + \mathbf{Z}_5) + \mathbf{Z}_3\mathbf{Z}_5]}{\mathbf{Z}_\Delta = (\mathbf{Z}_1 + \mathbf{Z}_3 + \mathbf{Z}_6)(\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5)(\mathbf{Z}_3 + \mathbf{Z}_4 + \mathbf{Z}_5) - \mathbf{Z}_5^2 - \mathbf{Z}_1[\mathbf{Z}_1(\mathbf{Z}_3 + \mathbf{Z}_4 + \mathbf{Z}_5) - \mathbf{Z}_3\mathbf{Z}_5] - \mathbf{Z}_3[\mathbf{Z}_1\mathbf{Z}_5 + \mathbf{Z}_3(\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5)]}$$

$$\mathbf{I}_3 = \frac{\mathbf{E}[\mathbf{Z}_1\mathbf{Z}_5 + \mathbf{Z}_3(\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5)]}{\mathbf{Z}_\Delta}$$

$$\mathbf{I}_{\mathbf{Z}_5} = \mathbf{I}_2 - \mathbf{I}_3 = \frac{\mathbf{E}[\mathbf{Z}_1\mathbf{Z}_4 - \mathbf{Z}_3\mathbf{Z}_2]}{\mathbf{Z}_\Delta} = \frac{\mathbf{E}[20 \times 10^6 \angle 90^\circ - 20 \times 10^6 \angle 90^\circ]}{\mathbf{Z}_\Delta} = \mathbf{0} \text{ A}$$

c.

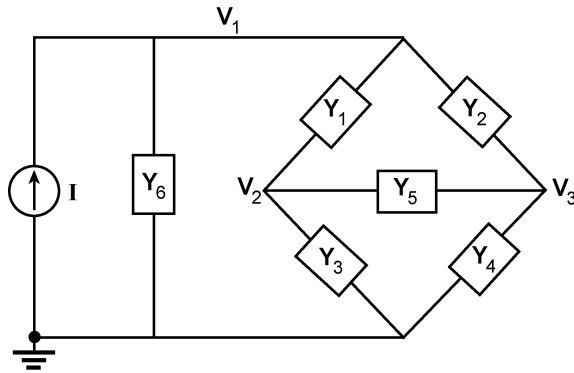

$$\begin{aligned} V_1[Y_1 + Y_2 + Y_6] - Y_1V_2 - Y_2V_3 &= I \\ V_2[Y_1 + Y_3 + Y_5] - Y_1V_1 - Y_5V_3 &= 0 \\ V_3[Y_2 + Y_4 + Y_5] - Y_2V_1 - Y_5V_2 &= 0 \end{aligned}$$

$$\begin{array}{rcl} [Y_1 + Y_2 + Y_6]V_1 & - Y_1V_2 & - Y_2V_3 = I \\ -Y_1V_1 + [Y_1 + Y_3 + Y_5]V_2 & & - Y_5V_3 = 0 \\ -Y_2V_1 & - Y_5V_2 + [Y_2 + Y_4 + Y_5]V_3 & = 0 \end{array}$$

$$I = \frac{E_s}{R_s} = \frac{10 \text{ V } \angle 0^\circ}{1 \text{ k}\Omega \angle 0^\circ} = 10 \text{ mA } \angle 0^\circ$$

$$Y_1 = \frac{1}{5 \text{ k}\Omega \angle 0^\circ} = 0.2 \text{ mS } \angle 0^\circ$$

$$Y_2 = \frac{1}{8 \text{ k}\Omega \angle 0^\circ} = 0.125 \text{ mS } \angle 0^\circ$$

$$Y_3 = \frac{1}{2.5 \text{ k}\Omega \angle 90^\circ} = 0.4 \text{ mS } \angle -90^\circ$$

$$Y_4 = \frac{1}{4 \text{ k}\Omega \angle 90^\circ} = 0.25 \text{ mS } \angle -90^\circ$$

$$Y_5 = \frac{1}{5 \text{ k}\Omega \angle -90^\circ} = 0.2 \text{ mS } \angle 90^\circ$$

$$Y_6 = \frac{1}{1 \text{ k}\Omega \angle 0^\circ} \\ V_2 = 1 \text{ mS } \angle 0^\circ$$

$$V_2 = \frac{I[Y_1(Y_2 + Y_4 + Y_5) + Y_2Y_5]}{Y_\Delta = (Y_1 + Y_2 + Y_6)(Y_1 + Y_3 + Y_5)(Y_2 + Y_4 + Y_5) - Y_1^2 - Y_1[Y_1(Y_2 + Y_4 + Y_5) + Y_2Y_5] - Y_2[Y_1Y_5 + Y_2(Y_1 + Y_3 + Y_5)]}$$

$$V_3 = \frac{I[Y_1Y_5 + Y_2(Y_1 + Y_3 + Y_5)]}{Y_\Delta}$$

$$V_{Z_5} = V_2 - V_3 = \frac{I[Y_1Y_4 - Y_4Y_3]}{Y_\Delta} = \frac{I[0.05 \times 10^{-3} \angle -90^\circ - 0.05 \times 10^{-3} \angle -90^\circ]}{Y_\Delta}$$

$$= 0 \text{ V}$$

31. a. $\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}$

$$\frac{4 \times 10^3 \angle 0^\circ}{4 \times 10^3 \angle 90^\circ} \stackrel{?}{=} \frac{4 \times 10^3 \angle 0^\circ}{4 \times 10^3 \angle -90^\circ} \\ 1 \angle -90^\circ \neq 1 \angle 90^\circ \text{ (not balanced)}$$

b. The solution to 26(b) resulted in

$$I_3 = I_{X_C} = \frac{E(Z_1Z_5 + Z_3(Z_1 + Z_2 + Z_5))}{Z_\Delta}$$

where $Z_\Delta = (Z_1 + Z_3 + Z_6)[(Z_1 + Z_2 + Z_5)(Z_3 + Z_4 + Z_5) - Z_5^2] - Z_1[Z_1(Z_3 + Z_4 + Z_5) - Z_3Z_5] - Z_3[Z_1Z_5 + Z_3(Z_1 + Z_2 + Z_5)]$

and $Z_1 = 5 \text{ k}\Omega \angle 0^\circ$, $Z_2 = 8 \text{ k}\Omega \angle 0^\circ$, $Z_3 = 2.5 \text{ k}\Omega \angle 90^\circ$
 $Z_4 = 4 \text{ k}\Omega \angle 90^\circ$, $Z_5 = 5 \text{ k}\Omega \angle -90^\circ$, $Z_6 = 1 \text{ k}\Omega \angle 0^\circ$

and $I_{X_C} = 1.76 \text{ mA } \angle -71.54^\circ$

c. The solution to 26(c) resulted in

$$\mathbf{V}_3 = \mathbf{V}_{X_C} = \frac{\mathbf{I}[\mathbf{Y}_1\mathbf{Y}_5 + \mathbf{Y}_2(\mathbf{Y}_1 + \mathbf{Y}_3 + \mathbf{Y}_5)]}{\mathbf{Y}_\Delta}$$

$$\text{where } \mathbf{Y}_\Delta = (\mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_6)[(\mathbf{Y}_1 + \mathbf{Y}_3 + \mathbf{Y}_5)(\mathbf{Y}_2 + \mathbf{Y}_4 + \mathbf{Y}_5) - \mathbf{Y}_5^2] \\ - \mathbf{Y}_1[\mathbf{Y}_1(\mathbf{Y}_2 + \mathbf{Y}_4 + \mathbf{Y}_5) + \mathbf{Y}_2\mathbf{Y}_5] \\ - \mathbf{Y}_2[\mathbf{Y}_1\mathbf{Y}_5 + \mathbf{Y}_2(\mathbf{Y}_1 + \mathbf{Y}_3 + \mathbf{Y}_5)]$$

$$\text{with } \mathbf{Y}_1 = 0.2 \text{ mS } \angle 0^\circ, \mathbf{Y}_2 = 0.125 \text{ mS } \angle 0^\circ, \mathbf{Y}_3 = 0.4 \text{ mS } \angle -90^\circ \\ \mathbf{Y}_4 = 0.25 \text{ mS } \angle -90^\circ, \mathbf{Y}_5 = 0.2 \text{ mS } \angle 90^\circ$$

$$\text{Source conversion: } \mathbf{Y}_6 = 1 \text{ mS } \angle 0^\circ, \mathbf{I} = 10 \text{ mA } \angle 0^\circ \\ \text{and } \mathbf{V}_3 = \mathbf{V}_{X_C} = 7.03 \text{ V } \angle -18.46^\circ$$

32. $\mathbf{Z}_1\mathbf{Z}_4 = \mathbf{Z}_3\mathbf{Z}_2$

$$(R_1 - jX_C)(R_x + jX_{L_x}) = R_3R_2 \quad X_C = \frac{1}{\omega C} = \frac{1}{(10^3 \text{ rad/s})(1 \mu\text{F})} = 1 \text{ k}\Omega$$

$$(1 \text{ k}\Omega - j1 \text{ k}\Omega)(R_x + jX_{L_x}) = (0.1 \text{ k}\Omega)(0.1 \text{ k}\Omega) = 10 \text{ k}\Omega$$

$$\text{and } R_x + jX_{L_x} = \frac{10 \times 10^3 \Omega}{1 \times 10^3 - j1 \times 10^3} = \frac{10 \times 10^3}{1.414 \times 10^3 \angle -45^\circ} = 5 \Omega + j5 \Omega$$

$$\therefore R_x = 5 \Omega, L_x = \frac{X_{L_x}}{\omega} = \frac{5 \Omega}{10^3 \text{ rad/s}} = 5 \text{ mH}$$

33. $X_{C_1} = \frac{1}{\omega C_1} = \frac{1}{(1000 \text{ rad/s})(3 \mu\text{F})} = \frac{1}{3} \text{ k}\Omega$

$$\mathbf{Z}_1 = R_1 \parallel X_{C_1} \angle -90^\circ = (2 \text{ k}\Omega \angle 0^\circ) \parallel \frac{1}{3} \text{ k}\Omega \angle -90^\circ = 328.8 \Omega \angle -80.54^\circ$$

$$\mathbf{Z}_2 = R_2 \angle 0^\circ = 0.5 \text{ k}\Omega \angle 0^\circ, \mathbf{Z}_3 = R_3 \angle 0^\circ = 4 \text{ k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_4 = R_x + jX_{L_x} = 1 \text{ k}\Omega + j6 \text{ k}\Omega$$

$$\frac{\mathbf{Z}_1}{\mathbf{Z}_3} = \frac{\mathbf{Z}_2}{\mathbf{Z}_4}$$

$$\frac{328.8 \Omega \angle -80.54^\circ}{4 \text{ k}\Omega \angle 0^\circ} \stackrel{?}{=} \frac{0.5 \text{ k}\Omega \angle 0^\circ}{6.083 \Omega \angle 80.54^\circ}$$

$$82.2 \times 10^{-3} \angle -80.54^\circ \stackrel{?}{=} 82.2 \times 10^{-3} \angle -80.54^\circ \text{ (balanced)}$$

34. Apply Eq. 18.6.

35. For balance:

$$R_1(R_x + jX_{L_x}) = R_2(R_3 + jX_{L_3})$$


$$R_1R_x + jR_1X_{L_x} = R_2R_3 + jR_2X_{L_3}$$

$$\therefore R_1R_x = R_2R_3 \text{ and } R_x = \frac{R_2R_3}{R_1}$$

$$R_1X_{L_x} = R_2X_{L_3} \text{ and } R_1\omega L_x = R_2\omega L_3$$

$$\text{so that } L_x = \frac{R_2L_3}{R_1}$$

36. a.

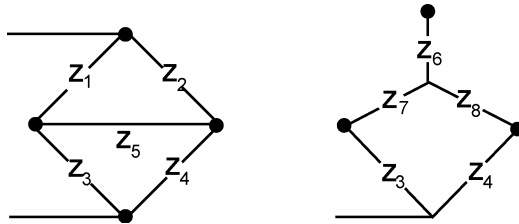

$$\mathbf{Z}_1 = 8 \Omega \angle -90^\circ = -j8 \Omega$$

$$\mathbf{Z}_2 = 4 \Omega \angle 90^\circ = +j4 \Omega$$

$$\mathbf{Z}_3 = 8 \Omega \angle 90^\circ = +j8 \Omega$$

$$\mathbf{Z}_4 = 6 \Omega \angle -90^\circ = -j6 \Omega$$

$$\mathbf{Z}_5 = 5 \Omega \angle 0^\circ$$

$$\mathbf{Z}_6 = \frac{\mathbf{Z}_1\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5} = 5 \Omega \angle 38.66^\circ$$

$$\mathbf{Z}_7 = \frac{\mathbf{Z}_1\mathbf{Z}_5}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5} = 6.25 \Omega \angle -51.34^\circ$$

$$\mathbf{Z}_8 = \frac{\mathbf{Z}_2\mathbf{Z}_5}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_5} = 3.125 \Omega \angle 128.66^\circ$$

$$\mathbf{Z}' = \mathbf{Z}_7 + \mathbf{Z}_3 = 3.9 \Omega + j3.12 \Omega = 4.99 \Omega \angle 38.66^\circ$$


$$\mathbf{Z}'' = \mathbf{Z}_8 + \mathbf{Z}_4 = -1.95 \Omega - j3.56 \Omega = 4.06 \Omega \angle -118.71^\circ$$

$$\mathbf{Z}' \parallel \mathbf{Z}'' = 10.13 \Omega \angle -67.33^\circ = 3.90 \Omega - j9.35 \Omega$$

$$\mathbf{Z}_T = \mathbf{Z}_6 + \mathbf{Z}' \parallel \mathbf{Z}'' = 7.80 \Omega - j6.23 \Omega = 9.98 \Omega \angle -38.61^\circ$$


$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{120 \text{ V} \angle 0^\circ}{9.98 \Omega \angle -38.61^\circ} = \mathbf{12.02 \text{ A} \angle 38.61^\circ}$$

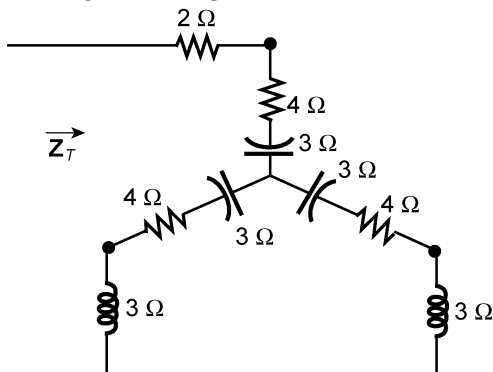37. $\mathbf{Z}_Y = \frac{\mathbf{Z}_\Delta}{3} = \frac{12 \Omega - j9 \Omega}{3} = 4 \Omega - j3 \Omega$



$$\begin{aligned}
 \mathbf{Z}_T &= 2 \Omega + 4 \Omega + j3 \Omega + [4 \Omega - j3 \Omega + j3 \Omega] \parallel [4 \Omega - j3 \Omega + j3 \Omega] \\
 &= 6 \Omega - j3 \Omega + 2 \Omega \\
 &= 8 \Omega - j3 \Omega = 8.544 \Omega \angle -20.56^\circ \\
 \mathbf{I} &= \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{60 \text{ V} \angle 0^\circ}{8.544 \Omega \angle -20.56^\circ} = 7.02 \text{ A} \angle 20.56^\circ
 \end{aligned}$$


38.

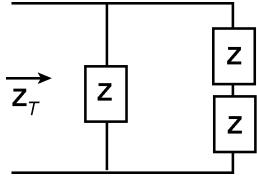

$$\begin{aligned}
 \mathbf{Z}_\Delta &= 3\mathbf{Z}_Y = 3(3 \Omega \angle 90^\circ) = 9 \Omega \angle 90^\circ \\
 \mathbf{Z} &= 9 \Omega \angle 90^\circ \parallel (12 \Omega - j16 \Omega) \\
 &= 9 \Omega \angle 90^\circ \parallel 20 \Omega \angle 53.13^\circ \\
 &= 12.96 \Omega \angle 67.13^\circ
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{Z}_T &= \mathbf{Z} \parallel 2\mathbf{Z} = \frac{2\mathbf{Z}^2}{\mathbf{Z} + 2\mathbf{Z}} = \frac{2}{3}\mathbf{Z} = \frac{2}{3} [12.96 \Omega \angle 67.13^\circ] = 8.64 \Omega \angle 67.13^\circ \\
 \mathbf{I} &= \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V} \angle 0^\circ}{8.64 \Omega \angle 67.13^\circ} = 11.57 \text{ A} \angle -67.13^\circ
 \end{aligned}$$

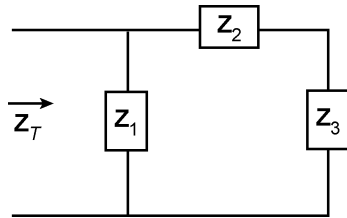39. $\mathbf{Z}_\Delta = 3\mathbf{Z}_Y = 3(5 \Omega) = 15 \Omega$



$$\begin{aligned}
 \mathbf{Z}_1 &= 15 \Omega \angle 0^\circ \parallel 5 \Omega \angle -90^\circ \\
 &= 4.74 \Omega \angle -71.57^\circ \\
 \mathbf{Z}_2 &= 15 \Omega \angle 0^\circ \parallel 5 \Omega \angle -90^\circ = 4.74 \Omega \angle -71.57^\circ \\
 \mathbf{Z}_3 &= \mathbf{Z}_1 = 4.74 \Omega \angle -71.57^\circ \\
 &= 1.5 \Omega - j4.5 \Omega
 \end{aligned}$$

$$\mathbf{Z}_T = \text{since } \mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3$$

$$\mathbf{Z}_T = \mathbf{Z}_1 \parallel (\mathbf{Z}_1 + \mathbf{Z}_1) = \mathbf{Z}_1 \parallel 2\mathbf{Z}_1 = \frac{2\mathbf{Z}_1^2}{\mathbf{Z}_1 + 2\mathbf{Z}_1} = \frac{2\mathbf{Z}_1^2}{3\mathbf{Z}_1} = \frac{2}{3}\mathbf{Z}_1$$

$$\mathbf{Z}_T = \frac{2}{3}(4.74 \Omega \angle -71.57^\circ) = 3.16 \Omega \angle -71.57^\circ$$

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V} \angle 0^\circ}{3.16 \Omega \angle -71.57^\circ} = 31.65 \text{ A} \angle 71.57^\circ$$