


Chapter 20

1. a. $P_T = 60 \text{ W} + 45 \text{ W} + 25 \text{ W} = \mathbf{130 \text{ W}}$

b. $Q_T = \mathbf{0 \text{ VARS}}, S_T = P_T = \mathbf{130 \text{ VA}}$

c. $S_T = EI_s, I_s = \frac{S_T}{E} = \frac{130 \text{ VA}}{240 \text{ V}} = \mathbf{0.542 \text{ A}}$

d.

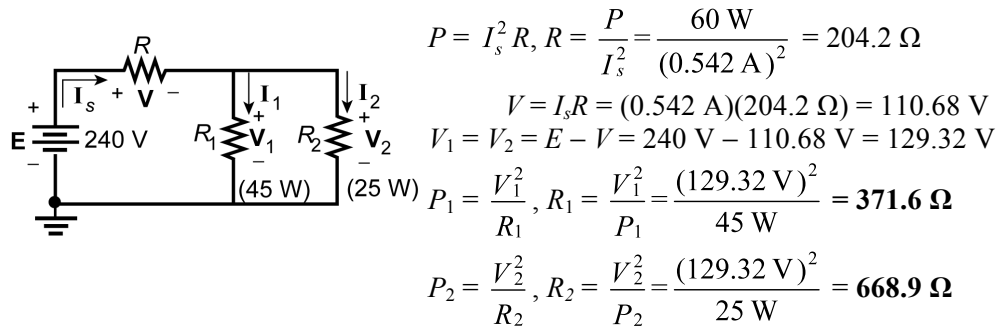

e. $I_1 = \frac{V_1}{R_1} = \frac{129.32 \text{ V}}{371.6 \Omega} = \mathbf{0.348 \text{ A}}, I_2 = \frac{V_2}{R_2} = \frac{129.32 \text{ V}}{668.9 \Omega} = \mathbf{0.193 \text{ A}}$

2. a. $Z_T = 3 \Omega - j5 \Omega + j9 \Omega = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$

$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{50 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 10 \text{ A} \angle -53.13^\circ$

R: $P = I^2 R = (10 \text{ A})^2 3 \Omega = \mathbf{300 \text{ W}}$

L: $P = \mathbf{0 \text{ W}}$

C: $P = \mathbf{0 \text{ W}}$

b. R: $Q = \mathbf{0 \text{ VAR}}$

C: $Q_C = I^2 X_C = (10 \text{ A})^2 5 \Omega = \mathbf{500 \text{ VAR}}$

L: $Q_L = I^2 X_L = (10 \text{ A})^2 9 \Omega = \mathbf{900 \text{ VAR}}$

c. R: $S = \mathbf{300 \text{ VA}}$

C: $S = \mathbf{500 \text{ VA}}$

L: $S = \mathbf{900 \text{ VA}}$

d. $P_T = 300 \text{ W}$

$Q_T = Q_L - Q_C = \mathbf{400 \text{ VAR}(L)}$

$S_T = \sqrt{P_T^2 + Q_T^2} = EI = (50 \text{ V})(10 \text{ A}) = \mathbf{500 \text{ VA}}$

$F_p = \frac{P_T}{S_T} = \frac{300 \text{ W}}{500 \text{ VA}} = \mathbf{0.6 \text{ lagging}}$

e. -

$$f. \quad W_R = \frac{VI}{f_1}; \quad W_R = 2 \left[\frac{VI}{f_2} \right] = 2 \left[\frac{VI}{2f_1} \right] = \frac{VI}{f_1}$$

$$V = IR = (10 \text{ A})(3 \Omega) = 30 \text{ V}$$

$$W_R = \frac{(30 \text{ V})(10 \text{ A})}{60 \text{ Hz}} = \mathbf{5 \text{ J}}$$

$$g. \quad V_C = IX_C = (10 \text{ A})(5 \Omega) = 50 \text{ V}$$

$$W_C = \frac{VI}{\omega_1} = \frac{(50 \text{ V})(10 \text{ A})}{(2\pi)(60 \text{ Hz})} = \mathbf{1.33 \text{ J}}$$

$$V_L = IX_L = (10 \text{ A})(9 \Omega) = 90 \text{ V}$$

$$W_L = \frac{VI}{\omega_1} = \frac{(90 \text{ V})(10 \text{ A})}{376.8} = \mathbf{2.39 \text{ J}}$$

3. a. R_1 :

$$\mathbf{I}_{R_1} = \frac{\mathbf{E}}{\mathbf{R}_1} = \frac{120 \text{ V} \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} = 60 \text{ mA} \angle 0^\circ$$

$$P_{R_1} = I^2 R = (60 \text{ mA})^2 2 \text{ k}\Omega = \mathbf{7.2 \text{ W}}$$

$$Q_T = \mathbf{0 \text{ VAR}}$$

$$S_{R_1} = P_{R_1} = \mathbf{7.2 \text{ VA}}$$

C :

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(5 \text{ kHz})(0.02 \mu\text{F})} = 3.98 \text{ k}\Omega$$

$$P_T = \mathbf{0 \text{ W}}$$

$$Q_T: \mathbf{I}_C = \frac{\mathbf{E}}{\mathbf{X}_C} = \frac{120 \text{ V} \angle 0^\circ}{3.98 \text{ k}\Omega \angle -90^\circ} = 30.15 \text{ mA} \angle 90^\circ$$

$$Q_C = I^2 X_C = (30.15 \text{ mA})^2 3.98 \text{ k}\Omega = \mathbf{3.62 \text{ VAR}}$$

$$S_T = Q_C = \mathbf{3.62 \text{ VA}}$$

R_2-L :

$$X_L = 2\pi fL = 2\pi(2 \text{ kHz})(80 \text{ mH}) = 1 \text{ k}\Omega$$

$$\mathbf{Z}' = 200 \Omega + j1 \text{ k}\Omega = 1.02 \text{ k}\Omega \angle 78.69^\circ$$

$$\mathbf{I}_L = \frac{\mathbf{E}}{\mathbf{Z}'} = \frac{120 \text{ V} \angle 0^\circ}{1.02 \text{ k}\Omega \angle 78.69^\circ} = 117.65 \text{ mA} \angle -78.69^\circ$$


$$Q_L = I^2 X_L = (117.6 \text{ mA})^2 (1 \text{ k}\Omega) = \mathbf{13.84 \text{ VAR}}$$

$$Q_T = Q_L = \mathbf{13.84 \text{ VAR}}$$

$$P_T = I^2 R = (117.65 \text{ mA})^2 (200 \Omega) = \mathbf{2.77 \text{ W}}$$

$$S_T = 2.77 \text{ W} - j13.84 \text{ VAR} \Rightarrow \mathbf{1.41 \text{ VA}}$$

b.

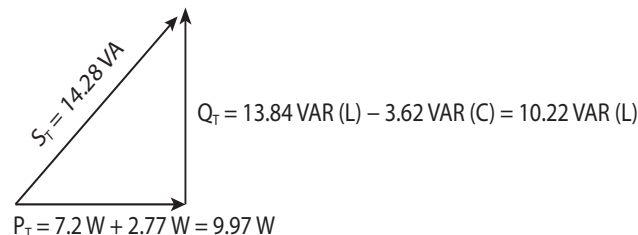

$$S_T = 9.97 + j10.22 = 14.28 \text{ VA } \angle 45.71^\circ$$

$$\begin{aligned} \text{c. } \mathbf{Z}' = \mathbf{R}_1 \parallel \mathbf{X}_C &= \frac{(2 \text{ k}\Omega \angle 0^\circ)(3.98 \text{ k}\Omega \angle -90^\circ)}{2 \text{ k}\Omega - j3.98 \text{ k}\Omega} = \frac{7.96 \text{ k}\Omega \angle -90^\circ}{4.45 \angle -63.32^\circ} \\ &= 1.79 \text{ k}\Omega \angle -26.68^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{Z}_T = \mathbf{Z}' \parallel (R_2 + jX_L) &= \frac{(1.79 \text{ k}\Omega \angle -26.68^\circ)(1.02 \text{ k}\Omega \angle 78.69^\circ)}{(1.6 \text{ k}\Omega - j0.8 \text{ k}\Omega) + (0.2 \text{ k}\Omega + j1 \text{ k}\Omega)} \\ &= \frac{1.83 \text{ k}\Omega \angle 52.06^\circ}{1.8 \text{ k}\Omega + j0.2 \text{ k}\Omega} = \frac{1.83 \text{ k}\Omega \angle 52.06^\circ}{1.81 \angle 6.34^\circ} \\ &= 1.01 \text{ k}\Omega \angle 45.72^\circ \end{aligned}$$

$$F_p = \frac{P_T}{S_T} = \frac{9.97 \text{ W}}{14.28 \text{ VA}} = \mathbf{0.698 \text{ lagging}}$$

$$\text{d. } \mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{120 \text{ V } \angle 0^\circ}{1.01 \text{ k}\Omega \angle 45.72^\circ} = \mathbf{118.81 \text{ mA } \angle -45.72^\circ}$$

$$\begin{aligned} \text{4. a. } P_T &= 0 + 100 \text{ W} + 300 \text{ W} = \mathbf{400 \text{ W}} \\ Q_T &= 200 \text{ VAR}(L) - 600 \text{ VAR}(C) + 0 = \mathbf{-400 \text{ VAR}(C)} \\ S_T &= \sqrt{P_T^2 + Q_T^2} = \mathbf{565.69 \text{ VA}} \\ F_p &= \frac{P_T}{S_T} = \frac{400 \text{ W}}{565.69 \text{ VA}} = \mathbf{0.707 \text{ (leading)}} \end{aligned}$$

b. —

$$\begin{aligned} \text{c. } P_T &= EI_s \cos \theta_T \\ 400 \text{ W} &= (100 \text{ V})I_s(0.7071) \\ I_s &= \frac{400 \text{ W}}{70.71 \text{ V}} = 5.66 \text{ A} \\ \mathbf{I}_s &= 5.66 \text{ A } \angle 135^\circ \end{aligned}$$

$$\begin{aligned} \text{5. a. } P_T &= 600 \text{ W} + 500 \text{ W} + 100 \text{ W} = \mathbf{1200 \text{ W}} \\ Q_T &= 1200 \text{ VAR}(L) + 600 \text{ VAR}(L) - 1800(C) = \mathbf{0 \text{ VAR}} \\ S_T &= P_T = \mathbf{1200 \text{ VA}} \end{aligned}$$

$$\text{b. } F_p = \frac{P_T}{S_T} = \frac{1200 \text{ W}}{1200 \text{ VA}} = 1$$

c. —

$$\begin{aligned} \text{d. } I_s &= \frac{S_T}{E} = \frac{1200 \text{ VA}}{200 \text{ V}} = 6 \text{ A}, 1 \Rightarrow 0^\circ \\ \mathbf{I}_s &= \mathbf{6 \text{ A } \angle 0^\circ} \end{aligned}$$

6. a. $P_T = 200 \text{ W} + 100 \text{ W} + 0 + 50 \text{ W} = \mathbf{350 \text{ W}}$
 $Q_T = 50 \text{ VAR}(L) + 100 \text{ VAR}(L) - 200 \text{ VAR}(C) - 400 \text{ VAR}(C) = \mathbf{-450 \text{ VAR}(C)}$
 $S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{570.09 \text{ VA}}$
- b. $F_p = \frac{P_T}{S_T} = \frac{350 \text{ W}}{570.09 \text{ VA}} = \mathbf{0.614 \text{ (leading)}}$
- c. -
- d. $P_T = EI_s \cos \theta_T$
 $350 \text{ W} = (50 \text{ V})I_s(0.614)$
 $I_s = \frac{350 \text{ W}}{30.7 \text{ V}} = 11.4 \text{ A}$
 $\mathbf{I_s = 11.4 \text{ A } \angle 52.12^\circ}$
7. a. 200 W: Resistive:
 $P = I^2 R \Rightarrow R = \frac{P}{I^2} = \frac{200 \text{ W}}{(2 \text{ A})^2} = \frac{200 \text{ W}}{4 \text{ A}^2} = \mathbf{50 \Omega}$
- 400 VAR(L): Inductive:
 $Q_L = I^2 X_L \Rightarrow X_L = \frac{Q_L}{I^2} = \frac{200 \text{ VAR}(L)}{4 \text{ A}^2} = 100 \Omega$
 $X_L = 2\pi fL \Rightarrow L = \frac{X_L}{2\pi f} = \frac{100 \Omega}{2\pi(5 \text{ kHz})} = \mathbf{3.18 \text{ mH}}$
- 600 VAR(C): Capacitive:
 $Q_C = I^2 X_C \Rightarrow X_C = \frac{Q_C}{I^2} = \frac{600 \text{ VAR}(C)}{4 \text{ A}^2} = 150 \Omega$
 $X_C = \frac{1}{2\pi fC} \Rightarrow C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi(5 \text{ kHz})(150 \Omega)} = \mathbf{212.2 \text{ nF}}$
- b. $\mathbf{Z_T = R + jX_L - jX_C = 50 \Omega + j100 \Omega - j150 \Omega = 50 \Omega - j50 \Omega}$
 $= 70.71 \Omega \angle -45^\circ$
- c. $\mathbf{V_s = IZ_T = (2 \text{ A } \angle 0^\circ)(70.71 \Omega \angle -45^\circ)}$
 $= \mathbf{141.42 \text{ V } \angle -45^\circ}$
- d. $F_p = \cos(45^\circ) = \mathbf{0.707 \text{ leading}}$
- e. $\mathbf{V_C = IX_C = (2 \text{ A } \angle 0^\circ)(150 \Omega \angle -90^\circ)}$
 $= \mathbf{300 \text{ V } \angle -90^\circ}$
8. a. $\mathbf{I_R = \frac{60 \text{ V } \angle 30^\circ}{20 \Omega \angle 0^\circ} = 3 \text{ A } \angle 30^\circ}$
 $P = I^2 R = (3 \text{ A})^2 20 \Omega = \mathbf{180 \text{ W}}$
 $Q_R = \mathbf{0 \text{ VAR}}$
 $S = P = \mathbf{180 \text{ VA}}$

$$b. \quad \mathbf{I}_L = \frac{60 \text{ V} \angle 30^\circ}{10 \Omega \angle 90^\circ} = 6 \text{ A} \angle -60^\circ$$

$$P_L = \mathbf{0} \text{ W}$$

$$Q_L = I^2 X_L = (6 \text{ A})^2 10 \Omega = \mathbf{360 \text{ VAR}(L)}$$

$$S = Q_L = \mathbf{360 \text{ VA}}$$

$$c. \quad P_T = 180 \text{ W} + 400 \text{ W} = \mathbf{580 \text{ W}}$$

$$Q_T = 600 \text{ VAR}(L) + 360 \text{ VAR}(L) = \mathbf{960 \text{ VAR}(L)}$$

$$S_T = \sqrt{(580 \text{ W})^2 + (960 \text{ VAR})^2} = \mathbf{1121.61 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{580 \text{ W}}{1121.61 \text{ VA}} = \mathbf{0.517 \text{ (lagging)}} \quad \theta = 58.87^\circ$$

$$d. \quad S_T = EI_s$$

$$I_s = \frac{S_T}{E} = \frac{1121.61 \text{ VA}}{60 \text{ V}} = 18.69 \text{ A}$$

$$\theta_{I_s} = 30^\circ - 58.87^\circ = -28.87^\circ$$

$$\mathbf{I_s = 18.69 \text{ A} \angle -28.87^\circ}$$

$$9. \quad a. \quad R_3 + jX_L = 4 \Omega + j4 \Omega = 5.66 \Omega \angle 45^\circ$$

$$R_2 \parallel X_C \angle -90^\circ = \frac{(2 \Omega \angle 0^\circ)(5 \Omega \angle -90^\circ)}{2 \Omega - j5 \Omega} = \frac{10 \Omega \angle -90^\circ}{5.39 \angle -68.2^\circ} = 1.86 \Omega \angle -21.8^\circ$$

$$\frac{(5.66 \Omega \angle 45^\circ)(1.86 \Omega \angle -21.8^\circ)}{(4 \Omega - j4 \Omega) + (1.73 \Omega - j0.69 \Omega)}$$

$$= \frac{10.53 \Omega \angle 23.2^\circ}{5.73 + j3.31} = \frac{10.53 \Omega \angle 23.2^\circ}{6.62 \angle 30.01^\circ} = 1.59 \Omega \angle -6.81^\circ = 1.58 \Omega - j0.19 \Omega$$

$$\mathbf{Z}_T = R_1 + 1.59 \Omega \angle -6.81^\circ = 2 \Omega + 1.58 \Omega - j0.19 \Omega$$

$$= 3.58 \Omega - j0.19 \Omega = 3.59 \Omega \angle -3.03^\circ$$

$$\mathbf{I_s} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{20 \text{ V} \angle 0^\circ}{3.59 \Omega \angle -3.03^\circ} = \mathbf{5.57 \text{ A} \angle 3.03^\circ}$$

$$b. \quad R_1: P_{R_1} = I_s^2 R_1 = (5.57 \text{ A})^2 2 \Omega = \mathbf{62.05 \text{ W}}$$

$$\mathbf{V}_{R_1} = \mathbf{I_s} \mathbf{R}_1 = (5.57 \text{ A} \angle 3.03^\circ)(2 \Omega \angle 0^\circ) = 11.14 \text{ V} \angle 3.03^\circ$$

$$\mathbf{V}_{R_2} = \mathbf{E} - \mathbf{V}_{R_1} = 20 \text{ V} \angle 0^\circ - 11.14 \text{ V} \angle 3.03^\circ$$

$$= 20 \text{ V} - (11.12 \text{ V} + j0.5 \text{ V}) = 8.88 \text{ V} - j0.59 \text{ V}$$

$$= 8.89 \text{ V} \angle -3.8^\circ$$

$$R_2: P_{R_2} = \frac{V_{R_2}^2}{R_2} = \frac{(8.89 \text{ V})^2}{2 \Omega} = \mathbf{39.52 \text{ W}}$$

$$\mathbf{I}_{R_3} = \frac{\mathbf{V}_{R_2}}{R_3 + jX_L} = \frac{8.89 \text{ V} \angle -3.8^\circ}{4 \Omega + j4 \Omega} = \frac{8.89 \text{ V} \angle -3.8^\circ}{5.66 \Omega \angle 45^\circ} = 1.57 \text{ A} \angle -48.8^\circ$$

$$R_3: P_{R_3} = I_{R_3}^2 R_3 = (1.57 \text{ A})^2 4 \Omega = \mathbf{9.86 \text{ W}}$$


- c. $X_C: Q_{X_C} = \frac{V_{R_3}^2}{X_C} = \frac{(8.89 \text{ V})^2}{5 \Omega} = \mathbf{15.81 \text{ VAR}(C)}$
 $X_L: Q_L = I^2 X_L = (1.57 \text{ A})^2 4 \Omega = \mathbf{9.86 \text{ VAR}(L)}$
- d. $R_1: S_T = P_{R_1} = \mathbf{62.05 \text{ VA}}$
 $R_2: S_T = P_{R_2} = \mathbf{39.52 \text{ VA}}$
 $R_3: S_T = P_{R_3} = \mathbf{9.86 \text{ VA}}$
 $C: S_T = Q_{X_C} = \mathbf{15.81 \text{ VA}}$
 $L: S_T = Q_L = \mathbf{9.86 \text{ VA}}$
- e. $P_T: P_{R_1} + P_{R_2} + P_{R_3} = 62.05 \text{ W} + 39.52 \text{ W} + 9.86 \text{ W}$
 $= \mathbf{111.43 \text{ W}}$
 $Q_T: Q_{X_C} - Q_{X_L} = 15.81 \text{ VAR}(C) - 9.86 \text{ VAR}(L)$
 $= \mathbf{5.95 \text{ VAR}(L)}$
 $S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{111.59 \text{ VA}}$
 $F_p = \frac{P_T}{S_T} = \frac{111.43 \text{ W}}{111.59 \text{ VA}} = \mathbf{0.998 \text{ (leading)}}$
- f. –
10. a. $Z_1 = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$
 $Z_2 = 3 \Omega - j4 \Omega = 5 \Omega \angle -53.13^\circ$
 $Z_T = Z_1 \parallel Z_2 = \frac{(5 \Omega \angle 53.13^\circ)(5 \Omega \angle -53.13^\circ)}{(3 \Omega + j4 \Omega) + (3 \Omega - j4 \Omega)} = \frac{25 \Omega \angle 0^\circ}{6} = 4.17 \Omega \angle 0^\circ$
 $I_s = \frac{E}{Z_T} = \frac{50 \text{ V} \angle 60^\circ}{4.17 \Omega \angle 0^\circ} = \mathbf{11.99 \text{ A} \angle 60^\circ}$
- b. $I_{R-L} = \frac{E}{Z_{R-L}} = \frac{50 \text{ V} \angle 60^\circ}{5 \Omega \angle 53.13^\circ} = 10 \text{ A} \angle 16.87^\circ$
 $P_{3\Omega} = I^2 R = (10 \text{ A})^2 \cdot 3 \Omega = \mathbf{300 \text{ W}}$
 $I_{R-C} = \frac{E}{Z_{R-C}} = \frac{50 \text{ V} \angle 60^\circ}{5 \Omega \angle -53.13^\circ} = 10 \text{ A} \angle 113.13^\circ$
 $P_{3\Omega} = I^2 R = (10 \text{ A})^2 \cdot 3 \Omega = \mathbf{300 \text{ W}}$
- c. $L: I_{R-L} = 10 \text{ A} \angle 16.87^\circ$
 $Q_L = I^2 X_L = (10 \text{ A})^2 \cdot 4 \Omega = \mathbf{400 \text{ VAR}(L)}$
 $C: I_{R-C} = 10 \text{ A} \angle 113.13^\circ$
 $Q_C = I^2 X_C = (10 \text{ A})^2 \cdot 4 \Omega = \mathbf{400 \text{ VAR}(C)}$
- d. $3 \Omega: S_T = P_{3\Omega} = \mathbf{300 \text{ VA}}$ for each resistor
 $L: S_T = Q_L = \mathbf{400 \text{ VA}}$
 $C: S_T = Q_C = \mathbf{400 \text{ VA}}$
- e. $P_T = 300 \text{ W} + 300 \text{ W} = \mathbf{600 \text{ W}}$

$$Q_T = 400 \text{ VAR}(L) + 400 \text{ VAR}(C) = \mathbf{0 \text{ VAR}}$$

$$S_T = P_T = \mathbf{600 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{600 \text{ VA}} = \mathbf{1}$$

11. a–c.

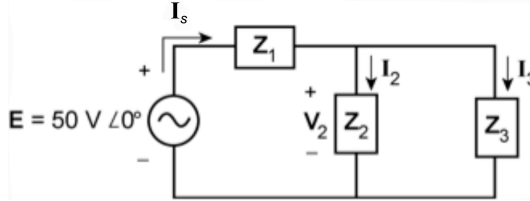

$$X_L = \omega L = (400 \text{ rad/s})(0.1 \text{ H}) = 40 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(400 \text{ rad/s})(100 \mu\text{F})} = 25 \Omega$$

$$\mathbf{Z_1 = 40 \Omega \angle 90^\circ, Z_2 = 25 \Omega \angle -90^\circ}$$

$$\mathbf{Z_3 = 30 \Omega \angle 0^\circ}$$

$$\mathbf{Z_T = Z_1 + Z_2 \parallel Z_3 = +j40 \Omega + (25 \Omega \angle -90^\circ) \parallel (30 \Omega \angle 0^\circ)}$$

$$= +j40 \Omega + 19.21 \Omega \angle -50.19^\circ$$

$$= +j40 \Omega + 12.3 \Omega - j14.76 \Omega$$

$$= 12.3 \Omega + j25.24 \Omega$$

$$= \mathbf{28.08 \Omega \angle 64.02^\circ}$$

$$\mathbf{I_s = \frac{E}{Z_T} = \frac{50 \text{ V} \angle 0^\circ}{28.08 \Omega \angle 64.02^\circ} = 1.78 \text{ A} \angle -64.02^\circ}$$

$$\mathbf{V_2 = I_s(Z_2 \parallel Z_3) = (1.78 \text{ A} \angle -64.02^\circ)(19.21 \Omega \angle -50.19^\circ)}$$

$$= 34.19 \text{ V} \angle -114.21^\circ$$

$$\mathbf{I_2 = \frac{V_2}{Z_2} = \frac{34.19 \text{ V} \angle -114.21^\circ}{25 \Omega \angle -90^\circ} = 1.37 \text{ A} \angle -24.21^\circ}$$

$$\mathbf{I_3 = \frac{V_2}{Z_3} = \frac{34.19 \text{ V} \angle -114.21^\circ}{30 \Omega \angle 0^\circ} = 1.14 \text{ A} \angle -114.21^\circ}$$

$$\mathbf{Z_1: P = 0 \text{ W}, Q_L = I_s^2 X_L = (1.78 \text{ A})^2 40 \Omega = 126.74 \text{ VAR}(L), S = 126.74 \text{ VA}}$$

$$\mathbf{Z_2: P = 0 \text{ W}, Q_C = I_2^2 X_C = (1.37 \text{ A})^2 25 \Omega = 46.92 \text{ VAR}(C), S = 46.92 \text{ VA}}$$

$$\mathbf{Z_3: P = I_3^2 R = (1.14 \text{ A})^2 30 \Omega = 38.99 \text{ W}, Q_R = 0 \text{ VAR}, S = 38.99 \text{ VA}}$$

d. $P_T = 0 + 0 + 38.99 \text{ W} = \mathbf{38.99 \text{ W}}$

$$Q_T = +126.74 \text{ VAR}(L) - 46.92 \text{ VAR}(C) + 0 = \mathbf{79.82 \text{ VAR}(L)}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{88.83 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{38.99 \text{ W}}{88.83 \text{ VA}} = \mathbf{0.439 \text{ (lagging)}}$$

e. –

f. $W_R = \frac{V_R I_R}{2f_1} = \frac{V_2 I_3}{2f_1} = \frac{(34.19 \text{ V})(1.14 \text{ A})}{2(63.69 \text{ Hz})} = \mathbf{0.31 \text{ J}}$

$$f_1 = \frac{\omega_1}{2\pi} = \frac{400 \text{ rad/s}}{6.28} = 63.69 \text{ Hz}$$

g.
$$W_L = \frac{V_L I_L}{\omega_1} = \frac{(I_s X_L) I_s}{\omega_1} = \frac{I_s^2 X_L}{\omega_1} = \frac{(1.78 \text{ A})^2 40 \Omega}{400 \text{ rad/s}} = \mathbf{0.32 \text{ J}}$$

$$W_C = \frac{V_C I_C}{\omega_1} = \frac{V_2 I_2}{\omega_1} = \frac{(34.19 \text{ V})(1.37 \text{ A})}{400 \text{ rad/s}} = \mathbf{0.12 \text{ J}}$$

12. a.
$$I_s = \frac{S_T}{E} = \frac{10,000 \text{ VA}}{200 \text{ V}} = 50 \text{ A}$$

$$0.5 \Rightarrow 60^\circ \text{ leading}$$

$$\therefore \mathbf{I_s \text{ leads } E \text{ by } 60^\circ}$$

$$\mathbf{Z_T} = \frac{\mathbf{E}}{\mathbf{I_s}} = \frac{200 \text{ V} \angle 0^\circ}{50 \text{ A} \angle 60^\circ} = 4 \Omega \angle -60^\circ = 2 \Omega - j3.464 \Omega = R - jX_C$$

b.
$$F_p = \frac{P_T}{S_T} \Rightarrow P_T = F_p S_T = (0.5)(10,000 \text{ VA}) = \mathbf{5000 \text{ W}}$$

13. a.
$$I = \frac{S_T}{E} = \frac{5000 \text{ VA}}{120 \text{ V}} = 41.67 \text{ A}$$

$$F_p = 0.8 \Rightarrow 36.87^\circ \text{ (lagging)}$$

$$\mathbf{E} = 120 \text{ V} \angle 0^\circ, \mathbf{I} = 41.67 \text{ A} \angle -36.87^\circ$$

$$\mathbf{Z} = \frac{\mathbf{E}}{\mathbf{I}} = \frac{120 \text{ V} \angle 0^\circ}{41.67 \text{ A} \angle -36.87^\circ} = 2.88 \Omega \angle 36.87^\circ = \mathbf{2.30 \Omega + j1.73 \Omega} = R + jX_L$$

b.
$$P = S \cos \theta = (5000 \text{ VA})(0.8) = \mathbf{4000 \text{ W}}$$

14. a.
$$P_T = 0 + 300 \text{ W} = \mathbf{300 \text{ W}}$$

$$Q_T = 600 \text{ VAR}(C) + 200(L) = \mathbf{400 \text{ VAR}(C)}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{500 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{300 \text{ W}}{500 \text{ VA}} = \mathbf{0.6 \text{ (leading)}}$$

b.
$$I_s = \frac{S_T}{E} = \frac{500 \text{ VA}}{30 \text{ V}} = 16.67 \text{ A}$$

$$F_p = 0.6 \Rightarrow 53.13^\circ$$

$$\mathbf{I_s} = \mathbf{16.67 \text{ A} \angle 53.13^\circ}$$

c. —

d. Load: 600 VAR(C), 0 W

$$R = 0, L = 0, Q_C = I^2 X_C \Rightarrow X_C = \frac{Q_C}{I^2} = \frac{600 \text{ VAR}}{(16.67 \text{ A})^2} = \mathbf{2.159 \Omega}$$

Load: 200 VAR(L), 300 W

$$C = 0, R = P/I^2 = 300 \text{ W}/(16.67 \text{ A})^2 = \mathbf{1.079 \Omega}$$

$$X_L = \frac{Q_L}{I^2} = \frac{200 \text{ VAR}}{(16.67 \text{ A})^2} = \mathbf{0.7197 \Omega}$$

$$\mathbf{Z_T} = -j2.159 \Omega + 1.0796 \Omega + j0.7197 \Omega$$


$$= \mathbf{1.08 \Omega - j1.44 \Omega}$$

15. a. $P_T = 0 + 300 \text{ W} + 600 \text{ W} = \mathbf{900 \text{ W}}$
 $Q_T = 500 \text{ VAR}(C) + 0 + 500 \text{ VAR}(L) = \mathbf{0 \text{ VAR}}$
 $S_T = P_T = \mathbf{900 \text{ VA}}$
 $F_p = \frac{P_T}{S_T} = \mathbf{1}$

b. $I_s = \frac{S_T}{E} = \frac{900 \text{ VA}}{100 \text{ V}} = 9 \text{ A}, \mathbf{I_s = 9 \text{ A} \angle 0^\circ}$

c. -

d.

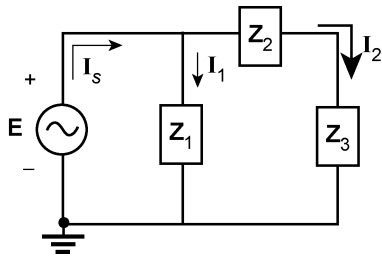

$Z_1: Q_C = \frac{V^2}{X_C} \Rightarrow X_C = \frac{V^2}{Q_C} = \frac{10^4}{500} = \mathbf{20 \Omega}$

$I_1 = \frac{\mathbf{E}}{Z_1} = \frac{100 \text{ V} \angle 0^\circ}{20 \Omega \angle -90^\circ} = 5 \text{ A} \angle 90^\circ$

$I_2 = I_s - I_1 = 9 \text{ A} - j5 \text{ A} = 10.296 \text{ A} \angle -29.05^\circ$

$Z_2: R = \frac{P}{I^2} = \frac{300 \text{ W}}{(10.296 \text{ A})^2} = \frac{300}{106} = \mathbf{2.83 \Omega}$

$X_{L,C} = \mathbf{0 \Omega}$


$Z_3: R = \frac{P}{I_2^2} = \frac{600 \text{ W}}{(10.296 \text{ A})^2} = \mathbf{5.66 \Omega}$

$X_L = \frac{Q}{I_2^2} = \frac{500}{(10.296 \text{ A})^2} = \mathbf{4.72 \Omega}, X_C = \mathbf{0 \Omega}$

16. a. $P_T = 200 \text{ W} + 30 \text{ W} + 0 = \mathbf{230 \text{ W}}$
 $Q_T = 0 + 40 \text{ VAR}(L) + 100 \text{ VAR}(L) = \mathbf{140 \text{ VAR}(L)}$
 $S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{269.26 \text{ VA}}$
 $F_p = \frac{P_T}{S_T} = \frac{230 \text{ W}}{269.26 \text{ VA}} = \mathbf{0.854 \text{ (lagging)}} \Rightarrow 31.35^\circ$

b. $I_s = \frac{S_T}{E} = \frac{269.26 \text{ VA}}{100 \text{ V}} = 2.6926 \text{ A}$
 $\mathbf{I_s = 2.69 \text{ A} \angle -31.35^\circ}$

c.

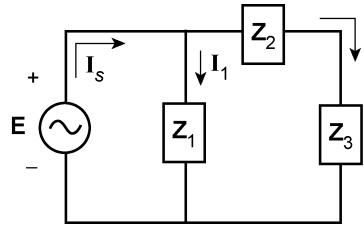

$$Z_1: R = \frac{V^2}{P} = \frac{10^4}{200} = 50 \Omega$$

$$X_L, X_C = 0 \Omega$$

$$I_1 = \frac{100 \text{ V} \angle 0^\circ}{50 \Omega \angle 0^\circ} = 2 \text{ A} \angle 0^\circ$$

$$I_2 = I_s - I_1$$

$$= 2.6926 \text{ A} \angle -31.35^\circ - 2 \text{ A} \angle 0^\circ$$

$$= 2.299 \text{ A} - j1.40 \text{ A} - 2.0 \text{ A}$$

$$= 0.299 \text{ A} - j1.40 \text{ A}$$


$$= 1.432 \text{ A} \angle -77.94^\circ$$

$$Z_2: R = \frac{P}{I_2^2} = \frac{30 \text{ W}}{(1.432 \text{ A})^2} = 14.63 \Omega, X_L = \frac{Q}{I_2^2} = \frac{40 \text{ VAR}}{(1.432 \text{ A})^2} = 19.50 \Omega$$

$$X_C = 0 \Omega$$

$$Z_3: X_L = \frac{Q}{I_2^2} = \frac{100 \text{ VAR}}{(1.432 \text{ A})^2} = 48.76 \Omega, R = 0 \Omega, X_C = 0 \Omega$$

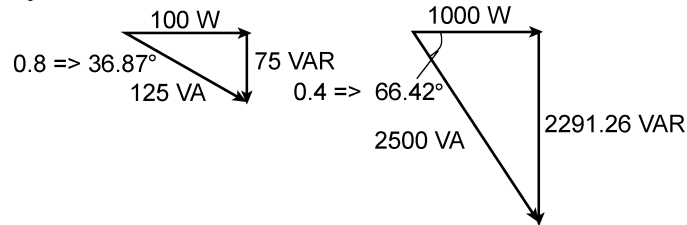17. a. $P_T = 100 \text{ W} + 1000 \text{ W} = 1100 \text{ W}$



$$Q_T = 75 \text{ VAR}(C) + 2291.26 \text{ VAR}(C) = 2366.26 \text{ VAR}(C)$$


$$S_T = \sqrt{P_T^2 + Q_T^2} = 2609.44 \text{ VA}$$

$$F_p = \frac{P_T}{S_T} = \frac{1100 \text{ W}}{2609.44 \text{ VA}} = 0.422 \text{ (leading)} \Rightarrow 65.04^\circ$$

b. $S_T = EI \Rightarrow E = \frac{S_T}{I} = \frac{2609.44 \text{ VA}}{5 \text{ A}} = 521.89 \text{ V}$

$$E = 521.89 \text{ V} \angle -65.07^\circ$$

c.

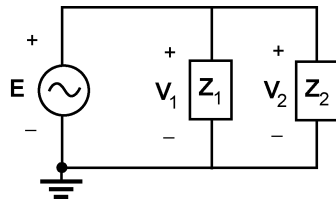

$$I_{Z_1} = \frac{S}{V_1} = \frac{S}{E} = \frac{125 \text{ VA}}{521.89 \text{ V}} = 0.2395 \text{ A}$$

$$I_{Z_2} = \frac{S}{V_2} = \frac{S}{E} = \frac{2500 \text{ VA}}{521.89 \text{ V}} = 4.79 \text{ A}$$


$$\mathbf{Z}_1: R = \frac{P}{I_{Z_1}^2} = \frac{100 \text{ W}}{(0.2395)^2} = \mathbf{1743.38 \Omega}$$

$$Q = I_{Z_1}^2 X_C \Rightarrow X_C = \frac{Q}{I_{Z_1}^2} = \frac{75 \text{ VAR}}{(0.2395 \text{ A})^2} = \mathbf{1307.53 \Omega}$$

$$\mathbf{Z}_2: R = \frac{P}{I_{Z_2}^2} = \frac{1000 \text{ W}}{(4.790 \text{ A})^2} = \mathbf{43.59 \Omega}$$

$$X_C = \frac{Q}{I_{Z_2}^2} = \frac{2291.26 \text{ VAR}}{(4.790 \text{ A})^2} = \mathbf{99.88 \Omega}$$

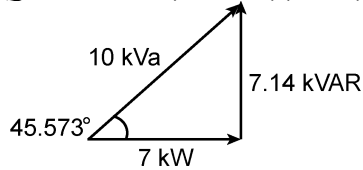18. a. $0.7 \Rightarrow 45.573^\circ$
 $P = S \cos \theta = (10 \text{ kVA})(0.7) = 7 \text{ kW}$
 $Q = S \sin \theta = (10 \text{ kVA})(0.714) = 7.14 \text{ kVAR}(L)$



- b. $Q_C = 7.14 \text{ kVAR} = \frac{V^2}{X_C}$
 $X_C = \frac{V^2}{Q_C} = \frac{(208 \text{ V})^2}{7.14 \text{ kVAR}} = 6.059 \Omega$
 $X_C = \frac{1}{2\pi fC} \Rightarrow C = \frac{1}{2\pi fX_C} = \frac{1}{(2\pi)(60 \text{ Hz})(6.059 \Omega)} = \mathbf{438 \mu\text{F}}$


- c. Uncompensated:

$$I_s = \frac{S_T}{E} = \frac{10,000 \text{ VA}}{208 \text{ V}} = \mathbf{48.08 \text{ A}}$$

- Compensated:

$$I_s = \frac{S_T}{E} = \frac{P_T}{E} = \frac{7,000 \text{ W}}{208 \text{ V}} = \mathbf{33.65 \text{ A}}$$

- d.

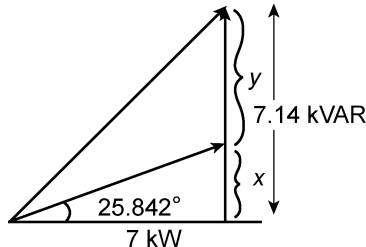

$$\begin{aligned} \cos \theta &= 0.9 \\ \theta &= \cos^{-1} 0.9 = 25.842^\circ \\ \tan \theta &= \frac{x}{7 \text{ kW}} \\ x &= (7 \text{ kW})(\tan 25.842^\circ) \\ &= (7 \text{ kW})(0.484) \\ &= 3.39 \text{ kVAR} \\ y &= (7.14 - 3.39) \text{ kVAR} \\ &= 3.75 \text{ kVAR} \end{aligned}$$

$$Q_C = 3.75 \text{ kVAR} = \frac{V^2}{X_C}$$

$$X_C = \frac{V^2}{Q_C} = \frac{(208 \text{ V})^2}{3.75 \text{ kVAR}} = 11.537 \Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(11.537 \Omega)} = \mathbf{230 \mu F}$$

Uncompensated:

$$I_s = \mathbf{48.08 \text{ A}}$$

Compensated:

$$S_T = \sqrt{(7 \text{ kW})^2 + (3.39 \text{ kVAR})^2} = 7.778 \text{ kVA}$$

$$I_s = \frac{S_T}{E} = \frac{7.778 \text{ kVA}}{208 \text{ V}} = \mathbf{37.39 \text{ A}}$$

$$\Delta I_s = 48.08 \text{ A} - 37.39 \text{ A} = \mathbf{10.69 \text{ A}}$$

19. a. $P_T = 5 \text{ kW}$, $Q_T = 6 \text{ kVAR}(L)$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{7.81 \text{ kVA}}$$

b. $F_p = \frac{P_T}{S_T} = \frac{5 \text{ kW}}{7.81 \text{ kVA}} = \mathbf{0.640 \text{ (lagging)}}$

c. $I_s = \frac{S_T}{E} = \frac{7,810 \text{ VA}}{120 \text{ V}} = \mathbf{65.08 \text{ A}}$


d. $X_C = \frac{1}{2\pi f C}$, $Q_C = I^2 X_C = \frac{E^2}{X_C} = \frac{(120 \text{ V})^2}{X_C}$
 and $X_C = \frac{(120 \text{ V})^2}{Q_C} = \frac{14,400}{6000} = 2.4 \Omega$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(2.4 \Omega)} = \mathbf{1105 \mu F}$$

e. $S_T = EI_s = P_T$

$$\therefore I_s = \frac{P_T}{E} = \frac{5000 \text{ W}}{120 \text{ V}} = \mathbf{41.67 \text{ A}}$$

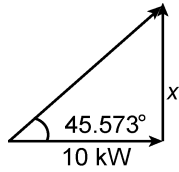20. a. Load 1: $P = 20,000 \text{ W}$, $Q = 0 \text{ VAR}$
 Load 2: $\theta = \cos^{-1}0.7 = 45.573^\circ$




$$\tan \theta = \frac{x}{10 \text{ kW}}$$

$$x = (10 \text{ kW})\tan 45.573^\circ$$

$$= (10 \text{ kW})(1.02)$$

$$= \mathbf{10,202 \text{ VAR(L)}}$$

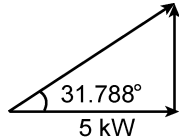- Load 3: $\theta = \cos^{-1}0.85 = 31.788^\circ$



$$\tan \theta = \frac{x}{5 \text{ kW}}$$

$$x = (5 \text{ kW})\tan 31.788^\circ$$


$$= (5 \text{ kW})(0.62)$$

$$= 3098.7 \text{ VAR(L)}$$

$$P_T = 20,000 \text{ W} + 10,000 \text{ W} + 5,000 \text{ W} = \mathbf{35 \text{ kW}}$$

$$Q_T = 0 + 10,202 \text{ VAR} + 3098.7 \text{ VAR} = \mathbf{13,300.7 \text{ VAR(L)}}$$
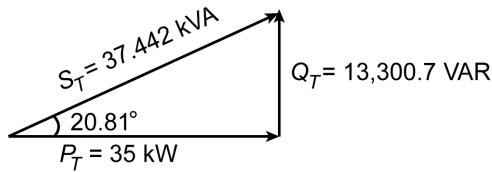
$$S_T = \sqrt{P_T^2 + Q_T^2} = \mathbf{37.442 \text{ kVA}}$$



- b. $Q_C = Q_L = 13,300.7 \text{ VAR}$

$$X_C = \frac{E^2}{Q_C} = \frac{(10^3 \text{ V})^2}{13,300.7 \text{ VAR}} = 75.184 \Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(75.184 \Omega)} = \mathbf{35.28 \mu\text{F}}$$

- c. Uncompensated:

$$I_s = \frac{S_T}{E} = \frac{37.442 \text{ kVA}}{1 \text{ kV}} = \mathbf{37.44 \text{ A}}$$

Compensated:

$$S_T = P_T = 35 \text{ kW}$$

$$I_s = \frac{S_T}{E} = \frac{35 \text{ kW}}{1 \text{ kV}} = \mathbf{35 \text{ A}}$$

$$\Delta I_s = 37.44 \text{ A} - 35 \text{ A} = \mathbf{2.44 \text{ A}}$$

21. a. $\mathbf{Z}_T = R_1 + R_2 + R_3 + jX_L - jX_C$
 $= 2 \Omega + 3 \Omega + 1 \Omega + j3 \Omega - j12 \Omega = 6 \Omega - j9 \Omega = 10.82 \Omega \angle -56.31^\circ$

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{50 \text{ V} \angle 0^\circ}{10.82 \Omega \angle -56.31^\circ} = 4.62 \text{ A} \angle 56.31^\circ$$

$$P = VI \cos \theta = (50 \text{ V})(4.62 \text{ A}) \cos 56.31^\circ = \mathbf{128.14 \text{ W}}$$

- b. a-b: $P = I^2 R = (4.62 \text{ A})^2 2 \Omega = \mathbf{42.69 \text{ W}}$
 b-c: $P = I^2 R = (4.62 \text{ A})^2 3 \Omega = \mathbf{64.03 \text{ W}}$
 a-c: $42.69 \text{ W} + 64.03 \text{ W} = \mathbf{106.72 \text{ W}}$
 a-d: $\mathbf{106.72 \text{ W}}$
 c-d: $\mathbf{0 \text{ W}}$
 d-e: $\mathbf{0 \text{ W}}$
 f-e: $P = I^2 R = (4.62 \text{ A})^2 1 \Omega = \mathbf{21.34 \text{ W}}$
22. a. $S_T = 660 \text{ VA} = EI_s$
 $I_s = \frac{660 \text{ VA}}{120 \text{ V}} = 5.5 \text{ A}$
 $\theta = \cos^{-1} 0.6 = 53.13^\circ$
 $\therefore \mathbf{E = 120 \text{ V} \angle 0^\circ, \mathbf{I_s = 5.5 \text{ A} \angle -53.13^\circ}$
 $P = EI \cos \theta = (120 \text{ V})(5.5 \text{ A})(0.6) = \mathbf{396 \text{ W}}$
 Wattmeter = $\mathbf{396 \text{ W}}$, Ammeter = $\mathbf{5.5 \text{ A}}$, Voltmeter = $\mathbf{120 \text{ V}}$
- b. $\mathbf{Z_T = \frac{E}{I} = \frac{120 \text{ V} \angle 0^\circ}{5.5 \text{ A} \angle -53.13^\circ} = \mathbf{21.82 \Omega \angle 53.13^\circ} = \mathbf{13.09 \Omega + j17.46 \Omega} = R + jX_L$
23. a. $R = \frac{P}{I^2} = \frac{80 \text{ W}}{(4 \text{ A})^2} = \mathbf{5 \Omega}, \mathbf{Z_T = \frac{E}{I} = \frac{200 \text{ V}}{4 \text{ A}} = 50 \Omega}$
 $X_L = \sqrt{Z_T^2 - R^2} = \sqrt{(50 \Omega)^2 - (5 \Omega)^2} = 49.75 \Omega$
 $L = \frac{X_L}{2\pi f} = \frac{49.75 \Omega}{(2\pi)(60 \text{ Hz})} = \mathbf{132.03 \text{ mH}}$
- b. $R = \frac{P}{I^2} = \frac{90 \text{ W}}{(3 \text{ A})^2} = \mathbf{10 \Omega}$
- c. $R = \frac{P}{I^2} = \frac{60 \text{ W}}{(2 \text{ A})^2} = \mathbf{15 \Omega}, \mathbf{Z_T = \frac{E}{I} = \frac{200 \text{ V}}{2 \text{ A}} = 100 \Omega}$
 $X_L = \sqrt{Z_T^2 - R^2} = \sqrt{(100 \Omega)^2 - (15 \Omega)^2} = 98.87 \Omega$
 $L = \frac{X_L}{2\pi f} = \frac{98.87 \Omega}{376.8} = \mathbf{262.39 \text{ mH}}$
24. a. $X_L = 2\pi f L = (6.28)(50 \text{ Hz})(0.08 \text{ H}) = 25.12 \Omega$
 $Z_T = \sqrt{R^2 + X_L^2} = \sqrt{(4 \Omega)^2 + (25.12 \Omega)^2} = 25.44 \Omega$
 $I = \frac{E}{Z_T} = \frac{60 \text{ V}}{25.44 \Omega} = 2.358 \text{ A}$
 $P = I^2 R = (2.358 \text{ A})^2 4 \Omega = \mathbf{22.24 \text{ W}}$
- b. $I = \sqrt{\frac{P}{R}} = \sqrt{\frac{30 \text{ W}}{7 \Omega}} = \mathbf{2.07 \text{ A}}$
 $Z_T = \frac{E}{I} = \frac{60 \text{ V}}{2.07 \text{ A}} = 28.99 \Omega$

$$X_L = \sqrt{(28.99 \Omega)^2 - (7 \Omega)^2} = 28.13 \Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{28.13 \Omega}{(2\pi)(50 \text{ Hz})} = \mathbf{89.54 \text{ mH}}$$

c. $P = I^2 R = (1.7 \text{ A})^2 10 \Omega = \mathbf{28.9 \text{ W}}$

$$Z_T = \frac{E}{I} = \frac{60 \text{ V}}{1.7 \text{ A}} = 35.29 \Omega$$

$$X_L = \sqrt{(35.29 \Omega)^2 - (10 \Omega)^2} = 33.84 \Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{33.84 \Omega}{314} = \mathbf{107.77 \text{ mH}}$$