

# Chapter 21

1. a.  $\omega_s = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1\text{ H}(16\ \mu\text{F})}} = \mathbf{250\text{ rad/s}}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{250\text{ rad/s}}{2\pi} = \mathbf{39.79\text{ Hz}}$$

b.  $\omega_s = \frac{1}{\sqrt{(0.51\text{ H})(0.16\ \mu\text{F})}} = \mathbf{3496.50\text{ rad/s}}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{3496.50\text{ rad/s}}{2\pi} = \mathbf{556.49\text{ Hz}}$$

c.  $\omega_s = \frac{1}{\sqrt{(0.27\text{ mH})(7.5\ \mu\text{F})}} = \mathbf{22,173\text{ rad/s}}$

$$f_s = \frac{\omega_s}{2\pi} = \frac{22,173\text{ rad/s}}{2\pi} = \mathbf{3528.93\text{ Hz}}$$

2. a.  $X_C = \mathbf{30\ \Omega}$       b.  $Z_{T_s} = \mathbf{2\ \Omega}$       c.  $I = \frac{E}{Z_{T_s}} = \frac{50\text{ mV}}{2\ \Omega} = \mathbf{25\text{ mA}}$

d.  $V_R = IR = (25\text{ mA})(10\ \Omega) = \mathbf{250\text{ mV}} = E$   
 $V_L = IX_L = (25\text{ mA})(30\ \Omega) = \mathbf{750\text{ mV}}$   
 $V_C = IX_C = (25\text{ mA})(30\ \Omega) = \mathbf{750\text{ mV}}$   
 $V_L = V_C$

e.  $Q_s = \frac{X_L}{R} = \frac{30\ \Omega}{2\ \Omega} = \mathbf{15}$  (medium  $Q$ )      f.  $P = I^2R = (25\text{ mA})^2 2\ \Omega = \mathbf{1.25\text{ mW}}$

3. a.  $X_L = \mathbf{2\text{ k}\Omega}$

b.  $I = \frac{E}{Z_{T_s}} = \frac{12\text{ V}}{100\ \Omega} = \mathbf{120\text{ mA}}$

c.  $V_R = IR = (120\text{ mA})(100\ \Omega) = \mathbf{12\text{ V}} = E$   
 $V_L = IX_L = (120\text{ mA})(2\text{ k}\Omega) = \mathbf{240\text{ V}}$   
 $V_C = IX_C = (120\text{ mA})(2\text{ k}\Omega) = \mathbf{240\text{ V}}$   
 $V_L = V_C = 20 V_R$

d.  $Q_s = \frac{X_L}{R} = \frac{20000\ \Omega}{100\ \Omega} = \mathbf{20}$  (high  $Q$ )

e.  $X_L = 2\pi fL, L = \frac{X_L}{2\pi f} = \frac{2\text{ k}\Omega}{2\pi(5\text{ kHz})} = \mathbf{63.7\text{ mH}}$

$$X_C = \frac{1}{2\pi f C}, C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(5\text{ kHz})(2\text{ k}\Omega)} = \mathbf{15,920\text{ pF}}$$

$$f. \quad BW = \frac{f_s}{Q_s} = \frac{5 \text{ kHz}}{20} = \mathbf{250 \text{ Hz}}$$

$$g. \quad f_2 = f_s + \frac{BW}{2} = 5 \text{ kHz} + \frac{0.25 \text{ kHz}}{2} = \mathbf{5.13 \text{ kHz}}$$

$$f_1 = f_s - \frac{BW}{2} = 5 \text{ kHz} - \frac{0.25 \text{ kHz}}{2} = \mathbf{4.88 \text{ kHz}}$$

$$4. \quad a. \quad f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_s)^2 C} = \frac{1}{(2\pi \cdot 1.8 \text{ kHz})^2 \cdot 2 \mu\text{F}} = \mathbf{3.91 \text{ mH}}$$

$$b. \quad X_L = 2\pi fL = 2\pi(1.8 \text{ kHz})(3.91 \text{ mH}) = \mathbf{44.2 \Omega}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(1.8 \text{ kHz})(2 \mu\text{F})} = \mathbf{44.2 \Omega}$$

$$X_L = X_C$$

$$c. \quad E_{\text{rms}} = (0.707)(20 \text{ mV}) = 14.14 \text{ mV}$$

$$I_{\text{rms}} = \frac{E_{\text{rms}}}{R} = \frac{14.14 \text{ mV}}{4.7 \Omega} = \mathbf{3.01 \text{ mA}}$$

$$d. \quad P = I^2 R = (3.01 \text{ mA})^2 \cdot 4.7 \Omega = \mathbf{42.58 \mu\text{W}}$$

$$e. \quad S_T = P_T = \mathbf{42.58 \mu\text{VA}}$$

$$f. \quad F_p = \mathbf{1}$$

$$g. \quad Q_s = \frac{X_L}{R} = \frac{44.2 \Omega}{4.7 \Omega} = \mathbf{9.4}$$

$$BW = \frac{f_s}{Q_s} = \frac{1.8 \text{ kHz}}{9.4} = \mathbf{191.49 \text{ Hz}}$$

$$h. \quad f_2 = \frac{1}{2\pi} \left[ \frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

$$= \frac{1}{2\pi} \left[ \frac{4.7 \Omega}{2(3.91 \text{ mH})} + \frac{1}{2} \sqrt{\left(\frac{4.7 \Omega}{3.91 \text{ mH}}\right)^2 + \frac{4}{(3.91 \text{ mH})(2 \mu\text{F})}} \right]$$

$$= \frac{1}{2\pi} [601.02 + 11.324 \times 10^3]$$

$$= \mathbf{1897.93 \text{ Hz}}$$

$$f_1 = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

$$= \frac{1}{2\pi} [-601.02 + 11.324 \times 10^3]$$

$$= \mathbf{1.71 \text{ kHz}}$$

$$P_{\text{HPF}} = \frac{1}{2} P_{\text{max}} = \frac{1}{2} (42.58 \mu\text{W}) = \mathbf{21.29 \mu\text{W}}$$

5. a.  $BW = f_s/Q_s = 6000 \text{ Hz}/15 = \mathbf{400 \text{ Hz}}$
- b.  $f_2 = f_s + \frac{BW}{2} = 6000 \text{ Hz} + 200 \text{ Hz} = \mathbf{6200 \text{ Hz}}$   
 $f_1 = f_s - \frac{BW}{2} = 6000 \text{ Hz} - 200 \text{ Hz} = \mathbf{5800 \text{ Hz}}$
- c.  $Q_s = \frac{X_L}{R} \Rightarrow X_L = Q_s R = (15)(3 \Omega) = \mathbf{45 \Omega} = X_C$
- d.  $P_{\text{HPF}} = \frac{1}{2} P_{\text{max}} = \frac{1}{2} (I^2 R) = \frac{1}{2} (0.5 \text{ A})^2 3 \Omega = \mathbf{375 \text{ mW}}$
6. a.  $L = \frac{X_L}{2\pi f} = \frac{200 \Omega}{2\pi(10^4 \text{ Hz})} = 3.185 \text{ mH}$   
 $BW = \frac{R}{2\pi L} = \frac{5 \Omega}{2\pi(3.185 \text{ mH})} \cong \mathbf{250 \text{ Hz}}$   
 or  $Q_s = \frac{X_L}{R} = \frac{X_C}{R} = \frac{200 \Omega}{5 \Omega} = 40, BW = \frac{f_s}{Q_s} = \frac{10,000 \text{ Hz}}{40} = \mathbf{250 \text{ Hz}}$
- b.  $f_2 = f_s + BW/2 = 10,000 \text{ Hz} + 250 \text{ Hz}/2 = \mathbf{10,125 \text{ Hz}}$   
 $f_1 = f_s - BW/2 = 10,000 \text{ Hz} - 125 \text{ Hz} = \mathbf{9,875 \text{ Hz}}$
- c.  $Q_s = \frac{X_L}{R} = \frac{200 \Omega}{5 \Omega} = \mathbf{40}$
- d.  $\mathbf{I} = \frac{E \angle 0^\circ}{R \angle 0^\circ} = \frac{30 \text{ V} \angle 0^\circ}{5 \Omega \angle 0^\circ} = 6 \text{ A} \angle 0^\circ, \mathbf{V}_L = (I \angle 0^\circ)(X_L \angle 90^\circ)$   
 $= (6 \text{ A} \angle 0^\circ)(200 \Omega \angle 90^\circ)$   
 $= \mathbf{1200 \text{ V} \angle 90^\circ}$   
 $\mathbf{V}_C = (I \angle 0^\circ)(X_C \angle -90^\circ) = \mathbf{1200 \text{ V} \angle -90^\circ}$
- e.  $P = I^2 R = (6 \text{ A})^2 5 \Omega = \mathbf{180 \text{ W}}$
7. a.  $BW = \frac{f_s}{Q_s} \Rightarrow Q_s = f_s/BW = 2000 \text{ Hz}/200 \text{ Hz} = \mathbf{10}$
- b.  $Q_s = \frac{X_L}{R} \Rightarrow X_L = Q_s R = (10)(2 \Omega) = \mathbf{20 \Omega}$
- c.  $L = \frac{X_L}{2\pi f} = \frac{20 \Omega}{(6.28)(2 \text{ kHz})} = \mathbf{1.59 \text{ mH}}$   
 $C = \frac{1}{2\pi f X_C} = \frac{1}{(6.28)(2 \text{ kHz})(20 \Omega)} = \mathbf{3.98 \mu\text{F}}$

- d.  $f_2 = f_s + BW/2 = 2000 \text{ Hz} + 100 \text{ Hz} = \mathbf{2100 \text{ Hz}}$   
 $f_1 = f_s - BW/2 = 2000 \text{ Hz} - 100 \text{ Hz} = \mathbf{1900 \text{ Hz}}$
8. a.  $BW = 6000 \text{ Hz} - 5400 \text{ Hz} = \mathbf{600 \text{ Hz}}$
- b.  $BW = f_s/Q_s \Rightarrow f_s = Q_s BW = (9.5)(600 \text{ Hz}) = \mathbf{5700 \text{ Hz}}$
- c.  $Q_s = \frac{X_L}{R} \Rightarrow X_L = X_C = Q_s R = (9.5)(2 \Omega) = \mathbf{19 \Omega}$
- d.  $L = \frac{X_L}{2\pi f} = \frac{19 \Omega}{2\pi(5700 \text{ Hz})} = \mathbf{0.53 \text{ mH}}$   
 $C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(5.7 \text{ kHz})(19 \Omega)} = \mathbf{1.47 \mu\text{F}}$
9.  $I_M = \frac{E}{R} \Rightarrow R = \frac{E}{I_M} = \frac{5 \text{ V}}{500 \text{ mA}} = \mathbf{10 \Omega}$   
 $BW = f_s/Q_s \Rightarrow Q_s = f_s/BW = 8400 \text{ Hz}/120 \text{ Hz} = 70$   
 $Q_s = \frac{X_L}{R} \Rightarrow X_L = Q_s R = (70)(10 \Omega) = \mathbf{700 \Omega}$   
 $X_C = X_L = \mathbf{700 \Omega}$   
 $L = \frac{X_L}{2\pi f} = \frac{700 \Omega}{(2\pi)(8.4 \text{ kHz})} = \mathbf{13.26 \text{ mH}}$   
 $C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(8.4 \text{ kHz})(0.7 \text{ k}\Omega)} = \mathbf{27.07 \text{ nF}}$   
 $f_2 = f_s + BW/2 = 8400 \text{ Hz} + 120 \text{ Hz}/2 = \mathbf{8.46 \text{ kHz}}$   
 $f_1 = f_s - BW/2 = 8400 \text{ Hz} - 60 \text{ Hz} = \mathbf{8.34 \text{ kHz}}$
10.  $Q_s = \frac{X_L}{R} \Rightarrow X_L = Q_s R = 20(2 \Omega) = \mathbf{40 \Omega} = X_C$   
 $BW = \frac{f_s}{Q_s} \Rightarrow f_s = Q_s BW = (20)(400 \text{ Hz}) = \mathbf{8 \text{ kHz}}$   
 $L = \frac{X_L}{2\pi f} = \frac{40 \Omega}{2\pi(8 \text{ kHz})} = \mathbf{795.77 \text{ mH}}$   
 $C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(8 \text{ kHz})(40 \Omega)} = \mathbf{497.36 \text{ nF}}$   
 $f_2 = f_s + BW/2 = 8000 \text{ Hz} + 400 \text{ Hz}/2 = \mathbf{8200 \text{ Hz}}$   
 $f_1 = f_s - BW/2 = 8000 \text{ Hz} - 200 \text{ Hz} = \mathbf{7800 \text{ Hz}}$

11. a.  $f_s = \frac{\omega_s}{2\pi} = \frac{2\pi \times 10^6 \text{ rad/s}}{2\pi} = \mathbf{1 \text{ MHz}}$

b.  $\frac{f_2 - f_1}{f_s} = 0.16 \Rightarrow BW = f_2 - f_1 = 0.16 f_s = 0.16(1 \text{ MHz}) = \mathbf{160 \text{ kHz}}$

c.  $P = \frac{V_R^2}{R} \Rightarrow R = \frac{V_R^2}{P} = \frac{(120 \text{ V})^2}{20 \text{ W}} = \mathbf{720 \Omega}$

$BW = \frac{R}{2\pi L} \Rightarrow L = \frac{R}{2\pi BW} = \frac{720 \Omega}{(6.28)(160 \text{ kHz})} = \mathbf{0.716 \text{ mH}}$

$f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{4\pi^2 f_s^2 L} = \frac{1}{4\pi^2 (10^6 \text{ Hz})^2 (0.716 \text{ mH})} = \mathbf{35.38 \text{ pF}}$

d.  $Q_\ell = \frac{X_L}{R_\ell} = 80 \Rightarrow R_\ell = \frac{X_L}{80} = \frac{2\pi f_s L}{80} = \frac{2\pi(10^6 \text{ Hz})(0.716 \text{ mH})}{80} = \mathbf{56.23 \Omega}$

12. a.  $Q_\ell = \frac{X_L}{R_\ell}$

$R_\ell = \frac{X_L}{Q_\ell} = \frac{2\pi f L}{Q_\ell} = \frac{2\pi(1 \text{ MHz})(100 \mu\text{H})}{12.5} = 50.27 \Omega$

$\frac{f_2 - f_1}{f_s} = \frac{1}{Q_s} = 0.2$

$Q_s = \frac{1}{0.2} = 5 = \frac{X_L}{R} = \frac{2\pi f L}{R} = \frac{2\pi(1 \text{ MHz})(100 \mu\text{H})}{R} = \frac{628.32 \Omega}{R}$

$R = \frac{628.32 \Omega}{5} = 125.66 \Omega$

$R = R_d + R_\ell$


$125.66 \Omega = R_d + 50.27 \Omega$

and  $R_d = 125.66 \Omega - 50.27 \Omega = \mathbf{75.39 \Omega}$

c.  $X_C = \frac{1}{2\pi f C} = X_L$

$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(1 \text{ MHz})(628.32 \Omega)} = \mathbf{253.3 \text{ pF}}$

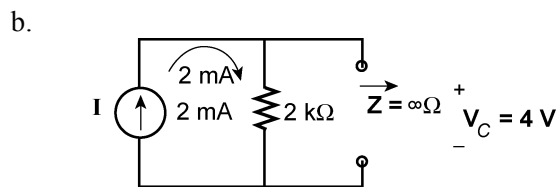13. a.  $f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{2}{2\pi\sqrt{(0.1 \text{ mH})(10 \text{ nF})}} = \mathbf{159.16 \text{ kHz}}$



$$c. \quad I_L = \frac{V_L}{X_L} = \frac{4 \text{ V}}{2\pi f_p L} = \frac{4 \text{ V}}{100 \Omega} = \mathbf{40 \text{ mA}}$$

$$I_C = \frac{V_L}{X_C} = \frac{4 \text{ V}}{1/2\pi f_p C} = \frac{4 \text{ V}}{100 \Omega} = \mathbf{40 \text{ mA}}$$

$$d. \quad Q_p = \frac{R_s}{X_{L_p}} = \frac{2 \text{ k}\Omega}{2\pi f_p L} = \frac{2 \text{ k}\Omega}{100 \Omega} = \mathbf{20}$$

$$14. \quad a. \quad f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(4.7 \text{ mH})(30 \text{ nF})}} = \mathbf{13.4 \text{ kHz}}$$

$$b. \quad Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi f L}{R_\ell} = \frac{2\pi(13.4 \text{ kHz})(4.7 \text{ mH})}{8 \Omega} = \mathbf{49.46} \geq 10 \text{ (yes)}$$

$$c. \quad \text{Since } Q_\ell \geq 10, f_p \cong f_s = \mathbf{13.4 \text{ kHz}}$$

$$d. \quad X_L = 2\pi f_p L = 2\pi(13.4 \text{ kHz})(4.7 \text{ mH}) = \mathbf{395.72 \Omega}$$

$$X_C = \frac{1}{2\pi f_p C} = \frac{1}{2\pi(13.4 \text{ kHz})(30 \text{ nF})} = \mathbf{395.91 \Omega}$$

$$X_L = X_C$$

$$e. \quad Z_{T_p} = Q_\ell^2 R_\ell = (49.46)^2 8 \Omega = \mathbf{19.57 \text{ k}\Omega}$$

$$f. \quad V_C = I Z_{T_p} = (10 \text{ mA})(19.57 \text{ k}\Omega) = \mathbf{195.7 \text{ V}}$$

$$g. \quad Q_\ell \geq 10, Q_p = Q_\ell = \mathbf{49.46}$$


$$BW = \frac{f_p}{Q_p} = \frac{13.4 \text{ kHz}}{49.46} = \mathbf{270.9 \text{ Hz}}$$

$$h. \quad I_L = I_C = Q_\ell I_T = (49.46)(10 \text{ mA}) = \mathbf{494.6 \text{ mA}}$$


15. a.  $f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(200\ \mu\text{H})(120\ \mu\text{F})}} = \mathbf{1.027\ \text{MHz}}$

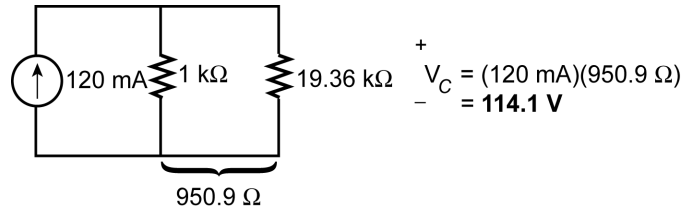b.  $Q_\ell = \frac{X_L}{R_\ell} \Rightarrow R_\ell = \frac{X_L}{Q_\ell} = \frac{2\pi(1.027\ \text{MHz})(200\ \mu\text{H})}{15} = 86.04\ \Omega$

$Z_p = Q_\ell^2 R_\ell = (15)^2 86.04\ \Omega = 19.36\ \text{k}\Omega$



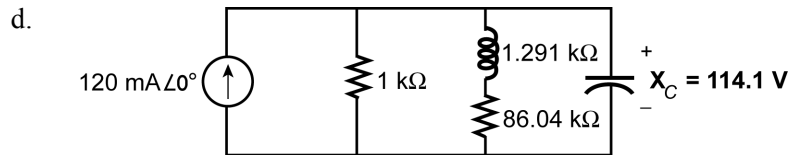c.  $P = I^2 R = (120\ \text{mA})^2 (950.9\ \Omega) = \mathbf{13.69\ \text{W}}$



$X_L = 2\pi fL = 2\pi(1.027\ \text{MHz})(200\ \mu\text{H}) = 1.291\ \text{k}\Omega$

$|V_{R_\ell}| = \frac{(86.04\ \Omega \angle 0^\circ)(114.1\ \text{V})}{86.04\ \Omega + j1.291\ \text{k}\Omega} = 7.587\ \text{V}$

$P = V_{R_\ell}^2 / R_\ell = (7.587\ \text{V})^2 / 86.04\ \Omega = \mathbf{669\ \text{mW}}$

$13.69\ \text{W} : 669\ \text{mW} \cong 20:1$

16. a.  $Q_\ell = \frac{X_L}{R_L} = \frac{100\ \Omega}{20\ \Omega} = 5 \leq 10$

$\therefore \frac{X_L}{R_\ell^2 + X_L^2} = \frac{1}{X_C} \Rightarrow X_C = \frac{R_\ell^2 + X_L^2}{X_L} = \frac{(20\ \Omega)^2 + (100\ \Omega)^2}{100\ \Omega} = \mathbf{104\ \Omega}$

b.  $Z_T = R_s \parallel R_p = R_s \parallel \frac{R_\ell^2 + X_L^2}{R_\ell} = 1000\ \Omega \parallel \frac{10,400\ \Omega}{20} = \mathbf{342.11\ \Omega}$

c.  $\mathbf{E} = \mathbf{I}Z_{T_p} = (5\ \text{mA} \angle 0^\circ)(342.11\ \Omega \angle 0^\circ) = 1.711\ \text{V} \angle 0^\circ$

$\mathbf{I}_C = \frac{\mathbf{E}}{X_C \angle -90^\circ} = \frac{1.711\ \text{V} \angle 0^\circ}{104\ \Omega \angle -90^\circ} = \mathbf{16.45\ \text{mA} \angle 90^\circ}$

$\mathbf{Z}_L = 20\ \Omega + j100\ \Omega = 101.98\ \Omega \angle 78.69^\circ$

$\mathbf{I}_L = \frac{\mathbf{E}}{\mathbf{Z}_L} = \frac{1.711\ \text{V} \angle 0^\circ}{101.98\ \Omega \angle 78.69^\circ} = \mathbf{16.78\ \text{mA} \angle -78.69^\circ}$

$$d. \quad L = \frac{X_L}{2\pi f} = \frac{100 \Omega}{2\pi(20 \text{ kHz})} = \mathbf{795.77 \text{ mH}}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(20 \text{ kHz})(104 \Omega)} = \mathbf{76.52 \text{ nF}}$$

$$e. \quad Q_p = \frac{R}{X_C} = \frac{342.11 \Omega}{104 \Omega} = \mathbf{3.29}$$

$$BW = f_p/Q_p = 20,000 \text{ Hz}/3.29 = \mathbf{6079.03 \text{ Hz}}$$

$$17. \quad Q_t = 35 = \frac{X_L}{R_t} \Rightarrow R_t = \frac{X_L}{35} = \frac{2\pi \left( \frac{2 \times 10^6}{2\pi} \text{ Hz} \right) (1 \text{ mH})}{35} = \frac{2000 \Omega}{35} = 57.14 \Omega$$

$$Q_t \geq 10 : Q_p = \frac{f_p}{BW} = \frac{2 \times 10^6 / 2\pi \text{ Hz}}{100,000 \text{ Hz}} = 20$$

$$Q_p = 20 = \frac{R \parallel Q_t^2 R_t}{X_L} = \frac{R \parallel (35)^2 57.14 \Omega}{2000}$$

$$\text{And } 40,000 = R \parallel 70,000$$

So  $R = 93.33 \text{ k}\Omega \Rightarrow$  use  $R = \mathbf{91 \text{ k}\Omega}$  (standard value)

$$Q_p \geq 10, X_C = X_L = 2000 \Omega = \frac{1}{2\pi f C} = \frac{1}{2\pi \left( \frac{2 \times 10^6}{2\pi} \text{ Hz} \right) C}$$

$C = 250 \text{ pF} \Rightarrow$  use  $C = \mathbf{240 \text{ pF}}$  (standard value)

$$18. \quad a. \quad f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(80 \mu\text{H})(0.03 \mu\text{F})}} = \mathbf{102.73 \text{ kHz}}$$

$$f_p = f_s \sqrt{1 - \frac{R_t^2 C}{L}} = 102.73 \text{ kHz} \sqrt{1 - \frac{(1.5 \Omega)^2 0.03 \mu\text{F}}{80 \mu\text{H}}} = 102.73 \text{ kHz}(.99958)$$

$$= \mathbf{102.69 \text{ kHz}}$$

$$f_m = f_s \sqrt{1 - \frac{1}{4} \left[ \frac{R_t^2 C}{L} \right]} = 102.73 \text{ kHz}(0.99989) = \mathbf{102.72 \text{ kHz}}$$

Since  $f_s \cong f_p \cong f_m \Rightarrow$  high  $Q_p$

$$b. \quad X_L = 2\pi f_p L = 2\pi(102.69 \text{ kHz})(80 \mu\text{H}) = \mathbf{51.62 \Omega}$$

$$X_C = \frac{1}{2\pi f_p C} = \frac{1}{2\pi(102.69 \text{ kHz})(0.03 \mu\text{F})} = \mathbf{51.66 \Omega}$$

$$X_L \cong X_C$$



c.  $Z_{T_p} = R_s \parallel Q_\ell^2 R_\ell$   
 $Q_\ell = \frac{X_L}{R_\ell} = \frac{51.62 \Omega}{1.5 \Omega} = 34.41$   
 $Z_{T_p} = 10 \text{ k}\Omega \parallel (34.41)^2 1.5 \Omega = 10 \text{ k}\Omega \parallel 1.776 \text{ k}\Omega = \mathbf{1.51 \text{ k}\Omega}$

d.  $Q_p = \frac{R_s \parallel Q_\ell^2 R_\ell}{X_L} = \frac{Z_{T_p}}{X_L} = \frac{1.51 \text{ k}\Omega}{51.62 \Omega} = \mathbf{29.25}$   
 $BW = \frac{f_p}{Q_p} = \frac{102.69 \text{ kHz}}{29.25} = \mathbf{3.51 \text{ kHz}}$

e. Converting the voltage source to a current source:

$$I_s = \frac{E}{R_s} = \frac{100 \text{ V}}{10 \text{ k}\Omega} = 10 \text{ mA}$$

$$\text{And } R_s = R_p = 10 \text{ k}\Omega$$

$$\text{Then } I_T = \frac{R_s I_s}{R_s + Q_\ell^2 R_\ell} = \frac{10 \text{ k}\Omega (10 \text{ mA})}{10 \text{ k}\Omega + 1.78 \text{ k}\Omega} = 8.49 \text{ mA}$$

$$I_C = I_L \cong Q_\ell I_T = (34.41)(8.49 \text{ mA}) = \mathbf{292.14 \text{ mA}}$$

f.  $V_C = I Z_{T_p} = (10 \text{ mA})(1.51 \text{ k}\Omega) = \mathbf{15.1 \text{ V}}$

19. a.  $f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.5 \text{ mH})(1 \mu\text{F})}} = \mathbf{7.12 \text{ kHz}}$   
 $f_p = f_s \sqrt{1 - \frac{R_\ell^2 C}{L}} = 7.12 \text{ kHz} \sqrt{1 - \frac{(8 \Omega)^2 (1 \mu\text{F})}{0.5 \text{ mH}}} = 7.12 \text{ kHz}(0.9338) = \mathbf{6.65 \text{ kHz}}$   
 $f_m = f_s \sqrt{1 - \frac{1}{4} \left[ \frac{R_\ell^2 C}{L} \right]} = 7.12 \text{ kHz} \sqrt{1 - \frac{1}{4} \left[ \frac{(8 \Omega)^2 (1 \mu\text{F})}{0.5 \text{ mH}} \right]} = 7.12 \text{ kHz} (0.9839)$   
 $\quad \quad \quad = \mathbf{7.01 \text{ kHz}}$

**Low  $Q_p$**

b.  $X_L = 2\pi f_p L = 2\pi(6.647 \text{ kHz})(0.5 \text{ mH}) = 20.88 \Omega$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(6.647 \text{ kHz})(1 \mu\text{F})} = 23.94 \Omega$$

$X_C > X_L$  (low  $Q$ )

c.  $Z_{T_p} = R_s \parallel R_p = R_s \parallel \frac{R_\ell^2 + X_L^2}{R_\ell} = 500 \Omega \parallel \frac{(8 \Omega)^2 + (20.88 \Omega)^2}{8 \Omega} = 500 \Omega \parallel 62.5 \Omega$   
 $\quad \quad \quad = \mathbf{55.56 \Omega}$

d.  $Q_p = \frac{Z_{T_p}}{X_{L_p}} = \frac{55.56 \Omega}{23.94 \Omega} = \mathbf{2.32}$

$$BW = \frac{f_p}{Q_p} = \frac{6.647 \text{ kHz}}{2.32} = \mathbf{2.87 \text{ kHz}}$$

e. One method:  $V_C = IZ_{T_p} = (40 \text{ mA})(55.56 \Omega) = 2.22 \text{ V}$

$$I_C = \frac{V_C}{X_C} = \frac{2.22 \text{ V}}{23.94 \Omega} = \mathbf{92.73 \text{ mA}}$$

$$I_L = \frac{|V_C|}{|R_\ell + jX_L|} = \frac{2.22 \text{ V}}{|8 + j20.88|} = \frac{2.22 \text{ V}}{22.36 \Omega} = \mathbf{99.28 \text{ mA}}$$

f.  $V_C = \mathbf{2.22 \text{ V}}$

20. a.  $Z_{T_p} = \frac{R_\ell^2 + X_L^2}{R_\ell} = 50 \text{ k}\Omega$

$$(50 \Omega)^2 + X_L^2 = (50 \text{ k}\Omega)(50 \Omega)$$

$$X_L = \sqrt{250 \times 10^4 - 2.5 \times 10^3} = \mathbf{1580.3 \Omega}$$

b.  $Q = \frac{X_L}{R_\ell} = \frac{1580.3}{50} = 31.61 \geq 10$

$$\therefore X_C = X_L = \mathbf{1580.3 \Omega}$$

c.  $X_L = 2\pi f_p L \Rightarrow f_p = \frac{X_L}{2\pi L} = \frac{1580.3 \Omega}{2\pi(16 \text{ mH})} = \mathbf{15.72 \text{ kHz}}$

d.  $X_C = \frac{1}{2\pi f_p C} \Rightarrow C = \frac{1}{2\pi f_s X_C} = \frac{1}{2\pi(15.72 \text{ kHz})(1580.3 \Omega)} = \mathbf{6.4 \text{ nF}}$

21. a.  $Q_\ell = 20 > 10 \therefore f_p = f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(200 \text{ mH})(10 \text{ nF})}} = \mathbf{3558.81 \text{ Hz}}$

b.  $Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi f L}{R_\ell} \Rightarrow R_\ell = \frac{2\pi f L}{Q_\ell} = \frac{2\pi(3558.81 \text{ Hz})(0.2 \text{ H})}{20} = 223.61 \Omega$

$$Z_{T_p} = R_s \parallel R_p = R_s \parallel Q_\ell^2 R_\ell = 40 \text{ k}\Omega \parallel (20)^2 223.61 \Omega$$

$$Z_{T_p} = 27.64 \text{ k}\Omega$$

Converting the voltage source to a current source:

$$I_s = \frac{E}{R_s} = \frac{200 \text{ V}}{40 \text{ k}\Omega} = 5 \text{ mA}$$

$$R_p = R_s = 40 \text{ k}\Omega$$

$$V_C = IZ_{T_p} = (5 \text{ mA})(27.64 \text{ k}\Omega) = \mathbf{138.2 \text{ V}}$$

- c.  $P = I^2 R = (5 \text{ mA})^2 27.64 \text{ k}\Omega = \mathbf{691 \text{ mW}}$
- d.  $Q_p = \frac{R}{X_L} = \frac{R_s \parallel R_p}{X_L} = \frac{27.64 \text{ k}\Omega}{2\pi(3558.81 \text{ Hz})(0.2 \text{ H})} = \mathbf{6.18}$   
 $BW = \frac{f_p}{Q_p} = \frac{3558.81 \text{ Hz}}{6.18} = \mathbf{575.86 \text{ Hz}}$
22. a. Ratio of  $X_C$  to  $R_\ell$  suggests high  $Q$  system.  
 $\therefore X_L = \mathbf{400 \Omega} = X_C$
- b.  $Q_\ell = \frac{X_L}{R_\ell} = \frac{400 \Omega}{8 \Omega} = \mathbf{50}$
- c.  $Q_p = \frac{R}{X_L} = \frac{R_s \parallel R_p}{X_L} = \frac{R_s \parallel Q_\ell^2 R_\ell}{X_L} = \frac{20 \text{ k}\Omega \parallel (50)^2 8 \Omega}{400 \Omega} = \frac{10 \text{ k}\Omega}{400 \Omega} = \mathbf{25}$   
 $BW = \frac{f_p}{Q_p} \Rightarrow f_p = Q_p BW = (25)(1000 \text{ Hz}) = \mathbf{25 \text{ kHz}}$
- d.  $V_{C_{\max}} = IZ_{T_p} = (0.1 \text{ mA})(10 \text{ k}\Omega) = \mathbf{1 \text{ V}}$
- e.  $f_2 = f_p + BW/2 = 25 \text{ kHz} + \frac{1 \text{ kHz}}{2} = \mathbf{25.5 \text{ kHz}}$   
 $f_1 = f_p - BW/2 = 25 \text{ kHz} - \frac{1 \text{ kHz}}{2} = \mathbf{24.5 \text{ kHz}}$
23. a.  $X_C = \frac{R_\ell^2 + X_L^2}{X_L} \Rightarrow X_L^2 - X_L X_C + R_\ell^2 = 0$   
 $X_L^2 - 100 X_L + 144 = 0$   
 $X_L = \frac{-(-100) \pm \sqrt{(100)^2 - 4(1)(144)}}{2}$   
 $= 50 \Omega \pm \frac{\sqrt{10^4 - 576}}{2} = 50 \Omega \pm 48.54 \Omega$   
 $X_L = \mathbf{98.54 \Omega}$  or  ~~$1.46 \Omega$~~
- b.  $Q_\ell = \frac{X_L}{R_\ell} = \frac{98.54 \Omega}{12 \Omega} = \mathbf{8.21}$
- c.  $Q_p = \frac{R_s \parallel R_p}{X_{L_p}} = \frac{40 \text{ k}\Omega \parallel \frac{R_\ell^2 + X_L^2}{R_\ell}}{X_C} = \frac{40 \text{ k}\Omega \parallel \frac{(12 \Omega)^2 + (98.54 \Omega)^2}{12 \Omega}}{100 \Omega}$   
 $= \frac{40 \text{ k}\Omega \parallel 821.18 \Omega}{100 \Omega} = \frac{804.66 \Omega}{100 \Omega} = \mathbf{8.05}$   
 $BW = f_p/Q_p \Rightarrow f_p = Q_p BW = (8.05)(1 \text{ kHz}) = \mathbf{8.05 \text{ kHz}}$

$$d. \quad V_{C_{\max}} = IZ_{T_p} = (6 \text{ mA})(804.66 \Omega) = \mathbf{4.83 \text{ V}}$$

$$e. \quad f_2 = f_p + BW/2 = 8.05 \text{ kHz} + \frac{1 \text{ kHz}}{2} = \mathbf{8.55 \text{ kHz}}$$

$$f_1 = f_p - BW/2 = 8.05 \text{ kHz} - \frac{1 \text{ kHz}}{2} = \mathbf{7.55 \text{ kHz}}$$

$$24. \quad a. \quad f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.5 \text{ mH})(30 \text{ nF})}} = \mathbf{41.09 \text{ kHz}}$$

$$f_p = f_s \sqrt{1 - \frac{R_\ell^2 C}{L}} = 41.09 \text{ kHz} \sqrt{1 - \frac{(6 \Omega)^2 30 \text{ nF}}{0.5 \text{ mH}}} = 41.09 \text{ kHz}(0.9978) = \mathbf{41 \text{ kHz}}$$

$$f_m = f_s \sqrt{1 - \frac{1}{4} \left[ \frac{R_\ell^2 C}{L} \right]} = 41.09 \text{ kHz} \sqrt{1 - \frac{1}{4} \left[ \frac{(6 \Omega)^2 (30 \text{ nF})}{0.5 \text{ mH}} \right]} = 41.09 \text{ kHz}(0.0995) \\ = \mathbf{41.07 \text{ kHz}}$$

**High  $Q_p$**

$$b. \quad \mathbf{I} = \frac{80 \text{ V} \angle 0^\circ}{20 \text{ k}\Omega \angle 0^\circ} = 4 \text{ mA} \angle 0^\circ, R_s = 20 \text{ k}\Omega$$

$$Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi fL}{R_\ell} = \frac{2\pi(41 \text{ kHz})(0.5 \text{ mH})}{6 \Omega} = \mathbf{21.47 \text{ (high } Q \text{ coil)}}$$

$$Q_p = \frac{R_s \parallel R_p}{X_{L_p}} = \frac{R_s \parallel \frac{R_\ell^2 + X_L^2}{R_\ell}}{X_L} = \frac{20 \text{ k}\Omega \parallel \frac{(6 \Omega)^2 + (128.81 \Omega)^2}{6 \Omega}}{\frac{(6 \Omega)^2 + (128.81 \Omega)^2}{128.81 \Omega}} \\ = \frac{20 \text{ k}\Omega \parallel 2.771 \text{ k}\Omega}{129.09 \Omega} = \frac{2.434 \text{ k}\Omega}{129.09 \Omega} = \mathbf{18.86 \text{ (high } Q_p)}$$

$$c. \quad Z_{T_p} = R_s \parallel R_p = 20 \text{ k}\Omega \parallel 2.771 \text{ k}\Omega = \mathbf{2.43 \text{ k}\Omega}$$

$$d. \quad V_C = IZ_{T_p} = (4 \text{ mA})(2.43 \text{ k}\Omega) = \mathbf{9.74 \text{ V}}$$

$$e. \quad BW = \frac{f_p}{Q_p} = \frac{41 \text{ kHz}}{18.86} = \mathbf{2.17 \text{ kHz}}$$

$$f. \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(41 \text{ kHz})(30 \text{ nF})} = \mathbf{129.39 \Omega}$$

$$I_C = \frac{V_C}{X_C} = \frac{9.736 \text{ V}}{129.39 \Omega} = \mathbf{75.25 \text{ mA}}$$

$$I_L = \frac{V_C}{|R + jX_L|} = \frac{9.736 \text{ V}}{6 \Omega + j128.81 \Omega} = \frac{9.736 \text{ V}}{128.95 \Omega} = \mathbf{75.50 \text{ mA}}$$

$$25. \quad Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi f_p L}{R_\ell} \Rightarrow R_\ell = \frac{2\pi f_p L}{Q_\ell} = \frac{2\pi(20 \text{ kHz})(2 \text{ mH})}{80} = \mathbf{3.14 \Omega}$$

$$BW = f_p/Q_p \Rightarrow Q_p = f_p/BW = 20 \text{ kHz}/1.8 \text{ kHz} = \mathbf{11.11}$$

$$\text{High } Q: \quad f_p \cong f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{4\pi^2 f_p^2 L} = \frac{1}{4\pi^2(20 \text{ kHz})^2 2 \text{ mH}} = \mathbf{31.66 \text{ nF}}$$

$$Q_p = \frac{R}{X_C} \Rightarrow R = Q_p X_C = \frac{Q_p}{2\pi f_p C} = \frac{11.11}{2\pi(20 \text{ kHz})(31.66 \text{ nF})} = \mathbf{2.79 \text{ k}\Omega}$$

$$R_p = Q_\ell^2 R_\ell = (80)^2 3.14 \Omega = 20.1 \text{ k}\Omega$$

$$R = R_s \parallel R_p = \frac{R_s R_p}{R_s + R_p} \Rightarrow R_s = \frac{R_p R}{R_p - R} = \frac{(20.1 \text{ k}\Omega)(2.793 \text{ k}\Omega)}{20.1 \text{ k}\Omega - 2.793 \text{ k}\Omega} = \mathbf{3.24 \text{ k}\Omega}$$

$$26. \quad V_{C_{\max}} = I Z_{T_p} \Rightarrow Z_{T_p} = \frac{V_{C_{\max}}}{I} = \frac{1.8 \text{ V}}{0.2 \text{ mA}} = 9 \text{ k}\Omega$$

$$Q_p = \frac{R}{X_L} = \frac{R_s \parallel R_p}{X_L} = \frac{R_p}{X_L} \Rightarrow X_L = \frac{R_p}{Q_p} = \frac{9 \text{ k}\Omega}{30} = \mathbf{300 \Omega} = X_C$$

$$BW = \frac{f_p}{Q_p} \Rightarrow f_p = Q_p BW = (30)(500 \text{ Hz}) = \mathbf{15 \text{ kHz}}$$

$$L = \frac{X_L}{2\pi f} = \frac{300 \Omega}{2\pi(15 \text{ kHz})} = \mathbf{3.18 \text{ mH}}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(15 \text{ kHz})(300 \Omega)} = \mathbf{35.37 \text{ nF}}$$

$$Q_p = Q_\ell (R_s = \infty \Omega) = \frac{X_L}{R_\ell} \Rightarrow R_\ell = \frac{X_L}{Q_p} = \frac{300 \Omega}{30} = \mathbf{10 \Omega}$$

$$27. \quad \text{a.} \quad f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(200 \mu\text{H})(2 \text{ nF})}} = 251.65 \text{ kHz}$$

$$Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi(251.65 \text{ kHz})(200 \mu\text{H})}{20 \Omega} = 15.81 \geq 10$$

$$\therefore f_p = f_s = \mathbf{251.65 \text{ kHz}}$$

$$\text{b.} \quad Z_{T_p} = R_s \parallel Q_\ell^2 R_\ell = 40 \text{ k}\Omega \parallel (15.81)^2 20 \Omega = \mathbf{4.44 \text{ k}\Omega}$$

$$\text{c.} \quad Q_p = \frac{R_s \parallel Q_\ell^2 R_\ell}{X_L} = \frac{4.444 \text{ k}\Omega}{316.23 \Omega} = \mathbf{14.05}$$

$$\text{d.} \quad BW = \frac{f_p}{Q_p} = \frac{251.65 \text{ kHz}}{14.05} = \mathbf{17.91 \text{ kHz}}$$

e. **20  $\mu$ H, 20 nF**

$f_s$  the same since product  $LC$  the same

$$f_s = 251.65 \text{ kHz}$$

$$Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi(251.65 \text{ kHz})(20 \mu\text{H})}{20 \Omega} = 1.581$$

Low  $Q_\ell$  :

$$f_p = f_s \sqrt{1 - \frac{R_\ell^2 C}{L}} = (251.65 \text{ kHz}) \sqrt{1 - \frac{(20 \Omega)^2 (20 \text{ nF})}{20 \mu\text{H}}}$$

$$= (251.65 \text{ kHz})(0.775) = \mathbf{194.93 \text{ kHz}}$$

$$X_L = 2\pi f_p L = 2\pi(194.93 \text{ kHz})(20 \mu\text{H}) = 24.496 \Omega$$

$$R_p = \frac{R_\ell^2 + X_L^2}{R_\ell} = \frac{(20 \Omega)^2 + (24.496 \Omega)^2}{20 \Omega} = 50 \Omega$$

$$Z_{T_p} = R_s \parallel R_p = 40 \text{ k}\Omega \parallel 50 \Omega = \mathbf{49.94 \Omega}$$

$$Q_p = \frac{R}{X_L} = \frac{49.94 \Omega}{24.496 \Omega} = \mathbf{2.04}$$

$$BW = \frac{f_p}{Q_p} = \frac{194.93 \text{ kHz}}{2.04} = \mathbf{95.55 \text{ kHz}}$$

f. **0.4 mH, 1 nF**

$f_s = 251.65 \text{ kHz}$  since  $LC$  product the same

$$Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi(251.65 \text{ kHz})(0.4 \text{ mH})}{20 \Omega} = 31.62 \geq 10$$

$$\therefore f_p = f_s = \mathbf{251.65 \text{ kHz}}$$

$$Z_{T_p} = R_s \parallel Q_\ell^2 R_\ell = 40 \text{ k}\Omega \parallel (31.62)^2 20 \Omega = 40 \text{ k}\Omega \parallel (\cong 20 \text{ k}\Omega) \cong \mathbf{13.33 \text{ k}\Omega}$$

$$Q_p = \frac{R_s \parallel Q_\ell^2 R_\ell}{X_L} = \frac{13.33 \text{ k}\Omega}{632.47 \Omega} = \mathbf{21.08}$$

$$BW = \frac{f_p}{Q_p} = \frac{251.65 \text{ kHz}}{21.08} = \mathbf{11.94 \text{ kHz}}$$

g. Network  $\frac{L}{C} = \frac{200 \mu\text{H}}{2 \text{ nF}} = \mathbf{100 \times 10^3}$

$$\text{part (e)} \frac{L}{C} = \frac{20 \mu\text{H}}{20 \text{ nF}} = \mathbf{1 \times 10^3}$$

$$\text{part (f)} \frac{L}{C} = \frac{0.4 \text{ mH}}{1 \text{ nF}} = \mathbf{400 \times 10^3}$$

h. Yes, as  $\frac{L}{C}$  ratio increased  $BW$  decreased.

Also,  $V_p = IZ_{T_p}$  and for a fixed  $I$ ,  $Z_{T_p}$  and therefore  $V_p$  will increase with increase in the  $L/C$  ratio.