

Chapter 22

1. a. left: $d_1 = \frac{3}{16}'' = 0.1875'', d_2 = 1''$

$$\begin{aligned}\text{Value} &= 10^3 \times 10^{0.1875''/1''} \\ &= 10^3 \times 1.54 \\ &= \mathbf{1.54 \text{ kHz}}\end{aligned}$$

center: $d_1 = \frac{1}{2}'' = 0.5'', d_2 = 1''$

$$\begin{aligned}\text{Value} &= 10^3 \times 10^{0.5/1} \\ &= 10^3 \times 10^5 \\ &= 10^3 \times 3.16 \\ &= \mathbf{3.16 \text{ kHz}}\end{aligned}$$

right: $d_1 = \frac{3}{4}'' = 0.75'', d_2 = 1''$

$$\begin{aligned}\text{Value} &= 10^3 \times 10^{0.75''/1''} \\ &= 10^3 \times 5.623 \\ &= \mathbf{5.62 \text{ kHz}}\end{aligned}$$

b. bottom: $d_1 = \frac{5}{16}'' = 0.3125'', d_2 = \frac{15}{16}'' = 0.9375''$

$$\begin{aligned}\text{Value} &= 10^{-1} \times 10^{0.3125''/0.9375''} = 10^{-1} \times 10^{0.333} \\ &= 10^{-1} \times 2.153 \\ &= \mathbf{0.22 \text{ V}}\end{aligned}$$

center: $d_1 = \frac{7.5}{16}'' = 0.469'', d_2 = 0.9375''$

$$\begin{aligned}\text{Value} &= 10^{-1} \times 10^{0.469/0.9375} \\ &= 10^{-1} \times 10^{0.5} \\ &= 10^{-1} \times 3.16 \\ &= \mathbf{0.316 \text{ V}}\end{aligned}$$

top: $d_1 = \frac{11}{16}'' = 0.6875'', d_2 = 0.9375''$

$$\begin{aligned}\text{Value} &= 10^{-1} \times 10^{0.6875''/0.9375''} = 10^{-1} \times 10^{0.720} \\ &= 10^{-1} \times 5.248 \\ &= \mathbf{0.52 \text{ V}}\end{aligned}$$

2. a. **5** b. **-4** c. **8** d. **-6**

e. **1.30** f. **3.94** g. **4.75** h. **-0.498**

3. a. **1000** b. **10^{12}** c. **1.59** d. **1.1**

e. **10^{10}** f. **1513.56** g. **10.02** h. **1,258,925.41**

4. a. **11.51** b. **-9.21** c. **2.996** d. **9.07**

5. $\log_{10} 48 = \mathbf{1.68}$

$$\log_{10} 8 + \log_{10} 6 = 0.903 + 0.778 = \mathbf{1.68}$$

6. $\log_{10} 0.2 = \mathbf{-0.699}$
 $\log_{10} 18 - \log_{10} 90 = 1.255 - 1.954 = \mathbf{-0.699}$

7. $\log_{10} 0.5 = \mathbf{-0.30}$
 $-\log_{10} 2 = -(0.301) = \mathbf{-0.30}$

8. $\log_{10} 27 = \mathbf{1.43}$
 $3 \log_{10} 3 = 3(0.4771) = \mathbf{1.43}$

9. a. $\text{bels} = \log_{10} \frac{P_2}{P_1} = \log_{10} \frac{280 \text{ mW}}{4 \text{ mW}} = \log_{10} 70 = \mathbf{1.85}$
b. $\text{dB} = 10 \log_{10} \frac{P_2}{P_1} = 10(\log_{10} 70) = 10(1.845) = \mathbf{18.45}$

10. $\text{dB} = 10 \log_{10} \frac{P_2}{P_1}$
 $6 \text{ dB} = 10 \log_{10} \frac{100 \text{ W}}{P_1}$
 $0.6 = \log_{10} x$
 $x = 3.981 = \frac{100 \text{ W}}{P_1}$
 $P_1 = \frac{100 \text{ W}}{3.981} = \mathbf{25.12 \text{ W}}$

11. $\text{dB} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{40 \text{ W}}{2 \text{ W}} = 10 \log_{10} 20 = \mathbf{13.01}$

12. $\text{dB}_m = 10 \log_{10} \frac{P}{1 \text{ mW}}$
 $\text{dB}_m = 10 \log_{10} \frac{120 \text{ mW}}{1 \text{ mW}} = 10 \log_{10} 120 = \mathbf{20.79}$

13. $\text{dB}_v = 20 \log_{10} \frac{V_2}{V_1} = 20 \log_{10} \frac{8.4 \text{ V}}{0.1 \text{ V}} = 20 \log_{10} 84 = \mathbf{38.49}$

14. $\text{dB}_o = 20 \log_{10} \frac{V_2}{V_1}$
 $22 = 20 \log_{10} \frac{V_o}{20 \text{ mV}}$
 $1.1 = \log_{10} x$
 $x = 12.589 = \frac{V_o}{20 \text{ mV}}$
 $V_o = \mathbf{251.79 \text{ mV}}$

$$15. \quad dB_s = 20 \log_{10} \frac{P}{0.0002 \mu\text{bar}}$$

$$dB_s = 20 \log_{10} \frac{0.001 \mu\text{bar}}{0.0002 \mu\text{bar}} = \mathbf{13.98}$$

$$dB_s = 20 \log_{10} \frac{0.016 \mu\text{bar}}{0.0002 \mu\text{bar}} = \mathbf{38.06}$$

Increase = **24.08 dB_s**

$$16. \quad 60 \text{ dB}_s \Rightarrow 90 \text{ dB}_s$$

quiet loud

$$60 \text{ dB}_s = 20 \log_{10} \frac{P_1}{0.002 \mu\text{bar}} = 20 \log_{10} x$$

$$\begin{aligned} 3 &= \log_{10} x \\ x &= \mathbf{1000} \end{aligned}$$

$$90 \text{ dB}_s = 20 \log_{10} \frac{P_2}{0.002 \mu\text{bar}} = 20 \log_{10} y$$

$$\begin{aligned} 4.5 &= \log_{10} y \\ y &= \mathbf{31.623 \times 10^3} \end{aligned}$$

$$\begin{aligned} \frac{x}{y} &= \frac{\frac{P_1}{0.002 \mu\text{bar}}}{\frac{P_2}{0.002 \mu\text{bar}}} = \frac{P_1}{P_2} = \frac{10^3}{31.623 \times 10^3} \end{aligned}$$

and $P_2 = \mathbf{31.62 P}_1$

$$17. \quad -$$

$$18. \quad \text{a.} \quad 8 \text{ dB} = 20 \log_{10} \frac{V_2}{0.775 \text{ V}}$$

$$0.4 = \log_{10} \frac{V_2}{0.775 \text{ V}}$$

$$\frac{V_2}{0.775 \text{ V}} = 2.512$$

$$V_2 = (2.512)(0.775 \text{ V}) = 1.947 \text{ V}$$

$$P = \frac{V^2}{R} = \frac{(1.947 \text{ V})^2}{600 \Omega} = \mathbf{6.32 \text{ mW}}$$

$$\text{b.} \quad -5 \text{ dB} = 20 \log_{10} \frac{V_2}{0.775 \text{ V}}$$

$$-0.25 = \log_{10} \frac{V_2}{0.775 \text{ V}}$$

$$\frac{V_2}{0.775 \text{ V}} = 0.562$$

$$V_2 = (0.562)(0.775 \text{ V}) = 0.436 \text{ V}$$

$$P = \frac{V^2}{R} = \frac{(0.436 \text{ V})^2}{600 \Omega} = \mathbf{0.32 \text{ mW}}$$

$$19. \quad a. \quad A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} \angle -90^\circ + \tan^{-1} X_C/R = \frac{1}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}} \angle -\tan^{-1} R/X_C$$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2 \text{ k}\Omega)(0.02 \mu\text{F})} = 3617.16 \text{ Hz}$$

$$f = f_c: \quad A_v = \frac{V_o}{V_i} = 0.707$$

$f = 0.1f_c$: At f_c , $X_C = R = 2.2 \text{ k}\Omega$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi 0.1 f_c C} = \frac{1}{0.1} \left[\frac{1}{2\pi f_c C} \right] = 10[2.2 \text{ k}\Omega] = 22 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}} = \frac{1}{\sqrt{\left(\frac{2.2 \text{ k}\Omega}{22 \text{ k}\Omega}\right)^2 + 1}} = \frac{1}{\sqrt{(0.1)^2 + 1}} = 0.995$$

$$f = 0.5f_c = \frac{1}{2}f_c: \quad X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \left(\frac{f_c}{2}\right) C} = 2 \left[\frac{1}{2\pi f_c C} \right] = 2[2.2 \text{ k}\Omega] = 4.4 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{\left(\frac{2.2 \text{ k}\Omega}{4.4 \text{ k}\Omega}\right)^2 + 1}} = \frac{1}{\sqrt{(0.5)^2 + 1}} = 0.894$$

$$f = 2f_c: \quad X_C = \frac{1}{2\pi(2f_c)C} = \frac{1}{2} \left[\frac{1}{2\pi f_c C} \right] = \frac{1}{2}[2.2 \text{ k}\Omega] = 1.1 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{\left(\frac{2.2 \text{ k}\Omega}{1.1 \text{ k}\Omega}\right)^2 + 1}} = \frac{1}{\sqrt{(2)^2 + 1}} = 0.447$$

$$f = 10f_c: \quad X_C = \frac{1}{2\pi(10f_c)C} = \frac{1}{10} \left[\frac{1}{2\pi f_c C} \right] = \frac{1}{10}[2.2 \text{ k}\Omega] = 0.22 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{\left(\frac{2.2 \text{ k}\Omega}{0.22 \text{ k}\Omega}\right)^2 + 1}} = \frac{1}{\sqrt{(10)^2 + 1}} = 0.0995$$

$$b. \quad \theta = -\tan^{-1} R/X_C$$

$$f = f_c: \quad \theta = -\tan^{-1} = -45^\circ$$

$$f = 0.1f_c: \quad \theta = -\tan^{-1} 2.2 \text{ k}\Omega/22 \text{ k}\Omega = -\tan^{-1} \frac{1}{10} = -5.71^\circ$$

$$f = 0.5f_c: \quad \theta = -\tan^{-1} 2.2 \text{ k}\Omega/4.4 \text{ k}\Omega = -\tan^{-1} \frac{1}{2} = -26.57^\circ$$

$$f = 2f_c: \quad \theta = -\tan^{-1} 2.2 \text{ k}\Omega/1.1 \text{ k}\Omega = -\tan^{-1} 2 = -63.43^\circ$$

$$f = 10f_c; \quad \theta = -\tan^{-1} 2.2 \text{ k}\Omega / 0.22 \text{ k}\Omega = -\tan^{-1} 10 = -\mathbf{84.29^\circ}$$

20. a. $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2 \text{ k}\Omega)(0.1 \mu\text{F})} = 723.43 \text{ Hz}$
 $f = 2f_c = 1.45 \text{ kHz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(1.45 \text{ kHz})(0.1 \mu\text{F})} = 1.1 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{1.1 \text{ k}\Omega}{\sqrt{(2.2 \text{ k}\Omega)^2 + (1 \text{ k}\Omega)^2}} = 0.4472$$

$$V_o = 0.4472 V_i = 0.4472(10 \text{ mV}) = \mathbf{4.47 \text{ mV}}$$

b. $f = \frac{1}{10} f_c = \frac{1}{10}(723.43 \text{ Hz}) = 72.34 \text{ Hz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(72.34 \text{ Hz})(0.1 \mu\text{F})} = 22 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{22 \text{ k}\Omega}{\sqrt{(2.2 \text{ k}\Omega)^2 + (22 \text{ k}\Omega)^2}} = \frac{22 \text{ k}\Omega}{22.11 \text{ k}\Omega} = 0.995$$

$$V_o = 0.995 V_i = 0.995(10 \text{ mV}) = \mathbf{9.95 \text{ mV}}$$

c. Yes, at $f = f_c$, $V_o = 7.07 \text{ mV}$

$$\text{at } f = \frac{1}{10} f_c, V_o = 9.95 \text{ mV} \text{ (much higher)}$$

$$\text{at } f = 2f_c, V_o = 4.47 \text{ mV} \text{ (much lower)}$$

21. $f_c = 500 \text{ Hz} = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.2 \text{ k}\Omega)C}$

$$C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi(1.2 \text{ k}\Omega)(500 \text{ Hz})} = \mathbf{0.265 \mu\text{F}}$$

$$A_v = \frac{V_o}{V_i} = \frac{1}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}}$$


At $f = 250 \text{ Hz}$, $X_C = 2402.33 \Omega$ and $A_v = 0.895$

At $f = 1000 \text{ Hz}$, $X_C = 600.58 \Omega$ and $A_v = 0.4475$

$$\theta = -\tan^{-1} R/X_C$$

$$\text{At } f = 250 \text{ Hz} = \frac{1}{2} f_c, \theta = -26.54^\circ$$
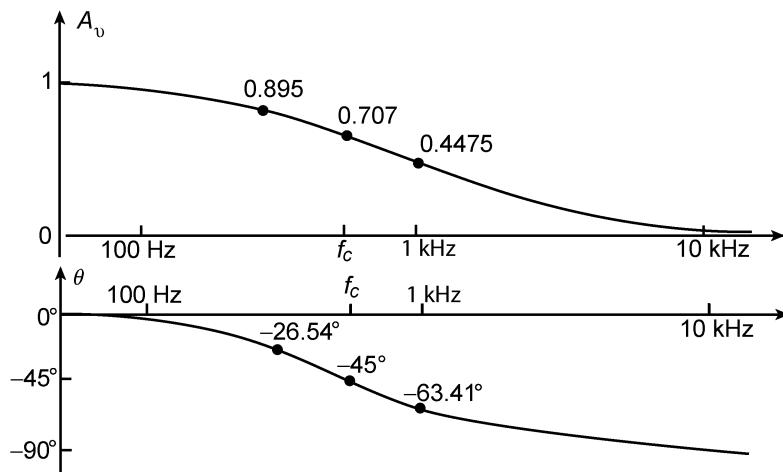
$$\text{At } f = 1 \text{ kHz} = 2f_c, \theta = -63.41^\circ$$



22. a. $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(4.7 \text{ k}\Omega)(500 \text{ pF})} = 67.73 \text{ kHz}$

b. $f = 0.1 f_c = 0.1(67.726 \text{ kHz}) \cong 6.773 \text{ kHz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(6.773 \text{ kHz})(500 \text{ pF})} = 46.997 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{46.997 \text{ k}\Omega}{\sqrt{(4.7 \text{ k}\Omega)^2 + (46.997 \text{ k}\Omega)^2}} = 0.995 \cong 1$$

c. $f = 10f_c = 677.26 \text{ kHz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(677.26 \text{ kHz})(500 \text{ pF})} \cong 470 \text{ }\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{470 \text{ }\Omega}{\sqrt{(4.7 \text{ k}\Omega)^2 + (470 \text{ }\Omega)^2}} = 0.0995 \cong 0.1$$

d. $A_v = \frac{V_o}{V_i} = 0.01 = \frac{X_C}{\sqrt{R^2 + X_C^2}}$

$$\sqrt{R^2 + X_C^2} = \frac{X_C}{0.01} = 100 X_C$$

$$R^2 + X_C^2 = 10^4 X_C^2$$

$$R^2 = 10^4 X_C^2 - X_C^2 = 9,999 X_C^2$$

$$X_C = \frac{R}{\sqrt{9,999}} = \frac{4.7 \text{ k}\Omega}{\sqrt{9,999}} \cong 47 \text{ }\Omega$$

$$X_C = \frac{1}{2\pi f C} \Rightarrow f = \frac{1}{2\pi X_C C} = \frac{1}{2\pi(47 \text{ }\Omega)(500 \text{ pF})} = 6.77 \text{ MHz}$$

23. a. $A_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{\sqrt{R^2 + X_C^2}} \angle \tan^{-1} X_C/R = \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}} \angle \tan^{-1} X_C/R$

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2 \text{ k}\Omega)(0.02 \mu\text{F})} = \mathbf{3.62 \text{ kHz}}$$

$$f = f_c: \quad A_v = \frac{V_o}{V_i} = \mathbf{0.707}$$

$$f = 2f_c: \quad \text{At } f_c, X_C = R = 2.2 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(2f_c)C} = \frac{1}{2} \left[\frac{1}{2\pi(2f_c)C} \right] = \frac{1}{2} [2.2 \text{ k}\Omega] = 1.1 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{1.1 \text{ k}\Omega}{2.2 \text{ k}\Omega}\right)^2}} = \mathbf{0.894}$$

$$f = \frac{1}{2}f_c: \quad X_C = \frac{1}{2\pi\left(\frac{f_c}{2}\right)C} = 2 \left[\frac{1}{2\pi f_c C} \right] = 2[2.2 \text{ k}\Omega] = 4.4 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{4.4 \text{ k}\Omega}{2.2 \text{ k}\Omega}\right)^2}} = \mathbf{0.447}$$

$$f = 10f_c: \quad X_C = \frac{1}{2\pi(10f_c)C} = \frac{1}{10} \left[\frac{1}{2\pi f_c C} \right] = \frac{2.2 \text{ k}\Omega}{10} = 0.22 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{0.22 \text{ k}\Omega}{2.2 \text{ k}\Omega}\right)^2}} = \mathbf{0.995}$$

$$f = \frac{1}{10}f_c: \quad X_C = \frac{1}{2\pi\left(\frac{f_c}{10}\right)C} = 10 \left[\frac{1}{2\pi f_c C} \right] = 10[2.2 \text{ k}\Omega] = 22 \text{ k}\Omega$$

$$A_v = \frac{1}{\sqrt{1 + \left(\frac{22 \text{ k}\Omega}{2.2 \text{ k}\Omega}\right)^2}} = \mathbf{0.0995}$$

b. $f = f_c, \quad \theta = \mathbf{45^\circ}$

$$f = 2f_c, \quad \theta = \tan^{-1}(X_C/R) = \tan^{-1} 1.1 \text{ k}\Omega/2.2 \text{ k}\Omega = \tan^{-1} \frac{1}{2} = \mathbf{26.57^\circ}$$

$$f = \frac{1}{2}f_c, \quad \theta = \tan^{-1} \frac{4.4 \text{ k}\Omega}{2.2 \text{ k}\Omega} = \tan^{-1} 2 = \mathbf{63.43^\circ}$$

$$f = 10f_c, \quad \theta = \tan^{-1} \frac{0.22 \text{ k}\Omega}{2.2 \text{ k}\Omega} = \mathbf{5.71^\circ}$$

$$f = \frac{1}{10} f_c, \quad \theta = \tan^{-1} \frac{22 \text{ k}\Omega}{2.2 \text{ k}\Omega} = \mathbf{84.29^\circ}$$

24. a. $f = f_c: A_v = \frac{V_o}{V_i} = \mathbf{0.707}$

b. $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(120 \text{ k}\Omega)(47 \text{ pF})} = 28.22 \text{ kHz}$

$$f = 4f_c = 4(28.22 \text{ kHz}) = 112.88 \text{ kHz}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(112.88 \text{ kHz})(47 \text{ pF})} = 30 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{120 \text{ k}\Omega}{\sqrt{(120 \text{ k}\Omega)^2 + (30 \text{ k}\Omega)^2}} = \mathbf{0.970} \text{ (significant rise)}$$

c. $f = 100f_c = 100(28.22 \text{ kHz}) = 2.82 \text{ MHz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(2.82 \text{ MHz})(47 \text{ pF})} = 1.2 \text{ k}\Omega$$

$$A_v = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{120 \text{ k}\Omega}{\sqrt{(120 \text{ k}\Omega)^2 + (1.2 \text{ k}\Omega)^2}} = 1$$

d. At $f = f_c$, $V_o = 0.707V_i = 0.707(10 \text{ mV}) = 7.07 \text{ mV}$

$$P_o = \frac{V_o^2}{R} = \frac{(7.07 \text{ mV})^2}{120 \text{ k}\Omega} \cong \mathbf{0.417 \text{ nW}}$$

25. $\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}} \angle \tan^{-1} X_C/R$

$$f_c = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi(2 \text{ kHz})(0.1 \mu \text{F})} = 795.77 \Omega$$

$$R = 795.77 \Omega \Rightarrow \underbrace{750 \Omega + 47 \Omega}_{\text{nominal values}} = 797 \Omega$$


$$\therefore f_c = \frac{1}{2\pi(797 \Omega)(0.1 \mu \text{F})} = \mathbf{1996.93 \text{ Hz}} \text{ using nominal values}$$

At $f = 1 \text{ kHz}, A_v = 0.458$
 $f = 4 \text{ kHz}, A_v \cong 0.9$

$$\theta = \tan^{-1} \frac{X_C}{R}$$

$$f = 1 \text{ kHz}, \theta = 63.4^\circ$$
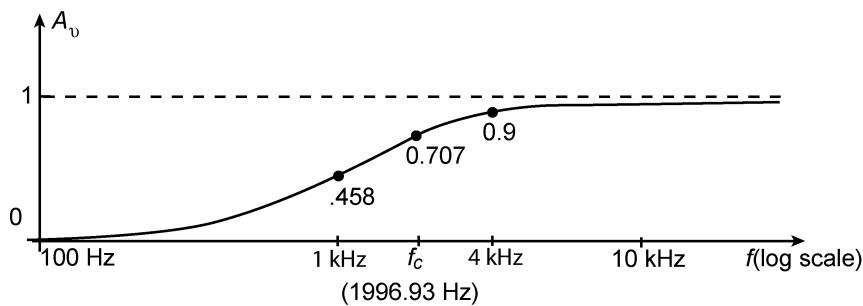
$$f = 4 \text{ kHz}, \theta = 26.53^\circ$$



26. a. $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(100 \text{ k}\Omega)(20 \text{ pF})} = 79.58 \text{ kHz}$

b. $f = 0.01f_c = 0.01(79.577 \text{ kHz}) = 0.7958 \text{ kHz} \approx 796 \text{ Hz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(796 \text{ Hz})(20 \text{ pF})} = 9.997 \text{ M}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{100 \text{ k}\Omega}{\sqrt{(100 \text{ k}\Omega)^2 + (9.997 \text{ M}\Omega)^2}} = 0.01 \approx 0$$

c. $f = 100f_c = 100(79.577 \text{ kHz}) \approx 7.96 \text{ MHz}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(7.96 \text{ MHz})(20 \text{ pF})} = 999.72 \text{ }\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{100 \text{ k}\Omega}{\sqrt{(100 \text{ k}\Omega)^2 + (999.72 \text{ }\Omega)^2}} = 0.99995 \approx 1$$

d. $A_v = \frac{V_o}{V_i} = 0.5 = \frac{R}{\sqrt{R^2 + X_C^2}}$

$$\sqrt{R^2 + X_C^2} = 2R$$

$$R^2 + X_C^2 = 4R^2$$

$$X_C^2 = 4R^2 - R^2 = 3R^2$$

$$X_C = \sqrt{3R^2} = \sqrt{3}R = \sqrt{3}(100 \text{ k}\Omega) = 173.2 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi f C} \Rightarrow f = \frac{1}{2\pi X_C C} = \frac{1}{2\pi(173.2 \text{ k}\Omega)(20 \text{ pF})}$$

$$f = 45.95 \text{ kHz}$$

27. a. low-pass section: $f_{c_1} = \frac{1}{2\pi RC} = \frac{1}{2\pi(0.1 \text{ k}\Omega)(2 \mu\text{F})} = 795.77 \text{ Hz}$

high-pass section: $f_{c_2} = \frac{1}{2\pi RC} = \frac{1}{2\pi(10 \text{ k}\Omega)(8200 \text{ pF})} = 1.94 \text{ Hz}$

For the analysis to follow, it is assumed $(R_2 + jX_{C_2}) \parallel R_1 \cong R_1$ for all frequencies of interest.

At $f_{c_1} = 795.77$ Hz:

$$V_{R_l} = 0.707 V_i$$

$$X_{C_2} = \frac{1}{2\pi f C_2} = 24.39 \text{ k}\Omega$$

$$|V_o| = \frac{24.39 \text{ k}\Omega(V_{R_l})}{\sqrt{(10 \text{ k}\Omega)^2 + (24.39 \text{ k}\Omega)^2}} = 0.925 V_{R_l}$$

$$V_o = (0.925)(0.707 V_i) = \mathbf{0.654} V_i$$

At $f_{c_2} = 1.94$ kHz:

$$V_o = 0.707 V_{R_l}$$

$$X_{C_1} = \frac{1}{2\pi f C_1} = 41 \Omega$$

$$|V_{R_l}| = \frac{R_l V_i}{\sqrt{R_l^2 + X_{C_1}^2}} = \frac{100 \Omega(V_i)}{\sqrt{(100 \Omega)^2 + (41 \Omega)^2}} = 0.925 V_i$$

$$|V_o| = (0.707)(0.925 V_i) = \mathbf{0.64} V_i$$

$$\text{At } f = 795.77 \text{ Hz} + \frac{(1.94 \text{ kHz} - 795.77 \text{ Hz})}{2} = 1.37 \text{ kHz}$$

$$X_{C_1} = 58.1 \Omega, X_{C_2} = 14.17 \text{ k}\Omega$$

$$|V_{R_l}| = \frac{100 \Omega(V_i)}{\sqrt{(100 \Omega)^2 + (58.1 \Omega)^2}} = 0.864 V_i$$

$$|V_o| = \frac{14.17 \text{ k}\Omega(V_{R_l})}{\sqrt{(10 \text{ k}\Omega)^2 + (14.17 \text{ k}\Omega)^2}} = 0.817 V_{R_l}$$

$$V_o = 0.817(0.864 V_i) = 0.706 V_i$$

$$\text{and } A_v = \frac{V_o}{V_i} = \mathbf{0.706} (\cong \text{maximum value})$$

After plotting the points it was determined that the gain should also be determined at $f = 500$ Hz and 4 kHz:

$$f = 500 \text{ Hz: } X_{C_1} = 159.15 \Omega, X_{C_2} = 38.82 \text{ k}\Omega,$$

$$V_{R_l} = 0.532 V_i, V_o = 0.968 V_{R_l}$$

$$V_o = \mathbf{0.515} V_i$$

$$f = 4 \text{ kHz: } X_{C_1} = 19.89 \Omega, X_{C_2} = 4.85 \text{ k}\Omega,$$

$$V_{R_l} = 0.981 V_i, V_o = 0.437 V_{R_l}$$


$$V_o = \mathbf{0.429} V_i$$

- b. Using $0.707(0.706) \cong 0.5$ to define the bandwidth

$$BW \cong 3.4 \text{ kHz} - 0.48 \text{ kHz} = 2.92 \text{ kHz}$$

$$\text{and } BW \cong \mathbf{2.9 \text{ kHz}}$$
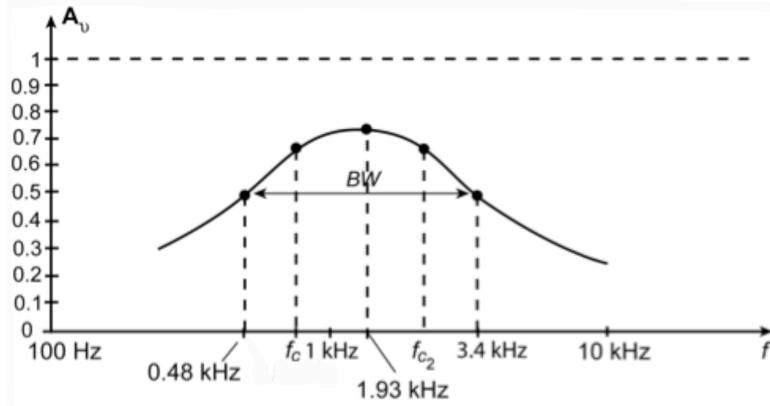
$$\text{with } f_{\text{center}} = 480 \text{ Hz} + \left(\frac{2.9 \text{ kHz}}{2} \right) = \mathbf{1930 \text{ Hz}}$$



$$28. \quad f_1 = \frac{1}{2\pi R_1 C_1} = 4 \text{ kHz}$$


Choose $R_1 = 1 \text{ k}\Omega$

$$C_1 = \frac{1}{2\pi f_1 R_1} = \frac{1}{2\pi(4 \text{ kHz})(1 \text{ k}\Omega)} = 39.8 \text{ nF} \therefore \text{Use } \mathbf{39 \text{ nF}}$$

$$f_2 = \frac{1}{2\pi R_2 C_2} = 80 \text{ kHz}$$

Choose $R_2 = 20 \text{ k}\Omega$
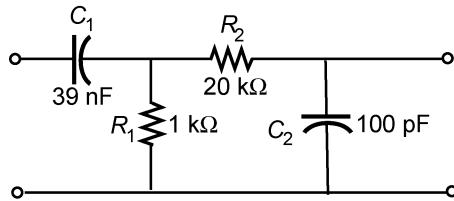
$$C_2 = \frac{1}{2\pi f_2 R_2} = \frac{1}{2\pi(80 \text{ kHz})(20 \text{ k}\Omega)} = 99.47 \text{ pF} \therefore \text{Use } 100 \text{ pF}$$



$$\text{Center frequency} = 4 \text{ kHz} + \frac{80 \text{ kHz} - 4 \text{ kHz}}{2} = 42 \text{ kHz}$$

At $f = 42 \text{ kHz}$, $X_{C_1} = 97.16 \Omega$, $X_{C_2} = 37.89 \text{ k}\Omega$

Assuming $Z_2 \gg Z_1$

$$|V_{R_1}| = \frac{R_1(V_i)}{\sqrt{R_1^2 + X_{C_1}^2}} = 0.995V_i$$

$$|V_o| = \frac{X_{C_2}(V_{R_1})}{\sqrt{R_2^2 + X_{C_1}^2}} = 0.884V_i$$

$$V_o = 0.884 V_{R_1} = 0.884(0.995V_i) = \mathbf{0.88 V_i}$$

$$\text{as } f = f_1: \quad V_{R_1} = 0.707V_i, \quad X_{C_2} = 221.05 \text{ k}\Omega$$

and $V_o = 0.996 V_{R_i}$

so that $V_o = 0.996 V_{R_i} = 0.996(0.707 V_i) = 0.704 V_i$

Although $A_v = 0.88$ is less than the desired level of 1, f_1 and f_2 do define a band of frequencies for which $A_v \geq 0.7$ and the power to the load is significant.

29. a. $f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(4.7 \text{ mH})(560 \text{ pF})}} = \mathbf{98.1 \text{ kHz}}$

b. $Q_s = \frac{X_L}{R + R_\ell} = \frac{2\pi(98.1 \text{ kHz})(4.7 \text{ mH})}{160 \Omega + 12 \Omega} = \mathbf{16.84}$

$$BW = \frac{f_s}{Q_s} = \frac{98.1 \text{ kHz}}{16.84} = \mathbf{5.83 \text{ kHz}}$$

c. At $f = f_s$: $V_{o_{\max}} = \frac{R}{R + R_\ell} V_i = \frac{160 \Omega(1 \text{ V})}{172 \Omega} = 0.93 \text{ V}$ and $A_v = \frac{V_o}{V_i} = \mathbf{0.93}$

Since $Q_s \geq 10$, $f_1 = f_s - \frac{BW}{2} = 98.1 \text{ kHz} - \frac{5.83 \text{ kHz}}{2} = 95.19 \text{ kHz}$

$$f_2 = f_s + \frac{BW}{2} = 101.02 \text{ kHz}$$

At $f = 95.19 \text{ kHz}$: $X_L = 2\pi f L = 2\pi(95.19 \text{ kHz})(4.7 \text{ mH}) = 2.81 \text{ k}\Omega$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(95.19 \text{ kHz})(560 \text{ pF})} = 2.99 \text{ k}\Omega$$

$$\begin{aligned} \mathbf{V}_o &= \frac{160 \Omega(1 \text{ V} \angle 0^\circ)}{172 + j2.81 \text{ k}\Omega - j2.99 \text{ k}\Omega} = \frac{160 \text{ V} \angle 0^\circ}{172 - j180} \\ &= \frac{160 \text{ V} \angle 0^\circ}{248.97 \angle -46.30^\circ} = \mathbf{0.643 \text{ V} \angle 46.30^\circ} \end{aligned}$$

At $f = 101.02 \text{ kHz}$: $X_L = 2\pi f L = 2\pi(101.02 \text{ kHz})(4.7 \text{ mH}) = 2.98 \text{ k}\Omega$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(101.02 \text{ kHz})(560 \text{ pF})} = 2.81 \text{ k}\Omega$$

$$\begin{aligned} \mathbf{V}_o &= \frac{160 \Omega(1 \text{ V} \angle 0^\circ)}{172 + j2.98 \text{ k}\Omega - j2.81 \text{ k}\Omega} = \frac{160 \text{ V} \angle 0^\circ}{172 + j170} \\ &= \frac{160 \text{ V} \angle 0^\circ}{241.83 \angle 44.66^\circ} = \mathbf{0.66 \text{ V} \angle -44.66^\circ} \end{aligned}$$

d. $f = f_s$: $V_{o_{\max}} = \mathbf{0.93 \text{ V}}$

$f = f_1 = 95.19 \text{ kHz}$, $V_o = 0.707(0.93 \text{ V}) = \mathbf{0.66 \text{ V}}$

$f = f_2 = 101.02 \text{ kHz}$, $V_o = 0.707(0.93 \text{ V}) = \mathbf{0.66 \text{ V}}$

30. a. $f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_\ell^2 C}{L}} \cong \mathbf{159.15 \text{ kHz}}$


$$Q_\ell = \frac{X_L}{R_\ell} = \frac{2\pi f_p L}{R_\ell} = \frac{2\pi(159.15 \text{ kHz})(1 \text{ mH})}{16 \Omega} = 62.5 \gg 10$$

$$Z_{T_p} = Q_\ell^2 R_\ell = (62.5)^2 16 \Omega = 62.5 \text{ k}\Omega \gg 4 \text{ k}\Omega$$

and $V_o \cong V_i$ at resonance.

However, $R = 3.3 \text{ k}\Omega$ affects the shape of the resonance curve and $BW = f_p/Q_\ell$ cannot be applied.

For $A_v = \frac{V_o}{V_i} = 0.707$, $|X| = R$ for the following configuration

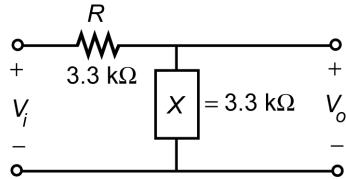

For frequencies near f_p , $X_L \gg R_\ell$ and $Z_L = R_\ell + jX_L \cong X_L$ and $X = X_L \parallel X_C$.

For frequencies near f_p but less than f_p

$$X = \frac{X_C X_L}{X_C - X_L}$$

and for $A_v = 0.707$

$$\frac{X_C X_L}{X_C - X_L} = R$$

Substituting $X_C = \frac{1}{2\pi f_1 C}$ and $X_L = 2\pi f_1 L$

the following equation can be derived:

$$f_1^2 + \frac{1}{2\pi RC} f_1 - \frac{1}{4\pi^2 LC} = 0$$

For this situation:

$$\frac{1}{2\pi RC} = \frac{1}{2\pi(3.3 \text{ k}\Omega)(0.001 \mu\text{F})} = 48.23 \times 10^3$$

$$\frac{1}{4\pi^2 LC} = \frac{1}{4\pi^2(1 \text{ mH})(0.001 \mu\text{F})} = 2.53 \times 10^{10}$$

and solving the quadratic equation, $f_1 = 135.83 \text{ kHz}$

$$\text{and } \frac{BW}{2} = f_p - f_1 = 159.15 \text{ kHz} - 135.83 \text{ kHz} = 22.32 \text{ kHz}$$

$$\text{so that } f_2 = f_p + \frac{BW}{2} = 159.15 \text{ kHz} + 18.75 \text{ kHz} = 177.9 \text{ kHz}$$


b. $Q_p = \frac{f_p}{BW} = \frac{159.15 \text{ kHz}}{44.64 \text{ kHz}} = 3.57$
 $BW = 2(18.75 \text{ kHz}) = 37.5 \text{ kHz}$

31. a. $Q_s = \frac{X_L}{R + R_\ell} = \frac{5000 \Omega}{390 \Omega + 10 \Omega} = \frac{5000 \Omega}{400 \Omega} = 12.5$

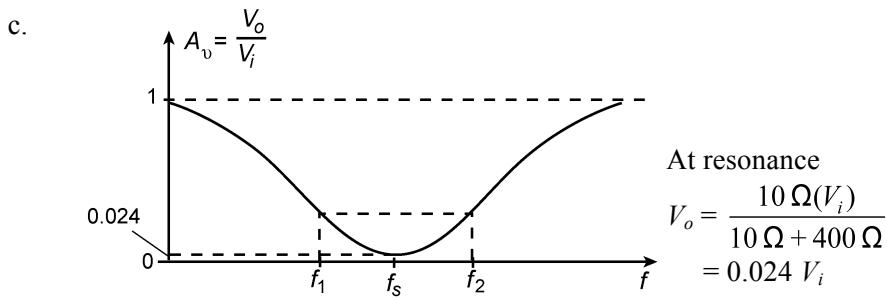b. $BW = \frac{f_s}{Q_s} = \frac{5000 \text{ Hz}}{12.5} = 400 \text{ Hz}$

$$f_1 = 5000 \text{ Hz} - \frac{400 \text{ Hz}}{2} = 4.8 \text{ kHz}$$

$$f_2 = 5000 \text{ Hz} + \frac{400 \text{ Hz}}{2} = 5.20 \text{ kHz}$$



d. At resonance, $10 \Omega \parallel 2 \text{ k}\Omega = 9.95 \Omega$
 $V_o = \frac{9.95 \Omega(V_i)}{9.95 \Omega + 400 \Omega} \approx 0.024 V_i$ as above!

32. a. $Q_\ell = \frac{X_L}{R_\ell} = \frac{400 \Omega}{10 \Omega} = 40$
 $Z_{T_p} = Q_\ell^2 R_\ell = (40)^2 20 \Omega = 32 \text{ k}\Omega \gg 1 \text{ k}\Omega$

At resonance, $V_o = \frac{32 \text{ k}\Omega V_i}{32 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.97 V_i$

and $A_v = \frac{V_o}{V_i} = 0.97$

For the low cutoff frequency note solution to Problem 30:

$$f_1^2 + \frac{1}{2\pi RC} f_1 - \frac{1}{4\pi^2 LC} = 0$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(20 \text{ kHz})(400 \Omega)} = 19.9 \text{ nF}$$

$$L = \frac{X_L}{2\pi f} = \frac{400 \Omega}{2\pi(20 \text{ kHz})} = 3.18 \text{ mH}$$

Substituting into the above equation and solving

$$f_1 = 16.4 \text{ kHz}$$

with $\frac{BW}{2} = 20 \text{ kHz} - 16.4 \text{ kHz} = 3.6 \text{ kHz}$

and $BW = 2(3.6 \text{ kHz}) = 7.2 \text{ kHz}$

$$Q_p = \frac{f_p}{BW} = \frac{20 \text{ kHz}}{7.2 \text{ kHz}} = 2.78$$

b. —

c. At resonance

$$Z_{T_p} = 32 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 24.24 \text{ k}\Omega$$

$$\text{with } V_o = \frac{24.24 \text{ k}\Omega V_i}{24.24 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.96 V_i$$

$$\text{and } A_v = \frac{V_o}{V_i} = 0.96 \text{ vs } 0.97 \text{ above}$$

At frequencies to the right and left of f_p , the impedance Z_{T_p} will decrease and be affected less and less by the parallel 100 kΩ load. The characteristics, therefore, are only slightly affected by the 100 kΩ load.

d. At resonance

$$Z_{T_p} = 32 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 12.31 \text{ k}\Omega$$

$$\text{with } V_o = \frac{12.31 \text{ k}\Omega V_i}{12.31 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.925 V_i \text{ vs } 0.97 V_i \text{ above}$$

At frequencies to the right and left of f_p , the impedance of each frequency will actually be less due to the parallel 20 kΩ load. The effect will be to narrow the resonance curve and decrease the bandwidth with an increase in Q_p .

33. a. $f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(400 \mu\text{H})(120 \text{ pF})}} = 726.44 \text{ kHz}$ (band-stop)

$$X_{L_s} \angle 90^\circ + (X_{L_p} \angle 90^\circ \parallel X_C \angle -90^\circ) = 0$$

$$jX_{L_s} + \frac{(X_{L_p} \angle 90^\circ)(X_C \angle -90^\circ)}{jX_{L_p} - jX_C} = 0$$

$$jX_{L_s} + \frac{X_{L_p} X_C}{j(X_{L_p} - X_C)} = 0$$

$$jX_{L_s} - j \frac{X_{L_p} X_C}{(X_{L_p} - X_C)} = 0$$

$$X_{L_s} - \frac{X_{L_p} X_C}{X_{L_p} - X_C} = 0$$

$$X_{L_s} X_C - X_{L_s} X_{L_p} + X_{L_p} X_C = 0$$

$$\begin{aligned}\frac{\omega L_s}{\omega C} - \omega L_s + \frac{\omega L_p}{\omega C} &= 0 \\ L_s L_p \omega^2 - \frac{1}{C} [L_s + L_p] &= 0 \\ \omega &= \sqrt{\frac{L_s + L_p}{C L_s L_p}} \\ f &= \frac{1}{2\pi} \sqrt{\frac{L_s + L_p}{C L_s L_p}} = \frac{1}{2\pi} \sqrt{\frac{460 \times 10^{-6}}{28.8 \times 10^{-19}}} = 2.01 \text{ MHz (pass-band)}\end{aligned}$$


34. a. $f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L_s = \frac{1}{4\pi^2 f_s^2 C} = \frac{1}{4\pi^2 (100 \text{ kHz})^2 (200 \text{ pF})} = 12.68 \text{ mH}$
 $X_L = 2\pi f L = 2\pi (30 \text{ kHz})(12.68 \text{ mH}) = 2388.91 \Omega$
 $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi (30 \text{ kHz})(200 \text{ pF})} = 26.54 \text{ k}\Omega$
 $X_C - X_L = 26.54 \text{ k}\Omega - 2388.91 \Omega = 24.15 \text{ k}\Omega(C)$
 $X_{L_p} = X_{C_{(\text{net})}} = 24.15 \text{ k}\Omega$
 $L_p = \frac{X_L}{2\pi f} = \frac{24.15 \text{ k}\Omega}{2\pi (30 \text{ kHz})} = 128.19 \text{ mH}$

35. a. At low frequencies, $L_1, L_2 \Rightarrow$ short circuits and $C \Rightarrow$ open circuit. The result is \mathbf{V}_L very close to \mathbf{V}_i at low frequencies. At high frequencies, X_C shorts to ground and X_{L_2} has a high impedance so \mathbf{V}_L approaches 0 V.

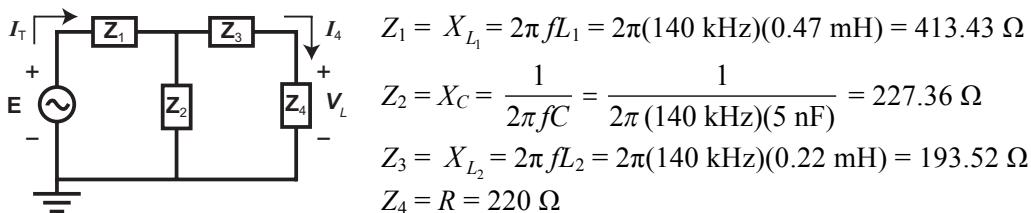b. Determine frequency when $R_L = X_{L_2}$ due to voltage divide action.

$$X_L = R \Rightarrow 2\pi f L = R \Rightarrow f = \frac{R}{2\pi L} = \frac{220 \Omega}{2\pi(0.22 \text{ mH})} = 159.15 \text{ kHz}$$

Since f_c less than split between X_L and R_L let us try 140 kHz.




$$\begin{aligned}\mathbf{Z}_T &= \mathbf{Z}_1 \parallel (\mathbf{Z}_3 + \mathbf{Z}_4) \\ &= j413.43 \Omega + \frac{(227.36 \Omega \angle -90^\circ)(220 \Omega + j193.52 \Omega)}{(-j227.36 \Omega) + (220 \Omega + j193.52 \Omega)} \\ &= j413.43 \Omega + \frac{(227.36 \Omega \angle -90^\circ)(293 \Omega \angle 41.34^\circ)}{220 \Omega - j33.84 \Omega} \\ &= j413.43 \Omega + \frac{66.61 \text{ k}\Omega \angle -48.66^\circ}{222.59 \angle -8.74^\circ} \\ &= j413.43 \Omega + 299.25 \Omega \angle -39.92^\circ\end{aligned}$$

$$\begin{aligned}
&= j413.43 \Omega + 229.51 \Omega - j192.03 \Omega \\
&= 229.51 \Omega + j221.40 \Omega \\
\mathbf{Z}_T &= 318.89 \Omega \angle 43.97^\circ
\end{aligned}$$

$$\mathbf{I}_T = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{10 \text{ V} \angle 0^\circ}{318.89 \Omega \angle 43.97^\circ} = 31.36 \text{ mA} \angle -43.97^\circ$$

$$\begin{aligned}
\mathbf{I}_4 &= \frac{\mathbf{Z}_2 \mathbf{I}_T}{\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4} = \frac{(227.36 \Omega \angle -90^\circ)(31.36 \text{ mA} \angle -43.97^\circ)}{-j227.36 \Omega + j193.52 \Omega + 220 \Omega} \\
&= \frac{7.13 \text{ A} \angle -133.97^\circ}{220 - j33.84^\circ} = \frac{7.13 \text{ A} \angle -133.97^\circ}{222.59 \angle -8.74^\circ} \\
&= 32.03 \text{ mA} \angle -125.23^\circ \\
\mathbf{V}_L &= \mathbf{I}_4 \mathbf{Z}_4 = (32.03 \text{ mA} \angle -125.23^\circ)(220 \Omega \angle 0^\circ) \\
&= 7.05 \text{ V} \angle -125.23^\circ
\end{aligned}$$

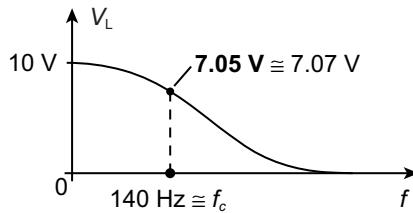

36. a. At very low frequencies $X_C \Rightarrow$ open-circuit and $X_L \Rightarrow$ short-circuit resulting in $\mathbf{V}_L \Rightarrow 0 \text{ V}$.

At very high frequencies $X_C \Rightarrow$ short-circuit and $X_L \Rightarrow$ open-circuit resulting in $\mathbf{V}_L \Rightarrow 20 \text{ V}$.

- b. Utilize $X_{L_2} = X_C$ as a starting point to establish a frequency of application:

$$2\pi f L_2 = \frac{1}{2\pi f C} \Rightarrow f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(100 \text{ mH})(0.12 \mu\text{F})}} = 1.45 \text{ kHz}$$

Try $f = 1 \text{ kHz}$:


$$\begin{aligned}
X_C &= \frac{1}{2\pi f C} = \frac{1}{2\pi (1 \text{ kHz})(0.12 \mu\text{F})} = 1.33 \text{ k}\Omega \\
X_{L_2} &= 2\pi f L_2 = 2\pi(1 \text{ kHz})(100 \text{ mH}) = 628.32 \Omega \\
\mathbf{Z}' &= \mathbf{X}_{L_2} \parallel \mathbf{R}_L = (628.32 \Omega \angle 90^\circ) \parallel (1.2 \text{ k}\Omega \angle 0^\circ) \\
&= \frac{(628.32 \Omega \angle 90^\circ)(1.2 \text{ k}\Omega \angle 0^\circ)}{1.2 \text{ k}\Omega + j628.32 \Omega} = \frac{753.98 \times 10^3 \Omega \angle 90^\circ}{1.35 \times 10^3 \angle 27.64^\circ} \\
\mathbf{Z}' &= 558.50 \Omega \angle 62.36^\circ
\end{aligned}$$

$$\begin{aligned}
\mathbf{V}_L &= \frac{\mathbf{Z}' \cdot \mathbf{E}}{\mathbf{Z}' + \mathbf{X}_C} = \frac{(558.50 \Omega \angle 62.36^\circ)(20 \text{ V} \angle 0^\circ)}{558.50 \Omega \angle 62.36^\circ - j1.33 \text{ k}\Omega} \\
&= \frac{11.17 \times 10^3 \text{ V} \angle 62.36^\circ}{2.591 + j494.76 - j1.33 \text{ k}\Omega}
\end{aligned}$$

$$= \frac{11.17 \times 10^3 \text{ V} \angle 62.36^\circ}{2.591 - j835} = \frac{11.17 \times 10^3 \text{ V} \angle 62.36^\circ}{874.28 \angle -72.76^\circ}$$

$$\mathbf{V}_L = 12.78 \text{ V} \angle 135.12^\circ$$

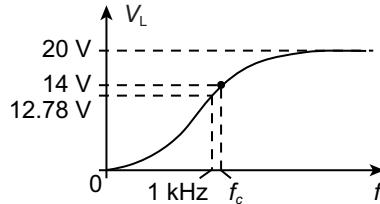
which is very close to the cutoff value of $0.707(20 \text{ V}) = 14.14 \text{ V}$. The cutoff frequency will be slightly higher than 1 kHz.




37. a. At very low frequencies $X_L \Rightarrow$ short-circuit and $X_C \Rightarrow$ open-circuit. The result is $\mathbf{V}_L \Rightarrow 60 \text{ V}$.

At very high frequencies $X_L \Rightarrow$ open-circuit and $X_C \Rightarrow$ short-circuit. The result is $\mathbf{V}_L \Rightarrow 0 \text{ V}$.


- b. Defining impedances:

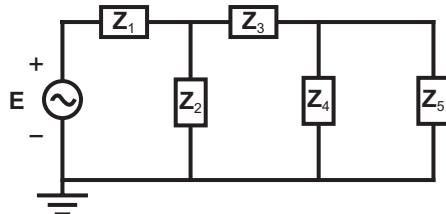

Source conversion:

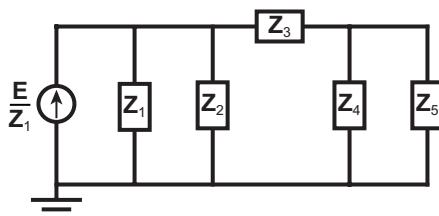

New definition:

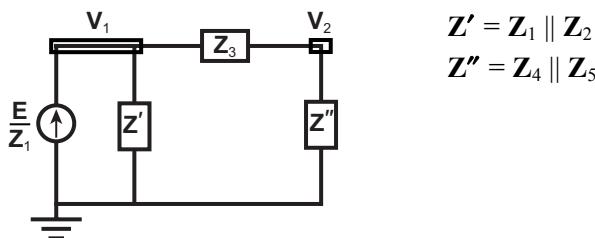

Applying Nodal Analysis

$$\mathbf{V}_1 \left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] - \frac{1}{\mathbf{Z}_3} \mathbf{V}_2 = \frac{\mathbf{E}}{\mathbf{Z}_1}$$

$$\mathbf{V}_2 \left[\frac{1}{\mathbf{Z}''} + \frac{1}{\mathbf{Z}_3} \right] - \frac{1}{\mathbf{Z}_3} \mathbf{V}_1 = 0$$

$$\begin{aligned}\mathbf{V}_1 \left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] - \frac{1}{\mathbf{Z}_3} \mathbf{V}_2 &= \frac{\mathbf{E}}{\mathbf{Z}_1} \\ -\mathbf{V}_1 \left[\frac{1}{\mathbf{Z}_3} \right] + \left[\frac{1}{\mathbf{Z}''} + \frac{1}{\mathbf{Z}_3} \right] \mathbf{V}_2 &= 0\end{aligned}$$

$$\begin{aligned}\mathbf{V}_L &= \mathbf{V}_2 = \begin{vmatrix} \frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} & \frac{\mathbf{E}}{\mathbf{Z}'} \\ -\frac{1}{\mathbf{Z}_3} & 0 \end{vmatrix} = \frac{\left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] [0] - \left[\frac{\mathbf{E}}{\mathbf{Z}_1} \right] \left[-\frac{1}{\mathbf{Z}_3} \right]}{\left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] \left[\frac{1}{\mathbf{Z}''} + \frac{1}{\mathbf{Z}_3} \right] - \left[-\frac{1}{\mathbf{Z}_3} \right] \left[-\frac{1}{\mathbf{Z}_3} \right]} \\ &= \frac{\mathbf{E} / \mathbf{Z}_1 \mathbf{Z}_3}{\left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] \left[\frac{1}{\mathbf{Z}''} + \frac{1}{\mathbf{Z}_3} \right] - \frac{1}{\mathbf{Z}_3^2}}\end{aligned}$$

Choosing $X_C = \frac{1}{3} X_L$ to bring \mathbf{V}_L down to 0.707 level

$$\frac{1}{2\pi fC} = \frac{1}{3} 2\pi fL \text{ and } f = \frac{\sqrt{3}}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(1 \text{ mH})(5 \text{ nF})}} = 123.13 \text{ kHz}$$

Using $f = 120 \text{ kHz}$

$$\mathbf{Z}_1: X_L = 2\pi fL = 2\pi(120 \text{ kHz})(1 \text{ mH}) = 754 \Omega \angle 90^\circ$$

$$\mathbf{Z}_2: X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(120 \text{ kHz})(5 \text{ nF})} = 265 \Omega \angle -90^\circ$$

$$\mathbf{Z}_3: 754 \Omega \angle 90^\circ$$

$$\mathbf{Z}_4: 265 \Omega \angle -90^\circ$$

$$\mathbf{Z}_5: 2.2 \text{ k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_1 \cdot \mathbf{Z}_3 = (754 \Omega \angle 90^\circ)(754 \Omega \angle 90^\circ) = 568.52 \times 10^3 \Omega^2 \angle 180^\circ$$

$$\frac{\mathbf{E}}{\mathbf{Z}_1 \mathbf{Z}_3} = \frac{60 \text{ V} \angle 0^\circ}{568.52 \times 10^3 \Omega^2 \angle 180^\circ} = 105.5 \times 10^{-6} \angle -180^\circ$$

$$\begin{aligned}\mathbf{Z}' &= \mathbf{Z}_1 \parallel \mathbf{Z}_2 = \frac{(754 \Omega \angle 90^\circ)(265 \Omega \angle -90^\circ)}{+j754 \Omega - j265 \Omega} \\ &= \frac{199.81 \times 10^3 \Omega \angle 0^\circ}{489 \angle 90^\circ} \\ &= 408.61 \Omega \angle -90^\circ\end{aligned}$$


$$\begin{aligned}
\mathbf{Z}'' &= \mathbf{Z}_4 \parallel \mathbf{Z}_5 = \frac{(265 \Omega \angle -90^\circ)(2.2 \text{ k}\Omega \angle 0^\circ)}{2.2 \text{ k}\Omega - j265 \Omega} = \frac{538 \times 10^3 \Omega \angle -90^\circ}{2.2 \angle -6.87^\circ} \\
&= 262.61 \Omega \angle -83.13^\circ \\
\left[\frac{1}{\mathbf{Z}'} + \frac{1}{\mathbf{Z}_3} \right] &= \left[\frac{1}{408.61 \Omega \angle -90^\circ} + \frac{1}{754 \Omega \angle 90^\circ} \right] \\
&= 2.44 \times 10^{-3} \angle 90^\circ + 1.33 \times 10^{-3} \angle -90^\circ \\
&= j2.44 \times 10^{-3} - j1.33 \times 10^{-3} \\
&= j1.11 \times 10^{-3} \\
\left[\frac{1}{\mathbf{Z}''} + \frac{1}{\mathbf{Z}_3} \right] &= \frac{1}{262.61 \angle -83.13^\circ} + \frac{1}{754 \Omega \angle 90^\circ} \\
&= 3.81 \times 10^{-3} \angle 83.13^\circ + 1.33 \times 10^{-3} \angle -90^\circ \\
&= 0.455 \times 10^{-3} + j3.78 \times 10^{-3} - j1.33 \times 10^{-3} \\
&= 0.455 \times 10^{-3} + j2.54 \times 10^{-3} \\
&= 2.49 \times 10^{-3} \angle 79.48^\circ \\
[1.11 \times 10^{-3} \angle 90^\circ][2.49 \times 10^{-3} \angle 79.48^\circ] &= 2.76 \times 10^{-6} \angle 169.48^\circ
\end{aligned}$$

$$\begin{aligned}
\mathbf{Z}_3^2 &= (754 \Omega \angle 90^\circ)(754 \Omega \angle 90^\circ) \\
&= 5.69 \times 10^{-6} \angle 180^\circ
\end{aligned}$$


$$\frac{1}{\mathbf{Z}_3^2} = \frac{1}{5.69 \times 10^{-6} \angle 180^\circ} = 0.176 \times 10^{-6} \angle -180^\circ$$

and
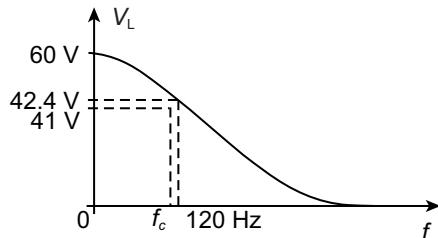
$$\begin{aligned}
\mathbf{V}_L &= \frac{105.5 \times 10^6 \angle -180^\circ}{2.58 \times 10^6 \angle 168.8^\circ} \\
&= 40.89 \text{ V} \angle -11.2^\circ \\
&\approx 41 \text{ V} \text{ which is very close to } 0.707(60 \text{ V}) = 42.42 \text{ V}
\end{aligned}$$


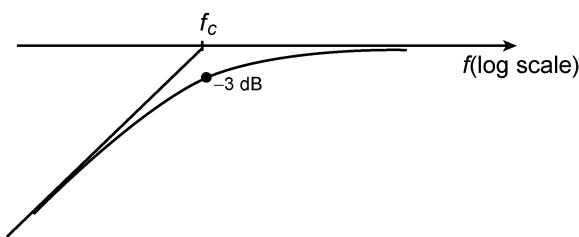
$$38. \text{ a, b. } f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(0.47 \text{ k}\Omega)(0.047 \mu\text{F})} = 7.2 \text{ kHz}$$



c. $f = \frac{1}{2}f_c$: $A_{v_{dB}} = 20 \log_{10} \frac{1}{\sqrt{1+(f_c/f)^2}} = 20 \log_{10} \frac{1}{\sqrt{1+(2)^2}} = -7 \text{ dB}$

$f = 2f_c$: $A_{v_{dB}} = 20 \log_{10} \frac{1}{\sqrt{1+(0.5)^2}} = -0.969 \text{ dB}$


$f = \frac{1}{10}f_c$: $A_{v_{dB}} = 20 \log_{10} \frac{1}{\sqrt{1+(10)^2}} = -20.04 \text{ dB}$

$f = 10f_c$: $A_{v_{dB}} = 20 \log_{10} \frac{1}{\sqrt{1+(0.1)^2}} = -0.043 \text{ dB}$

d. $f = \frac{1}{2}f_c$: $A_v = \frac{1}{\sqrt{1+(f_c/f)^2}} = \frac{1}{\sqrt{1+(2)^2}} = 0.447$

$f = 2f_c$: $A_v = \frac{1}{\sqrt{1+(0.5)^2}} = 0.894$


e.

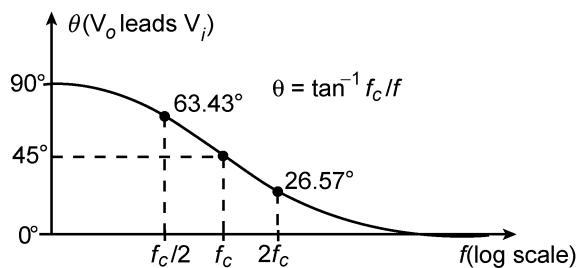

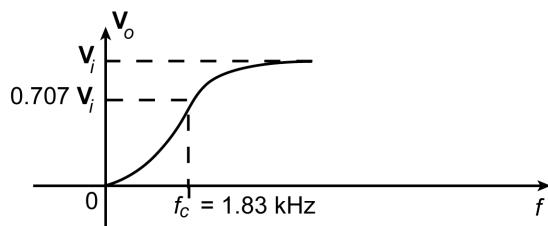
39. a. $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(6.8 \text{ k}\Omega \parallel 12 \text{ k}\Omega)0.02 \mu\text{F}} = \frac{1}{2\pi(4.34 \text{ k}\Omega)(0.02 \mu\text{F})} = 1.83 \text{ kHz}$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1+(f_c/f)^2}}$$


and $V_o = \left(\frac{1}{\sqrt{1+(f_c/f)^2}} \right) V_i$



b.

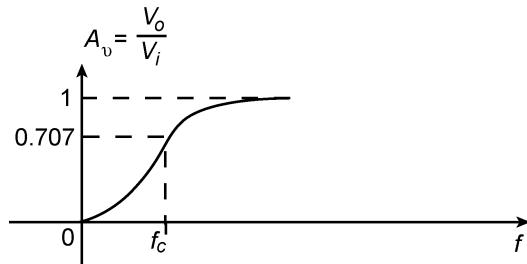

c. & d.

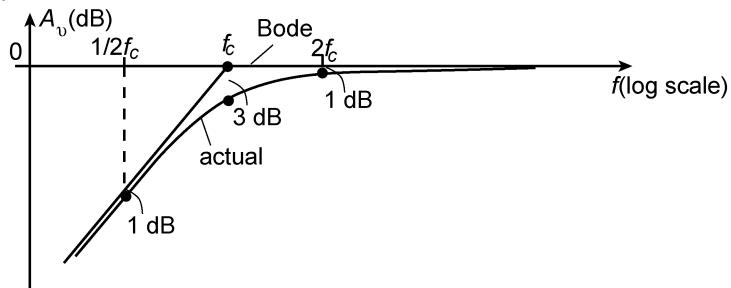

e. Remember the log scale! $1.5f_c$ is not midway between f_c and $2f_c$


$$A_{v_{\text{dB}}} = 20 \log_{10} A_v$$

$$-1.5 = 20 \log_{10} A_v$$

$$-0.075 = \log_{10} A_v$$

$$A_v = \frac{V_o}{V_i} = \mathbf{0.84}$$

f. $\theta = \tan^{-1} f/f_c$

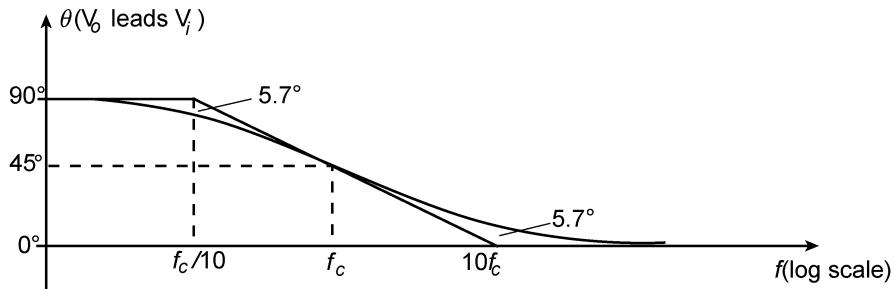

40. a, b. $A_v = \frac{V_o}{V_i} = A_v \angle \theta = \frac{1}{\sqrt{1 + (f/f_c)^2}} \angle -\tan^{-1} f/f_c$
 $f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(12 \text{ k}\Omega)(1000 \text{ pF})} = \mathbf{13.26 \text{ kHz}}$

c. $f = f_c/2 = 6.63 \text{ kHz}$

$$A_{v_{\text{dB}}} = 20 \log_{10} \frac{1}{\sqrt{1+(0.5)^2}} = \mathbf{-0.97 \text{ dB}}$$

$$f = 2f_c = 26.52 \text{ kHz}$$

$$A_{v_{\text{dB}}} = 20 \log_{10} \frac{1}{\sqrt{1+(2)^2}} = \mathbf{-6.99 \text{ dB}}$$

$$f = f_c/10 = 1.326 \text{ kHz}$$

$$A_{v_{\text{dB}}} = 20 \log_{10} \frac{1}{\sqrt{1+(0.1)^2}} = \mathbf{-0.04 \text{ dB}}$$



$$f = 10f_c = 132.6 \text{ kHz}$$

$$A_{v_{\text{dB}}} = 20 \log_{10} \frac{1}{\sqrt{1+(10)^2}} = \mathbf{-20.04 \text{ dB}}$$

d. $f = f_c/2: A_v = \frac{1}{\sqrt{1+(0.5)^2}} = \mathbf{0.894}$

$$f = 2f_c: A_v = \frac{1}{\sqrt{1+(2)^2}} = \mathbf{0.447}$$

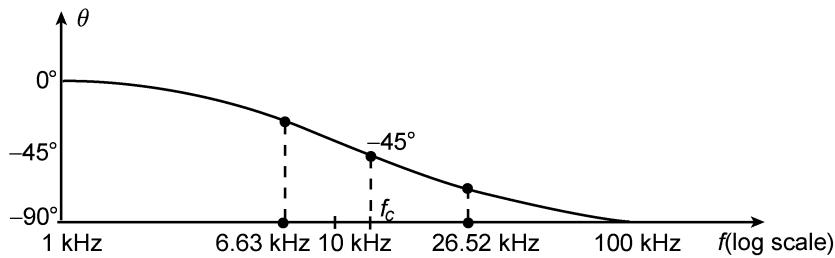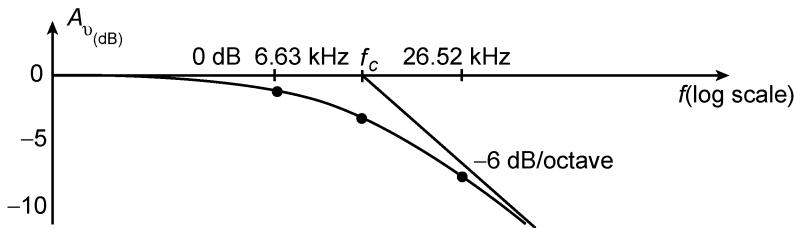e. $\theta = \tan^{-1} f/f_c$
 $f = f_c/2: \theta = -\tan^{-1} 0.5 = -26.57^\circ$
 $f = f_c: \theta = -\tan^{-1} 1 = -45^\circ$
 $f = 2f_c: \theta = -\tan^{-1} 2 = -63.43^\circ$



41. a. $R_2 \parallel X_C = \frac{(R_2)(-jX_C)}{R_2 - jX_C} = -j \frac{R_2 X_C}{R_2 - jX_C}$

$$\mathbf{V}_o = \frac{\left(\frac{-jR_2 X_C}{R_2 - jX_C} \right) \mathbf{V}_i}{R_l - j \frac{R_2 X_C}{R_2 - jX_C}} = -j \frac{R_2 X_C \mathbf{V}_i}{R_l(R_2 - jX_C) - jR_2 X_C}$$

$$\begin{aligned}
&= \frac{-jR_2X_C\mathbf{V}_i}{R_lR_2 - jR_lX_C - jR_2X_C} = \frac{-jR_2X_C\mathbf{V}_i}{R_lR_2 - j(R_l + R_2)X_C} \\
&= \frac{R_2X_C\mathbf{V}_i}{jR_lR_2 + (R_l + R_2)X_C} = \frac{R_2\mathbf{V}_i}{j\frac{R_lR_2}{X_C} + (R_l + R_2)} \\
&= \frac{R_2\mathbf{V}_i}{R_l + R_2 + j\frac{R_lR_2}{X_C}} = \frac{\left(\frac{R_2}{R_l + R_2}\right)\mathbf{V}_i}{1 + j\left(\frac{R_lR_2}{R_l + R_2}\right)\frac{1}{X_C}}
\end{aligned}$$

and $\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\frac{R_2}{R_l + R_2}}{1 + j\omega\left(\frac{R_lR_2}{R_l + R_2}\right)C}$

or $\mathbf{A}_v = \frac{R_2}{R_l + R_2} \left[\frac{1}{1 + j2\pi f(R_l \parallel R_2)C} \right]$

defining $f_c = \frac{1}{2\pi(R_l \parallel R_2)C}$

$$\mathbf{A}_v = \frac{R_2}{R_l + R_2} \left[\frac{1}{1 + jf/f_c} \right]$$


and $\mathbf{A}_v = \frac{R_2}{R_l + R_2} \left[\frac{1}{\sqrt{1 + (f/f_c)^2}} \angle -\tan^{-1} f/f_c \right]$

with $|V_o| = \frac{R_2}{R_l + R_2} \left[\frac{1}{\sqrt{1 + (f/f_c)^2}} \right] |V_i|$


for $f \ll f_c$, $V_o = \frac{R_2}{R_l + R_2} V_i = \frac{27 \text{ k}\Omega}{4.7 \text{ k}\Omega + 27 \text{ k}\Omega} V_i = 0.852 V_i$

at $f = f_c$: $V_o = 0.852[0.707]V_i = 0.602V_i$

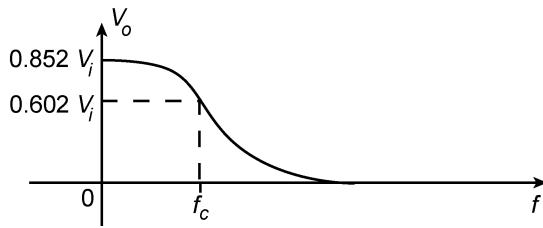
$$f_c = \frac{1}{2\pi(R_l \parallel R_2)C} = \frac{1}{2\pi(4.7 \text{ k}\Omega \parallel 27 \text{ k}\Omega)0.039 \mu\text{F}} = 1.02 \text{ kHz}$$



b.

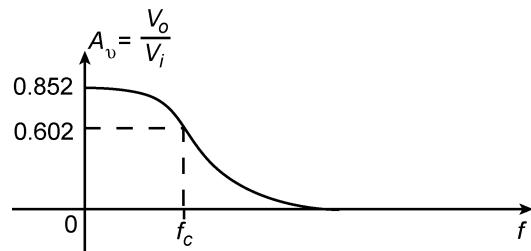

c. & d.

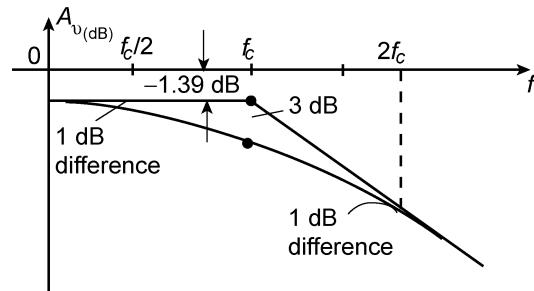

$$\begin{aligned} -20 \log_{10} \frac{R_1 + R_2}{R_2} &= -20 \log_{10} \frac{4.7 \text{ k}\Omega + 27 \text{ k}\Omega}{27 \text{ k}\Omega} \\ &= -20 \log_{10} 1.174 = -1.39 \text{ dB} \end{aligned}$$

e. $A_{v_{\text{dB}}} \approx -1.39 \text{ dB} - 0.5 \text{ dB} = -1.89 \text{ dB}$


$$A_{v_{\text{dB}}} = 20 \log_{10} A_v$$

$$-1.89 = 20 \log_{10} A_v$$


$$0.0945 = \log_{10} A_v$$

$$A_v = \frac{V_o}{V_i} = \mathbf{0.80}$$

f. $\theta = -\tan^{-1} f/f_c$

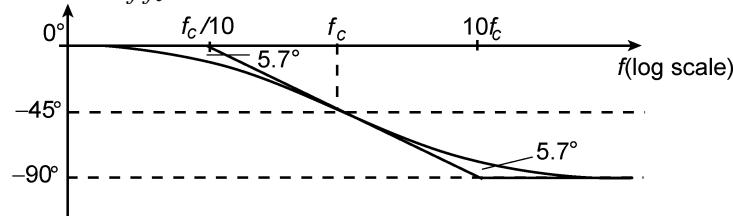

42.

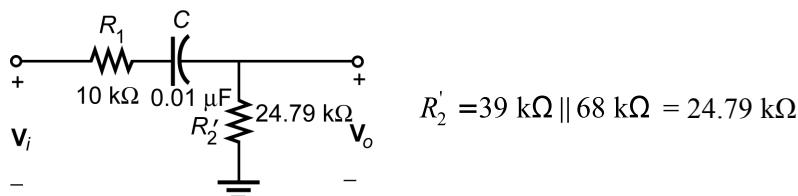


a. From Section 21.11,

$$A_v = \frac{V_o}{V_i} = \frac{jf/f_1}{1 + jf/f_c}$$

$$f_1 = \frac{1}{2\pi R'_2 C} = \frac{1}{2\pi(24.79 \text{ k}\Omega)(0.01 \mu\text{F})} = 642.01 \text{ Hz}$$
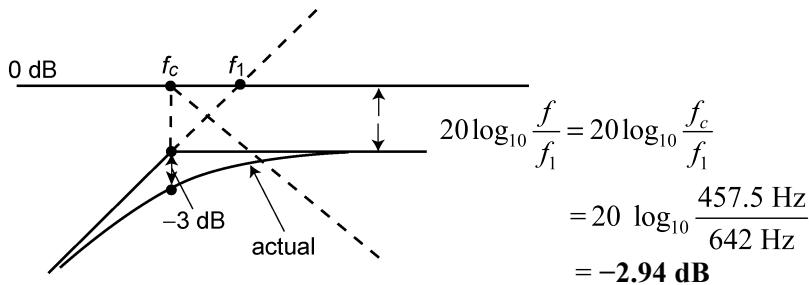
$$f_c = \frac{1}{2\pi(R_l + R'_2)C} = \frac{1}{2\pi(10 \text{ k}\Omega + 24.79 \text{ k}\Omega)(0.01 \mu\text{F})} = 457.47 \text{ Hz}$$



b. $\theta = 90^\circ - \tan^{-1} \frac{f}{f_1} = + \tan^{-1} \frac{f_1}{f}$

$$f = f_1: \quad \theta = 45^\circ$$


$$f = f_c: \quad \theta = 54.52^\circ$$

$$f = \frac{1}{2}f_1 = 321 \text{ Hz}, \theta = 63.44^\circ$$


$$f = \frac{1}{10}f_1 = 64.2 \text{ Hz}, \theta = 84.29^\circ$$

$$f = 2f_1 = 1,284 \text{ Hz}, \theta = 26.57^\circ$$
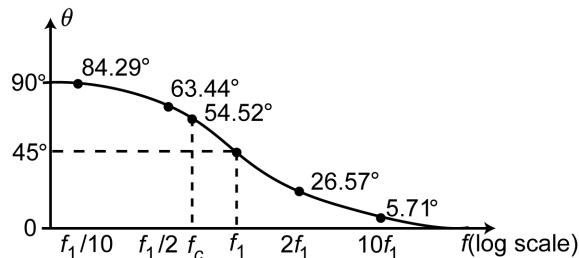
$$f = 10f_1 = 6420 \text{ Hz}, \theta = 5.71^\circ$$




43. a.

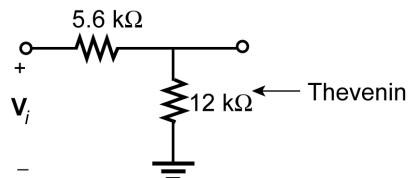


$$V_{Th} = \frac{12 \text{ k}\Omega V_i}{12 \text{ k}\Omega + 5.6 \text{ k}\Omega} = 0.682 V_i$$
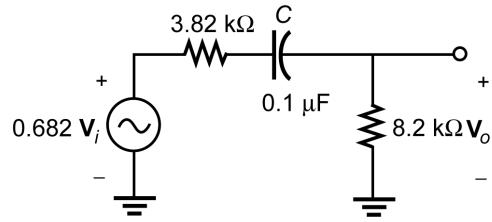
$$R_{Th} = 5.6 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 3.82 \text{ k}\Omega$$



$f = \infty$ Hz: ($C \Rightarrow$ short circuit)
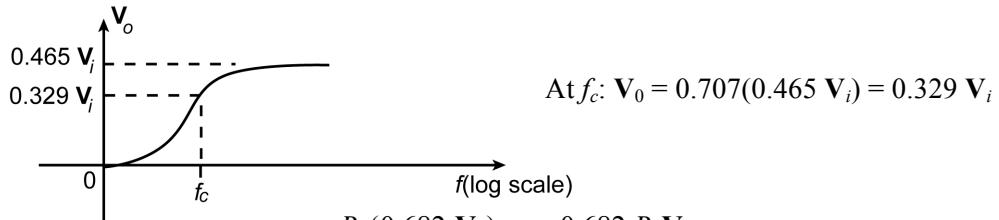
$$V_o = \frac{8.2 \text{ k}\Omega (0.682 \text{ V}_i)}{8.2 \text{ k}\Omega + 3.82 \text{ k}\Omega} = 0.465 \text{ V}_i$$




$$\text{At } f_c: V_o = 0.707(0.465 \text{ V}_i) = 0.329 \text{ V}_i$$

$$\text{voltage-divider rule: } V_o = \frac{R_2(0.682 \text{ V}_i)}{R_1 + R_2 - jX_C} = \frac{0.682 R_2 \text{ V}_i}{R_1 + R_2 - jX_C}$$

$$\text{and } A_v = \frac{V_o}{V_i} = \frac{0.682 R_2}{R_1 + R_2 - jX_C} = \frac{j2\pi f(0.682 R_2)C}{1 + j2\pi f(R_1 + R_2)C}$$


$$\text{so that } A_v = \frac{jf/f_1}{1 + jf/f_c} \text{ with } f_1 = \frac{1}{2\pi 0.682 R_2 C} = \frac{1}{2\pi 0.682(8.2 \text{ k}\Omega)(0.1 \mu\text{F})} \\ = 284.59 \text{ Hz}$$
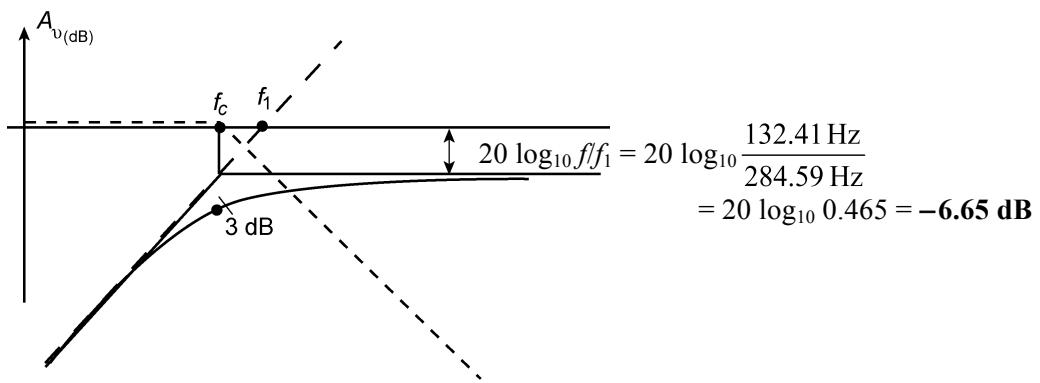
$$\text{and } f_c = \frac{1}{2\pi(R_1 + R_2)C} = \frac{1}{2\pi(3.82 \text{ k}\Omega + 8.2 \text{ k}\Omega)(0.1 \mu\text{F})} \\ = \mathbf{132.41 \text{ Hz}}$$



$$\text{b. } \theta = 90^\circ - \tan^{-1} f/f_c = +\tan^{-1} f_c/f = \tan^{-1} 132.6 \text{ Hz}/f$$



or

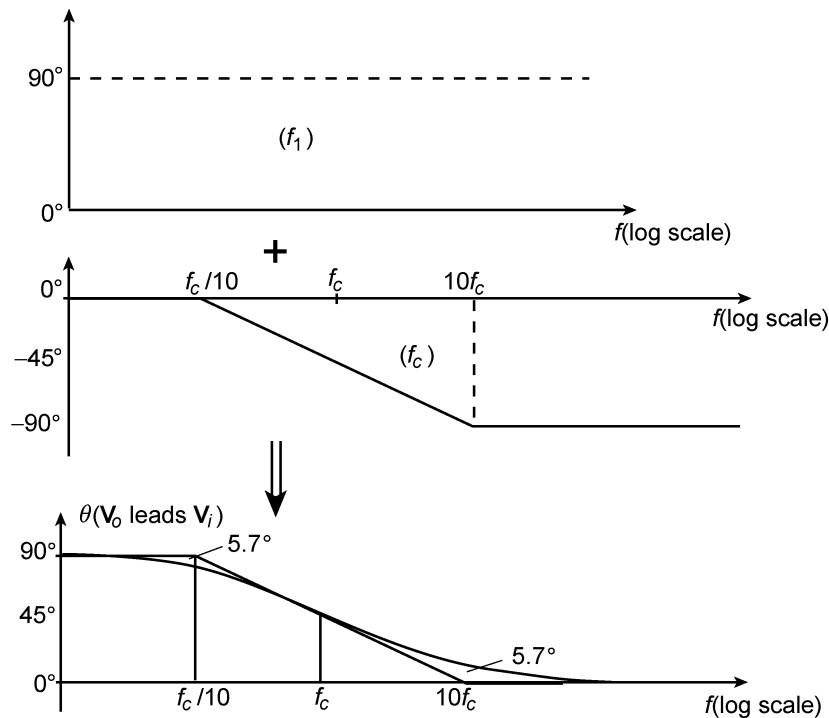

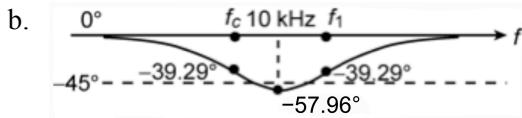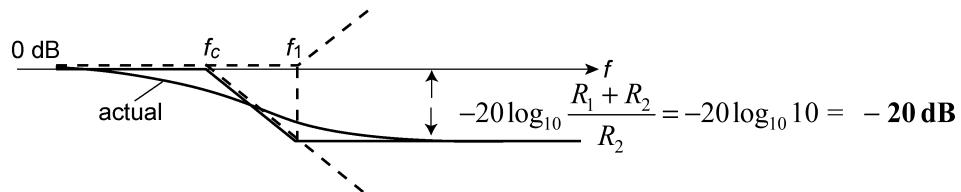44. a. $A_v = \frac{1+j\frac{f}{f_1}}{1+j\frac{f}{f_c}}$

$$f_1 = \frac{1}{2\pi R_2 C} = \frac{1}{2\pi(10 \text{ k}\Omega)(800 \text{ pF})} = 19.89 \text{ kHz}$$

$$f_c = \frac{1}{2\pi(R_l + R_2)C} = \frac{1}{2\pi(10 \text{ k}\Omega + 91 \text{ k}\Omega)(800 \text{ pF})} = 1.97 \text{ kHz}$$



$$\theta = \tan^{-1} \frac{f}{f_1} - \tan^{-1} \frac{f}{f_c}$$

$$f = 10 \text{ kHz}$$

$$\theta = \tan^{-1} \frac{10 \text{ kHz}}{19.89 \text{ kHz}} - \tan^{-1} \frac{10 \text{ kHz}}{1.97 \text{ kHz}} = 29.66^\circ - 87.62^\circ = -57.96^\circ$$

$$f = f_c : (f_1 = 10 f_c)$$

$$\theta = \tan^{-1} \frac{f_c}{10 f_c} - \tan^{-1} \frac{f_c}{f_c} = \tan^{-1} 0.1 \tan^{-1} 1 = 5.71^\circ - 45^\circ = -39.29^\circ$$

45. a. R_1 no effect!
Note Section 22.12.

$$\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1 + j(f/f_1)}{1 + j(f/f_c)}$$

$$f_1 = \frac{1}{2\pi(5.6 \text{ k}\Omega)(0.01 \mu\text{F})} = 2.84 \text{ kHz}$$

$$f_c = \frac{1}{2\pi(12 \text{ k}\Omega + 5.6 \text{ k}\Omega)(0.01 \mu\text{F})} = 904.3 \text{ Hz}$$

Note Fig. 22.65.

Asymptote at 0 dB from $0 \rightarrow f_c$
 -6 dB/octave from f_c to f_1
 -9.95 dB from f_1 on $\left(-20 \log \frac{12 \text{ k}\Omega + 5.6 \text{ k}\Omega}{5.6 \text{ k}\Omega} = -9.5 \text{ dB} \right)$

- (b) Note Fig. 22.67.


From 0° to -26.50° at f_c and f_1
 $\theta = \tan^{-1} f/f_1 - \tan^{-1} f/f_c$
At $f = 1500 \text{ Hz}$ (between f_c and f_1)
 $\theta = \tan^{-1} 1500 \text{ Hz}/2.84 \text{ kHz} - \tan^{-1} 1500 \text{ Hz}/904.3 \text{ Hz}$
 $= 27.83^\circ - 58.92^\circ = -31.09^\circ$

46. a. $\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1 - jf/f}{1 - jf_c/f}$


$$f_1 = \frac{1}{2\pi R_1 C} = \frac{1}{2\pi(3.3 \text{ k}\Omega)(0.05 \mu\text{F})} = 964.58 \text{ Hz}$$

$$f_c = \frac{1}{2\pi(R_1 \parallel R_2)C} = \frac{1}{2\pi \underbrace{(3.3 \text{ k}\Omega \parallel 0.47 \text{ k}\Omega)(0.05 \mu\text{F})}_{0.411 \text{ k}\Omega}} = 7.74 \text{ kHz}$$
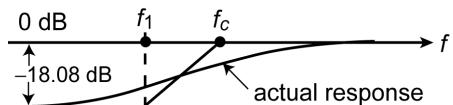
$$-20 \log_{10} \frac{R_1 + R_2}{R_2} = -20 \log_{10} \frac{3.3 \text{ k}\Omega + 0.47 \text{ k}\Omega}{0.47 \text{ k}\Omega} = -20 \log_{10} 8.02 = -18.08 \text{ dB}$$



b.

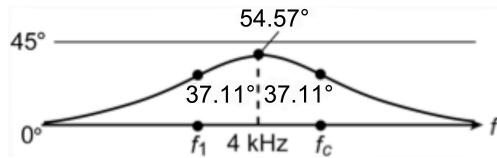

$$\theta = -\tan^{-1} \frac{f_1}{f} + \tan^{-1} \frac{f_c}{f}$$

$$f = f_1 : \theta = -\tan^{-1} \frac{f_1}{f_1} + \tan^{-1} \frac{f_c}{f_1}$$

$$= -\tan^{-1} 1 + \tan^{-1} \frac{7.74 \text{ kHz}}{964.58 \text{ Hz}}$$

$$= -45^\circ + 92.1^\circ = \mathbf{47.1^\circ}$$

$$f = 4 \text{ kHz} : \theta = -\tan^{-1} \frac{964.58 \text{ Hz}}{4 \text{ kHz}} + \tan^{-1} \frac{7.74 \text{ kHz}}{4 \text{ kHz}}$$

$$= -15.06^\circ + 69.63^\circ = \mathbf{54.57^\circ}$$


$$f = f_c : \theta = -\tan^{-1} \frac{964.58 \text{ Hz}}{7.74 \text{ kHz}} + \tan^{-1} \frac{f_c}{f_c}$$

$$= -\tan^{-1} 0.1246 + \tan^{-1} 1$$

$$= -7.89^\circ + 45^\circ = \mathbf{37.11^\circ}$$

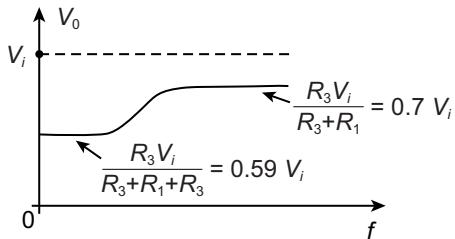47. $f = 0 \text{ Hz}: V_o = \frac{R_3 V_i}{R_3 + R_1 + R_2} = \frac{4.7 \text{ k}\Omega V_i}{4.7 \text{ k}\Omega + 2 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 0.59 V_i$

$f = \text{high}: V_o = \frac{R_3 V_i}{R_3 + R_1} = \frac{4.7 \text{ k}\Omega V_i}{4.7 \text{ k}\Omega + 2 \text{ k}\Omega} = 0.7 V_i$



$$\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R_3}{R_3 + R_1 + R_2 \parallel X_C \angle -90^\circ}$$

Define $R' = R_3 + R_1$

$$\text{and } \mathbf{A}_v = \frac{R_3}{R' + R_2 \parallel X_C \angle -90^\circ} = \frac{R_3}{R' + \frac{R_2(-jX_C)}{R_2 - jX_C}}$$

$$= \frac{R_3(R_2 - jX_C)}{R'(R_2 - jX_C) - jR_2X_C}$$

$$= \frac{R_2R_3 - jR_3X_C}{R'R_2 - jR'X_C - jR_2X_C}$$

$$= \frac{R_2 R_3 - j R_3 X_C}{R' R_2 - j(R' + R_2) X_C} = \frac{1 - j \frac{R_3 X_C}{R_2 R_3}}{\frac{R' R_2}{R_2 R_3} - j \frac{(R' + R_2)}{R_2 R_3} X_C}$$

$$= \frac{1 - j \frac{X_C}{R_2}}{\frac{R'}{R_3} \left[1 - j \frac{(R' + R_2)}{R_2 R_3} \frac{R_3}{R'} X_C \right]}$$

$$= \frac{1 - j \frac{X_C}{R_2}}{\frac{R'}{R_3} \left[1 - j \frac{R' + R_2}{R' R_2} X_C \right]}$$

$$= \frac{R_3}{R'} \frac{[1 - j X_C / R_2]}{\left[1 - j \left(\frac{R' + R_2}{R' R_2} \right) X_C \right]}$$

$$= \frac{R_3}{R_1 + R_3} \frac{\left[1 - j \frac{1}{2\pi R_2 C} \right]}{\left[1 - j \frac{1}{2\pi (R' \parallel R_2) C} \right]}$$

and $\mathbf{A}_v = \frac{R_3}{R_1 + R_3} \frac{[1 - j(f_1/f)]}{[1 - j(f_c/f)]}$

$$f_1 = \frac{1}{2\pi R_2 C}$$

$$f_c = \frac{1}{2\pi (R' \parallel R_2) C}$$


$$\mathbf{A}_{v_{dB}} = 20 \log_{10} \frac{R_3}{R_1 + R_3} + 20 \log_{10} \sqrt{1 + (f_1/f)^2} + 20 \log_{10} \frac{1}{\sqrt{1 + (f_c/f)^2}}$$

$$= -20 \log_{10} \frac{R_1 + R_3}{R_3} + 20 \log_{10} \sqrt{1 + (f_1/f)^2} + 20 \log_{10} \frac{1}{\sqrt{1 + (f_c/f)^2}}$$

with $f_1 = \frac{1}{2\pi R_2 C}$, $f_c = \frac{1}{2\pi (R' \parallel R_2) C}$, $R' = R_1 + R_3$

$$\theta = -\tan^{-1}(f_1/f) + \tan^{-1}(f_c/f)$$

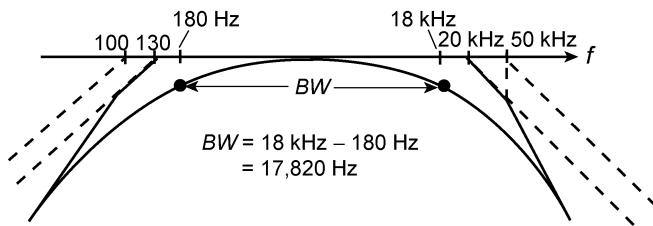48. a. $\frac{A_v}{A_{v_{max}}} = \frac{1}{\left(1 - j \frac{100 \text{ Hz}}{f} \right) \left(1 - j \frac{130 \text{ Hz}}{f} \right) \left(1 + j \frac{f}{20 \text{ kHz}} \right) \left(1 + j \frac{f}{50 \text{ kHz}} \right)}$



Proximity of 100 Hz to 130 Hz will raise lower cutoff frequency above 130 Hz:

Testing: $f = 180 \text{ Hz}$: (with lower terms only)


$$\begin{aligned} A_{v_{dB}} &= -20 \log_{10} \sqrt{1 + \left(\frac{100}{f}\right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{130}{f}\right)^2} \\ &= -20 \log_{10} \sqrt{1 + \left(\frac{100}{180}\right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{130}{180}\right)^2} \\ &= 1.17 \text{ dB} - 1.82 \text{ dB} = \mathbf{-2.99 \text{ dB} \cong -3 \text{ dB}} \end{aligned}$$

Proximity of 50 kHz to 20 kHz will lower high cutoff frequency below 20 kHz:

Testing: $f = 18 \text{ kHz}$: (with upper terms only)

$$\begin{aligned} A_{v_{dB}} &= -20 \log_{10} \sqrt{1 + \left(\frac{f}{20 \text{ kHz}}\right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{f}{50 \text{ kHz}}\right)^2} \\ &= -20 \log_{10} \sqrt{1 + \left(\frac{18 \text{ kHz}}{20 \text{ kHz}}\right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{13 \text{ kHz}}{20 \text{ kHz}}\right)^2} \\ &= -2.576 \text{ dB} - 0.529 \text{ dB} = \mathbf{-3.105 \text{ dB}} \end{aligned}$$


b.

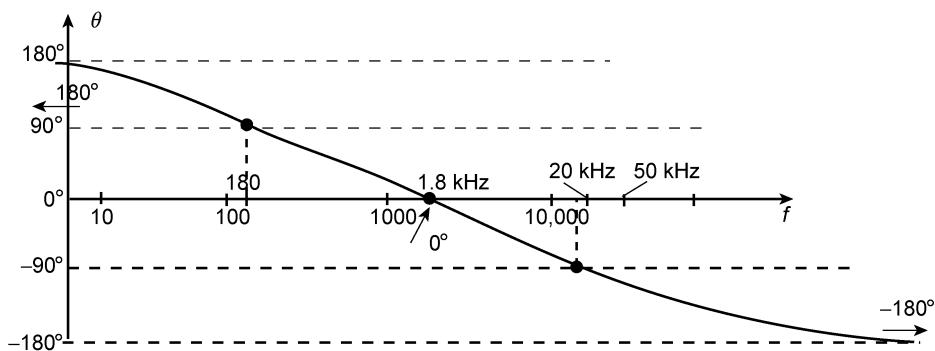

Testing: $f = 1.8 \text{ kHz}$:

$$\begin{aligned} \theta &= \tan^{-1} \frac{100}{1.8 \text{ kHz}} + \tan^{-1} \frac{130}{1.8 \text{ kHz}} - \tan^{-1} \frac{1.8 \text{ kHz}}{20 \text{ kHz}} - \tan^{-1} \frac{1.8 \text{ kHz}}{50 \text{ kHz}} \\ &= 3.18^\circ + 4.14^\circ - 5.14^\circ - 2.06^\circ \\ &= \mathbf{0.12^\circ \cong 0^\circ} \end{aligned}$$

49.

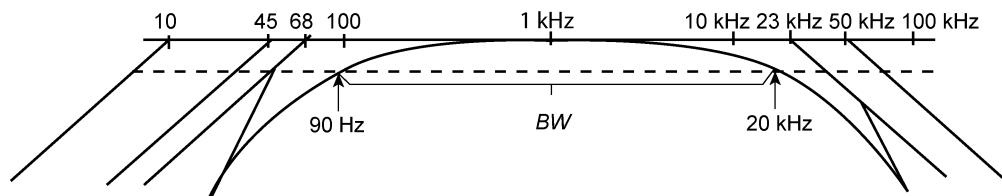

50 kHz vs $23 \text{ kHz} \rightarrow$ drop about 1 dB at 23 kHz due to 50 kHz break.

Ignore effect of break frequency at 10 Hz .

Assume -2 dB drop at 68 Hz due to break frequency at 45 Hz .

Rough sketch suggests low cut-off frequency of 90 Hz .

Checking: Ignoring upper terms and using $f = 90 \text{ Hz}$:


$$\begin{aligned} A'_{\text{dB}} &= -20 \log_{10} \sqrt{1 + \left(\frac{10 \text{ Hz}}{f} \right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{45 \text{ Hz}}{f} \right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{68 \text{ Hz}}{f} \right)^2} \\ &= -0.0532 \text{ dB} - 0.969 \text{ dB} - 1.96 \text{ dB} \\ &= -2.98 \text{ dB} \quad (\text{excellent}) \end{aligned}$$

High frequency cutoff: Try $f = 20 \text{ kHz}$

$$\begin{aligned} A'_{\text{dB}} &= -20 \log_{10} \sqrt{1 + \left(\frac{f}{23 \text{ kHz}} \right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{f}{50 \text{ kHz}} \right)^2} \\ &= -2.445 \text{ dB} - 0.6445 \text{ dB} \\ &= -3.09 \text{ dB} \quad (\text{excellent}) \end{aligned}$$

$$\therefore BW = 20 \text{ kHz} - 90 \text{ Hz} = 19,910 \text{ Hz} \approx 20 \text{ kHz}$$
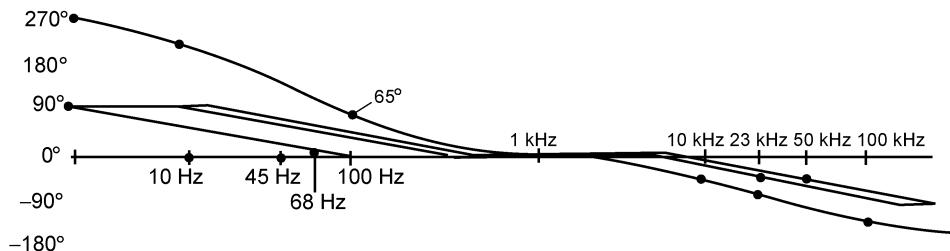
$$f_1 = 90 \text{ Hz}, f_2 = 20 \text{ kHz}$$




Testing: $f = 100 \text{ Hz}$


$$\begin{aligned} \theta &= \tan^{-1} \frac{10 \text{ Hz}}{f} + \tan^{-1} \frac{45 \text{ Hz}}{f} + \tan^{-1} \frac{68 \text{ Hz}}{f} - \tan^{-1} \frac{f}{23 \text{ kHz}} - \tan^{-1} \frac{f}{50 \text{ kHz}} \\ &= \tan^{-1} 0.1 + \tan^{-1} 0.45 + \tan^{-1} 0.68 - \tan^{-1} 0.00435 - \tan^{-1} .002 \\ &= 5.71^\circ + 24.23^\circ + 34.22^\circ - 0.249^\circ - 0.115^\circ \\ &= 63.8^\circ \text{ vs about } 65^\circ \text{ on the plot} \end{aligned}$$

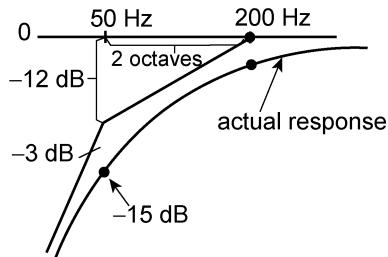50. $f_{\text{low}} = f_{\text{high}} - BW = 36 \text{ kHz} - 35.8 \text{ kHz} = 0.2 \text{ kHz} = 200 \text{ Hz}$

$$A_v = \frac{-120}{\left(1 - j \frac{50}{f}\right) \left(1 - j \frac{200}{f}\right) \left(1 + j \frac{f}{36 \text{ kHz}}\right)}$$



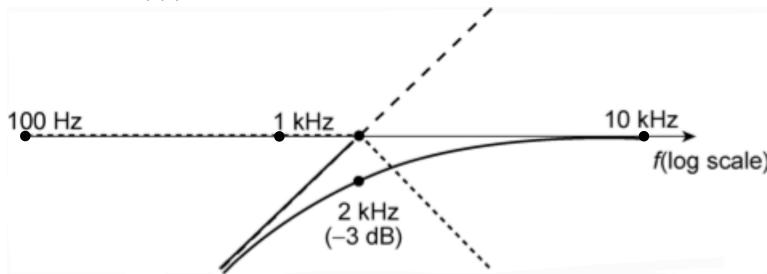
$$\begin{aligned} 51. \quad A_v &= \frac{0.05}{0.05 - j \frac{100}{f}} = \frac{1}{1 - j \frac{100}{0.05 f}} = \frac{1}{1 - j \frac{2000}{f}} = \frac{+j f}{+j f + 2000} \\ &= \frac{+j \frac{f}{2000}}{1 + j \frac{f}{2000}} \text{ and } f_l = 2000 \text{ Hz} \end{aligned}$$




$$52. \quad A_v = \frac{200}{200 + j0.1f} = \frac{1}{1 + j \frac{0.1f}{200}} = \frac{1}{1 + j \frac{f}{2000}}$$
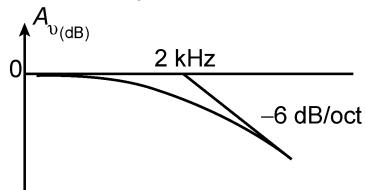
$$A_{\text{v dB}} = -20 \log_{20} \sqrt{\frac{1}{1 + \left(\frac{f}{2000}\right)^2}}, \frac{f}{2000} = 1 \text{ and } f = 2 \text{ kHz}$$




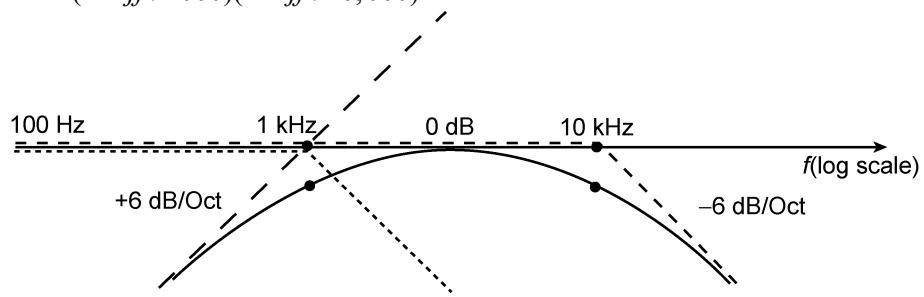53. $A_v = \frac{jf/1000}{(1+jf/1000)(1+jf/10,000)}$




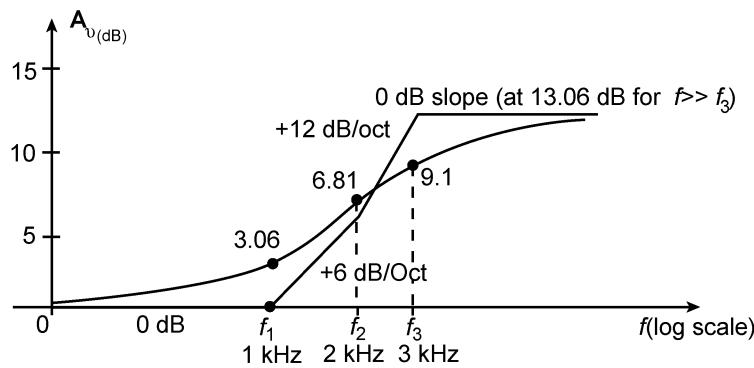
54. $A_v = \frac{\left(1 + j\frac{f}{1000}\right)\left(1 + j\frac{f}{2000}\right)}{\left(1 + j\frac{f}{3000}\right)^2}$

$$A_{v\text{dB}} = -20 \log_{10} \sqrt{1 + \left(\frac{f_1}{1000}\right)^2} + 20 \log_{10} \sqrt{1 + \left(\frac{f_2}{2000}\right)^2} + 40 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_3}{3000}\right)^2}}$$



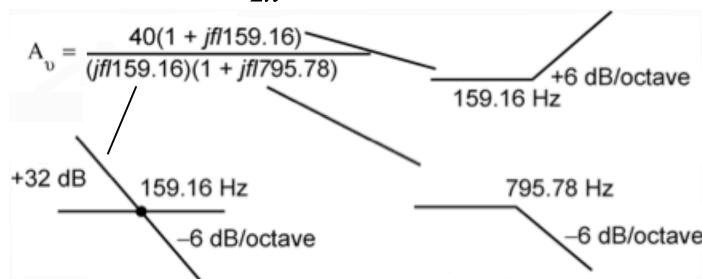55. $\frac{j\omega}{1000} = j\frac{2\pi f}{1000} = j\frac{f}{1000} = j\frac{f}{159.16 \text{ Hz}}, \frac{j\omega}{5000} = j\frac{f}{795.78 \text{ Hz}}$



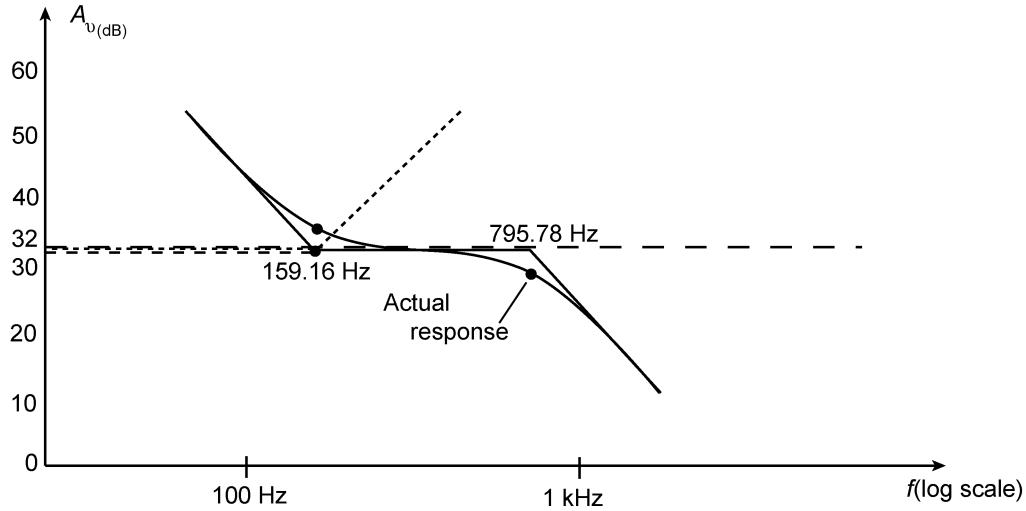

56. a. Woofer – 400 Hz:

$$X_L = 2\pi f L = 2\pi(400 \text{ Hz})(4.7 \text{ mH}) = 11.81 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(400 \text{ Hz})(39 \mu\text{F})} = 10.20 \Omega$$

$$R \parallel X_C = 8 \Omega \angle 0^\circ \parallel 10.20 \angle -90^\circ = 6.3 \Omega \angle -38.11^\circ$$

$$\mathbf{V}_o = \frac{(R \parallel X_C)(\mathbf{V}_i)}{(R \parallel X_C) + j X_L} = \frac{(6.3 \Omega \angle -38.11^\circ)(\mathbf{V}_i)}{(6.3 \Omega \angle -38.11^\circ) + j 11.81}$$

$$\mathbf{V}_o = 0.673 \angle -96.11^\circ \mathbf{V}_i$$

$$\text{and } A_o = \frac{V_o}{V_i} = \mathbf{0.673} \text{ vs desired } 0.707 \text{ (off by less than 5%)}$$

Tweeter – 5 kHz:

$$X_L = 2\pi f L = 2\pi(5 \text{ kHz})(0.39 \text{ mH}) = 12.25 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(5 \text{ kHz})(2.7 \mu\text{F})} = 11.79 \Omega$$

$$R \parallel X_L = 8 \Omega \angle 0^\circ \parallel 12.25 \Omega \angle 90^\circ = 6.7 \Omega \angle 33.15^\circ$$

$$\mathbf{V}_o = \frac{(6.7 \Omega \angle 33.15^\circ)(\mathbf{V}_i)}{(6.7 \Omega \angle 33.15^\circ) - j 11.79}$$

$$\mathbf{V}_o = 0.678 \angle 88.54^\circ \mathbf{V}_i$$

$$\text{and } A_o = \frac{V_o}{V_i} = \mathbf{0.678} \text{ vs } 0.707 \text{ (off by less than 5%)}$$

b. Woofer – 3 kHz:

$$X_L = 2\pi f L = 2\pi(3 \text{ kHz})(4.7 \text{ mH}) = 88.59 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(3 \text{ kHz})(39 \mu\text{F})} = 1.36 \Omega$$

$$R \parallel X_C = 8 \Omega \angle 0^\circ \parallel 1.36 \Omega \angle -90^\circ = 1.341 \Omega \angle -80.35^\circ$$

$$\mathbf{V}_o = \frac{(R \parallel X_C)(\mathbf{V}_i)}{(R \parallel X_C) + j X_L} = \frac{(1.341 \Omega \angle -80.35^\circ)(\mathbf{V}_i)}{(1.341 \Omega \angle -80.35^\circ) + j 88.59}$$

$$\mathbf{V}_o = 0.015 \angle -170.2^\circ \mathbf{V}_i$$

$$\text{and } A_v = \frac{V_o}{V_i} = \mathbf{0.015} \text{ vs desired 0 (excellent)}$$

Tweeter – 3 kHz:

$$X_L = 2\pi f L = 2\pi(3 \text{ kHz})(0.39 \text{ mH}) = 7.35 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(3 \text{ kHz})(2.7 \mu\text{F})} = 19.65 \Omega$$


$$R \parallel X_L = 8 \Omega \angle 0^\circ \parallel 7.35 \Omega \angle 90^\circ = 5.42 \Omega \angle 47.42^\circ$$

$$\mathbf{V}_o = \frac{(R \parallel X_L)(\mathbf{V}_i)}{(R \parallel X_L) + jX_C} = \frac{(5.42 \Omega \angle 47.42^\circ)(\mathbf{V}_i)}{(5.42 \Omega \angle 47.42^\circ) - j19.65}$$

$$\mathbf{V}_o = 0.337 \angle 124.24^\circ \mathbf{V}_i$$

$$\text{and } A_v = \frac{V_o}{V_i} = \mathbf{0.337} \text{ (acceptable since relatively close to cut frequency for tweeter)}$$

c. Mid-range speaker – 3 kHz:

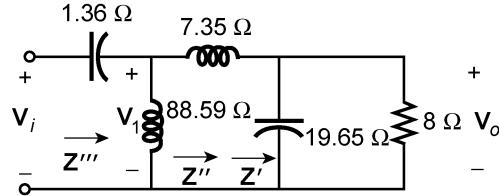

$$\mathbf{Z}' = \overbrace{7.41 \Omega}^{\text{Z}'} \angle -22.15^\circ$$

$$\mathbf{Z}'' = \overbrace{8.24 \Omega}^{\text{Z}''} \angle 33.58^\circ$$

$$\mathbf{Z}''' = \overbrace{7.816 \Omega}^{\text{Z}'''} \angle 37.79^\circ$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}'' \mathbf{V}_i}{\mathbf{Z}''' - jX_C} = \frac{(7.816 \Omega \angle 37.79^\circ) \mathbf{V}_i}{7.816 \Omega \angle 37.79^\circ - j1.36} = 1.11 \angle 8.83^\circ \mathbf{V}_i$$

$$\mathbf{V}_o = \frac{\mathbf{Z} \mathbf{V}_1}{\mathbf{Z}' + jX_L} = \frac{(7.41 \Omega \angle -22.15^\circ) \mathbf{V}_i}{7.41 \Omega \angle -22.15^\circ + j7.35} = 0.998 \angle -46.9^\circ \mathbf{V}_i$$

$$\text{and } A_v = \frac{V_o}{V_i} = \mathbf{0.998} \text{ (excellent)}$$