

# Chapter 17

1. a. 
$$\mathbf{Z}_T = j4 \Omega + \frac{(8 \Omega \angle -90^\circ)(12 \Omega \angle 0^\circ)}{-j8 \Omega + 12 \Omega} = 3.69 \Omega - j1.54 \Omega \cong 4 \Omega \angle -22.65^\circ$$
- b. 
$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{14 \text{ V} \angle 0^\circ}{4 \Omega \angle -22.65^\circ} = 3.5 \text{ A} \angle 22.65^\circ$$
- c. 
$$\mathbf{I}_1 = 3.5 \text{ A} \angle 22.65^\circ$$
- d. 
$$\mathbf{I}_2 = \frac{(8 \Omega \angle -90^\circ)(3.5 \text{ A} \angle 22.65^\circ)}{12 \Omega - j8 \Omega} = 1.94 \text{ A} \angle -33.66^\circ$$
- e. 
$$\mathbf{V}_L = \mathbf{I}_s \mathbf{X}_L = (3.5 \text{ A} \angle 22.65^\circ)(4 \Omega \angle 90^\circ) = 14 \text{ V} \angle 112.65^\circ$$
2. a. 
$$\begin{aligned} \mathbf{Z}_T &= 3 \Omega + j6 \Omega + 2 \Omega \angle 0^\circ \parallel 8 \Omega \angle -90^\circ \\ &= 3 \Omega + j6 \Omega + 1.94 \Omega \angle -14.04^\circ \\ &= 3 \Omega + j6 \Omega + 1.88 \Omega - j0.47 \Omega \\ &= 4.88 \Omega + j5.53 \Omega = 7.38 \Omega \angle 48.57^\circ \end{aligned}$$
- b. 
$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{30 \text{ V} \angle 0^\circ}{7.38 \Omega \angle 48.57^\circ} = 4.07 \text{ A} \angle -48.57^\circ$$
- c. 
$$\begin{aligned} \mathbf{I}_C &= \frac{\mathbf{Z}_{R_2} \mathbf{I}_s}{\mathbf{Z}_{R_2} + \mathbf{Z}_C} = \frac{(2 \Omega \angle 0^\circ)(4.07 \text{ A} \angle -48.57^\circ)}{2 \Omega - j8 \Omega} \\ &= \frac{8.14 \text{ A} \angle -48.57^\circ}{8.25 \angle -75.96^\circ} = 0.987 \text{ A} \angle 27.39^\circ \end{aligned}$$
- d. 
$$\begin{aligned} \mathbf{V}_L &= \frac{\mathbf{Z}_L \mathbf{E}}{\mathbf{Z}_T} = \frac{(6 \Omega \angle 90^\circ)(30 \text{ V} \angle 0^\circ)}{7.38 \Omega \angle 48.57^\circ} = \frac{180 \text{ V} \angle 90^\circ}{7.38 \Omega \angle 48.57^\circ} \\ &= 24.39 \text{ V} \angle 41.43^\circ \end{aligned}$$
3. a. 
$$\begin{aligned} \mathbf{Z}_T &= 12 \Omega \angle 90^\circ \parallel (9.1 \Omega - j12 \Omega) = 12 \Omega \angle 90^\circ \parallel 15.06 \Omega \angle -52.826^\circ \\ &= \frac{180.72 \Omega \angle 37.17^\circ}{9.10 \angle 0^\circ} \\ &= 19.86 \Omega \angle 37.17^\circ \end{aligned}$$
- b. 
$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{60 \text{ V} \angle 0^\circ}{19.86 \Omega \angle 37.17^\circ} = 3.02 \text{ A} \angle -37.17^\circ$$
- c. (CDR) 
$$\begin{aligned} \mathbf{I}_2 &= \frac{(12 \Omega \angle 90^\circ)(3.02 \text{ A} \angle -37.17^\circ)}{j12 \Omega + 9.1 \Omega - j12 \Omega} = \frac{36.24 \text{ A} \angle 52.83^\circ}{9.1 \angle 0^\circ} \\ &= 3.98 \text{ A} \angle 52.83^\circ \end{aligned}$$

$$\begin{aligned} \text{d. } (\text{VDR}) V_C &= \frac{(12 \Omega \angle -90^\circ)(60 \text{ V} \angle 0^\circ)}{9.1 \Omega - j12 \Omega} = \frac{720 \text{ V} \angle -90^\circ}{15.06 \angle -52.826^\circ} \\ &= \mathbf{47.81 \text{ V} \angle -37.17^\circ} \end{aligned}$$

$$\begin{aligned} \text{e. } P &= EI \cos \theta = (60 \text{ V})(3.02 \text{ A}) \cos(37.17^\circ) \\ &= 181.20(0.797) = \mathbf{144.42 \text{ W}} \end{aligned}$$

$$\begin{aligned} 4. \quad \text{a. } Z_T &= 2 \text{ k}\Omega \angle 0^\circ + \frac{(4 \text{ k}\Omega \angle -90^\circ)(6 \text{ k}\Omega \angle 90^\circ)}{-j4 \text{ k}\Omega + j6 \text{ k}\Omega} + \frac{\left(\frac{6.8 \text{ k}\Omega}{2} \angle 0^\circ\right)(8 \text{ k}\Omega \angle 90^\circ)}{\underbrace{\frac{6.8 \text{ k}\Omega}{2} + j8 \text{ k}\Omega}_{Z_T'}} \\ &= 2 \text{ k}\Omega + \frac{24 \text{ k}\Omega \angle 0^\circ}{2 \angle 90^\circ} + \frac{27.2 \text{ k}\Omega \angle 90^\circ}{\underbrace{3.4 \text{ k}\Omega + j8 \text{ k}\Omega}_{8.69 \text{ k}\Omega \angle 66.97^\circ}} \\ &= 2 \text{ k}\Omega + j12 \text{ k}\Omega + \frac{3.13 \text{ k}\Omega \angle 23.03^\circ}{2.88 \text{ k}\Omega + j1.22 \text{ k}\Omega} \\ &= 2 \text{ k}\Omega + 7.88 \text{ k}\Omega - j12 \text{ k}\Omega + j1.22 \text{ k}\Omega \\ Z_T &= \mathbf{4.88 \text{ k}\Omega - j10.78 \text{ k}\Omega = 11.83 \text{ k}\Omega \angle -65.64^\circ} \end{aligned}$$

$$\text{b. } V_2 = \frac{Z_T' E}{Z_T} = \frac{(3.13 \text{ k}\Omega \angle 23.03^\circ)(240 \text{ V} \angle 60^\circ)}{11.83 \text{ k}\Omega \angle -65.64^\circ} = \mathbf{63 \text{ V} \angle 148.67^\circ}$$

$$I_L = \frac{V_2}{X_{L_2}} = \frac{63 \text{ V} \angle 148.67^\circ}{8 \text{ k}\Omega \angle 90^\circ} = \mathbf{7.88 \text{ mA} \angle 58.67^\circ}$$

$$\text{c. } F_p = \frac{R}{Z_T} = \frac{4.88 \text{ k}\Omega}{11.83 \text{ k}\Omega} = \mathbf{0.413 \text{ (leading)}}$$

$$\begin{aligned} 5. \quad \text{a. } 400 \Omega \angle -90^\circ \parallel 400 \Omega \angle -90^\circ &= \frac{400 \Omega \angle -90^\circ}{2} = 200 \Omega \angle -90^\circ \\ Z' &= 100 \Omega - j200 \Omega = 223.61 \Omega \angle -63.43^\circ \\ Z'' &= -j200 \Omega + j600 \Omega = +j400 \Omega = 400 \Omega \angle 90^\circ \\ Z_T = Z' \parallel Z'' &= \frac{(223.61 \Omega \angle -63.43^\circ)(400 \Omega \angle 90^\circ)}{(100 \Omega - j200 \Omega) + j400 \Omega} = \frac{89,444.00 \Omega \angle 26.57^\circ}{223.61 \angle 63.43^\circ} \\ &= 400 \Omega \angle -36.86^\circ \\ I &= \frac{E}{Z_T} = \frac{100 \text{ V} \angle 0^\circ}{400 \Omega \angle -36.86^\circ} = \mathbf{0.25 \text{ A} \angle 36.86^\circ} \end{aligned}$$

$$\text{b. } V_C = \frac{(200 \Omega \angle -90^\circ)(100 \Omega \angle 0^\circ)}{100 \Omega - j200 \Omega} = \frac{20,000 \text{ V} \angle -90^\circ}{223.61 \angle -63.43^\circ} = \mathbf{89.44 \text{ V} \angle -26.57^\circ}$$

$$\begin{aligned} \text{c. } P &= EI \cos \theta = (100 \text{ V})(0.25 \text{ A}) \cos 36.86^\circ \\ &= (25)(0.8) = \mathbf{20 \text{ W}} \end{aligned}$$

6. a. 
$$\mathbf{I}_L = \frac{\mathbf{Z}_2 \mathbf{I}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(6 \angle -90^\circ)(2 \text{ A} \angle 30^\circ)}{(3 \Omega + j4 \Omega) + (-j6 \Omega)} = \frac{12 \text{ A} \angle -60^\circ}{3.61 \angle -33.69^\circ} = \mathbf{3.32 \text{ A} \angle -26.31^\circ}$$

b. 
$$\mathbf{Z}_T = \mathbf{Z}_1 \parallel \mathbf{Z}_2 = (5 \Omega \angle 53.13^\circ) \parallel (6 \Omega \angle -90^\circ) = 8.31 \Omega \angle -3.2^\circ$$
  

$$\mathbf{E}_T = \mathbf{I} \mathbf{Z}_T = (2 \text{ A} \angle 30^\circ)(8.31 \Omega \angle -3.2^\circ) = 16.62 \text{ V} \angle 26.8^\circ$$
  


$$\mathbf{V}_C = \frac{(X_C \angle -90^\circ)(\mathbf{E}_T)}{X_C \angle -90^\circ + X_{L_2} \angle 90^\circ} = \frac{(13 \Omega \angle -90^\circ)(16.62 \text{ V} \angle 26.8^\circ)}{-j13 \Omega + j7 \Omega} = \mathbf{36 \text{ V} \angle 26.8^\circ}$$

c. 
$$\mathbf{V}_{ab} = \mathbf{V}_{R_1} - \mathbf{V}_C = (\mathbf{I}_L)(3 \Omega \angle 0^\circ) - 36 \text{ V} \angle 26.8^\circ$$
  

$$= (3.32 \text{ A} \angle -26.31^\circ)(3 \Omega \angle 0^\circ) - 36 \text{ V} \angle 26.8^\circ = 9.96 \text{ V} \angle -26.31^\circ - 36 \text{ V} \angle 26.8^\circ$$
  

$$= \mathbf{31.05 \text{ V} \angle -138.34^\circ}$$

7. a.

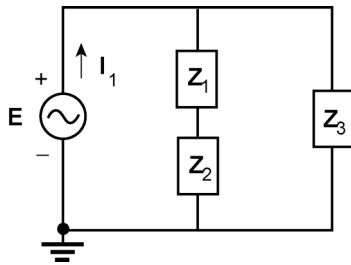

$$\mathbf{Z}_1 = 10 \Omega \angle 0^\circ$$

$$\mathbf{Z}_2 = 80 \Omega \angle 90^\circ \parallel 20 \Omega \angle 0^\circ$$

$$= \frac{1600 \Omega \angle 90^\circ}{20 + j80} = \frac{1600 \Omega \angle 90^\circ}{82.462 \angle 75.964^\circ}$$

$$= 19.403 \Omega \angle 14.036^\circ$$

$$\mathbf{Z}_3 = 60 \Omega \angle -90^\circ$$

$$\mathbf{Z}_T = (\mathbf{Z}_1 + \mathbf{Z}_2) \parallel \mathbf{Z}_3$$

$$= (10 \Omega + 18.824 \Omega + j4.706 \Omega) \parallel 60 \Omega \angle -90^\circ$$

$$= 29.206 \Omega \angle 9.273^\circ \parallel 6 \Omega \angle -90^\circ = \frac{1752.36 \Omega \angle -80.727^\circ}{28.824 + j4.706 - j60}$$

$$= \frac{1752.36 \Omega \angle -80.727^\circ}{62.356 \angle -62.468^\circ} = \mathbf{28.103 \Omega \angle -18.259^\circ}$$

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{40 \text{ V} \angle 0^\circ}{28.103 \Omega \angle -18.259^\circ} = \mathbf{1.42 \text{ A} \angle 18.26^\circ}$$

b. 
$$\mathbf{V}_1 = \frac{\mathbf{Z}_2 \mathbf{E}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(19.403 \Omega \angle 14.036^\circ)(40 \text{ V} \angle 0^\circ)}{29.206 \Omega \angle 9.273^\circ} = \frac{776.12 \text{ V} \angle 14.036^\circ}{29.206 \angle 9.273^\circ}$$
  


$$= \mathbf{26.57 \text{ V} \angle 4.76^\circ}$$

c. 
$$P = EI \cos \theta = (40 \text{ V})(1.423 \text{ A}) \cos 18.259^\circ$$
  

$$= \mathbf{54.07 \text{ W}}$$

8. !!  $R_2 = 1 \text{ k}\Omega$

a.

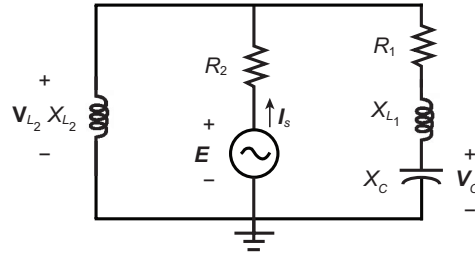

$$X_{L_1} = 2\pi fL_1 = 2\pi(5 \text{ kHz})(68 \text{ mH}) = 2.14 \text{ k}\Omega$$

$$X_{L_2} = 2\pi fL_2 = 2\pi(5 \text{ kHz})(100 \text{ mH}) = 3.14 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(5 \text{ kHz})(3 \text{ nF})} = 10.61 \text{ k}\Omega$$

$$\begin{aligned} Z_T &= R_2 + X_{L_2} \parallel (R_1 + X_{L_1} + X_C) \\ &= 1 \text{ k}\Omega + (3.14 \text{ k}\Omega \angle 90^\circ) \parallel \underbrace{(6.8 \text{ k}\Omega + j2.14 \text{ k}\Omega - j10.61 \text{ k}\Omega)}_{\substack{6.8 \text{ k}\Omega - j8.47 \text{ k}\Omega \\ 10.86 \text{ k}\Omega \angle -51.24^\circ}} \end{aligned}$$

$$= 1 \text{ k}\Omega + (3.14 \text{ k}\Omega \angle 90^\circ) \parallel (10.86 \text{ k}\Omega \angle -51.24^\circ)$$

$$= 1 \text{ k}\Omega + \frac{(3.14 \text{ k}\Omega \angle 90^\circ)(10.86 \text{ k}\Omega \angle -51.24^\circ)}{+j3.14 \text{ k}\Omega + 6.8 \text{ k}\Omega - j8.47 \text{ k}\Omega}$$

$$= 1 \text{ k}\Omega + \frac{34.10 \text{ k}\Omega \angle 38.76^\circ}{6.8 - j5.33} = 1 \text{ k}\Omega + \frac{34.10 \text{ k}\Omega \angle 38.76^\circ}{8.64 \angle -38^\circ}$$

$$= 1 \text{ k}\Omega + 3.95 \text{ k}\Omega \angle 76.76^\circ$$

$$= 1 \text{ k}\Omega + 0.904 \text{ k}\Omega + j3.85 \text{ k}\Omega$$

$$= 1.904 \text{ k}\Omega + j3.85 \text{ k}\Omega$$

$$Z_T = 4.3 \text{ k}\Omega \angle 63.69^\circ$$


$$I_s = \frac{E}{Z_T} = \frac{10 \text{ V} \angle 0^\circ}{4.3 \text{ k}\Omega \angle 63.69^\circ} = 2.33 \text{ mA} \angle -63.69^\circ$$

$$\begin{aligned} \text{b. } I_C &= \frac{X_{L_2} I_s}{X_{L_2} + (R_1 + X_{L_1} + X_C)} = \frac{(3.14 \text{ k}\Omega \angle 90^\circ)(2.33 \text{ mA} \angle -63.69^\circ)}{+j3.14 \text{ k}\Omega + 6.8 \text{ k}\Omega - j8.47 \text{ k}\Omega} \\ &= \frac{7.32 \text{ mA} \angle 26.3^\circ}{6.8 - j5.33} = \frac{7.32 \text{ mA} \angle 26.3^\circ}{8.64 \angle -38.1^\circ} = 0.847 \text{ mA} \angle 64.4^\circ \end{aligned}$$

$$\begin{aligned} V_C &= I_C X_C = (0.847 \text{ mA} \angle 64.4^\circ)(10.61 \text{ k}\Omega \angle -90^\circ) \\ &= 8.99 \text{ V} \angle -25.60^\circ \end{aligned}$$

$$\begin{aligned} \text{c. } V_{L_2} &= E - I_s R_2 = 10 \text{ V} \angle 0^\circ - (2.33 \text{ mA} \angle -63.69^\circ)(1 \text{ k}\Omega \angle 0^\circ) \\ &= 10 \text{ V} - 2.33 \text{ V} \angle -63.69^\circ = 10 \text{ V} - (1.03 \text{ V} - j2.09 \text{ V}) \\ &= 8.97 \text{ V} + j2.09 \text{ V} \\ &= 9.21 \text{ V} \angle 13.12^\circ \end{aligned}$$

9. a.

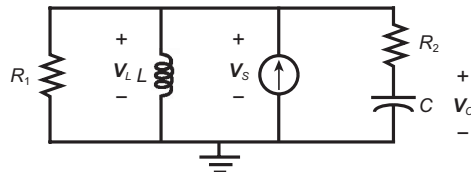

$$X_L = 2\pi fL = 2\pi(10 \text{ kHz})(47 \text{ mH}) = 2.95 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \text{ kHz})(0.01 \mu\text{F})} = 1.59 \text{ k}\Omega$$

$$\frac{1}{Z_T} = \frac{1}{R_1} + \frac{1}{X_L} + \frac{1}{R_2 + X_C}$$

$$\frac{1}{Z_T} = \frac{1}{4.7 \text{ k}\Omega} + \frac{1}{2.95 \text{ k}\Omega \angle 90^\circ} + \frac{1}{1.8 \text{ k}\Omega - j1.59 \text{ k}\Omega}$$

$$= 212.77 \mu\text{S} \angle 0^\circ + 338.98 \mu\text{S} \angle -90^\circ + \frac{1}{2.40 \text{ k}\Omega \angle -41.46^\circ}$$

$$= 212.77 \mu\text{S} - j338.98 \mu\text{S} + 312.26 \mu\text{S} + j275.88 \mu\text{S}$$

$$= 525.03 \mu\text{S} - j63.1 \mu\text{S}$$

$$= 528.81 \mu\text{S} \angle -6.85^\circ$$

$$\text{and } Z_T = \frac{1}{528.81 \mu\text{S} \angle -6.85^\circ} = 1.89 \text{ k}\Omega \angle 6.85^\circ$$

$$V_s = (\mathbf{I})(Z_T) = (8 \text{ mA} \angle 0^\circ)(1.89 \text{ k}\Omega \angle 6.85^\circ) \\ = \mathbf{15.12 \text{ V} \angle 6.85^\circ}$$

$$\text{b. } V_C = \frac{X_C V_s}{R + X_C} = \frac{(1.59 \text{ k}\Omega \angle -90^\circ)(15.12 \text{ V} \angle 6.85^\circ)}{1.8 \text{ k}\Omega - j1.59 \text{ k}\Omega} \\ = \frac{24 \text{ V} \angle -83.15^\circ}{2.40 \angle -41.46^\circ} = \mathbf{10 \text{ V} \angle -41.69^\circ}$$

$$\text{c. } V_L = V_s = \mathbf{15.12 \text{ V} \angle 6.85^\circ}$$

$$10. \text{ a. } Z_T = 1.2 \text{ k}\Omega + \frac{(1.2 \text{ k}\Omega \angle 0^\circ)(1.8 \text{ k}\Omega \angle -90^\circ)}{1.2 \text{ k}\Omega - j1.8 \text{ k}\Omega} + \frac{2.4 \text{ k}\Omega \angle 90^\circ}{2} \\ = 1.2 \text{ k}\Omega + \frac{2.16 \text{ k}\Omega \angle -90^\circ}{2.16 \angle -56.31^\circ} + 1.2 \text{ k}\Omega \angle 90^\circ \\ = 1.2 \text{ k}\Omega + 1 \text{ k}\Omega \angle -33.69^\circ + j1.2 \text{ k}\Omega \\ = 1.2 \text{ k}\Omega + 832.05 \Omega - j554.70 \Omega + j1.2 \text{ k}\Omega \\ = \mathbf{2.03 \text{ k}\Omega + j645.30 \Omega = 2.13 \text{ k}\Omega \angle 17.63^\circ}$$


$$\text{b. } V_1 = \mathbf{I}R_1 = (20 \text{ mA} \angle 0^\circ)(1.2 \text{ k}\Omega \angle 0^\circ) = \mathbf{24 \text{ V} \angle 0^\circ}$$

$$\text{c. } \mathbf{I}_1 = \frac{(1.2 \text{ k}\Omega \angle 0^\circ)(20 \text{ mA} \angle 0^\circ)}{1.2 \text{ k}\Omega - j1.8 \text{ k}\Omega} = \frac{2.4 \text{ A} \angle 0^\circ}{2.16 \times 10^3 \angle -56.31^\circ} = \mathbf{11.11 \text{ mA} \angle 56.31^\circ}$$

$$\text{d. } V_2 = \mathbf{I}(X_{L_1} \parallel X_{L_2}) = (20 \text{ mA} \angle 0^\circ) \left( \frac{(2.4 \text{ k}\Omega)}{2} \angle 90^\circ \right) = \mathbf{24 \text{ V} \angle 90^\circ}$$

$$\text{e. } V_s = \mathbf{I}Z_T = (20 \text{ mA} \angle 0^\circ)(2.13 \text{ k}\Omega \angle 17.63^\circ) = \mathbf{42.60 \text{ V} \angle 17.63^\circ}$$

11. a.

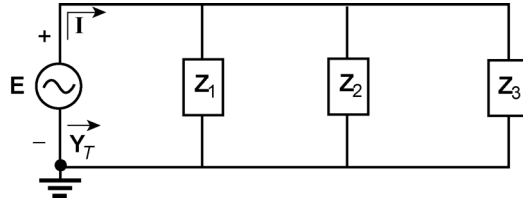

$$\begin{aligned} \mathbf{Z}_1 &= 2 \Omega - j2 \Omega = 2.828 \Omega \angle -45^\circ \\ \mathbf{Z}_2 &= 3 \Omega - j9 \Omega + j6 \Omega \\ &= 3 \Omega - j3 \Omega = 4.243 \Omega \angle -45^\circ \\ \mathbf{Z}_3 &= 10 \Omega \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{Y}_T &= \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} = \frac{1}{2.828 \Omega \angle -45^\circ} + \frac{1}{4.243 \Omega \angle -45^\circ} + \frac{1}{10 \Omega \angle 0^\circ} \\ &= 0.354 \text{ S} \angle 45^\circ + 0.236 \text{ S} \angle 45^\circ + 0.1 \text{ S} \angle 0^\circ = 0.59 \text{ S} \angle 45^\circ + 0.1 \text{ S} \angle 0^\circ \\ &= 0.417 \text{ S} + j0.417 \text{ S} + 0.1 \text{ S} \end{aligned}$$

$$\mathbf{Y}_T = 0.517 \text{ S} + j0.417 \text{ S} = \mathbf{0.66 \text{ S} \angle 38.89^\circ}$$

$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.66 \text{ S} \angle 38.89^\circ} = \mathbf{1.52 \Omega \angle -38.89^\circ}$$

b. 
$$\mathbf{V}_1 = \frac{(2 \Omega \angle 0^\circ)(60 \text{ V} \angle 0^\circ)}{2 \text{ k}\Omega - j2 \Omega} = \frac{120 \text{ V} \angle 0^\circ}{2.828 \angle -45^\circ} = \mathbf{42.43 \text{ V} \angle 45^\circ}$$

c. 
$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}'} = \frac{60 \text{ V} \angle 0^\circ}{3 \Omega - j9 \Omega + j6 \Omega} = \frac{60 \text{ V} \angle 0^\circ}{3 \Omega - j3 \Omega} = \frac{60 \text{ V} \angle 0^\circ}{4.243 \angle -45^\circ} = \mathbf{14.14 \text{ A} \angle 45^\circ}$$

d. 
$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{60 \text{ V} \angle 0^\circ}{1.52 \Omega \angle -38.89^\circ} = \mathbf{39.47 \text{ A} \angle 38.89^\circ}$$

12. 
$$\mathbf{Z}' = 12 \Omega - j20 \Omega = 23.32 \Omega \angle -59.04^\circ$$

$$R_4 \angle 0^\circ \parallel \mathbf{Z}' = 20 \Omega \angle 0^\circ \parallel 23.32 \Omega \angle -59.04^\circ = 12.36 \Omega \angle -27.03^\circ$$

$$\begin{aligned} \mathbf{Z}'' &= R_3 \angle 0^\circ + R_4 \angle 0^\circ \parallel \mathbf{Z}' = 12 \Omega + 12.36 \Omega \angle -27.03^\circ \\ &= 12 \Omega + (11.01 \Omega - j5.62 \Omega) \\ &= 23.01 \Omega - j5.62 \Omega = 23.69 \Omega \angle -13.73^\circ \end{aligned}$$

$$R_2 \angle 0^\circ \parallel \mathbf{Z}'' = 20 \Omega \angle 0^\circ \parallel 23.69 \Omega \angle -13.73^\circ = 10.92 \Omega \angle -6.29^\circ$$

$$\begin{aligned} \mathbf{Z}_T &= R_1 \angle 0^\circ + R_2 \angle 0^\circ \parallel \mathbf{Z}'' = 12 \Omega + 10.92 \Omega \angle -6.29^\circ \\ &= 12 \Omega + (10.85 \Omega - j1.25 \Omega) \\ &= 22.85 \Omega - j1.2 \Omega = \mathbf{22.88 \Omega \angle -3.01^\circ} \end{aligned}$$

$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V} \angle 0^\circ}{22.88 \Omega \angle -3.01^\circ} = \mathbf{4.37 \text{ A} \angle +3.01^\circ}$$

$$\mathbf{I}_{R_1} = \mathbf{I}$$

$$\begin{aligned} \mathbf{I}_{R_3} &= \frac{(R_2 \angle 0^\circ) \mathbf{I}_s}{R_2 \angle 0^\circ + \mathbf{Z}''} = \frac{(20 \Omega \angle 0^\circ)(4.37 \text{ A} \angle 3.01^\circ)}{20 \Omega + 23.01 \Omega - j5.62 \Omega} = \frac{87.40 \text{ A} \angle 3.01^\circ}{43.38 \angle -7.44^\circ} \\ &= \mathbf{2.01 \text{ A} \angle 10.45^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_4 &= \frac{(R_4 \angle 0^\circ) \mathbf{I}_{R_3}}{R_4 \angle 0^\circ + \mathbf{Z}'} = \frac{(20 \Omega \angle 0^\circ)(2.01 \text{ A} \angle 10.45^\circ)}{20 \Omega + 12 \Omega - j20 \Omega} = \frac{40.20 \text{ A} \angle 10.45^\circ}{32 \Omega - j20 \Omega} = \frac{40.20 \text{ A} \angle 10.45^\circ}{37.74 \angle -32.01^\circ} \\ &= \mathbf{1.07 \text{ A} \angle 42.46^\circ} \end{aligned}$$

13.  $R_3 + R_4 = 2.7 \text{ k}\Omega + 4.3 \text{ k}\Omega = 7 \text{ k}\Omega$   
 $R' = 3 \text{ k}\Omega \parallel 7 \text{ k}\Omega = 2.1 \text{ k}\Omega$   
 $Z' = 2.1 \text{ k}\Omega - j10 \Omega$

(CDR)  $I'$  (of  $10 \Omega$  cap.) =  $\frac{(40 \text{ k}\Omega \angle 0^\circ)(20 \text{ mA} \angle 0^\circ)}{40 \text{ k}\Omega + 2.1 \text{ k}\Omega - j10 \Omega}$   
 $= 19 \text{ mA} \angle +0.014^\circ$  as expected since  $R_1 \gg Z'$


(CDR)  $I_4 = \frac{(3 \text{ k}\Omega \angle 0^\circ)(19 \text{ mA} \angle 0.014^\circ)}{3 \text{ k}\Omega + 7 \text{ k}\Omega} = \frac{57 \text{ mA} \angle 0.014^\circ}{10}$   
 $= 5.7 \text{ mA} \angle 0.014^\circ$   
 $P = I^2 R = (5.7 \text{ mA})^2 4.3 \text{ k}\Omega = \mathbf{139.71 \text{ mW}}$

14.  $Z' = X_{C_2} \angle -90^\circ \parallel R_1 \angle 0^\circ = 2 \Omega \angle -90^\circ \parallel 1 \Omega \angle 0^\circ$   
 $= \frac{2 \Omega \angle -90^\circ}{1 - j2} = \frac{2 \Omega \angle -90^\circ}{2.236 \angle -63.435^\circ}$   
 $= 0.894 \Omega \angle -26.565^\circ$   
 $Z'' = X_{L_2} \angle 90^\circ + Z' = +j8 \Omega + 0.894 \Omega \angle -26.565^\circ$   
 $= +j8 \Omega + (0.8 \Omega - j4 \Omega)$   
 $= 0.8 \Omega + j4 = 4.079 \Omega \angle 78.69^\circ$

$I_{X_{L_2}} = \frac{(X_{C_1} \angle -90^\circ)I}{X_{C_1} \angle -90^\circ + Z''} = \frac{(2 \Omega \angle -90^\circ)(0.5 \text{ A} \angle 0^\circ)}{-j2 \Omega + (0.8 \Omega + j4 \Omega)} = \frac{1 \text{ A} \angle -90^\circ}{0.8 + -j2}$   
 $= \frac{1 \text{ A} \angle -90^\circ}{2.154 \angle 68.199^\circ} = 0.464 \text{ A} \angle -158.99^\circ$

$I_1 = \frac{(X_{C_2} \angle -90^\circ)I_{X_{C_2}}}{X_{C_2} \angle -90^\circ + R_1} = \frac{(2 \Omega \angle -90^\circ)(0.464 \text{ A} \angle -158.99^\circ)}{-j2 \Omega + 1 \Omega} = \frac{0.928 \text{ A} \angle -248.99^\circ}{2.236 \angle -63.435^\circ}$   
 $= \mathbf{0.42 \text{ A} \angle 174.45^\circ}$


15. a. !!  $X_C = 10 \text{ k}\Omega$

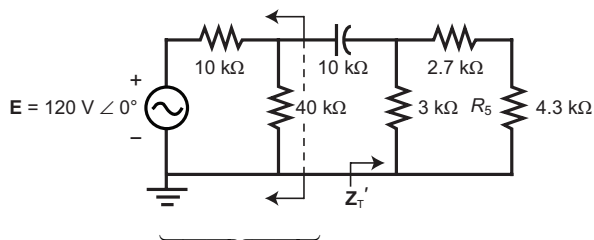

$E_{Th} = \frac{(40 \text{ k}\Omega \angle 0^\circ)(120 \text{ V} \angle 0^\circ)}{40 \text{ k}\Omega + 10 \text{ k}\Omega} = 96 \text{ V} \angle 0^\circ$

$R_{Th} = 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega = 8 \text{ k}\Omega$

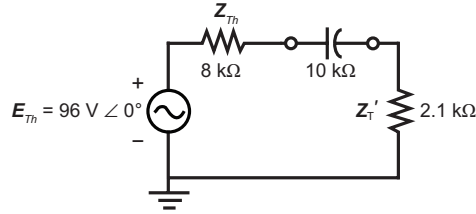$Z_T' = 3 \text{ k}\Omega \parallel (2.7 \text{ k}\Omega + 4.3 \text{ k}\Omega) = 3 \text{ k}\Omega \parallel 7 \text{ k}\Omega = 2.1 \text{ k}\Omega$




$$\begin{aligned} \mathbf{I}_C = \mathbf{I}_s &= \frac{\mathbf{E}_{Th}}{\mathbf{Z}_T} = \frac{96 \text{ V} \angle 0^\circ}{8 \text{ k}\Omega + 2.1 \text{ k}\Omega - j10 \text{ k}\Omega} = \frac{96 \text{ V} \angle 0^\circ}{10.1 \text{ k}\Omega - j10 \text{ k}\Omega} \\ &= \frac{96 \text{ V} \angle 0^\circ}{14.21 \text{ k}\Omega \angle -44.72^\circ} = 6.76 \text{ mA} \angle 44.72^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{R_5} &= \frac{(3 \text{ k}\Omega \angle 0^\circ)(\mathbf{I}_C)}{3 \text{ k}\Omega + 2.7 \text{ k}\Omega + 4.3 \text{ k}\Omega} = \frac{(3 \text{ k}\Omega \angle 0^\circ)(6.76 \text{ mA} \angle 44.72^\circ)}{10 \text{ k}\Omega \angle 0^\circ} \\ &= \frac{20.28 \text{ mA} \angle 44.72^\circ}{10} \end{aligned}$$

$$= 2.03 \text{ mA} \angle 44.72^\circ$$

$$\begin{aligned} P_{R_5} &= I^2 R = (2.03 \text{ mA})^2 4.3 \text{ k}\Omega \\ &= 17.72 \text{ mW} \end{aligned}$$

16. a.

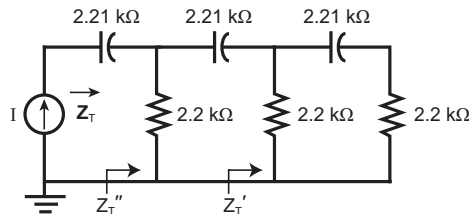

$$\begin{aligned} X_C &= \frac{1}{2\pi fC} = \frac{1}{2\pi(40 \text{ kHz})(1.8 \text{ nF})} \\ &= 2.21 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \mathbf{Z}_{T'} &= (2.2 \text{ k}\Omega \angle 0^\circ) \parallel \underbrace{(2.2 \text{ k}\Omega - j2.21 \text{ k}\Omega)}_{3.12 \text{ k}\Omega \angle -45.13^\circ} \\ &= \frac{6.86 \text{ k}\Omega \angle -45.13^\circ}{2.2 + 2.2 - j2.21} = \frac{6.86 \text{ k}\Omega \angle -45.13^\circ}{4.4 - j2.21} \\ &= \frac{6.86 \text{ k}\Omega \angle -45.13^\circ}{4.92 \angle -26.67^\circ} = 1.36 \text{ k}\Omega \angle -18.46^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{Z}_{T''} &= 2.2 \text{ k}\Omega \angle 0^\circ \parallel (2.21 \text{ k}\Omega \angle -90^\circ + 1.36 \text{ k}\Omega \angle -18.46^\circ) \\ &= 2.2 \text{ k}\Omega \angle 0^\circ \parallel (-j2.21 \text{ k}\Omega + 1.29 \text{ k}\Omega - j0.43 \text{ k}\Omega) \\ &= 2.2 \text{ k}\Omega \angle 0^\circ \parallel \underbrace{(1.29 \text{ k}\Omega - j2.64 \text{ k}\Omega)}_{2.94 \text{ k}\Omega \angle -63.96^\circ} \end{aligned}$$


$$\begin{aligned} &= \frac{(2.2 \text{ k}\Omega \angle 0^\circ)(2.94 \text{ k}\Omega \angle -63.96^\circ)}{2.2 \text{ k}\Omega + 1.29 \text{ k}\Omega - j2.64 \text{ k}\Omega} \\ &= \frac{6.47 \text{ k}\Omega \angle -63.96^\circ}{3.49 - j2.64} = \frac{6.47 \text{ k}\Omega \angle -63.96^\circ}{4.38 \angle -37.11^\circ} \end{aligned}$$

$$\mathbf{Z}_{T''} = 1.48 \text{ k}\Omega \angle -26.85^\circ = 1.32 \text{ k}\Omega - j0.668 \text{ k}\Omega$$


$$\begin{aligned} \mathbf{Z}_T &= 2.21 \text{ k}\Omega \angle -90^\circ + \mathbf{Z}_{T''} = -j2.21 \text{ k}\Omega + 1.32 \text{ k}\Omega - j0.668 \text{ k}\Omega \\ &= 1.32 \text{ k}\Omega - j2.89 \text{ k}\Omega = R - jX_C \\ &= 3.18 \text{ k}\Omega \angle -65.45^\circ \end{aligned}$$



b. Source conversion:

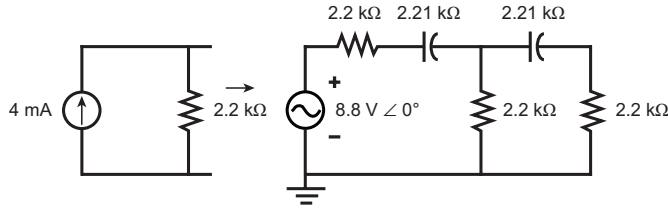


Second source conversion:

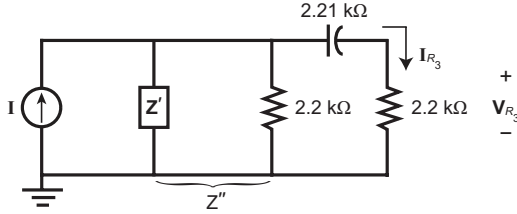

$$\begin{aligned}
 \mathbf{Z}' &= 2.2 \text{ k}\Omega - j2.21 \text{ k}\Omega = 3.12 \text{ k}\Omega \angle -45.13^\circ \\
 \mathbf{I} &= \frac{8.8 \text{ V} \angle 0^\circ}{3.12 \text{ k}\Omega \angle -45.13^\circ} = 2.82 \text{ mA} \angle 45.13^\circ \quad \left. \vphantom{\frac{8.8 \text{ V} \angle 0^\circ}{3.12 \text{ k}\Omega \angle -45.13^\circ}} \right\} \text{source conversion} \\
 \mathbf{Z}_T'' &= 2.2 \text{ k}\Omega \angle 0^\circ \parallel 3.12 \text{ k}\Omega \angle -45.13^\circ \\
 &= \frac{(2.2 \text{ k}\Omega \angle 0^\circ)(3.12 \text{ k}\Omega \angle -45.13^\circ)}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega - j2.21 \text{ k}\Omega} = \frac{6.86 \text{ k}\Omega \angle -45.13^\circ}{4.4 - j2.21} \\
 &= \frac{6.86 \text{ k}\Omega \angle -45.13^\circ}{4.92 \angle -26.67^\circ} = 1.39 \text{ k}\Omega \angle -18.46^\circ = 1.32 \text{ k}\Omega - j0.44 \text{ k}\Omega \\
 \mathbf{I}_{R_3} &= \frac{(\mathbf{Z}'')(\mathbf{I})}{\mathbf{Z}'' + 2.2 \text{ k}\Omega - j2.21 \text{ k}\Omega} = \frac{(1.39 \text{ k}\Omega \angle -18.46^\circ)(2.82 \text{ mA} \angle 45.13^\circ)}{1.32 \text{ k}\Omega - j0.44 \text{ k}\Omega + 2.2 \text{ k}\Omega - j2.21 \text{ k}\Omega} \\
 &= \frac{3.92 \text{ mA} \angle 26.67^\circ}{3.52 - j2.65} = \frac{3.92 \text{ mA} \angle 26.67^\circ}{4.41 \angle -36.97^\circ} \\
 &= 0.89 \text{ mA} \angle 63.64^\circ \\
 \mathbf{V}_{R_3} &= \mathbf{I}_{R_3} \mathbf{R}_3 = (0.89 \text{ mA} \angle 63.64^\circ)(2.2 \text{ k}\Omega \angle 0^\circ) \\
 &= \mathbf{1.96 \text{ V} \angle 63.64^\circ}
 \end{aligned}$$

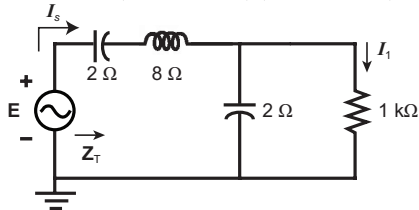17. Source conversion:

$$\mathbf{E} = \mathbf{I}\mathbf{Z} = (0.5 \text{ A} \angle 0^\circ)(2\Omega \angle -90^\circ) = 1 \text{ V} \angle -90^\circ$$



$$\begin{aligned}
 \mathbf{Z}_T &= -j2 \Omega + j8 \Omega + \underbrace{2 \Omega \angle -90^\circ \parallel 1 \Omega \angle 0^\circ}_{\frac{(2 \Omega \angle -90^\circ)(1 \Omega \angle 0^\circ)}{1 - j2}} = \frac{2 \Omega \angle -90^\circ}{2.24 \angle -63.44^\circ} \\
 &= -j2 \Omega + j8 \Omega + 0.89 \Omega \angle -26.56^\circ \\
 &= +j6 \Omega + 0.796 \Omega - j0.398 \Omega
 \end{aligned}$$

$$= 0.796 \Omega + j5.6 \Omega$$

$$= 5.66 \Omega \angle 81.91^\circ$$

$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{1 \text{ V} \angle -90^\circ}{5.66 \Omega \angle 81.91^\circ} = 0.177 \text{ A} \angle -171.91^\circ$$

$$\mathbf{I}_1 = \frac{(2 \angle -90^\circ)(\mathbf{I}_s)}{(2 \angle -90^\circ) + 1 \angle 0^\circ} = \frac{(2 \angle -90^\circ)(0.177 \text{ A} \angle -171.91^\circ)}{1 - j2}$$

$$= \frac{354 \text{ mA} \angle -261.91^\circ}{2.24 \angle -63.44^\circ}$$

$$= 158 \text{ mA} \angle -198.47^\circ$$

$$\mathbf{V}_1 = \mathbf{I}_1 \mathbf{R}_1 = (158 \text{ mA} \angle -198.47^\circ)(1 \Omega \angle 0^\circ)$$

$$= \mathbf{158 \text{ mV} \angle -198.47^\circ}$$