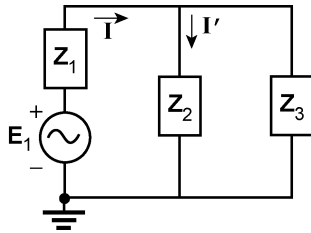


Chapter 19

1.




$$\mathbf{Z}_1 = 3 \Omega \angle 0^\circ, \mathbf{Z}_2 = 8 \Omega \angle 90^\circ, \mathbf{Z}_3 = 6 \Omega \angle -90^\circ$$

$$\mathbf{Z}_2 \parallel \mathbf{Z}_3 = 8 \Omega \angle 90^\circ \parallel 6 \Omega \angle -90^\circ = 24 \Omega \angle -90^\circ$$

$$\mathbf{I} = \frac{\mathbf{E}_1}{\mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3} = \frac{30 \text{ V} \angle 30^\circ}{3 \Omega - j24 \Omega} = 1.24 \text{ A} \angle 112.875^\circ$$
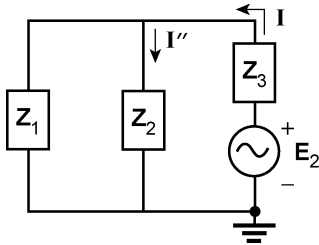
$$\mathbf{I}' = \frac{\mathbf{Z}_3 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_3} = \frac{(6 \Omega \angle -90^\circ)(1.24 \text{ A} \angle 112.875^\circ)}{2 \Omega \angle 90^\circ} = 3.72 \text{ A} \angle -67.125^\circ$$



$$\mathbf{Z}_1 \parallel \mathbf{Z}_2 = 3 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ = 2.809 \Omega \angle 20.556^\circ$$

$$\mathbf{I} = \frac{\mathbf{E}_2}{\mathbf{Z}_3 + \mathbf{Z}_1 \parallel \mathbf{Z}_2} = \frac{60 \text{ V} \angle 10^\circ}{-j6 \Omega + 2.630 \Omega + j0.986 \Omega} = 10.597 \text{ A} \angle 72.322^\circ$$

$$\mathbf{I}'' = \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(3 \Omega \angle 0^\circ)(10.597 \text{ A} \angle 72.322^\circ)}{3 \Omega + j8 \Omega} = 3.721 \text{ A} \angle 2.878^\circ$$


$$\mathbf{I}_{L_1} = \mathbf{I}' + \mathbf{I}'' = 3.72 \text{ A} \angle -67.125^\circ + 3.721 \text{ A} \angle 2.878^\circ$$

$$= 1.446 \text{ A} - j3.427 \text{ A} + 3.716 \text{ A} + j0.187 \text{ A}$$

$$= 5.162 \text{ A} - j3.24 \text{ A}$$

$$= \mathbf{6.09 \text{ A} \angle -32.12^\circ}$$

2.

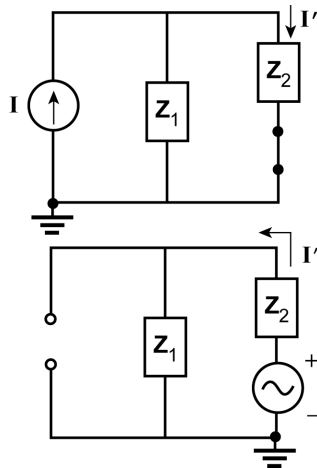

$$\mathbf{Z}_1 = 8 \Omega \angle 90^\circ, \mathbf{Z}_2 = 5 \Omega \angle -90^\circ$$

$$\mathbf{I} = 0.3 \text{ A} \angle 60^\circ, \mathbf{E} = 10 \text{ V} \angle 0^\circ$$

$$\mathbf{I}' = \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(8 \Omega \angle 90^\circ)(0.3 \text{ A} \angle 60^\circ)}{+j8 \Omega - j5 \Omega} = \frac{2.4 \text{ A} \angle 150^\circ}{3 \angle 90^\circ} = 0.8 \text{ A} \angle 60^\circ$$

$$\mathbf{I}'' = \frac{\mathbf{E}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{10 \text{ V} \angle 0^\circ}{+j8 \Omega - j5 \Omega} = \frac{10 \text{ A} \angle 0^\circ}{3 \angle 90^\circ} = 3.33 \text{ A} \angle -90^\circ$$


$$\mathbf{I}_C = \mathbf{I}' - \mathbf{I}'' = 0.8 \text{ A} \angle 60^\circ - 3.33 \text{ A} \angle -90^\circ$$

$$= (0.4 \text{ A} + j0.69 \text{ A}) + j3.33 \text{ A}$$

$$= 0.4 \text{ A} + j4.02 \text{ A}$$

$$= \mathbf{4.04 \text{ A} \angle 84.32^\circ}$$

3. E:

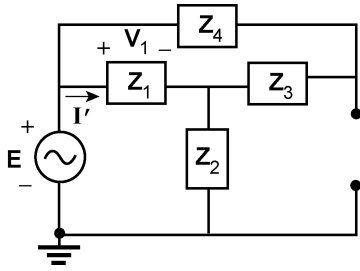

$$\mathbf{Z}_1 = 3 \Omega \angle 90^\circ, \mathbf{Z}_2 = 7 \Omega \angle -90^\circ$$

$$\mathbf{E} = 10 \text{ V} \angle 90^\circ$$

$$\mathbf{Z}_3 = 6 \Omega \angle -90^\circ, \mathbf{Z}_4 = 4 \Omega \angle 0^\circ$$

$$\mathbf{Z}' = \mathbf{Z}_1 \parallel (\mathbf{Z}_3 + \mathbf{Z}_4)$$

$$= 3 \Omega \angle 90^\circ \parallel (4 \Omega - j6 \Omega)$$

$$= 3 \Omega \angle 90^\circ \parallel 7.21 \Omega \angle -56.31^\circ$$

$$= 4.33 \Omega \angle 70.56^\circ$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}' \mathbf{E}}{\mathbf{Z}' + \mathbf{Z}_2}$$


$$= \frac{(4.33 \Omega \angle 70.56^\circ)(10 \text{ V} \angle 90^\circ)}{(1.44 \Omega + j4.08 \Omega) - j7 \Omega}$$

$$= \frac{43.3 \text{ V} \angle 160.56^\circ}{3.26 \angle -63.75^\circ} = 13.28 \text{ V} \angle 224.31^\circ$$

$$\mathbf{I}' = \frac{\mathbf{V}_1}{\mathbf{Z}_1} = \frac{13.28 \text{ V} \angle 224.31^\circ}{3 \Omega \angle 90^\circ}$$

$$= 4.43 \text{ A} \angle 134.31^\circ$$

I:

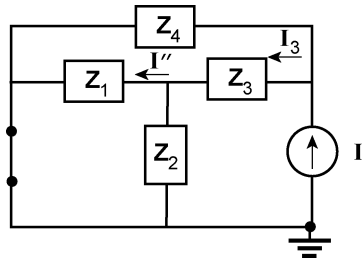

$$\mathbf{Z}'' = \mathbf{Z}_3 + \mathbf{Z}_1 \parallel \mathbf{Z}_2$$

$$= -j6 \Omega + 3 \Omega \angle 90^\circ \parallel 7 \Omega \angle -90^\circ$$

$$= -j6 \Omega + 5.25 \Omega \angle 90^\circ$$

$$= -j6 \Omega + j5.25 \Omega$$

$$= -j0.75 \Omega = 0.75 \Omega \angle -90^\circ$$

$$\text{CDR: } \mathbf{I}_3 = \frac{\mathbf{Z}_4 \mathbf{I}}{\mathbf{Z}_4 + \mathbf{Z}''} = \frac{(4 \Omega \angle 0^\circ)(0.6 \text{ A} \angle 120^\circ)}{4 \Omega - j0.75 \Omega} = \frac{2.4 \text{ A} \angle 120^\circ}{4.07 \angle -10.62^\circ}$$

$$= 0.59 \text{ A} \angle 130.62^\circ$$

$$\mathbf{I}'' = \frac{\mathbf{Z}_2 \mathbf{I}_3}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(7 \Omega \angle -90^\circ)(0.59 \text{ A} \angle 130.62^\circ)}{-j7 \Omega + j3 \Omega} = \frac{4.13 \text{ A} \angle 40.62^\circ}{4 \angle -90^\circ}$$

$$= 1.03 \text{ A} \angle 130.62^\circ$$


$$\mathbf{I}_L = \mathbf{I}' - \mathbf{I}'' \text{ (direction of } \mathbf{I}') \text{)}$$

$$= 4.43 \text{ A} \angle 134.31^\circ - 1.03 \text{ A} \angle 130.62^\circ$$

$$= (-3.09 \text{ A} + j3.17 \text{ A}) - (-0.67 \text{ A} + j0.78 \text{ A}) = -2.42 \text{ A} + j2.39 \text{ A}$$

$$= 3.40 \text{ A} \angle 135.36^\circ$$

4. I:

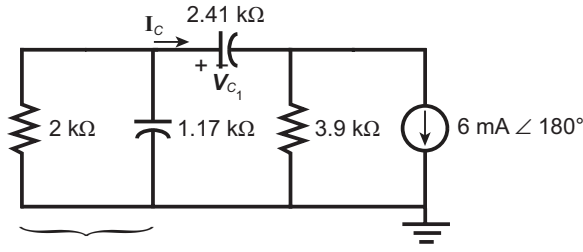

$$(2 \text{ k}\Omega \angle 0^\circ) \parallel (1.17 \text{ k}\Omega \angle -90^\circ) = 1.01 \text{ k}\Omega \angle -59.67^\circ$$

$$X_{C_1} = \frac{1}{2\pi(20 \text{ kHz})(6.8 \text{ nF})} = 1.17 \text{ k}\Omega$$


$$X_{C_2} = \frac{1}{2\pi(20 \text{ kHz})(3.3 \text{ nF})} = 2.41 \text{ k}\Omega$$

$$\begin{aligned} Z' &= 2.41 \text{ k}\Omega \angle -90^\circ + 1.01 \text{ k}\Omega \angle -59.67^\circ \\ &= -j2.41 \text{ k}\Omega + 0.510 \text{ k}\Omega - j0.871 \text{ k}\Omega \\ &= 0.510 \text{ k}\Omega - j3.28 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} I_C &= \frac{\mathbf{R}_2 \mathbf{I}}{\mathbf{R}_2 + \mathbf{Z}'} = \frac{(3.9 \text{ k}\Omega \angle 0^\circ)(6 \text{ mA} \angle 180^\circ)}{3.9 \text{ k}\Omega + 0.510 \text{ k}\Omega - j3.28 \text{ k}\Omega} \\ &= \frac{23.4 \text{ mA} \angle 180^\circ}{4.41 \angle -j3.28} = \frac{23.4 \text{ mA} \angle 180^\circ}{5.5 \angle -36.64^\circ} \\ &= 4.25 \text{ mA} \angle 216.64^\circ \end{aligned}$$

$$\begin{aligned} V_{C_1} &= I_C X_{C_2} = (4.25 \text{ mA} \angle 216.64^\circ)(2.41 \text{ k}\Omega \angle -90^\circ) \\ &= 10.24 \text{ V} \angle 126.64^\circ \end{aligned}$$

E:

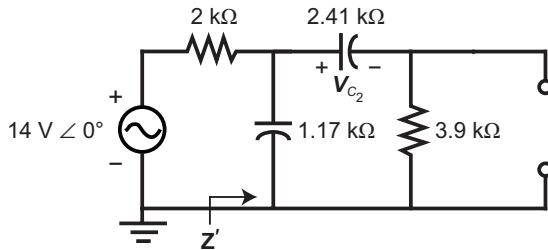


$$\begin{aligned} Z' &= (1.17 \text{ k}\Omega \angle -90^\circ) \parallel (3.9 \text{ k}\Omega - j2.41 \text{ k}\Omega) = (1.17 \text{ k}\Omega \angle -90^\circ) \parallel (4.58 \text{ k}\Omega \angle -31.71^\circ) \\ &= \frac{(1.17 \text{ k}\Omega \angle -90^\circ)(4.58 \text{ k}\Omega \angle -31.71^\circ)}{-j1.17 \text{ k}\Omega + j3.9 \text{ k}\Omega - j2.41 \text{ k}\Omega} = \frac{5.36 \text{ k}\Omega \angle -121.71^\circ}{3.9 - j3.58} \\ &= \frac{5.36 \text{ k}\Omega \angle -121.71^\circ}{5.29 \angle -42.55^\circ} = 1.01 \text{ k}\Omega \angle -79.16^\circ \end{aligned}$$

$$\begin{aligned} V_{Z'} &= \frac{\mathbf{Z}'(\mathbf{E})}{\mathbf{Z}' + \mathbf{R}_1} = \frac{(1.01 \text{ k}\Omega \angle -79.16^\circ)(14 \text{ V} \angle 0^\circ)}{2 \text{ k}\Omega + 1.01 \text{ k}\Omega \angle -79.16^\circ} \\ &= \frac{14.14 \text{ V} \angle -79.16^\circ}{2 + 0.189 - j0.991} = \frac{14.14 \text{ V} \angle -79.16^\circ}{2.189 - j0.991} = \frac{14.14 \text{ V} \angle -79.16^\circ}{2.4 \angle -24.36^\circ} \\ &= 5.89 \text{ V} \angle -54.8^\circ \end{aligned}$$

$$\begin{aligned} V_{C_2} &= \frac{\mathbf{X}_{C_2} V_{Z'}}{\mathbf{X}_{C_2} + \mathbf{R}_2} = \frac{(2.41 \text{ k}\Omega \angle -90^\circ)(5.89 \text{ V} \angle -54.8^\circ)}{-j2.41 \text{ k}\Omega + 3.9 \text{ k}\Omega} = \frac{14.195 \text{ V} \angle -144.8^\circ}{3.9 \text{ k}\Omega - j2.41 \text{ k}\Omega} \\ &= \frac{14.195 \text{ V} \angle -144.8^\circ}{4.58 \angle -31.71^\circ} = 3.1 \text{ V} \angle -113^\circ \end{aligned}$$

$$\begin{aligned}
 \mathbf{V}_C &= \mathbf{V}_{C_1} + \mathbf{V}_{C_2} \\
 &= 10.24 \text{ V } \angle 126.64^\circ + 3.1 \text{ V } \angle -113^\circ \\
 &= (-6.11 \text{ V} + j8.21 \text{ V}) + (-1.21 \text{ V} - j2.85 \text{ V}) \\
 &= -7.31 \text{ V} + j5.36 \text{ V} \\
 &= \mathbf{9.06 \text{ V } \angle 143.75^\circ}
 \end{aligned}$$

5. E:

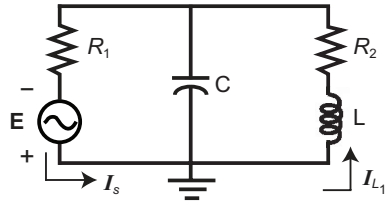

$$\begin{aligned}
 X_L &= 2\pi fL = 2\pi(10 \text{ kHz})(20 \text{ mH}) \\
 &= 1.26 \text{ k}\Omega
 \end{aligned}$$


$$\begin{aligned}
 X_C &= \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \text{ kHz})(0.01 \mu\text{F})} \\
 &= 1.59 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{Z}_T &= R_1 \angle 0^\circ + X_C \angle -90^\circ \parallel (R_2 \angle 0^\circ + X_L \angle 90^\circ) \\
 &= 1 \text{ k}\Omega + (1.59 \text{ k}\Omega \angle -90^\circ) \parallel (2.2 \text{ k}\Omega + j1.26 \text{ k}\Omega) \\
 &= 1 \text{ k}\Omega + \frac{(1.59 \text{ k}\Omega \angle -90^\circ)(2.54 \text{ k}\Omega \angle 29.8^\circ)}{2.54 \text{ k}\Omega \angle 29.8^\circ} \\
 &= 1 \text{ k}\Omega + \frac{(1.59 \text{ k}\Omega \angle -90^\circ)(2.54 \text{ k}\Omega \angle 29.8^\circ)}{-j1.59 \text{ k}\Omega + 2.2 \text{ k}\Omega + j1.26 \text{ k}\Omega} \\
 &= 1 \text{ k}\Omega + \frac{4.04 \text{ k}\Omega \angle -60.2^\circ}{2.2 - j0.33} = 1 \text{ k}\Omega + \frac{4.04 \text{ k}\Omega \angle -60.2^\circ}{2.23 \angle -8.46^\circ} \\
 &= 1 \text{ k}\Omega + 1.81 \text{ k}\Omega \angle -51.74^\circ = 1 \text{ k}\Omega + (1.12 \text{ k}\Omega - j1.42 \text{ k}\Omega) \\
 &= 2.12 \text{ k}\Omega - j1.42 \text{ k}\Omega \\
 &= 2.55 \text{ k}\Omega \angle -33.82^\circ
 \end{aligned}$$

$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{16 \text{ V } \angle 60^\circ}{2.55 \text{ k}\Omega \angle -33.82^\circ} = 6.27 \text{ mA } \angle 93.82^\circ$$

$$\begin{aligned}
 \mathbf{I}_{L_1} &= \frac{(X_C \angle -90^\circ)(\mathbf{I}_s)}{X_C \angle -90^\circ + R_2 \angle 0^\circ + X_L \angle 90^\circ} \\
 &= \frac{(1.59 \text{ k}\Omega \angle -90^\circ)(6.27 \text{ mA } \angle 93.82^\circ)}{-j1.59 \text{ k}\Omega + 2.2 \text{ k}\Omega + j1.26 \text{ k}\Omega} \\
 &= \frac{9.97 \text{ mA } \angle 3.82^\circ}{2.2 - j0.33} = \frac{9.97 \text{ mA } \angle 3.82^\circ}{2.22 \angle -8.53^\circ} \\
 \uparrow \mathbf{I}_{L_1} &= 4.49 \text{ mA } \angle 12.35^\circ
 \end{aligned}$$

I:

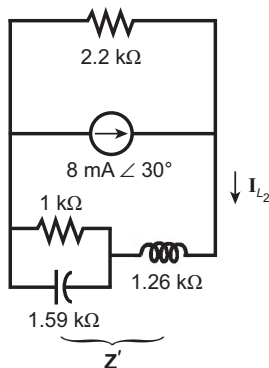


$$\begin{aligned}
 (1 \text{ k}\Omega \angle 0^\circ) \parallel (1.59 \text{ k}\Omega \angle -90^\circ) &= 847.74 \Omega \angle -32.17^\circ \\
 \mathbf{Z}' &= \mathbf{X}_L + 847.74 \Omega \angle -32.17^\circ \\
 &= j1.26 \text{ k}\Omega + 717.59 \Omega - j451.36 \Omega \\
 &= 0.72 \text{ k}\Omega + j0.81 \text{ k}\Omega \\
 &= 1.08 \text{ k}\Omega \angle 48.36^\circ
 \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{L_2} &= \frac{\mathbf{R}_2(\mathbf{I})}{\mathbf{R}_2 + \mathbf{Z}'} = \frac{(2.2 \text{ k}\Omega \angle 0^\circ)(8 \text{ mA} \angle 30^\circ)}{2.2 \text{ k}\Omega + 0.72 \text{ k}\Omega + j0.81 \text{ k}\Omega} \\ &= \frac{17.6 \text{ mA} \angle 30^\circ}{2.92 + j0.81} = \frac{17.6 \text{ mA} \angle 30^\circ}{3.03 \angle 15.50^\circ} \\ &= 5.81 \text{ mA} \angle 14.5^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_L &= \mathbf{I}_{L_1} - \mathbf{I}_{L_2} \text{ (direction of } \mathbf{I}_{L_1}\text{)} \\ &= (4.49 \text{ mA} \angle 12.35^\circ) - (5.81 \text{ mA} \angle 14.5^\circ) \\ &= (4.39 \text{ mA} + j0.96 \text{ mA}) - (5.62 \text{ mA} + j1.45 \text{ mA}) \\ &= -1.23 \text{ mA} - j0.49 \text{ mA} \\ &= \mathbf{1.32 \text{ mA} \angle -158.2^\circ} \end{aligned}$$

6. AC:

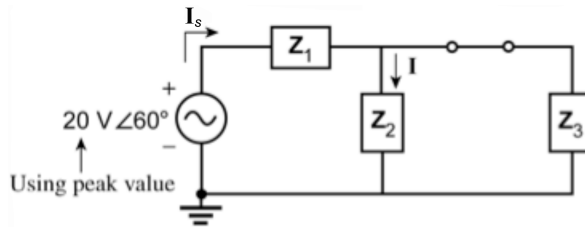

$$\begin{aligned} X_C &= \frac{1}{2\pi fC} = \frac{1}{\omega C} = \frac{1}{(1000)(4.7 \mu\text{F})} \\ &= 212.77 \Omega \\ X_L &= 2\pi fL = \omega L = (1000)(47 \text{ mH}) \\ &= 47 \Omega \end{aligned}$$

$$\mathbf{Z}_1 = 212.77 \Omega \angle -90^\circ, \mathbf{Z}_2 = 47 \Omega \angle 0^\circ, \mathbf{Z}_3 = 22 \Omega + j47 \Omega = 51.89 \Omega \angle 64.92^\circ$$

$$\mathbf{Z}_2 \parallel \mathbf{Z}_3 = 29.23 \Omega \angle 30.66^\circ$$

$$\begin{aligned} \mathbf{Z}_T &= \mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3 = -j212.77 \Omega + 25.14 \Omega + j14.91 \Omega \\ &= 25.14 \Omega - j197.86 \Omega = 199.45 \Omega \angle -82.76^\circ \end{aligned}$$


$$\mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{20 \text{ V} \angle 60^\circ}{199.45 \Omega \angle -82.76^\circ} = 0.1 \text{ A} \angle 142.76^\circ$$

$$\mathbf{I} = \frac{\mathbf{Z}_3 \mathbf{I}_s}{\mathbf{Z}_3 + \mathbf{Z}_2} = \frac{(51.89 \Omega \angle 64.92^\circ)(0.1 \text{ A} \angle 142.76^\circ)}{22 \Omega + j47 \Omega + 47 \Omega} = \frac{5.19 \text{ A} \angle 207.68^\circ}{83.49 \angle 34.26^\circ}$$

$$\mathbf{I} = 62.16 \text{ mA} \angle 173.42^\circ$$

$$\text{and } i = 62.16 \times 10^{-3} \sin(1000t + 173.42^\circ)$$


DC:

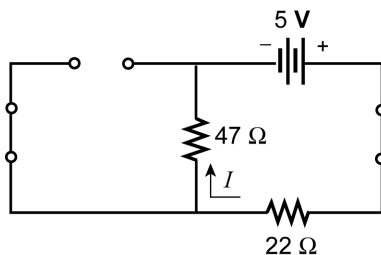


$$\begin{aligned} I &= \frac{5 \text{ V}}{22 \Omega + 47 \Omega} = \frac{5 \text{ V}}{69 \Omega} \\ &= 72.46 \text{ mA} \end{aligned}$$

$$i = -72.46 \text{ mA} + 62.16 \times 10^{-3} \sin(1000t + 173.42^\circ)$$

7. DC:

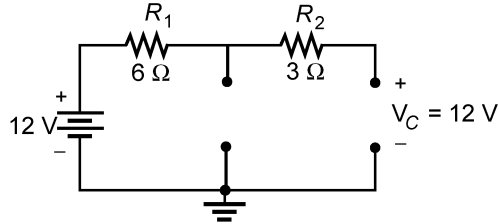


AC:

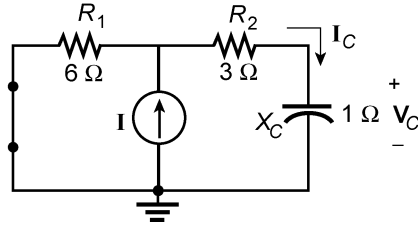

$$\begin{aligned} I_C &= \frac{(6 \Omega \angle 0^\circ)(I)}{6 \Omega + 3 \Omega - j1 \Omega} \\ &= \frac{(6 \Omega \angle 0^\circ)(4 \text{ A} \angle 0^\circ)}{9 \Omega - j1 \Omega} \\ &= \frac{24 \text{ A} \angle 0^\circ}{9.055 \angle -6.34^\circ} \\ &= 2.65 \text{ A} \angle 6.34^\circ \end{aligned}$$

$$\begin{aligned} V_C &= I_C X_C = (2.65 \text{ A} \angle 6.34^\circ)(1 \Omega \angle -90^\circ) = 2.65 \text{ V} \angle -83.66^\circ \\ &= 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ \\ v_C &= 12 \text{ V} + 3.75 \sin(\omega t - 83.66^\circ) \end{aligned}$$


8.

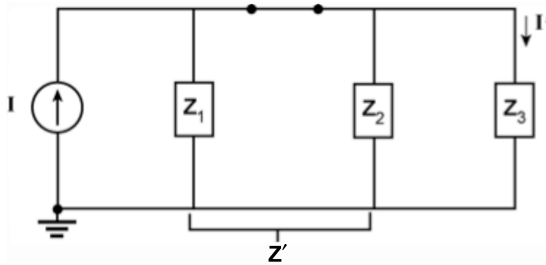

$$\begin{aligned} E &= 20 \text{ V} \angle 0^\circ \\ Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega - j5 \text{ k}\Omega \\ &= 7.071 \text{ k}\Omega \angle -45^\circ \\ Z_3 &= 5 \text{ k}\Omega \angle 90^\circ \\ I &= 5 \text{ mA} \angle 0^\circ \end{aligned}$$

$$Z' = Z_1 \parallel Z_2 = 10 \text{ k}\Omega \angle 0^\circ \parallel 7.071 \text{ k}\Omega \angle -45^\circ = 4.472 \text{ k}\Omega \angle -26.57^\circ$$
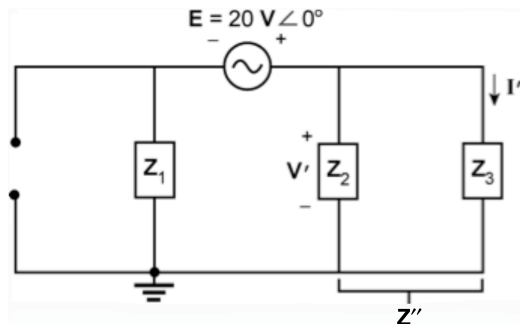
$$\begin{aligned} \text{(CDR)} \quad I' &= \frac{Z I}{Z' + Z_3} = \frac{(4.472 \text{ k}\Omega \angle -26.57^\circ)(5 \text{ mA} \angle 0^\circ)}{4 \text{ k}\Omega - j2 \text{ k}\Omega + j5 \text{ k}\Omega} = \frac{22.36 \text{ mA} \angle -26.57^\circ}{5 \angle 36.87^\circ} \\ &= 4.472 \text{ mA} \angle -63.44^\circ \end{aligned}$$




$$\begin{aligned} Z'' &= Z_2 \parallel Z_3 \\ &= 7.071 \text{ k}\Omega \angle -45^\circ \parallel 5 \text{ k}\Omega \angle 90^\circ \\ &= 7.071 \text{ k}\Omega \angle 45^\circ \end{aligned}$$

$$\begin{aligned} \text{(VDR)} \quad V' &= \frac{Z'' E}{Z'' + Z_1} = \frac{(7.071 \text{ k}\Omega \angle 45^\circ)(20 \text{ V} \angle 0^\circ)}{(5 \text{ k}\Omega + j5 \text{ k}\Omega) + (10 \text{ k}\Omega)} = \frac{141.42 \text{ V} \angle 45^\circ}{15.81 \angle 18.435^\circ} \\ &= 8.945 \text{ V} \angle 26.565^\circ \end{aligned}$$

$$\mathbf{I}'' = \frac{\mathbf{V}'}{\mathbf{Z}_3} = \frac{8.945 \text{ V} \angle 26.565^\circ}{5 \text{ k}\Omega \angle 90^\circ} = 1.789 \text{ mA} \angle -63.435^\circ = 0.8 \text{ mA} - j1.6 \text{ mA}$$


$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' = (2 \text{ mA} - j4 \text{ mA}) + (0.8 \text{ mA} - j1.6 \text{ mA}) = 2.8 \text{ mA} - j5.6 \text{ mA} \\ = \mathbf{6.26 \text{ mA} \angle -63.43^\circ}$$

9.

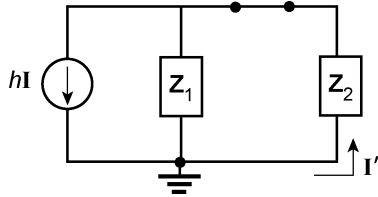

$$\begin{aligned} \mathbf{Z}_1 &= 20 \text{ k}\Omega \angle 0^\circ \\ \mathbf{Z}_2 &= 10 \text{ k}\Omega \angle 90^\circ \\ \mathbf{I} &= 2 \text{ mA} \angle 0^\circ \\ \mathbf{E} &= 10 \text{ V} \angle 0^\circ \end{aligned}$$

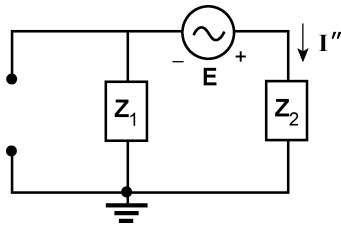
$$\mathbf{I}' = \frac{\mathbf{Z}_1(h\mathbf{I})}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(20 \text{ k}\Omega \angle 0^\circ)(100)(2 \text{ mA} \angle 0^\circ)}{20 \text{ k}\Omega + j10 \text{ k}\Omega} = 0.179 \text{ A} \angle -26.57^\circ$$



$$\begin{aligned} \mathbf{I}'' &= \frac{\mathbf{E}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{10 \text{ V} \angle 0^\circ}{22.36 \text{ k}\Omega \angle 26.57^\circ} \\ &= 0.447 \text{ mA} \angle -26.57^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_L &= \mathbf{I}' - \mathbf{I}'' \text{ (direction of } \mathbf{I}') \\ &= 179 \text{ mA} \angle -26.57^\circ - 0.447 \text{ mA} \angle -26.57^\circ \\ &= \mathbf{178.55 \text{ mA} \angle -26.57^\circ} \end{aligned}$$


10. μV :

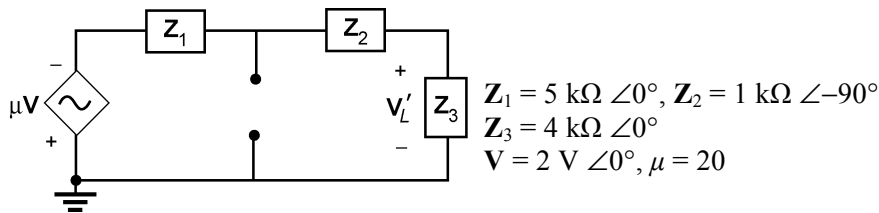

$$\begin{aligned} \mathbf{Z}_1 &= 5 \text{ k}\Omega \angle 0^\circ, \mathbf{Z}_2 = 1 \text{ k}\Omega \angle -90^\circ \\ \mathbf{Z}_3 &= 4 \text{ k}\Omega \angle 0^\circ \\ \mathbf{V} &= 2 \text{ V} \angle 0^\circ, \mu = 20 \end{aligned}$$

$$\mathbf{V}'_L = \frac{-\mathbf{Z}_3(\mu\mathbf{V})}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} = \frac{-(4 \text{ k}\Omega \angle 0^\circ)(20)(2 \text{ V} \angle 0^\circ)}{5 \text{ k}\Omega - j1 \text{ k}\Omega + 4 \text{ k}\Omega} = -17.67 \text{ V} \angle 6.34^\circ$$

I:

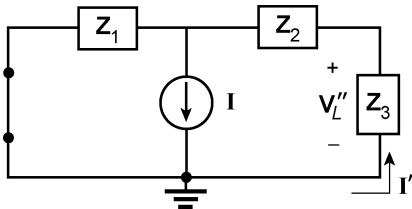


$$\begin{aligned} \text{CDR: } \mathbf{I}' &= \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} \\ &= \frac{(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{9.056 \text{ k}\Omega \angle -6.34^\circ} \\ &= 1.104 \text{ mA} \angle 6.34^\circ \end{aligned}$$

$$\mathbf{V}''_L = -\mathbf{I}' \mathbf{Z}_3 = -(1.104 \text{ mA} \angle 6.34^\circ)(4 \text{ k}\Omega \angle 0^\circ) = -4.416 \text{ V} \angle 6.34^\circ$$

$$\mathbf{V}_L = \mathbf{V}'_L + \mathbf{V}''_L = -17.67 \text{ V} \angle 6.34^\circ - 4.416 \text{ V} \angle 6.34^\circ = \mathbf{-22.09 \text{ V} \angle 6.34^\circ}$$


11.

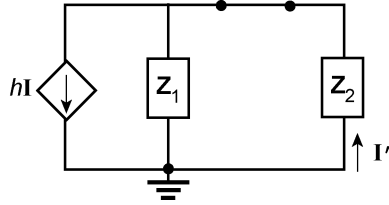

$$Z_1 = 20 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 5 \text{ k}\Omega + j5 \text{ k}\Omega$$
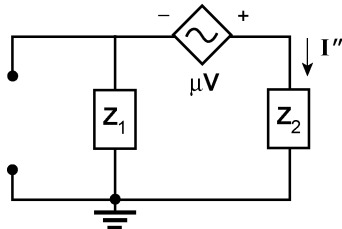
$$I' = \frac{Z_1(hI)}{Z_1 + Z_2} = \frac{(20 \text{ k}\Omega \angle 0^\circ)(100)(1 \text{ mA} \angle 0^\circ)}{20 \text{ k}\Omega + 5 \text{ k}\Omega + j5 \text{ k}\Omega} = 78.45 \text{ mA} \angle -11.31^\circ$$




$$I'' = \frac{\mu\text{V}}{Z_1 + Z_2} = \frac{(20)(10 \text{ V} \angle 0^\circ)}{25.495 \text{ k}\Omega \angle 11.31^\circ} = 7.845 \text{ mA} \angle -11.31^\circ$$

$$I_L = I' - I'' \text{ (direction of } I')$$

$$= 78.45 \text{ mA} \angle -11.31^\circ - 7.845 \text{ mA} \angle -11.31^\circ$$

$$= 70.61 \text{ mA} \angle -11.31^\circ$$

12.

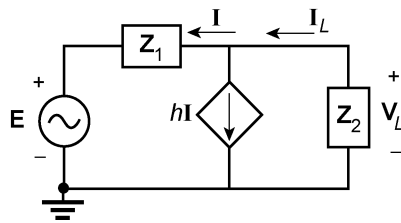

$$Z_1 = 2 \text{ k}\Omega \angle 0^\circ, Z_2 = 2 \text{ k}\Omega \angle 0^\circ$$

$$V_L = -I_L Z_2$$

$$I_L = hI + I = (h + 1)I$$

$$V_L = -(h + 1)IZ_2$$

$$\text{and by KVL: } V_L = IZ_1 + E$$

$$\text{so that } I = \frac{V_L - E}{Z_1}$$

$$V_L = -(h + 1)IZ_2 = -(h + 1) \left[\frac{V_L - E}{Z_1} \right] Z_2$$


Subst. for Z_1, Z_2

$$V_L = -(h + 1)(V_L - E)$$

$$V_L(2 + h) = E(h + 1)$$

$$V_L = \frac{(h + 1)}{(h + 2)} E = \frac{51}{52} (20 \text{ V} \angle 53^\circ) = 19.62 \text{ V} \angle 53^\circ$$

13. I_1 :

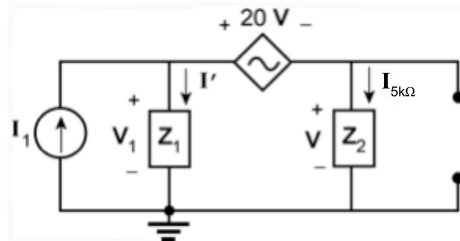

$$I_1 = 1 \text{ mA} \angle 0^\circ$$

$$Z_1 = 2 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 5 \text{ k}\Omega \angle 0^\circ$$

$$\text{KVL: } V_1 - 20 \text{ V} - V = 0$$

$$I' = \frac{V_1}{Z_1} \therefore I' = \frac{21 \text{ V}}{Z_1} \text{ or } V = \frac{Z_1 I'}{21}$$

$$V_1 = 21 \text{ V}$$


$$V = I_{5k\Omega} Z_2 = [I_1 - I'] Z_2$$

$$\frac{Z_1}{21} I' = I_1 Z_2 - I' Z_2$$

$$I' \left[\frac{Z_1}{21} + Z_2 \right] = I_1 Z_2$$

$$\text{and } I' = \frac{Z_2}{\frac{Z_1}{21} + Z_2} [I_1] = \frac{(5 \text{ k}\Omega \angle 0^\circ)(1 \text{ mA} \angle 0^\circ)}{\left(\frac{2 \text{ k}\Omega \angle 0^\circ}{21} \right) + 5 \text{ k}\Omega \angle 0^\circ} = 0.981 \text{ mA} \angle 0^\circ$$

I_2 :

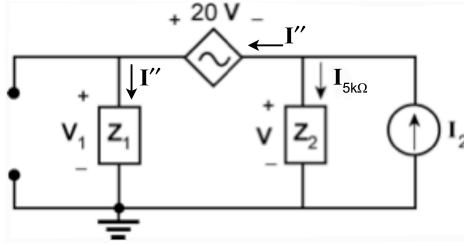

$$V_1 = 20 \text{ V} + V = 21 \text{ V}$$

$$I'' = \frac{V_1}{Z_1} = \frac{21 \text{ V}}{Z_1} \Rightarrow V = \frac{Z_1}{21} I''$$

$$I_{5k\Omega} = \frac{V}{Z_2} = \frac{Z_1}{21 Z_2} I''$$


$$I'' = I_2 - I_{5k\Omega} = I_2 - \frac{Z_1}{21 Z_2} I''$$

$$I'' \left[1 + \frac{Z_1}{21 Z_2} \right] = I_2$$

$$I'' = \frac{I_2}{1 + \frac{Z_1}{21 Z_2}} = \frac{2 \text{ mA} \angle 0^\circ}{1 + \frac{2 \text{ k}\Omega}{21(5 \text{ k}\Omega)}} = 1.963 \text{ mA} \angle 0^\circ$$

$$I = I' + I'' = 0.981 \text{ mA} \angle 0^\circ + 1.963 \text{ mA} \angle 0^\circ = 2.94 \text{ mA} \angle 0^\circ$$

14. E_1 :

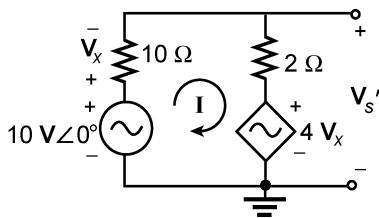

$$10 \text{ V} \angle 0^\circ - I 10 \Omega - I 2 \Omega - 4 V_x = 0$$


with $V_x = I 10 \Omega$

Solving for I :

$$I = \frac{10 \text{ V} \angle 0^\circ}{52 \Omega} = 192.31 \text{ mA} \angle 0^\circ$$

$$V'_s = 10 \text{ V} \angle 0^\circ - I(10 \Omega) = 10 \text{ V} - (192.31 \text{ mA} \angle 0^\circ)(10 \Omega \angle 0^\circ) = 8.08 \text{ V} \angle 0^\circ$$

I:

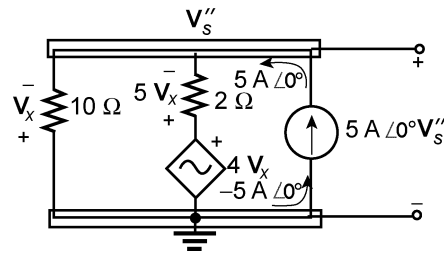

$$\Sigma I_i = \Sigma I_o$$

$$5 \text{ A } \angle 0^\circ + \frac{V_x}{10 \Omega} + \frac{5 V_x}{2 \Omega} = 0$$

$$5 \text{ A} + 0.1 V_x + 2.5 V_x = 0$$


$$2.6 V_x = -5 \text{ A}$$

$$V_x = -\frac{5}{2.6} \text{ V} = -1.923 \text{ V}$$

$$V_s'' = -V_x = -(-1.923 \text{ V}) = 1.923 \text{ V } \angle 0^\circ$$

$$V_s = V_s' + V_s'' = 8.08 \text{ V } \angle 0^\circ + 1.923 \text{ V } \angle 0^\circ = 10 \text{ V } \angle 0^\circ$$

15. Z_{Th} :

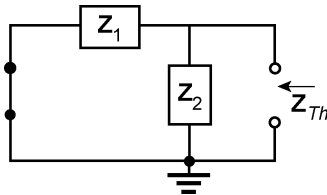


$$Z_1 = 3 \Omega \angle 0^\circ, Z_2 = 4 \Omega \angle 90^\circ$$

$$E = 100 \text{ V } \angle 0^\circ$$


$$Z_{Th} = Z_1 \parallel Z_2 = (3 \Omega \angle 0^\circ \parallel 4 \Omega \angle 90^\circ) \\ = 2.4 \Omega \angle 36.87^\circ = 1.92 \Omega + j1.44 \Omega$$

E_{Th} :

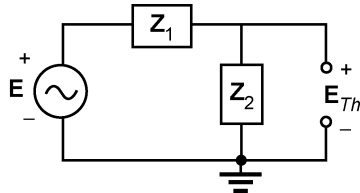


$$E_{Th} = \frac{Z_2 E}{Z_2 + Z_1} = \frac{(4 \Omega \angle 90^\circ)(100 \text{ V } \angle 0^\circ)}{5 \Omega \angle 53.13^\circ} \\ = 80 \text{ V } \angle 36.87^\circ$$

16. Z_{Th} :

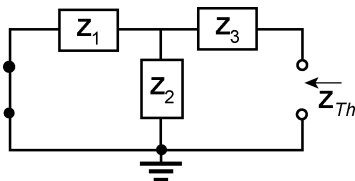


$$Z_{Th} = Z_3 + Z_1 \parallel Z_2 \\ = +j6 \text{ k}\Omega + (2 \text{ k}\Omega \angle 0^\circ \parallel 3 \text{ k}\Omega \angle -90^\circ) \\ = +j6 \text{ k}\Omega + 1.664 \text{ k}\Omega \angle -33.69^\circ \\ = +j6 \text{ k}\Omega + 1.385 \text{ k}\Omega - j0.923 \text{ k}\Omega \\ = 1.385 \text{ k}\Omega + j5.077 \text{ k}\Omega \\ = 5.26 \text{ k}\Omega \angle 74.74^\circ$$

E_{Th} :

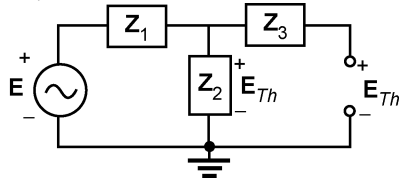


$$E_{Th} = \frac{Z_2 E}{Z_2 + Z_1} = \frac{(3 \text{ k}\Omega \angle -90^\circ)(20 \text{ V } \angle 0^\circ)}{2 \text{ k}\Omega - j3 \text{ k}\Omega} \\ = \frac{60 \text{ V } \angle -90^\circ}{3.606 \angle -56.31^\circ} = 16.64 \text{ V } \angle -33.69^\circ$$

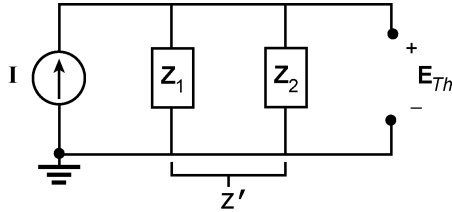17. From #35. $Z_{Th} = Z_1 \parallel Z_2$
 $Z_{Th} = Z_N = 21.31 \Omega \angle 32.2^\circ$


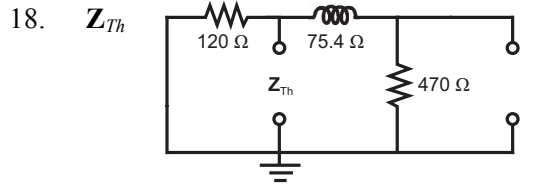
$$\begin{aligned} E_{Th} &= IZ' = IZ_{Th} \\ &= (0.1 \text{ A } \angle 0^\circ)(21.31 \Omega \angle 32.12^\circ) \\ &= 2.13 \text{ V } \angle 32.2^\circ \end{aligned}$$




$$X_L = 2\pi fL = 2\pi(1 \text{ kHz})(12 \text{ mH}) = 75.4 \Omega$$

$$\begin{aligned} Z_{Th} &= (120 \Omega \angle 0^\circ) \parallel \underbrace{470 \Omega + j75.4 \Omega}_{476.01 \angle 9.11^\circ} \\ &= \frac{(120 \Omega \angle 0^\circ)(476.01 \Omega \angle 9.11^\circ)}{120 \Omega + 470 \Omega + j75.4 \Omega} \\ &= \frac{57.12 \text{ k}\Omega \angle 9.11^\circ}{590 + j75.4 \Omega} \\ &= \frac{594.8 \angle 7.28^\circ}{594.8 \angle 7.28^\circ} \\ Z_{Th} &= 96.03 \Omega \angle 1.83^\circ \end{aligned}$$

E_{Th} Source conversion:
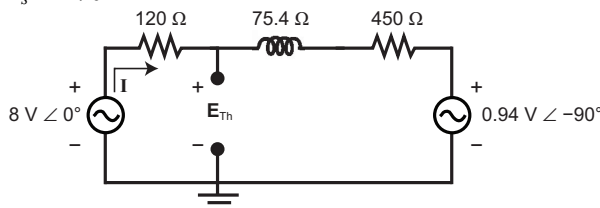
$$\begin{aligned} E_2 &= IZ = (2 \text{ mA } \angle -90^\circ)(470 \Omega \angle 0^\circ) = 0.94 \text{ V } \angle -90^\circ \\ R_s &= 470 \Omega \end{aligned}$$



$$\begin{aligned} I &= \frac{8 \text{ V } \angle 0^\circ - 0.94 \text{ V } \angle -90^\circ}{120 \Omega + 470 \Omega + j75.4 \Omega} \\ &= \frac{8 \text{ V } \angle 0^\circ - (-j0.94 \text{ V})}{590 \Omega + j75.4 \Omega} = \frac{8 \text{ V} + j0.94 \text{ V}}{594.8 \Omega \angle 7.28^\circ} \\ &= \frac{8.055 \text{ V } \angle 6.70^\circ}{594.8 \Omega \angle 7.28^\circ} \\ &= 13.54 \text{ mA } \angle -0.58^\circ \end{aligned}$$

$$\begin{aligned} E_{Th} &= 8 \text{ V } \angle 0^\circ - IR = 8 \text{ V } \angle 0^\circ - (13.54 \text{ mA } \angle -0.58^\circ)(120 \Omega) \\ &= 8 \text{ V } \angle 0^\circ - 1.62 \text{ V } \angle -0.58^\circ \\ &= 8 \text{ V} - (1.62 \text{ V} - j16.4 \times 10^{-3} \text{ V}) \\ &= 8 \text{ V} - 1.62 \text{ V} + j16.4 \times 10^{-3} \text{ V} \\ &= 8 \text{ V} - 1.62 \text{ V} + j0.016 \text{ V} \\ &= 6.38 \text{ V} + j16.4 \times 10^{-3} \text{ V} \end{aligned}$$


$$19. \quad X_{C_1} = X_{C_2} = \frac{1}{2\pi fC} = \frac{1}{2\pi(1 \text{ kHz})(0.047 \mu\text{F})} = 3.39 \text{ k}\Omega$$

Source conversions:

$$\mathbf{Z}' = \mathbf{R}_1 + \mathbf{X}_{C_1} = 2 \text{ k}\Omega - j3.39 \text{ k}\Omega = 3.94 \text{ k}\Omega \angle -59.46^\circ$$

$$\mathbf{I}_1 = \frac{\mathbf{E}_1}{\mathbf{Z}'} = \frac{10 \text{ V} \angle 0^\circ}{3.94 \text{ k}\Omega \angle -59.46^\circ} = 2.53 \text{ mA} \angle 59.46^\circ$$
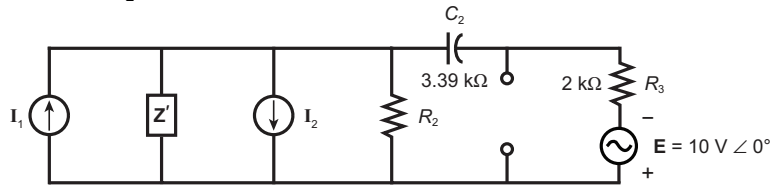
$$\mathbf{I}_2 = \frac{\mathbf{E}_2}{\mathbf{R}_2} = \frac{10 \text{ V} \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} = 5 \text{ mA} \angle 0^\circ, \quad \mathbf{E} = \mathbf{I}\mathbf{Z} = (5 \text{ mA} \angle 0^\circ)(2 \text{ k}\Omega \angle 0^\circ) = 10 \text{ V} \angle 0^\circ$$




$$\begin{aligned} \mathbf{I}_T &= \mathbf{I}_1 - \mathbf{I}_2 = 2.53 \text{ mA} \angle 59.46^\circ - 5 \text{ mA} \angle 0^\circ \\ &= 1.29 \text{ mA} + j2.18 \text{ mA} - 5 \text{ mA} \\ &= -2.47 \text{ mA} + j2.18 \text{ mA} \\ &= 3.29 \text{ mA} \angle 138.57^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{Z}' \parallel \mathbf{R}_2 &= (3.94 \text{ k}\Omega \angle -59.46^\circ) \parallel (2 \text{ k}\Omega \angle 0^\circ) \\ &= \frac{(3.94 \text{ k}\Omega \angle -59.46^\circ)(2 \text{ k}\Omega \angle 0^\circ)}{2 \text{ k}\Omega - j3.39 \text{ k}\Omega + 2 \text{ k}\Omega} \\ &= \frac{7.88 \text{ k}\Omega \angle -59.46^\circ}{4 - j3.39} = \frac{7.88 \text{ k}\Omega \angle -59.46^\circ}{5.24 \angle -40.28^\circ} \\ &= 1.51 \text{ k}\Omega \angle -19.18^\circ \end{aligned}$$

Source conversion:

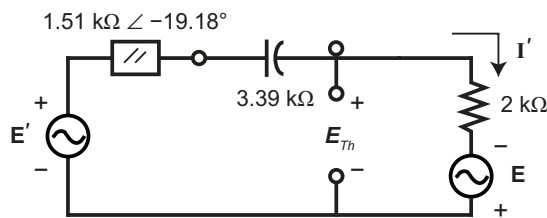
$$\begin{aligned} \mathbf{E}' &= \mathbf{I}\mathbf{Z} = (3.29 \text{ mA} \angle 138.57^\circ)(1.51 \text{ k}\Omega \angle -19.18^\circ) \\ &= 4.97 \text{ V} \angle 119.39^\circ \end{aligned}$$




$$\begin{aligned} \mathbf{Z}_{Th} &= (2 \text{ k}\Omega \angle 0^\circ) \parallel (1.51 \text{ k}\Omega \angle -19.18^\circ - j3.39 \text{ k}\Omega) \\ &= (2 \text{ k}\Omega \angle 0^\circ) \parallel (1.43 \text{ k}\Omega - j0.496 \text{ k}\Omega - j3.39 \text{ k}\Omega) \\ &= (2 \text{ k}\Omega \angle 0^\circ) \parallel (1.43 \text{ k}\Omega - j3.89 \text{ k}\Omega) \\ &= (2 \text{ k}\Omega \angle 0^\circ) \parallel (4.14 \text{ k}\Omega \angle -69.82^\circ) \\ &= \frac{(2 \text{ k}\Omega \angle 0^\circ)(4.14 \text{ k}\Omega \angle -69.82^\circ)}{2 \text{ k}\Omega + 1.43 \text{ k}\Omega - j3.89 \text{ k}\Omega} \\ &= \frac{8.28 \text{ k}\Omega \angle -69.82^\circ}{3.43 - j3.89} \end{aligned}$$

$$\begin{aligned}
&= \frac{8.28 \text{ k}\Omega \angle -69.82^\circ}{5.19 \angle -48.6^\circ} \\
\mathbf{Z}_{Th} &= \mathbf{1.6 \text{ k}\Omega \angle -21.22^\circ} \\
\mathbf{I}' &= \frac{\mathbf{E}' + \mathbf{E}}{2 \text{ k}\Omega - j3.39 \text{ k}\Omega + 1.51 \text{ k}\Omega \angle -19.18^\circ} \\
&= \frac{4.97 \text{ V} \angle 119.39^\circ + 10 \text{ V} \angle 0^\circ}{2 \text{ k}\Omega - j3.39 \text{ k}\Omega + 1.43 \text{ k}\Omega \angle -j0.496 \text{ k}\Omega} \\
&= \frac{-2.44 \text{ V} + j4.33 \text{ V} + 10 \text{ V}}{3.43 \text{ k}\Omega - j3.89 \text{ k}\Omega} \\
&= \frac{7.56 \text{ V} + j4.33 \text{ V}}{5.19 \text{ k}\Omega \angle -48.6^\circ} = \frac{8.71 \text{ V} \angle 29.8^\circ}{5.19 \text{ k}\Omega \angle -48.6^\circ} \\
&= 1.68 \text{ mA} \angle 78.4^\circ \\
\mathbf{E}_{Th} - \mathbf{V}_{2\text{k}\Omega} + \mathbf{E} &= 0 \\
\mathbf{E}_{Th} &= \mathbf{V}_{2\text{k}\Omega} - \mathbf{E} \\
&= (\mathbf{I}') (2 \text{ k}\Omega) - 10 \text{ V} \angle 0^\circ \\
&= (1.68 \text{ mA} \angle 78.4^\circ) (2 \text{ k}\Omega \angle 0^\circ) - 10 \text{ V} \\
&= 3.36 \text{ V} \angle 78.4^\circ - 10 \text{ V} \\
&= 0.68 \text{ V} + j3.29 \text{ V} - 10 \text{ V} \\
&= -9.32 \text{ V} + j3.29 \text{ V} \\
\mathbf{E}_{Th} &= \mathbf{9.88 \text{ V} \angle 160.56^\circ}
\end{aligned}$$

20.

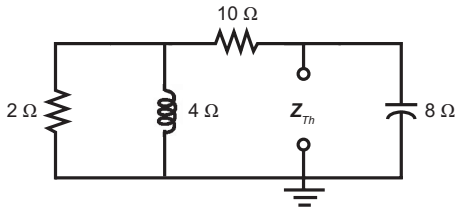

$$\begin{aligned}
\mathbf{Z}_{Th} &= (8 \Omega \angle -90^\circ) \parallel (10 \Omega + 2 \Omega \parallel 4 \Omega \angle 90^\circ) \\
&= (8 \Omega \angle -90^\circ) \parallel \left(10 \Omega + \frac{8 \Omega \angle 90^\circ}{2 + j4} \right) \\
&= (8 \Omega \angle -90^\circ) \parallel \left(10 \Omega + \frac{8 \Omega \angle 90^\circ}{4.47 \angle 63.44^\circ} \right) \\
&= (8 \Omega \angle -90^\circ) \parallel \left(10 \Omega + 1.79 \Omega \angle 26.56^\circ \right) \\
&= (8 \Omega \angle -90^\circ) \parallel \left(10 \Omega + 1.6 \Omega + j0.8 \Omega \right) \\
&= (8 \Omega \angle -90^\circ) \parallel \left(11.6 \Omega + j0.8 \Omega \right) \\
&= (8 \Omega \angle -90^\circ) \parallel (11.63 \Omega \angle 3.95^\circ) \\
&= \frac{92.8 \Omega \angle -86.05^\circ}{-j8 + 11.6 + j0.8} = \frac{92.8 \Omega \angle -86.05^\circ}{11.6 - j7.2} \\
&= \frac{92.8 \Omega \angle -86.05^\circ}{13.65 \angle -31.83^\circ} \\
\mathbf{Z}_{Th} = \mathbf{Z}_N &= \mathbf{6.79 \Omega \angle -54.22^\circ}
\end{aligned}$$

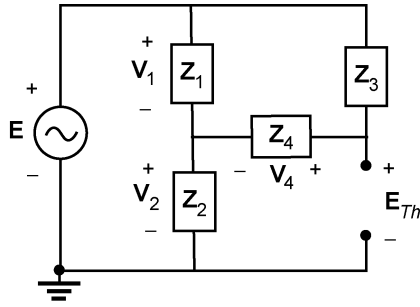


$$\begin{aligned}
 \mathbf{Z}_1 &= 2 \Omega \angle 0^\circ, \mathbf{Z}_3 = 8 \Omega \angle -90^\circ \\
 \mathbf{Z}_2 &= 4 \Omega \angle 90^\circ, \mathbf{Z}_4 = 10 \Omega \angle 0^\circ \\
 \mathbf{E} &= 50 \text{ V} \angle 0^\circ \\
 \mathbf{E}_{Th} &= \mathbf{V}_2 + \mathbf{V}_4 \\
 \mathbf{V}_2 &= \frac{\mathbf{Z}_2 \mathbf{E}}{\mathbf{Z}_2 + \mathbf{Z}_1 \parallel (\mathbf{Z}_3 + \mathbf{Z}_4)} \\
 &= \frac{(4 \Omega \angle 90^\circ)(50 \text{ V} \angle 0^\circ)}{+j4 \text{ k}\Omega + 2 \Omega \angle 0^\circ \parallel (10 \Omega - j8 \Omega)} \\
 &= 47.248 \text{ V} \angle 24.7^\circ
 \end{aligned}$$

$$\mathbf{V}_1 = \mathbf{E} - \mathbf{V}_2 = 50 \text{ V} \angle 0^\circ - 47.248 \text{ V} \angle 24.7^\circ = 20.972 \text{ V} \angle -70.285^\circ$$

$$\mathbf{V}_4 = \frac{\mathbf{Z}_4 \mathbf{V}_1}{\mathbf{Z}_4 + \mathbf{Z}_3} = \frac{(10 \Omega \angle 0^\circ)(20.972 \text{ V} \angle -70.285^\circ)}{10 \Omega - j8 \Omega} = 16.377 \text{ V} \angle -31.625^\circ$$

$$\begin{aligned}
 \mathbf{E}_{Th} &= \mathbf{V}_2 + \mathbf{V}_4 = 47.248 \text{ V} \angle 24.7^\circ + 16.377 \text{ V} \angle -31.625^\circ \\
 &= (42.925 \text{ V} + j19.743 \text{ V}) + (13.945 \text{ V} - j8.587 \text{ V}) \\
 &= 56.870 \text{ V} + j11.156 \text{ V} = \mathbf{57.95 \text{ V} \angle 11.10^\circ}
 \end{aligned}$$

21. \mathbf{Z}_{Th} :

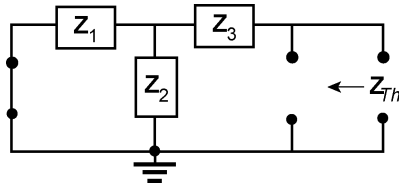


$$\begin{aligned}
 \mathbf{Z}_1 &= 10 \Omega \angle 0^\circ, \mathbf{Z}_2 = 8 \Omega \angle 90^\circ \\
 \mathbf{Z}_3 &= 8 \Omega \angle -90^\circ
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{Z}_{Th} &= \mathbf{Z}_3 + \mathbf{Z}_1 \parallel \mathbf{Z}_2 \\
 &= -j8 \Omega + 10 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ \\
 &= -j8 \Omega + 6.247 \Omega \angle 51.34^\circ \\
 &= -j8 \Omega + 3.902 \Omega + j4.878 \Omega \\
 &= 3.902 \Omega - j3.122 \Omega \\
 &= \mathbf{5.00 \Omega \angle -38.66^\circ}
 \end{aligned}$$


\mathbf{E}_{Th} : Superposition:

(\mathbf{E}_1)

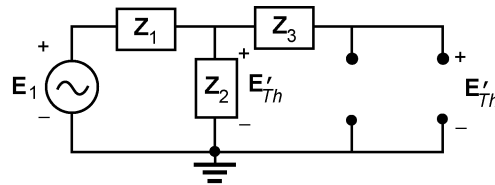

$$\begin{aligned}
 \mathbf{E}'_{Th} &= \frac{(8 \Omega \angle 90^\circ)(120 \text{ V} \angle 0^\circ)}{10 \Omega + j8 \Omega} \\
 &= \frac{960 \text{ V} \angle 90^\circ}{12.806 \angle 38.66^\circ} \\
 &= 74.965 \text{ V} \angle 51.34^\circ
 \end{aligned}$$


(\mathbf{I})

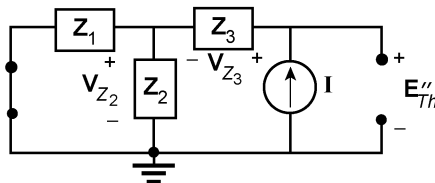

$$\begin{aligned}
 \mathbf{E}''_{Th} &= \mathbf{V}_{Z_2} + \mathbf{V}_{Z_3} \\
 &= \mathbf{I}\mathbf{Z}_3 + \mathbf{I}(\mathbf{Z}_1 \parallel \mathbf{Z}_2) \\
 &= \mathbf{I}(\mathbf{Z}_3 + \mathbf{Z}_1 \parallel \mathbf{Z}_2) \\
 &= (0.5 \text{ A } \angle 60^\circ)(-j8 \Omega + 10 \Omega \angle 0^\circ \parallel 8 \Omega \angle 90^\circ) \\
 &= (0.5 \text{ A } \angle 60^\circ)(-j8 \Omega + 3.902 \Omega + j4.878 \Omega) \\
 &= (0.5 \text{ A } \angle 60^\circ)(3.902 \Omega - j3.122 \Omega) \\
 &= (0.5 \text{ A } \angle 60^\circ)(4.997 \Omega \angle -38.663^\circ) \\
 &= 2.499 \text{ V } \angle 21.337^\circ
 \end{aligned}$$


$$\begin{aligned}
 \mathbf{E}_{Th} &= \mathbf{E}'_{Th} + \mathbf{E}''_{Th} \\
 &= 74.965 \text{ V } \angle 51.34^\circ + 2.449 \text{ V } \angle 21.337^\circ \\
 &= (46.83 \text{ V} + j58.538 \text{ V}) + (2.328 \text{ V} + j0.909 \text{ V}) \\
 &= 49.158 \text{ V} + j59.447 \text{ V} = \mathbf{77.14 \text{ V } \angle 50.41^\circ}
 \end{aligned}$$

22. \mathbf{Z}_{Th} :

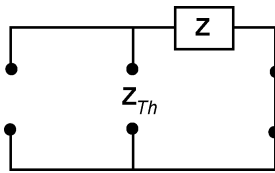


$$\mathbf{Z}_{Th} = \mathbf{Z} = 10 \Omega - j10 \Omega = \mathbf{14.14 \Omega \angle -45^\circ}$$

\mathbf{E}_{Th} :

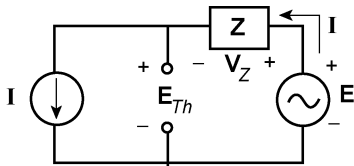

$$\begin{aligned}
 \mathbf{E}_{Th} &= \mathbf{E} - \mathbf{V}_Z \\
 &= 20 \text{ V } \angle 40^\circ - \mathbf{I}\mathbf{Z} \\
 &= 20 \text{ V } \angle 40^\circ - (0.6 \text{ A } \angle 90^\circ)(14.14 \Omega \angle -45^\circ) \\
 &= 20 \text{ V } \angle 40^\circ - 8.484 \text{ V } \angle 45^\circ \\
 &= (15.321 \text{ V} + j12.856 \text{ V}) - (6 \text{ V} + j6 \text{ V}) \\
 &= 9.321 \text{ V} + j6.856 \text{ V} \\
 &= \mathbf{11.57 \text{ V } \angle 36.34^\circ}
 \end{aligned}$$


23. a. AC:
 \mathbf{E}_{Th} :

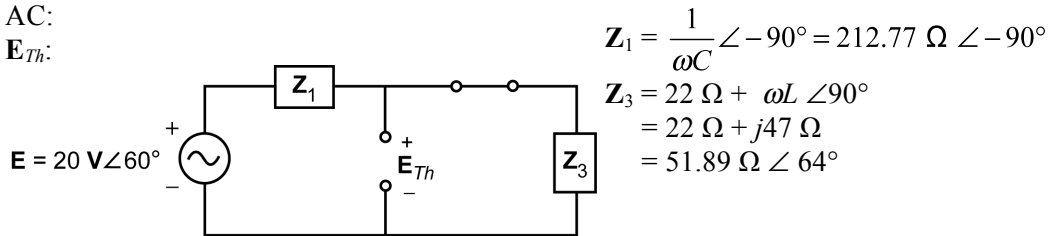

$$\begin{aligned}
 \mathbf{Z}_1 &= \frac{1}{\omega C} \angle -90^\circ = 212.77 \Omega \angle -90^\circ \\
 \mathbf{Z}_3 &= 22 \Omega + \omega L \angle 90^\circ \\
 &= 22 \Omega + j47 \Omega \\
 &= 51.89 \Omega \angle 64^\circ
 \end{aligned}$$



$$\mathbf{E}_{Th} = \frac{\mathbf{Z}_3 \mathbf{E}}{\mathbf{Z}_3 + \mathbf{Z}_1} = \frac{(51.89 \Omega \angle 64.92^\circ)(20 \text{ V } \angle 60^\circ)}{22 \Omega + j47 \text{ k}\Omega - j212.77 \Omega} = \mathbf{6.21 \text{ V } \angle 207.36^\circ}$$

\mathbf{Z}_{Th} :

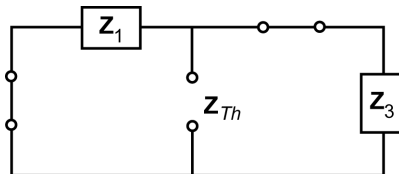


$$\begin{aligned} Z_{Th} = Z_1 \parallel Z_2 &= \frac{(212.77 \Omega \angle -90^\circ)(51.89 \Omega \angle 64.92^\circ)}{-j212.77 \Omega + 22 \Omega + j47 \text{ k}\Omega} \\ &= 66.04 \Omega \angle 57.36^\circ = 35.62 \Omega + j55.61 \Omega \end{aligned}$$

DC: E_{Th} :

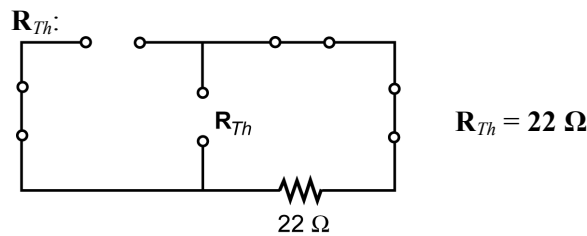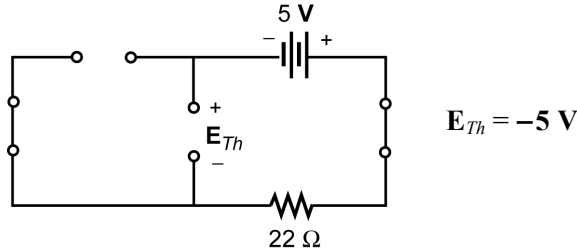


b. AC:

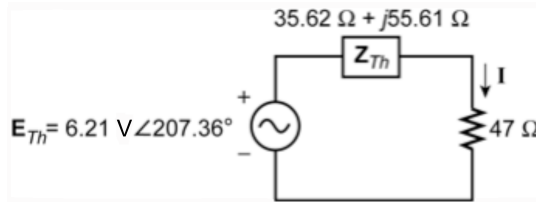

$$\begin{aligned} I &= \frac{E_{Th}}{Z_{Th} + R_L} \\ &= \frac{6.21 \text{ V} \angle 207.36^\circ}{35.62 \Omega + j55.61 \Omega + 47 \Omega} \\ &= \frac{6.21 \text{ V} \angle 207.36^\circ}{82.62 \Omega + j55.61 \Omega} \\ &= \frac{6.21 \text{ V} \angle 207.36^\circ}{99.59 \Omega \angle 33.94^\circ} \\ &= 62.36 \text{ mA} \angle 173.42^\circ \end{aligned}$$


DC:

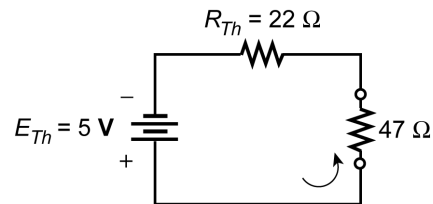

$$\begin{aligned} I &= \frac{5 \text{ V}}{22 \Omega + 47 \Omega} = \frac{5 \text{ V}}{69 \Omega} \\ &= 72.46 \text{ mA} \end{aligned}$$


$i = -72.46 \text{ mA} + 62.36 \times 10^{-3} \sin(1000t + 173.42^\circ)$
matching the results of Problem 4.

24. a. Z_{Th} :

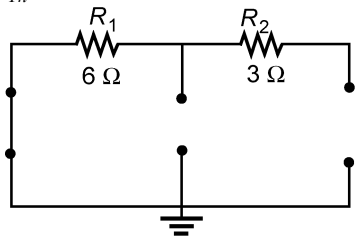


$$\leftarrow Z_{Th} = Z_{R_1} + Z_{R_2} = 6 \Omega + 3 \Omega = 9 \Omega$$

DC:

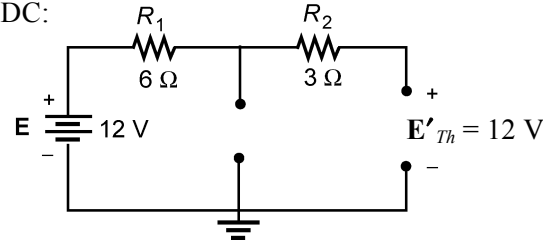

AC:

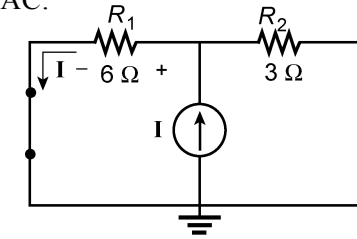


$$\leftarrow E''_{Th} = I Z_{R_1} = (4 \text{ A} \angle 0^\circ)(6 \Omega \angle 0^\circ) = 24 \text{ V} \angle 0^\circ$$

$$E_{Th} = 12 \text{ V} + 24 \text{ V} \angle 0^\circ$$

(DC) (AC)

b.

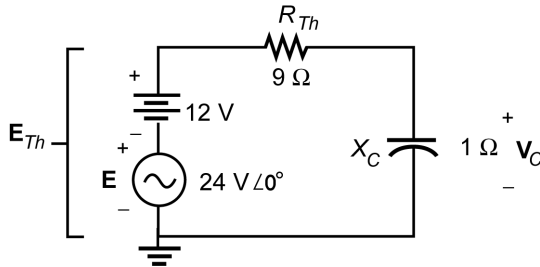


DC: $V_C = 12 \text{ V}$

$$\begin{aligned} \text{AC: } V_C &= \frac{Z_C E}{Z_C + Z_{R_{Th}}} \\ &= \frac{(1 \Omega \angle -90^\circ)(24 \text{ V} \angle 0^\circ)}{-j1 \Omega + 9 \Omega} \\ &= \frac{24 \text{ V} \angle -90^\circ}{9.055 \angle -6.34^\circ} \\ V_C &= 2.65 \text{ V} \angle -83.66^\circ \end{aligned}$$

$$\begin{aligned} v_C &= 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ \\ &= 12 \text{ V} + 3.75 \sin(\omega t - 83.66^\circ) \end{aligned}$$

25. a. Z_{Th} :

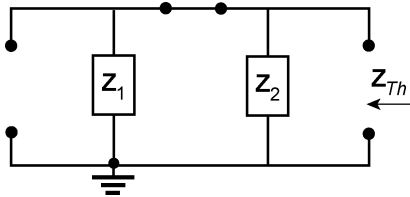


$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega - j5 \text{ k}\Omega \\ &= 7.071 \text{ k}\Omega \angle -45^\circ \end{aligned}$$

$$Z_{Th} = Z_1 \parallel Z_2 = (10 \text{ k}\Omega \angle 0^\circ) \parallel (7.071 \text{ k}\Omega \angle -45^\circ) = 4.47 \text{ k}\Omega \angle -26.57^\circ$$

Source conversion:
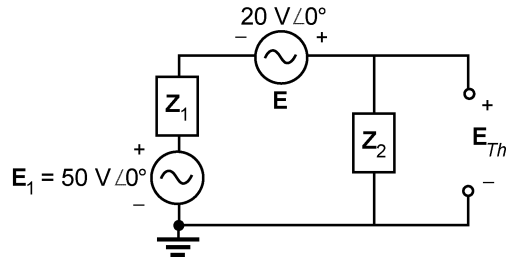
$$E_1 = (I\angle\theta)(R_1\angle 0^\circ) = (5 \text{ mA } \angle 0^\circ)(10 \text{ k}\Omega \angle 0^\circ) = 50 \text{ V } \angle 0^\circ$$




$$\begin{aligned} E_{Th} &= \frac{Z_2(E + E_1)}{Z_2 + Z_1} \\ &= \frac{(7.071 \text{ k}\Omega \angle -45^\circ)(20 \text{ V } \angle 0^\circ + 50 \text{ V } \angle 0^\circ)}{(5 \text{ k}\Omega - j5 \text{ k}\Omega) + (10 \text{ k}\Omega)} \\ &= \frac{(7.071 \text{ k}\Omega \angle -45^\circ)(70 \text{ V } \angle 0^\circ)}{(15 \text{ k}\Omega - j5 \text{ k}\Omega)} \\ &= \frac{494.97 \text{ V } \angle -45^\circ}{15.811 \angle -18.435^\circ} \\ &= \mathbf{31.31 \text{ V } \angle -26.57^\circ} \end{aligned}$$

b.
$$I = \frac{E_{Th}}{Z_{Th} + Z_L} = \frac{31.31 \text{ V } \angle -26.565^\circ}{4.472 \text{ k}\Omega \angle -26.565^\circ + 5 \text{ k}\Omega \angle 90^\circ}$$

$$= \frac{31.31 \text{ V } \angle -26.565^\circ}{4 \text{ k}\Omega - j2 \text{ k}\Omega + j5 \text{ k}\Omega} = \frac{31.31 \text{ V } \angle -26.565^\circ}{4 \text{ k}\Omega + j3 \text{ k}\Omega}$$

$$= \frac{31.31 \text{ V } \angle -26.565^\circ}{5 \text{ k}\Omega \angle 36.87^\circ} = \mathbf{6.26 \text{ mA } \angle 63.44^\circ}$$

26.

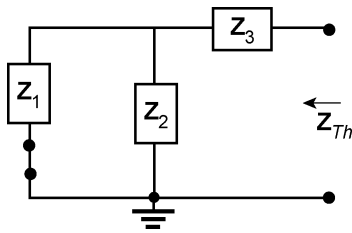


$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= 1 \text{ k}\Omega \angle -90^\circ \end{aligned}$$

$$Z_{Th} = Z_3 + Z_1 \parallel Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \cong \mathbf{5.1 \text{ k}\Omega \angle -11.31^\circ}$$


$$E_{Th}: \text{ (VDR)} \quad E_{Th} = \frac{Z_2(20 \text{ V})}{Z_2 + Z_1} = \frac{(10 \text{ k}\Omega \angle 0^\circ)(20 \text{ V})}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = \mathbf{10 \text{ V}}$$

27. Z_{Th} :

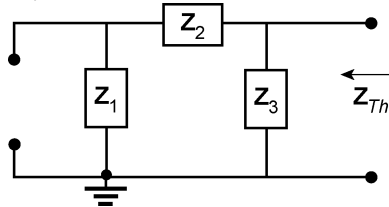

$$\begin{aligned} Z_1 &= 40 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 0.2 \text{ k}\Omega \angle -90^\circ \\ Z_3 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$

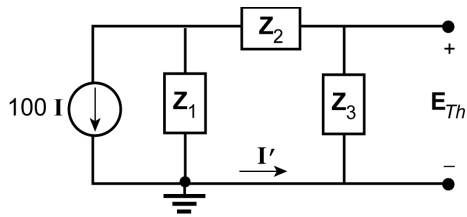
$$Z_{Th} = Z_3 \parallel (Z_1 + Z_2) = 5 \text{ k}\Omega \angle 0^\circ \parallel (40 \text{ k}\Omega - j0.2 \text{ k}\Omega) = \mathbf{4.44 \text{ k}\Omega \angle -0.03^\circ}$$



$$\begin{aligned} \mathbf{I}' &= \frac{\mathbf{Z}_1(100 \mathbf{I})}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} \\ &= \frac{(40 \text{ k}\Omega \angle 0^\circ)(100 \mathbf{I})}{45 \text{ k}\Omega \angle -0.255^\circ} \\ &= 88.89 \mathbf{I} \angle 0.255^\circ \end{aligned}$$


$$\mathbf{E}_{Th} = -\mathbf{I}'\mathbf{Z}_3 = -(88.89 \mathbf{I} \angle 0.255^\circ)(5 \text{ k}\Omega \angle 0^\circ) = -444.45 \times 10^3 \mathbf{I} \angle 0.26^\circ$$

28. \mathbf{Z}_{Th} :

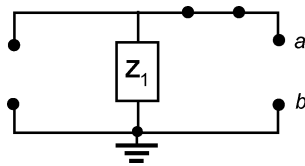


$$\leftarrow \mathbf{Z}_{Th} = \mathbf{Z}_1 = 20 \text{ k}\Omega \angle 0^\circ$$

\mathbf{E}_{Th} :

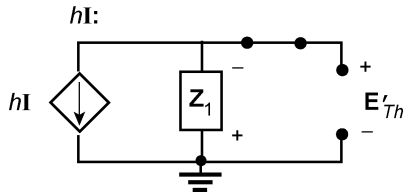

$$\begin{aligned} \mathbf{E}'_{Th} &= -(h\mathbf{I})(\mathbf{Z}_1) \\ &= -(100)(2 \text{ mA} \angle 0^\circ)(20 \text{ k}\Omega \angle 0^\circ) \\ &= -4 \text{ kV} \angle 0^\circ \end{aligned}$$


\mathbf{E} :

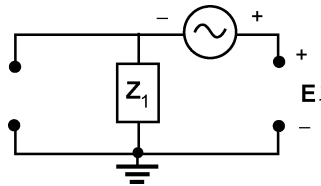


$$\mathbf{E}''_{Th} = \mathbf{E} = 10 \text{ V} \angle 0^\circ$$

$$\begin{aligned} \mathbf{E}_{Th} &= \mathbf{E}'_{Th} + \mathbf{E}''_{Th} \\ &= -4 \text{ kV} \angle 0^\circ + 10 \text{ V} \angle 0^\circ \\ &= -3990 \text{ V} \angle 0^\circ \end{aligned}$$


29. \mathbf{Z}_{Th} :

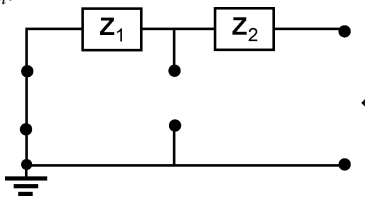

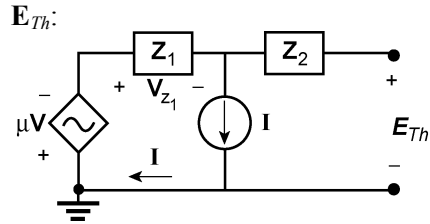
$$\begin{aligned} \mathbf{Z}_1 &= 5 \text{ k}\Omega \angle 0^\circ & \mathbf{Z}_2 &= -j1 \\ \leftarrow \mathbf{Z}_{Th} &= \mathbf{Z}_1 + \mathbf{Z}_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \\ &= 5.10 \text{ k}\Omega \angle -11.31^\circ \end{aligned}$$



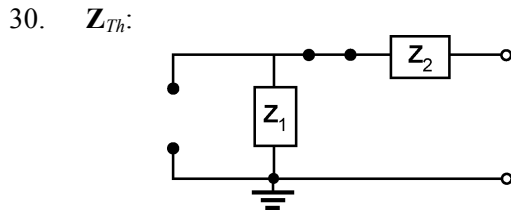
$$\begin{aligned}
 E_{Th} &= [\mu V + V_{Z_1}] \\
 &= -\mu V - IZ_1 \\
 &= -(20)(2 \text{ V } \angle 0^\circ) - (2 \text{ mA } \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ) \\
 &= -50 \text{ V } \angle 0^\circ
 \end{aligned}$$



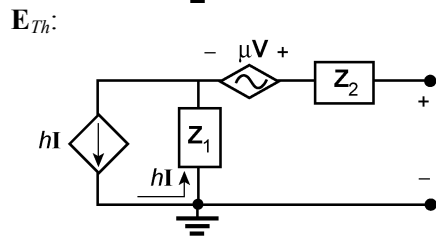
$$\begin{aligned}
 Z_1 &= 20 \text{ k}\Omega \angle 0^\circ \\
 Z_2 &= 5 \text{ k}\Omega \angle 0^\circ \\
 \leftarrow Z_{Th} &= Z_1 + Z_2 = 25 \text{ k}\Omega \angle 0^\circ
 \end{aligned}$$


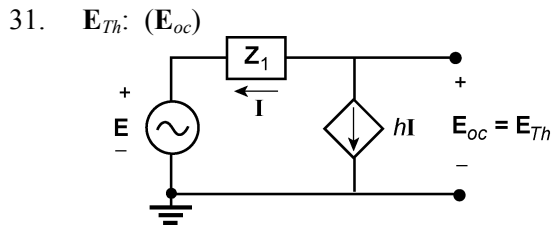
$$\begin{aligned}
 E_{Th} &= \mu V - (hI)(Z_1) \\
 &= (20)(10 \text{ V } \angle 0^\circ) - (100)(1 \text{ mA } \angle 0^\circ)(20 \text{ k}\Omega \angle 0^\circ) \\
 &= -1800 \text{ V } \angle 0^\circ
 \end{aligned}$$



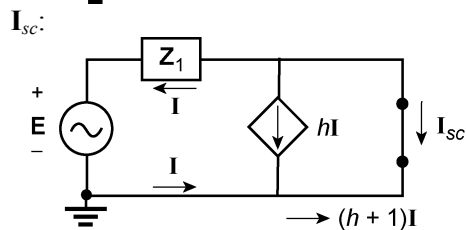
$$\begin{aligned}
 hI &= -I & Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\
 \therefore I &= 0 \\
 \text{and } hI &= 0 \\
 \text{with } E_{oc} &= E_{Th} = E = 20 \text{ V } \angle 53^\circ
 \end{aligned}$$



$$\begin{aligned}
 I_{sc} &= -(h+1)I \\
 &= -(h+1)(10 \text{ mA } \angle 53^\circ) \\
 &= -510 \text{ mA } \angle 53^\circ
 \end{aligned}$$

$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{20 \text{ V } \angle 53^\circ}{-510 \text{ mA } \angle 53^\circ} = -39.22 \Omega \angle 0^\circ \text{ (negative resistance)}$$


32. E_{Th} :

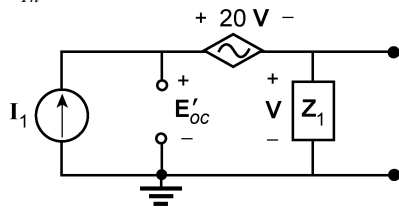

$$E'_{oc} = 21 \text{ V} \quad Z_1 = 5 \text{ k}\Omega \angle 0^\circ$$

$$V = I_1 Z_1 = (1 \text{ mA} \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ) = 5 \text{ V} \angle 0^\circ$$

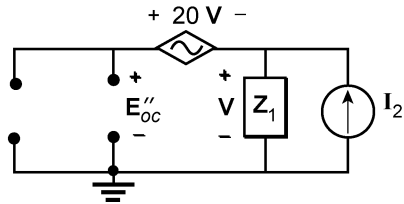
$$E'_{oc} = E'_{Th} = 21 \text{ V} = 21(5 \text{ V} \angle 0^\circ) = 105 \text{ V} \angle 0^\circ$$




$$V = I_2 Z_1 = (2 \text{ mA} \angle 0^\circ)(5 \text{ k}\Omega \angle 0^\circ) = 10 \text{ V} \angle 0^\circ$$

$$E''_{oc} = E''_{Th} = V + 20 \text{ V} = 21 \text{ V} = 210 \text{ V} \angle 0^\circ$$

I_{sc} :

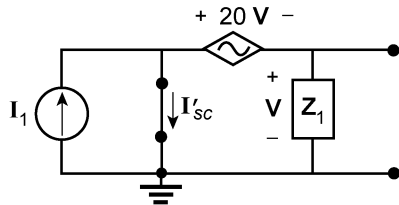

$$I'_{sc} = I_1$$

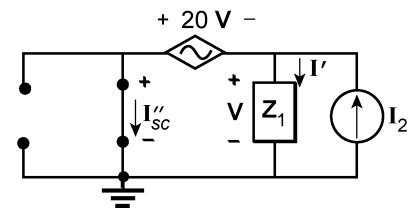

$$20 \text{ V} = V \therefore V = 0 \text{ V} \text{ and } I' = 0 \text{ A}$$


$$\therefore I''_{sc} = I_2$$

$$I_{sc} = I'_{sc} + I''_{sc} = 3 \text{ mA} \angle 0^\circ$$

$$E_{oc} = E'_{oc} + E''_{oc} = 105 \angle 0^\circ + 210 \text{ V} \angle 0^\circ = 315 \text{ V} \angle 0^\circ = E_{Th}$$

$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{315 \text{ V} \angle 0^\circ}{3 \text{ mA} \angle 0^\circ} = 105 \text{ k}\Omega \angle 0^\circ$$

33. E_{oc} :
(E_{Th})

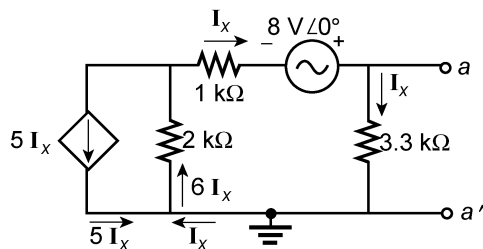


$$\text{KVL: } -6 I_x(2 \text{ k}\Omega) - I_x(1 \text{ k}\Omega) + 8 \text{ V} \angle 0^\circ - I_x(3.3 \text{ k}\Omega) = 0$$

$$I_x = \frac{8 \text{ V} \angle 0^\circ}{16.3 \text{ k}\Omega} = 0.491 \text{ mA} \angle 0^\circ$$


$$E_{oc} = E_{Th} = I_x(3.3 \text{ k}\Omega) = 1.62 \text{ V} \angle 0^\circ$$

I_{sc} :

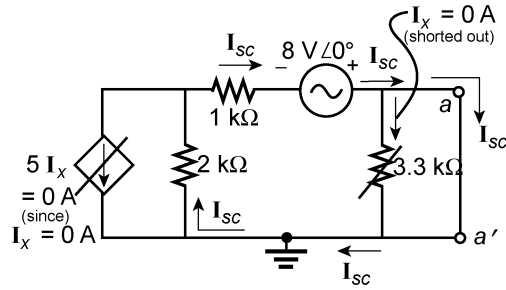


$$I_{sc} = \frac{8 \text{ V}}{3 \text{ k}\Omega} = 2.667 \text{ mA } \angle 0^\circ$$
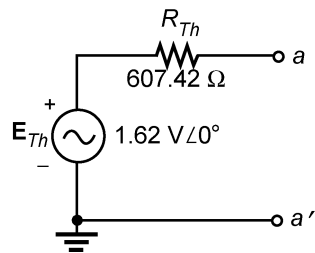
$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{1.62 \text{ V } \angle 0^\circ}{2.667 \text{ mA } \angle 0^\circ} = 607.42 \Omega \angle 0^\circ$$



34. From Problem 15: $Z_N = Z_{Th} = 1.92 \Omega + j1.44 \Omega = 2.4 \Omega \angle 36.87^\circ$


I_N :

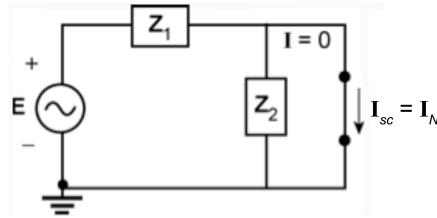

$$Z_1 = 3 \Omega \angle 0^\circ, Z_2 = 4 \Omega \angle 90^\circ$$

$$I_{sc} = I_N = \frac{E}{Z_1} = \frac{100 \text{ V } \angle 0^\circ}{3 \Omega \angle 0^\circ} = 33.33 \text{ A } \angle 0^\circ$$

- 35.

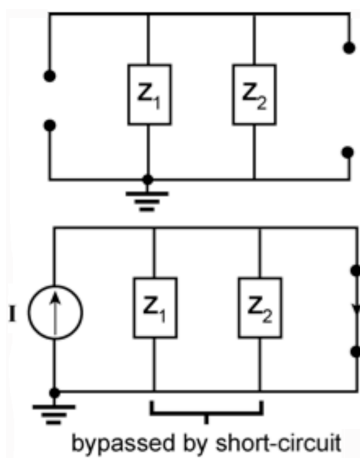

$$Z_1 = 20 \Omega + j20 \Omega = 28.284 \Omega \angle 45^\circ$$

$$Z_2 = 68 \Omega \angle 0^\circ$$


$$\leftarrow Z_N = Z_1 \parallel Z_2 = (28.284 \Omega \angle 45^\circ) \parallel (68 \Omega \angle 0^\circ) = 21.31 \Omega \angle 32.2^\circ$$

$$\leftarrow I_{sc} = I = I_N = 0.1 \text{ A } \angle 0^\circ$$

36. From Problem 21: $Z_N = Z_{Th} = 5.00 \Omega \angle -38.66^\circ$

I_N : Superposition:

(E₁)

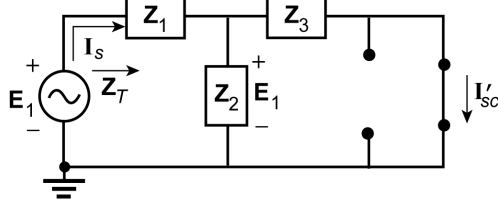

$$\begin{aligned} Z_T &= Z_1 + Z_2 \parallel Z_3 \\ &= 10 \Omega + 8 \Omega \angle 90^\circ \parallel 8 \Omega \angle -90^\circ \\ &= 10 \Omega + \frac{64 \Omega \angle 0^\circ}{0} \end{aligned}$$

= very large impedance


$$I_s = \frac{E}{Z_T} = 0 \text{ A}$$

and $V_{Z_1} = 0 \text{ V}$

with $V_{Z_2} = V_{Z_3} = E_1 = 120 \text{ V} \angle 0^\circ$

$$\begin{aligned} \text{so that } I'_{sc} &= \frac{E_1}{Z_3} = \frac{120 \text{ V} \angle 0^\circ}{8 \Omega \angle -90^\circ} \\ &= 15 \text{ A} \angle 90^\circ \end{aligned}$$


(I)

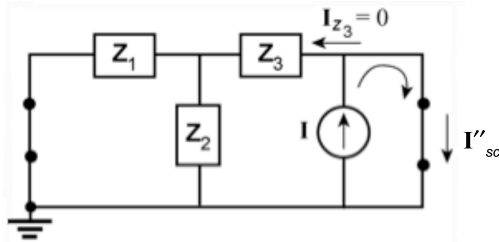

$$I''_{sc} = I = 0.5 \text{ A} \angle 60^\circ$$


$$\begin{aligned} I_N &= I'_{sc} + I''_{sc} = +j15 \text{ A} + 0.5 \text{ A} \angle 60^\circ = +j15 \text{ A} + 0.25 \text{ A} + j0.433 \text{ A} \\ &= 0.25 \text{ A} + j15.433 \text{ A} = 15.44 \text{ A} \angle 89.07^\circ \end{aligned}$$

37. a. Z_N :

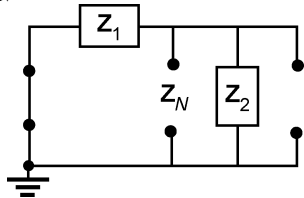

$$\begin{aligned} E &= 20 \text{ V} \angle 0^\circ, I_2 = 0.4 \text{ A} \angle 20^\circ \\ Z_1 &= 6 \Omega + j8 \Omega = 10 \Omega \angle 53.13^\circ \\ Z_2 &= 9 \Omega - j12 \Omega = 15 \Omega \angle -53.13^\circ \\ Z_N &= Z_1 \parallel Z_2 = (10 \Omega \angle 53.13^\circ) \parallel (15 \Omega \angle -53.13^\circ) \\ &= 9.66 \Omega \angle 14.93^\circ \end{aligned}$$


I_N :
(E)

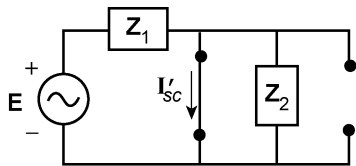

$$\begin{aligned} I'_{sc} &= E/Z_1 = 20 \text{ V} \angle 0^\circ / 10 \Omega \angle 53.13^\circ \\ &= 2 \text{ A} \angle -53.13^\circ \end{aligned}$$


$$\begin{aligned} I_N &= I'_{sc} + I''_{sc} = 2 \text{ A} \angle -53.13^\circ + 0.4 \text{ A} \angle 20^\circ \\ &= 2.15 \text{ A} \angle -42.87^\circ \end{aligned}$$

(I₂)

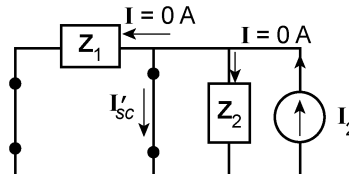

$$I''_{sc} = I_2 = 0.4 \text{ A} \angle 20^\circ$$


38. Z_N :

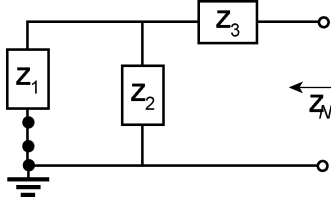

$$E_1 = 120 \text{ V } \angle 30^\circ, Z_1 = 3 \Omega \angle 0^\circ \\ Z_2 = 8 \Omega - j8 \Omega, Z_3 = 4 \Omega \angle 90^\circ$$

$$Z_N = Z_3 + Z_1 \parallel Z_2 \\ = 4 \Omega \angle 90^\circ + (3 \Omega \angle 0^\circ) \parallel (8 \Omega - j8 \Omega) \\ = 4.37 \Omega \angle 55.67^\circ = 2.47 \Omega + j3.61 \Omega$$

I_N :

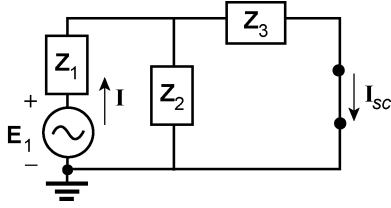


$$I = \frac{E_1}{Z_T} = \frac{120 \text{ V } \angle 30^\circ}{Z_1 + Z_2 \parallel Z_3} \\ = \frac{120 \text{ V } \angle 30^\circ}{3 \Omega + (8 \Omega - j8 \Omega) \parallel 4 \Omega \angle 90^\circ} \\ = \frac{120 \text{ V } \angle 30^\circ}{6.65 \Omega \angle 46.22^\circ} \\ = 18.05 \text{ A } \angle -16.22^\circ$$

$$I_{sc} = I_N = \frac{Z_2(I)}{Z_2 + Z_3} = \frac{(8 \Omega - j8 \Omega)(18.05 \text{ A } \angle -16.22^\circ)}{8 \Omega - j8 \Omega + j4 \Omega} = 22.83 \text{ A } \angle -34.65^\circ$$

39. a. AC:

I_N :

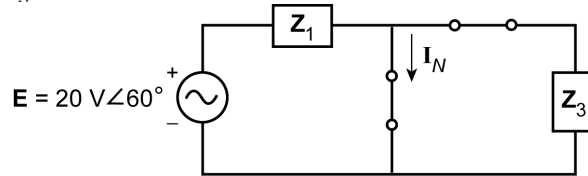


$$Z_1 = 212.77 \Omega \angle -90^\circ \\ Z_3 = 22 \Omega + j47 \Omega \\ = 51.89 \Omega \angle 64^\circ$$

$$I_N = \frac{E}{Z_1} = \frac{20 \text{ V } \angle 60^\circ}{212.77 \Omega \angle -90^\circ} = 94 \text{ mA } \angle 150^\circ$$

$$Z_N = Z_{Th} \text{ (problem 23)} = 66.04 \angle 57.36^\circ = 35.62 \Omega + j55.61 \Omega$$

DC:


I_N :

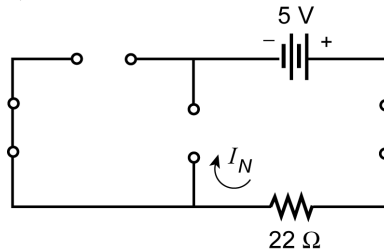

$$I_N = \frac{5 \text{ V}}{22 \Omega} = 227.27 \text{ mA}$$

$$R_N = R_{Th} \text{ (problem 23)} = 22 \Omega$$


- b. AC:
 \mathbf{I}_N :

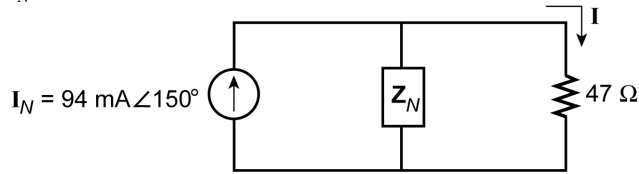

$$\mathbf{I} = \frac{\mathbf{Z}_N(\mathbf{I}_N)}{\mathbf{Z}_N + 47 \Omega} = \frac{(66.04 \Omega \angle 57.36^\circ)(94 \text{ mA} \angle 150^\circ)}{35.62 \Omega + j55.61 \Omega + 47 \Omega}$$

$$= \frac{6.21 \text{ A} \angle 207.36^\circ}{99.08 \angle 34.14^\circ} = \mathbf{62.68 \text{ mA} \angle 173.22^\circ}$$

DC:

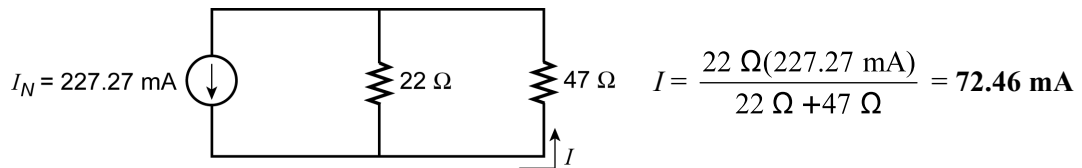


$$I = \frac{22 \Omega (227.27 \text{ mA})}{22 \Omega + 47 \Omega} = \mathbf{72.46 \text{ mA}}$$

and $i = -72.46 \text{ mA} + 62.68 \times 10^{-3} \sin(1000t + 173.22^\circ)$
 Same as Problem 6 and 23.


40. a. From #24 $\mathbf{Z}_N = \mathbf{Z}_{Th} = 9 \Omega \angle 0^\circ$

DC:

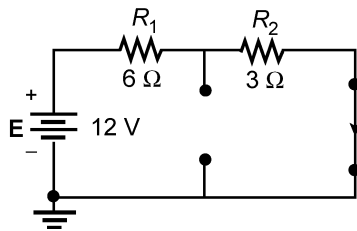

$$I'_N = \frac{E}{R_T} = \frac{12 \text{ V}}{9 \Omega} = 1.33 \text{ A}$$

AC:

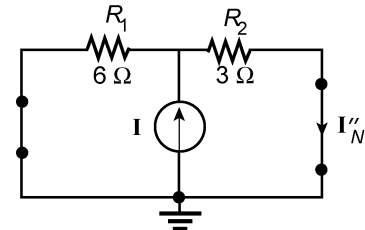


$$\mathbf{I}''_N = \frac{R_1 \mathbf{I}}{R_1 + R_2} = \frac{(6 \Omega \angle 0^\circ)(4 \text{ A} \angle 0^\circ)}{9 \Omega \angle 0^\circ}$$

$$= \frac{24 \text{ V} \angle 0^\circ}{9 \Omega \angle 0^\circ} = 2.67 \text{ A} \angle 0^\circ$$

$$\mathbf{I}_N = 1.33 \text{ A} + 2.67 \text{ A} \angle 0^\circ$$

b.

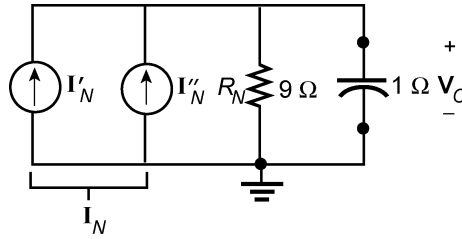

$$\begin{aligned} \text{DC: } V_C &= IR \\ &= (1.33 \text{ A})(9 \Omega) \\ &= 12 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{AC: } Z' &= 9 \Omega \angle 0^\circ \parallel 1 \Omega \angle -90^\circ \\ &= 0.994 \Omega \angle -83.66^\circ \end{aligned}$$


$$\begin{aligned} V_C &= IZ' = (2.667 \text{ A} \angle 0^\circ)(0.994 \Omega \angle -83.66^\circ) \\ &= 2.65 \text{ V} \angle -83.66^\circ \end{aligned}$$

$$V_C = 12 \text{ V} + 2.65 \text{ V} \angle -83.66^\circ$$

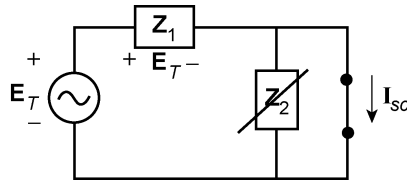41. a. Note Problem 25(a): $Z_N = Z_{Th} = 4.47 \text{ k}\Omega \angle -26.57^\circ$

Using the same source conversion: $E_1 = 50 \text{ V} \angle 0^\circ$

Defining $E_T = E_1 + E = 50 \text{ V} \angle 0^\circ + 20 \text{ V} \angle 0^\circ = 70 \text{ V} \angle 0^\circ$



$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 5 \text{ k}\Omega - j5 \text{ k}\Omega = 7.071 \text{ k}\Omega \angle -45^\circ \end{aligned}$$


$$I_{sc} = \frac{E_T}{Z_1} = \frac{70 \text{ V} \angle 0^\circ}{10 \text{ k}\Omega \angle 0^\circ} = 7 \text{ mA} \angle 0^\circ$$

$$I_N = I_{sc} = 7 \text{ mA} \angle 0^\circ$$


$$\begin{aligned} \text{b. } I &= \frac{Z_N(I_N)}{Z_N + Z_L} = \frac{(4.472 \text{ k}\Omega \angle -26.565^\circ)(7 \text{ mA} \angle 0^\circ)}{4.472 \text{ k}\Omega \angle -26.565^\circ + 5 \text{ k}\Omega \angle 90^\circ} \\ &= \frac{31.30 \text{ mA} \angle -26.565^\circ}{4 - j2 + j5} = \frac{31.30 \text{ mA} \angle -26.565^\circ}{4 + j3} \\ &= \frac{31.30 \text{ mA} \angle -26.565^\circ}{5 \angle 36.87^\circ} = 6.26 \text{ mA} \angle 63.44^\circ \text{ as obtained in Problem 25.} \end{aligned}$$

42.

Z_N :

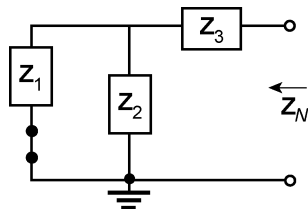
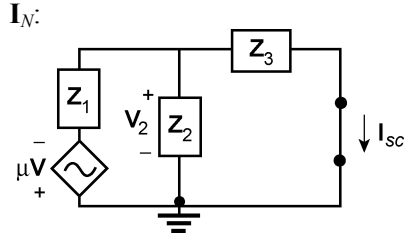
$$\begin{aligned} Z_1 &= 10 \text{ k}\Omega \angle 0^\circ, Z_2 = 10 \text{ k}\Omega \angle 0^\circ \\ Z_3 &= -j1 \text{ k}\Omega \\ Z_N &= Z_3 + Z_1 \parallel Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega \\ &= 5.1 \text{ k}\Omega \angle -11.31^\circ \end{aligned}$$




$$V_2 = \frac{-(Z_2 \parallel Z_3)20 \text{ V}}{(Z_2 \parallel Z_3) + Z_1}$$

$$= \frac{-(0.995 \text{ k}\Omega \angle -84.29^\circ)(20 \text{ V})}{0.1 \text{ k}\Omega - j0.99 \text{ k}\Omega + 10 \text{ k}\Omega}$$

$$V_2 = -1.961 \text{ V} \angle -78.69^\circ$$

$$I_N = I_{sc} = \frac{V_2}{Z_3} = \frac{-1.961 \text{ V} \angle -78.69^\circ}{1 \text{ k}\Omega \angle -90^\circ} = -1.96 \times 10^{-3} \text{ V} \angle 11.31^\circ$$

43. Z_N :

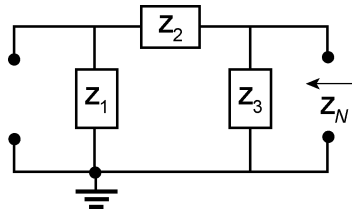

$$Z_1 = 40 \text{ k}\Omega \angle 0^\circ, Z_2 = 0.2 \text{ k}\Omega \angle -90^\circ$$


$$Z_3 = 5 \text{ k}\Omega \angle 0^\circ$$

$$Z_N = Z_3 \parallel (Z_1 + Z_2)$$

$$= 5 \text{ k}\Omega \angle 0^\circ \parallel (40 \text{ k}\Omega - j0.2 \text{ k}\Omega)$$

$$= 4.44 \text{ k}\Omega \angle -0.03^\circ$$

I_N :

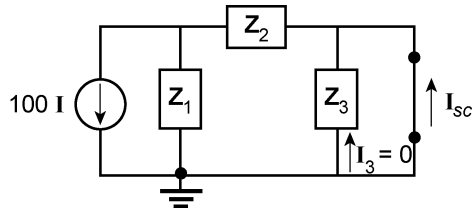


$$I_N = I_{sc} = \frac{Z_1(100 \text{ I})}{Z_1 + Z_2}$$

$$= \frac{(40 \text{ k}\Omega \angle 0^\circ)(100 \text{ I})}{40 \text{ k}\Omega \angle -0.286^\circ}$$

$$= 100 \text{ I} \angle 0.29^\circ$$

44. Z_N :

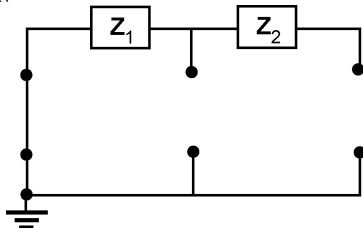


$$Z_1 = 5 \text{ k}\Omega \angle 0^\circ, Z_2 = 1 \text{ k}\Omega \angle -90^\circ$$

$$\leftarrow Z_N = Z_1 + Z_2 = 5 \text{ k}\Omega - j1 \text{ k}\Omega$$

$$= 5.1 \text{ k}\Omega \angle -11.31^\circ$$


I_N :

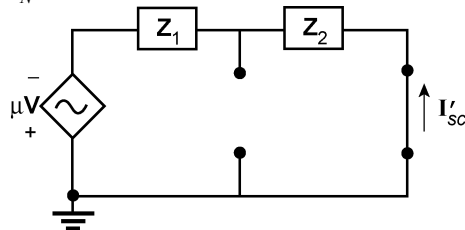

$$I'_{sc} = \frac{\mu\text{V}}{Z_1 + Z_2} = \frac{(20)(2 \text{ V} \angle 0^\circ)}{5.1 \text{ k}\Omega \angle -11.31^\circ}$$

$$= 7.843 \text{ mA} \angle 11.31^\circ$$

(I):

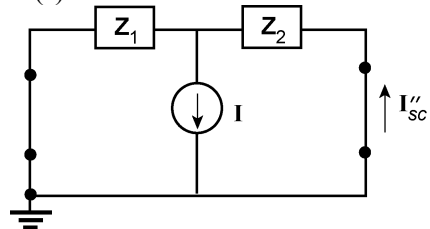


$$I''_{sc} = \frac{Z_1(I)}{Z_1 + Z_2}$$

$$= \frac{(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA} \angle 0^\circ)}{5.1 \text{ k}\Omega \angle -11.31^\circ}$$

$$= 1.96 \text{ mA} \angle 11.31^\circ$$

$$\begin{aligned} \mathbf{I}_N &= \mathbf{I}'_{sc} + \mathbf{I}''_{sc} = 7.843 \text{ mA } \angle 11.31^\circ + 1.96 \text{ mA } \angle 11.31^\circ \\ &= \mathbf{9.81 \text{ mA } \angle 11.31^\circ} \end{aligned}$$


45. \mathbf{Z}_N :

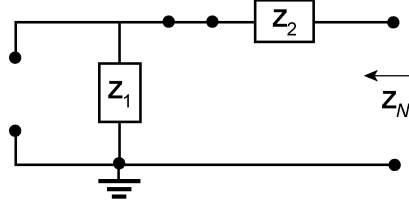

$$\begin{aligned} \mathbf{Z}_1 &= 20 \text{ k}\Omega \angle 0^\circ, \mathbf{Z}_2 = 5 \text{ k}\Omega \angle 0^\circ \\ \mathbf{V} &= 10 \text{ V } \angle 0^\circ, \mu = 20, h = 100 \\ \mathbf{I} &= 1 \text{ mA } \angle 0^\circ \end{aligned}$$


$$\mathbf{Z}_N = \mathbf{Z}_1 + \mathbf{Z}_2 = \mathbf{25 \text{ k}\Omega \angle 0^\circ}$$

\mathbf{I}_N : ($h\mathbf{I}$)

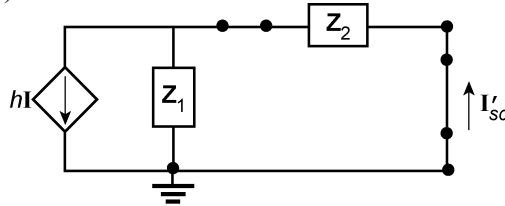

$$\begin{aligned} \mathbf{I}'_{sc} &= \frac{\mathbf{Z}_1(h\mathbf{I})}{\mathbf{Z}_1 + \mathbf{Z}_2} \\ &= \frac{(20 \text{ k}\Omega \angle 0^\circ)(h\mathbf{I})}{20 \text{ k}\Omega \angle 0^\circ + 5 \text{ k}\Omega \angle 0^\circ} \\ &= \mathbf{80 \text{ mA } \angle 0^\circ} \end{aligned}$$


($\mu\mathbf{V}$)

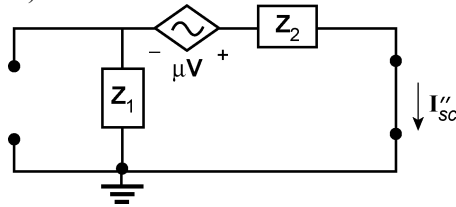

$$\begin{aligned} \mathbf{I}''_{sc} &= \frac{\mu\mathbf{V}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(20)(10 \text{ V } \angle 0^\circ)}{25 \text{ k}\Omega} \\ &= \mathbf{8 \text{ mA } \angle 0^\circ} \end{aligned}$$

$$\mathbf{I}_N \text{ (direction of } \mathbf{I}'_{sc}) = \mathbf{I}'_{sc} - \mathbf{I}''_{sc} = 80 \text{ mA } \angle 0^\circ - 8 \text{ mA } \angle 0^\circ = \mathbf{72 \text{ mA } \angle 0^\circ}$$

46.

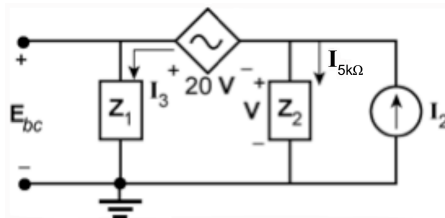


$$\begin{aligned} \mathbf{Z}_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ \mathbf{Z}_2 &= 5 \text{ k}\Omega \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_2 &= \mathbf{I}_3 + \mathbf{I}_{5\text{k}\Omega} \\ \mathbf{V} &= \mathbf{I}_{5\text{k}\Omega} \mathbf{Z}_2 = (\mathbf{I}_2 - \mathbf{I}_3) \mathbf{Z}_2 \\ \mathbf{E}_{oc} = \mathbf{E}_{Th} &= 21 \text{ V} = 21(\mathbf{I}_2 - \mathbf{I}_3) \mathbf{Z}_2 \\ &= 21 \left(\mathbf{I}_2 - \frac{\mathbf{E}_{oc}}{\mathbf{Z}_1} \right) \mathbf{Z}_2 \end{aligned}$$

$$\mathbf{E}_{oc} \left[1 + 21 \frac{\mathbf{Z}_2}{\mathbf{Z}_1} \right] = 21 \mathbf{Z}_2 \mathbf{I}_2$$

$$\mathbf{E}_{oc} = \frac{21 \mathbf{Z}_2 \mathbf{I}_2}{1 + 21 \frac{\mathbf{Z}_2}{\mathbf{Z}_1}} = \frac{21(5 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA } \angle 0^\circ)}{1 + 21 \left(\frac{5 \text{ k}\Omega \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} \right)}$$
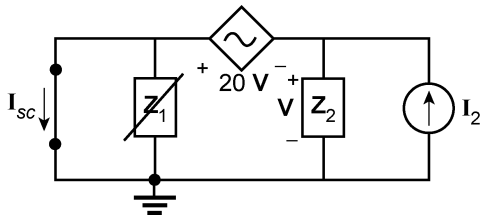
$$\mathbf{E}_{Th} = \mathbf{E}_{oc} = \mathbf{3.925 \text{ V } \angle 0^\circ}$$




$$20 \text{ V} \neq -V \therefore V = 0$$

$$\text{and } I_N = I_{sc} = I_2 = 2 \text{ mA } \angle 0^\circ$$

$$Z_N = \frac{E_{oc}}{I_{sc}} = \frac{3.925 \text{ V } \angle 0^\circ}{2 \text{ mA } \angle 0^\circ} = 1.96 \text{ k}\Omega$$

47.

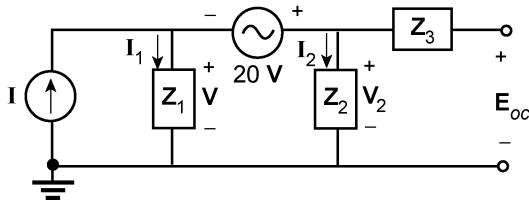

$$Z_1 = 1 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 3 \text{ k}\Omega \angle 0^\circ$$

$$Z_3 = 4 \text{ k}\Omega \angle 0^\circ$$

$$V_2 = 21 \text{ V} = E_{oc} \Rightarrow V = \frac{E_{oc}}{21}$$


$$I = I_1 + I_2, I_1 = \frac{V}{Z_1} = \frac{E_{oc}}{21 Z_1}$$

$$I_2 = \frac{E_{oc}}{Z_2}, I = I_1 + I_2 = \frac{E_{oc}}{21 Z_1} + \frac{E_{oc}}{Z_2} = E_{oc} \left[\frac{1}{21 Z_1} + \frac{1}{Z_2} \right]$$

$$I = E_{oc} \left[\frac{Z_2 + 21 Z_1}{21 Z_1 Z_2} \right]$$

$$\text{and } E_{oc} = \frac{21 Z_1 Z_2 I}{Z_2 + 21 Z_1} = \frac{(21)(1 \text{ k}\Omega \angle 0^\circ)(3 \text{ k}\Omega \angle 0^\circ)(2 \text{ mA } \angle 0^\circ)}{3 \text{ k}\Omega + 21(1 \text{ k}\Omega \angle 0^\circ)}$$
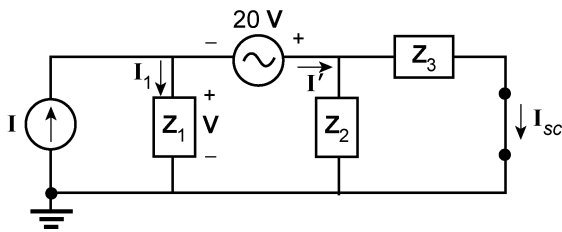
$$E_{Th} = E_{oc} = 5.25 \text{ V } \angle 0^\circ$$



$$I_{sc} = \frac{V_3}{Z_3} = \frac{21 \text{ V}}{Z_3} \Rightarrow V = \frac{Z_3}{21} I_{sc}$$

$$V = I_1 Z_1$$

$$I = I_1 + I'$$

$$I_{sc} = \frac{Z_2 I'}{Z_2 + Z_3} \Rightarrow I' = \left(\frac{Z_2 + Z_3}{Z_2} \right) I_{sc}$$


$$I = I_1 + I' = \frac{V}{Z_1} + \left(\frac{Z_2 + Z_3}{Z_2} \right) I_{sc} = \left[\frac{Z_3}{21 Z_1} + \frac{Z_2 + Z_3}{Z_2} \right] I_{sc}$$

$$I_{sc} = \frac{I}{\frac{Z_3}{21 Z_1} + \frac{Z_2 + Z_3}{Z_2}} = \frac{2 \text{ mA } \angle 0^\circ}{\frac{4 \text{ k}\Omega}{21 \text{ k}\Omega} + \frac{7 \text{ k}\Omega}{3 \text{ k}\Omega}} = 0.79 \text{ mA } \angle 0^\circ$$


$$\therefore I_N = 0.79 \text{ mA } \angle 0^\circ$$

$$Z_N = \frac{E_{oc}}{I_{sc}} = \frac{5.25 \text{ V } \angle 0^\circ}{0.79 \text{ mA } \angle 0^\circ} = 6.65 \text{ k}\Omega \angle 0^\circ$$

48.

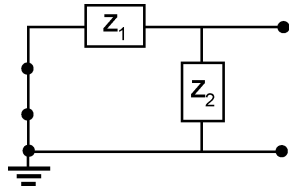

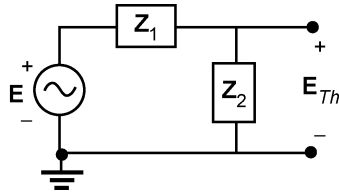
$$\begin{aligned} Z_1 &= 3 \Omega + j4 \Omega, Z_2 = -j6 \Omega \\ \leftarrow Z_{Th} &= Z_1 \parallel Z_2 \\ &= 5 \Omega \angle 53.13^\circ \parallel 6 \Omega \angle -90^\circ \\ &= 8.32 \Omega \angle -3.18^\circ \\ Z_L &= 8.32 \Omega \angle 3.18^\circ = 8.31 \Omega - j0.46 \Omega \end{aligned}$$




$$\begin{aligned} E_{Th} &= \frac{Z_2 E}{Z_2 + Z_1} \\ &= \frac{(6 \Omega \angle -90^\circ)(120 \text{ V} \angle 0^\circ)}{3.61 \Omega \angle -33.69^\circ} \\ &= 199.45 \text{ V} \angle -56.31^\circ \\ P_{\max} &= \frac{E_{Th}^2}{4R_{Th}} = \frac{(3.124 \text{ V})^2}{4(8.31 \Omega)} = 1198.2 \text{ W} \end{aligned}$$

49.

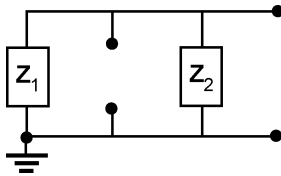


$$\begin{aligned} Z_1 &= 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ \\ Z_2 &= 2 \Omega \angle 0^\circ \\ \leftarrow Z_N = Z_{Th} &= Z_1 \parallel Z_2 \\ &= 5 \Omega \angle 53.13^\circ \parallel 2 \Omega \angle 0^\circ \\ &= \frac{10 \Omega \angle 53.13^\circ}{2 + 3 + j4} \\ &= \frac{10 \Omega \angle 53.13^\circ}{5 + j4} \\ &= \frac{10 \Omega \angle 53.13^\circ}{6.403 \angle 38.66^\circ} \\ &= 1.56 \Omega \angle 14.47^\circ \\ Z_{Th} &= 1.56 \Omega \angle 14.47^\circ \\ &= 1.51 \Omega + j0.39 \Omega \\ Z_L &= 1.51 \Omega - j0.39 \Omega \end{aligned}$$

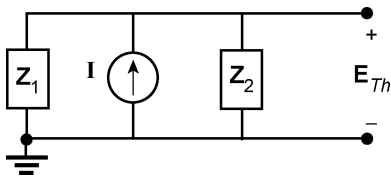

$$\begin{aligned} E_{Th} &= I(Z_1 \parallel Z_2) \\ &= (2 \text{ A} \angle 30^\circ)(1.562 \Omega \angle 14.47^\circ) \\ &= 3.12 \text{ V} \angle 44.47^\circ \\ P_{\max} &= \frac{E_{Th}^2}{4R_{Th}} = \frac{(3.12 \text{ V})^2}{4(1.51 \Omega)} = 1.61 \text{ W} \end{aligned}$$


50. Z_{Th} :

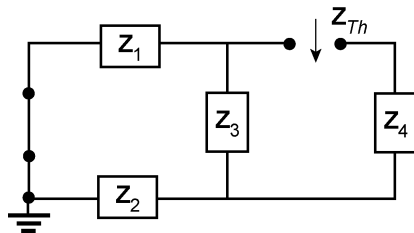

$$\begin{aligned} Z_1 &= 4 \Omega \angle 90^\circ, Z_2 = 10 \Omega \angle 0^\circ \\ Z_3 &= 5 \Omega \angle -90^\circ, Z_4 = 6 \Omega \angle -90^\circ \\ E &= 60 \text{ V} \angle 60^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{Z}_{Th} &= \mathbf{Z}_4 + \mathbf{Z}_3 \parallel (\mathbf{Z}_1 + \mathbf{Z}_2) = -j6 \Omega + (5 \Omega \angle -90^\circ) \parallel (10 \Omega + j4 \Omega) \\ &= 2.475 \Omega - j4.754 \Omega \\ &= 11.04 \Omega \angle -77.03^\circ \\ \mathbf{Z}_L &= 11.04 \Omega \angle 77.03^\circ \end{aligned}$$


\mathbf{E}_{Th} :

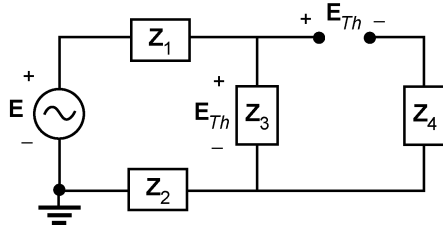

$$\begin{aligned} \mathbf{E}_{Th} &= \frac{\mathbf{Z}_3(\mathbf{E})}{\mathbf{Z}_3 + \mathbf{Z}_1 + \mathbf{Z}_2} \\ &= \frac{(5 \Omega \angle -90^\circ)(60 \text{ V} \angle 60^\circ)}{-j5 \Omega + j4 \Omega + 10 \Omega} \\ &= 29.85 \text{ V} \angle -24.29^\circ \end{aligned}$$


$$P_{\max} = E_{Th}^2 / 4R_{Th} = (29.85 \text{ V})^2 / 4(2.475 \Omega) = 90 \text{ W}$$

51.

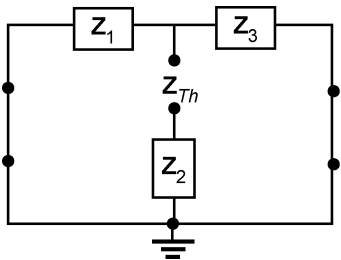

$$\begin{aligned} \mathbf{Z}_1 &= 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ \\ \mathbf{Z}_2 &= -j8 \Omega \\ \mathbf{Z}_3 &= 12 \Omega + j9 \Omega \end{aligned}$$
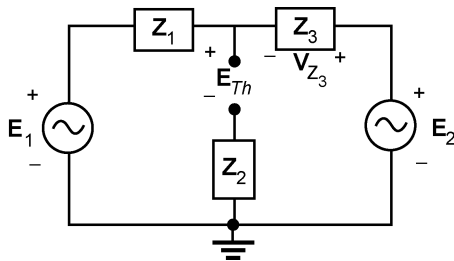
$$\begin{aligned} \mathbf{Z}_{Th} &= \mathbf{Z}_2 + \mathbf{Z}_1 \parallel \mathbf{Z}_3 = -j8 \Omega + (5 \Omega \angle 53.13^\circ) \parallel (15 \Omega \angle 36.87^\circ) \\ &= 5.71 \Omega \angle -64.30^\circ = 2.475 \Omega - j5.143 \Omega \\ \mathbf{Z}_L &= 5.71 \Omega \angle 64.30^\circ = 2.48 \Omega + j5.15 \Omega \end{aligned}$$



$$\begin{aligned} \mathbf{E}_{Th} + \mathbf{V}_{Z_3} - \mathbf{E}_2 &= 0 \\ \mathbf{E}_{Th} &= \mathbf{E}_2 - \mathbf{V}_{Z_3} \\ \mathbf{V}_{Z_3} &= \frac{\mathbf{Z}_3(\mathbf{E}_2 - \mathbf{E}_1)}{\mathbf{Z}_3 + \mathbf{Z}_1} \\ &= 168.97 \text{ V} \angle 112.53^\circ \end{aligned}$$

$$\mathbf{E}_{Th} = \mathbf{E}_2 - \mathbf{V}_{Z_3} = 200 \text{ V} \angle 90^\circ - 168.97 \text{ V} \angle 112.53^\circ = 78.24 \text{ V} \angle 34.16^\circ$$

$$P_{\max} = E_{Th}^2 / 4R_{Th} = (78.24 \text{ V})^2 / 4(2.475 \Omega) = 618.33 \text{ W}$$


$$52. \quad \mathbf{I} = \frac{E \angle 0^\circ}{R_1 \angle 0^\circ} = \frac{1 \text{ V} \angle 0^\circ}{1 \text{ k}\Omega \angle 0^\circ} = 1 \text{ mA} \angle 0^\circ$$

$$\mathbf{Z}_{Th} = 40 \text{ k}\Omega \angle 0^\circ$$

$$\mathbf{E}_{Th} = (50 \text{ I})(40 \text{ k}\Omega \angle 0^\circ) = (50)(1 \text{ mA} \angle 0^\circ)(40 \text{ k}\Omega \angle 0^\circ) = 2000 \text{ V} \angle 0^\circ$$

$$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(2 \text{ kV})^2}{4(40 \text{ k}\Omega)} = 25 \text{ W}$$


53. E_{Th} :

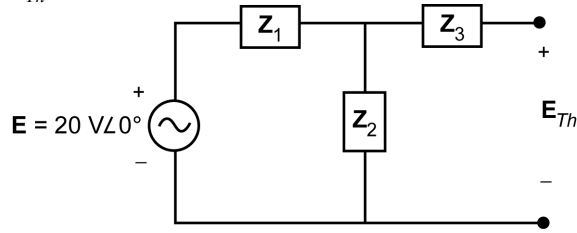

$$\begin{aligned} Z_1 &= 2 \text{ k}\Omega \angle 0^\circ \\ Z_2 &= 3 \text{ k}\Omega \angle -90^\circ \\ Z_3 &= 6 \text{ k}\Omega \angle 90^\circ \end{aligned}$$

$$\begin{aligned} E_{Th} &= \frac{Z_2 E}{Z_2 + Z_1} = \frac{(3 \text{ k}\Omega \angle 90^\circ)(20 \text{ V} \angle 0^\circ)}{-j3 \text{ k}\Omega + 2 \text{ k}\Omega} \\ &= \frac{60 \text{ V} \angle -90^\circ}{3.61 \angle -56.31^\circ} = \mathbf{16.62 \text{ V} \angle -33.69^\circ} \end{aligned}$$

Z_{Th} :

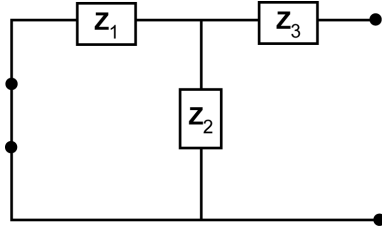

$$\leftarrow Z_{Th} = Z_3 + Z_1 \parallel Z_2$$

$$\begin{aligned} Z_{Th} &= +j6 \text{ k}\Omega + \frac{(2 \text{ k}\Omega \angle 0^\circ)(3 \text{ k}\Omega \angle -90^\circ)}{2 \text{ k}\Omega - j3 \text{ k}\Omega} \\ &= +j6 \text{ k}\Omega + 1.66 \text{ k}\Omega \angle -33.69^\circ \\ &= +j6 \text{ k}\Omega + 1.38 \text{ k}\Omega - j920.8 \Omega \\ &= 1.38 \text{ k}\Omega + j5.08 \text{ k}\Omega \\ &= 5.26 \text{ k}\Omega \angle +74.80^\circ \end{aligned}$$

$$\therefore Z_L = 5.36 \text{ k}\Omega \angle -74.80^\circ = 1.38 \text{ k}\Omega - j5.08 \text{ k}\Omega$$

b.
$$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(16.62 \text{ V})^2}{4(1.38 \text{ k}\Omega)} = \mathbf{50.04 \text{ mW}}$$

54. From #24, $Z_{Th} = 9 \Omega$, $E_{Th} = 12 \text{ V} + 24 \text{ V} \angle 0^\circ$

a. $\therefore Z_L = 9 \Omega$

b.
$$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(12 \text{ V})^2}{4(9 \Omega)} + \frac{(24 \text{ V})^2}{4(9 \Omega)} = 4 \text{ W} + 16 \text{ W} = \mathbf{20 \text{ W}}$$


or
$$E_{Th} = \sqrt{V_0^2 + V_{\text{eff}}^2} = 26.833 \text{ V}$$

and
$$P_{\max} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(26.833 \text{ V})^2}{4(9 \Omega)} = \mathbf{20 \text{ W}}$$

55. a. Problem 25(a):
 $\mathbf{Z}_{Th} = 4.47 \text{ k}\Omega \angle -26.57^\circ = 4 \text{ k}\Omega - j2 \text{ k}\Omega$
 $\mathbf{Z}_L = 4 \text{ k}\Omega + j2 \text{ k}\Omega$
 $\mathbf{E}_{Th} = 31.31 \text{ V} \angle -26.57^\circ$
- b. $P_{\max} = E_{Th}^2 / 4R_{Th} = (31.31 \text{ V})^2 / 4(4 \text{ k}\Omega) = 61.27 \text{ mW}$

56. a. $\mathbf{Z}_{Th} = 2 \text{ k}\Omega \angle 0^\circ \parallel 2 \text{ k}\Omega \angle -90^\circ = 1 \text{ k}\Omega - j1 \text{ k}\Omega$
 $R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_{Load})^2}$
 $= \sqrt{(1 \text{ k}\Omega)^2 + (-1 \text{ k}\Omega + 2 \text{ k}\Omega)^2}$
 $= \sqrt{(1 \text{ k}\Omega)^2 + (1 \text{ k}\Omega)^2}$
 $= 1.41 \text{ k}\Omega$

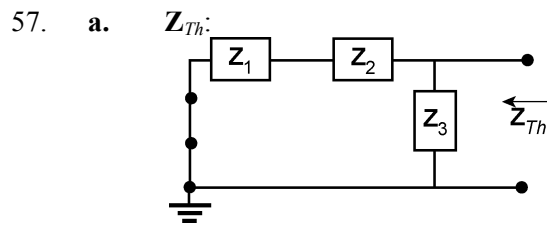- b. $R_{av} = (R_{Th} + R_{Load}) / 2 = (1 \text{ k}\Omega + 1.41 \text{ k}\Omega) / 2 = 1.21 \text{ k}\Omega$
 $P_{\max} = \frac{E_{Th}^2}{4R_{av}} = \frac{(50 \text{ V})^2}{4(1.21 \text{ k}\Omega)} = 516.53 \text{ mW}$



$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(10 \text{ kHz})(4 \text{ nF})}$$

$$\cong 3978.87 \Omega$$

$$X_L = 2\pi f L = 2\pi(10 \text{ kHz})(30 \text{ mH})$$

$$\cong 1884.96 \Omega$$

$$\mathbf{Z}_1 = 1 \text{ k}\Omega \angle 0^\circ, \mathbf{Z}_2 = 1884.96 \Omega \angle 90^\circ$$

$$\mathbf{Z}_3 = 3978.87 \Omega \angle -90^\circ$$

$$\mathbf{Z}_{Th} = (\mathbf{Z}_1 + \mathbf{Z}_2) \parallel \mathbf{Z}_3 = (1 \text{ k}\Omega + j1884.96 \Omega) \parallel 3978.87 \Omega \angle -90^\circ$$

$$= 2133.79 \Omega \angle 62.05^\circ \parallel 3978.87 \Omega \angle -90^\circ$$

$$= 3658.65 \Omega \angle 36.52^\circ$$

$$\therefore \mathbf{Z}_L = 3658.65 \Omega \angle -36.52^\circ = 2940.27 \Omega - j2177.27 \Omega$$


$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(10 \text{ kHz})(2177.27 \Omega)} = 7.31 \text{ nF}$$

- b. $R_L = R_{Th} = 2940.27 \Omega$


c. $\mathbf{E}_{Th} = \frac{\mathbf{Z}_3(\mathbf{E})}{\mathbf{Z}_3 + \mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(3978.87 \Omega \angle -90^\circ)(2 \text{ V} \angle 0^\circ)}{1 \text{ k}\Omega + j1884.96 \Omega - j3978.87 \Omega} = 3.43 \text{ V} \angle -25.53^\circ$

$$P_{\max} = E_{Th}^2 / 4R_{Th} = (3.43 \text{ V})^2 / 4(2940.27 \Omega) = 1 \text{ mW}$$

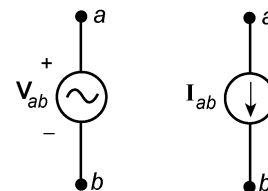58. $\mathbf{I}_{ab} = \frac{(4 \text{ k}\Omega \angle 0^\circ)(4 \text{ mA} \angle 0^\circ)}{4 \text{ k}\Omega + 8 \text{ k}\Omega} = 1.33 \text{ mA} \angle 0^\circ$
 $\mathbf{V}_{ab} = (\mathbf{I}_{ab})(8 \text{ k}\Omega \angle 0^\circ) = 10.67 \text{ V} \angle 0^\circ$



59. a.

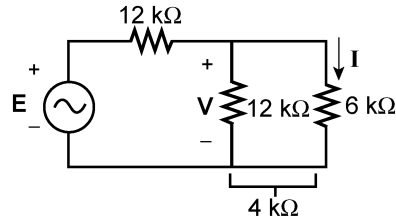


$$V = \frac{4 \text{ k}\Omega(E)}{4 \text{ k}\Omega + 12 \text{ k}\Omega} = \frac{1}{4}(20 \text{ V } \angle 0^\circ)$$

$$= 5 \text{ V } \angle 0^\circ$$

$$I = \frac{5 \text{ V } \angle 0^\circ}{6 \text{ k}\Omega} = 0.83 \text{ mA } \angle 0^\circ$$

b.

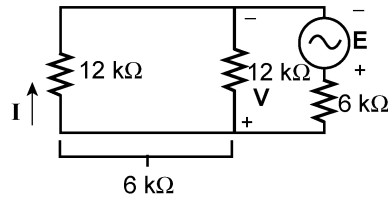


$$V = \frac{6 \text{ k}\Omega(E)}{6 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{1}{2}(20 \text{ V } \angle 0^\circ)$$

$$= 10 \text{ V } \angle 0^\circ$$

$$I = \frac{10 \text{ V } \angle 0^\circ}{12 \text{ k}\Omega} = 0.83 \text{ mA } \angle 0^\circ$$

60.

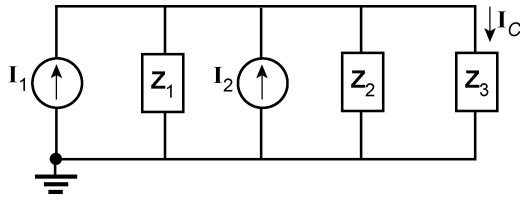

$$I_1 = \frac{100 \text{ V } \angle 0^\circ}{2 \text{ k}\Omega \angle 0^\circ} = 50 \text{ mA } \angle 0^\circ$$

$$I_2 = \frac{50 \text{ V } \angle 0^\circ}{4 \text{ k}\Omega \angle 90^\circ}$$

$$= 12.5 \text{ mA } \angle -90^\circ$$

$$Z_1 = 2 \text{ k}\Omega \angle 0^\circ$$

$$Z_2 = 4 \text{ k}\Omega \angle 90^\circ$$

$$Z_3 = 4 \text{ k}\Omega \angle -90^\circ$$

$$I_T = I_1 - I_2 = (50 \text{ mA } \angle 0^\circ - 12.5 \text{ mA } \angle -90^\circ) = 50 \text{ mA} + j12.5 \text{ mA}$$

$$= 51.54 \text{ mA } \angle 14.04^\circ$$

$$Z' = Z_1 \parallel Z_2 = (2 \text{ k}\Omega \angle 0^\circ) \parallel (4 \text{ k}\Omega \angle 90^\circ) = 1.79 \text{ k}\Omega \angle 26.57^\circ$$

$$I_C = \frac{Z' I_T}{Z' + Z_3} = \frac{(1.79 \text{ k}\Omega \angle 26.57^\circ)(51.54 \text{ mA } \angle 14.04^\circ)}{1.6 \text{ k}\Omega + j0.8 \text{ k}\Omega - j4 \text{ k}\Omega}$$

$$= 25.77 \text{ mA } \angle 104.04^\circ$$